





# RRB JE | SSE 2023

## Foundation Batch

### Analog Electronics

#### Day-1

> LIVE

LAWRENCE Sir



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount

Adda247

WELCOME

we are limitless

TO Adda247

# APP FEATURES



**Download Now**  
**Adda247 APP**

*Play Store*



Premium Study Material



Current Affairs



Job Alerts



Daily Quizzes



Subject-wise Quizzes



Magazines




Power Capsule



Notes & Articles



Videos

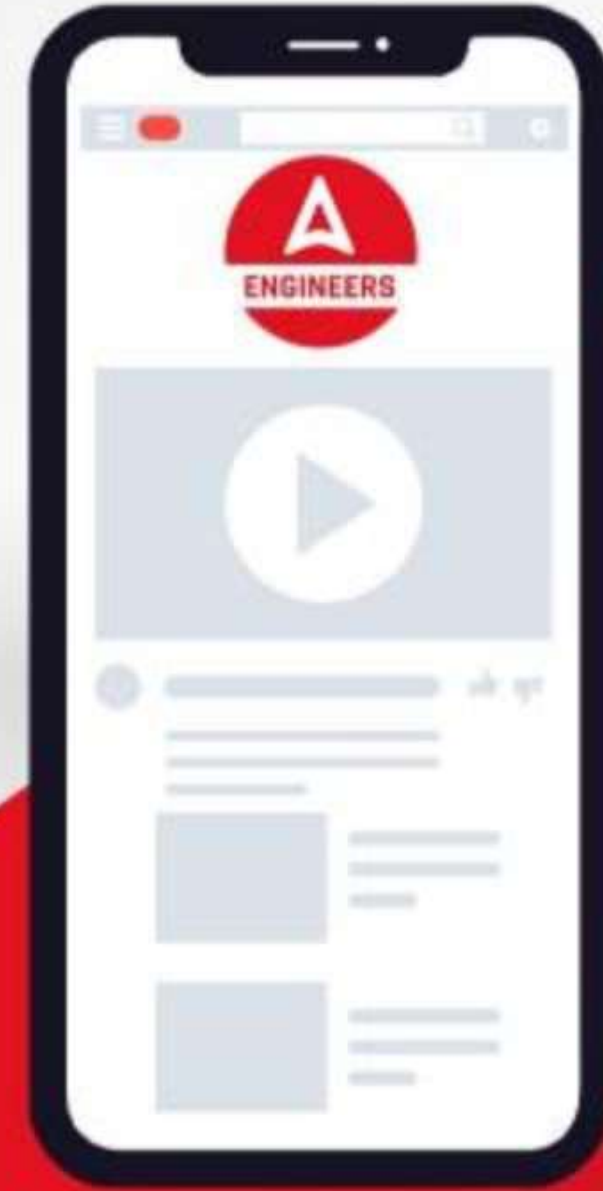

**SUBSCRIBE NOW**

**Engineers Adda247**  
YouTube Channel

# Analog Electronics

- Operational Amplifier
- Mode of Operation


# → Application of OP-Amp

Linear

$$y = x$$

Non-linear
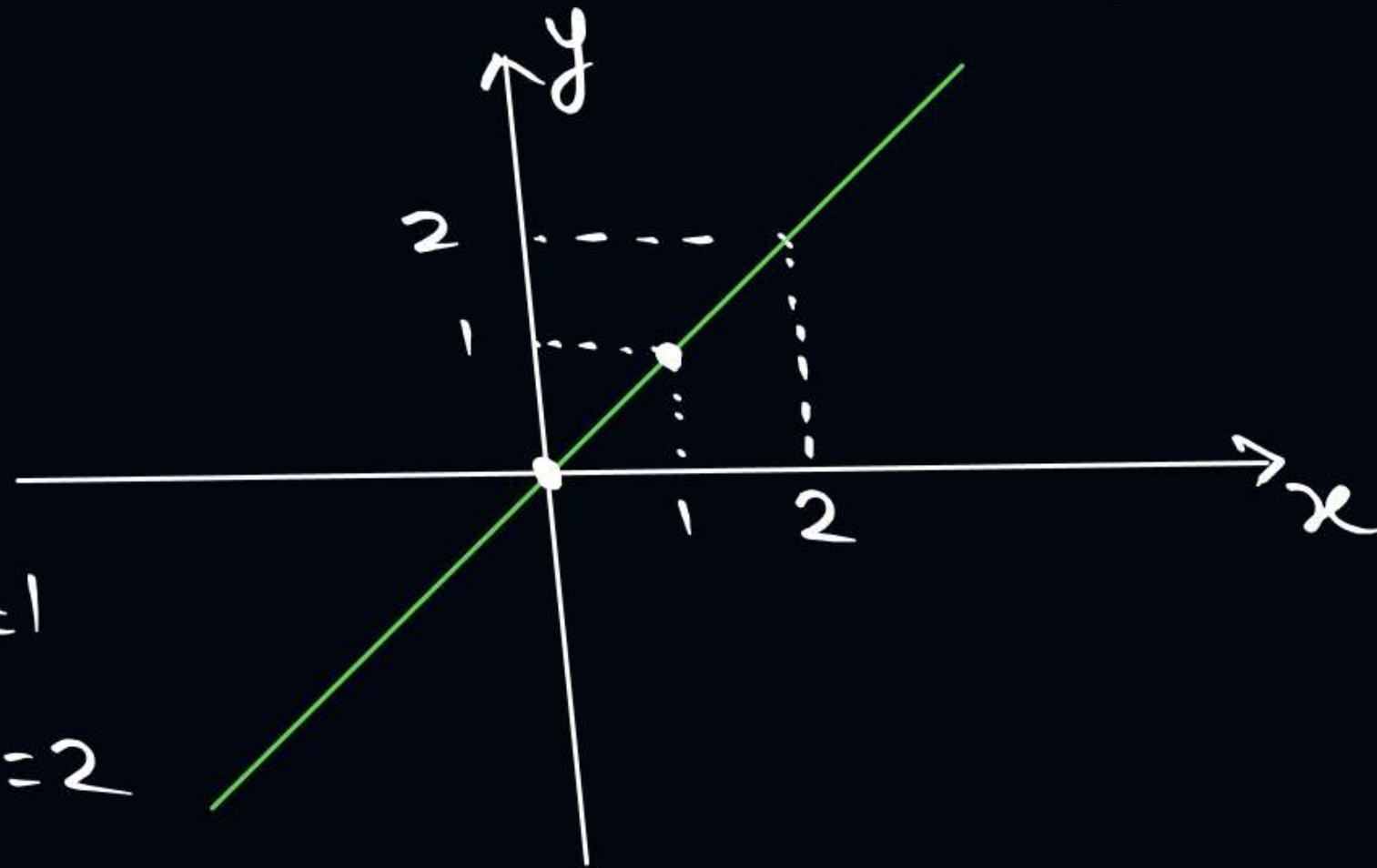
$$\begin{aligned} x=1, y=1 \\ x=2, y=2 \end{aligned}$$



linear Application:

Negative feedback  $\rightarrow$  OP-Amp

Non-linear Application:

Positive feedback  $\rightarrow$  OP-Amp



→ Voltage Regulators


→ Timer

→ PLL
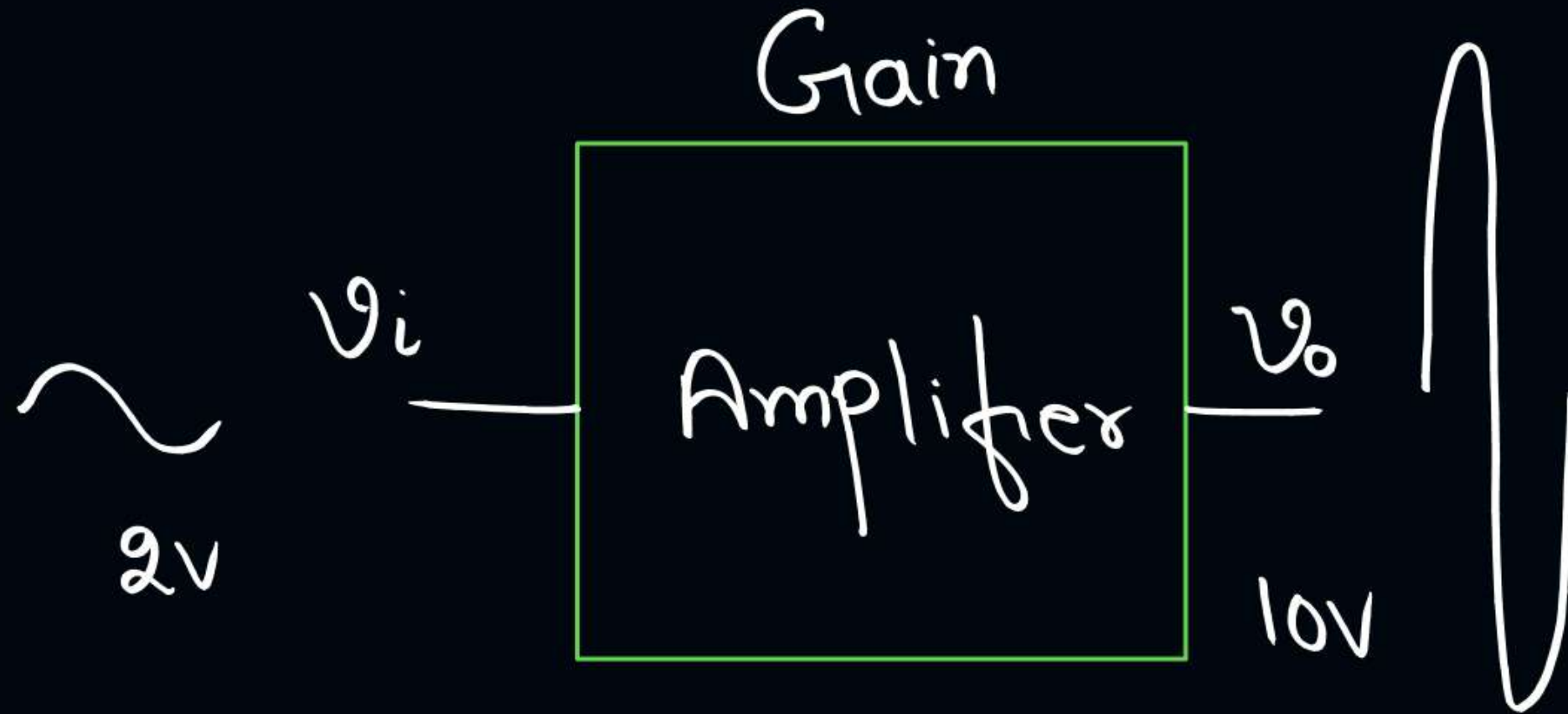
## Operation Amplifier:

What is amplifier?

It is circuit which amplifies the voltage signal.



$$\text{Gain} = \frac{10}{2} = 5 \rightarrow \underline{\text{Constant}}$$

Voltage =  $V$  volt

Current =  $I$  Amp

$\frac{I}{V}$  = Conductance  
( $G$ )

$\frac{\text{Volt}}{\text{amp}}$   $\frac{V}{I}$  = Resistor =  $\Omega$  (ohm)

$$G = \frac{1}{R}$$

( $\sigma$ )

(mho)


(Siemens)

Resistor:  $R$  (ohm  $\rightarrow \Omega$ )

Oppose  $\rightarrow$  Electric current

Conductor:  $(G)$   $\rightarrow$  mho ( $\Omega^{-1}$ )

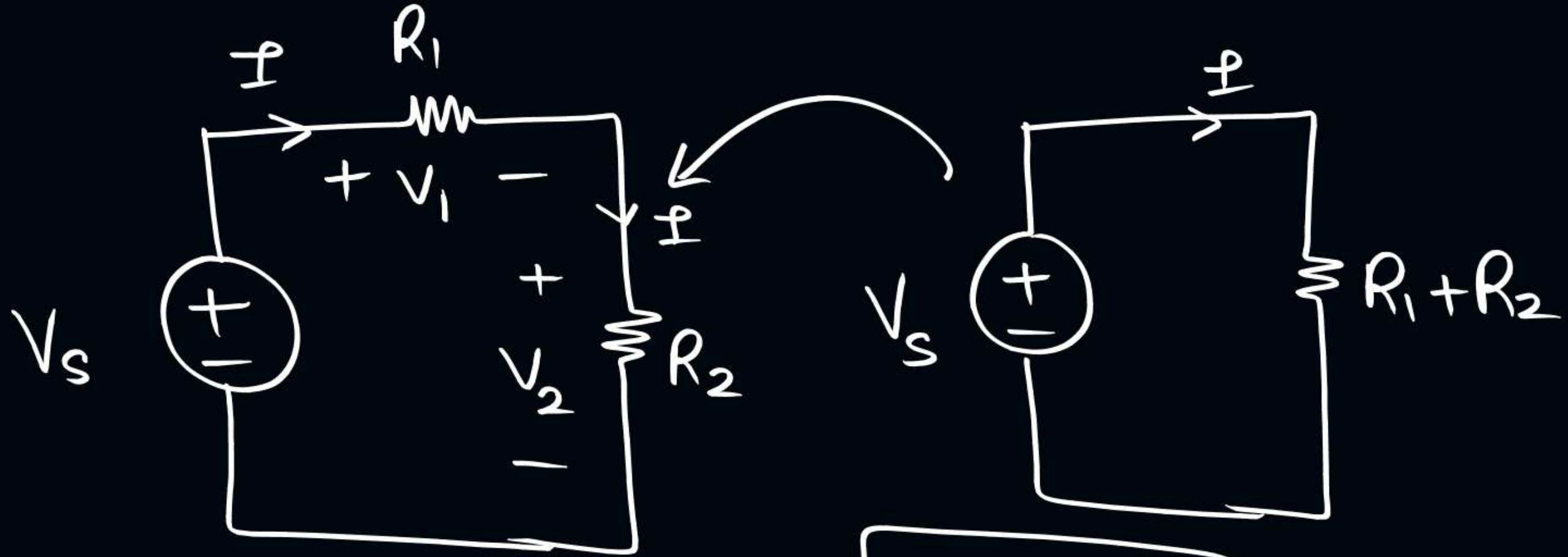$\rightarrow$  Support  $\rightarrow$  Electric current



$$V_2 = I \cdot R_2$$

$$V_2 = \frac{R_2 \cdot V_s}{R_1 + R_2}$$

$$I = \frac{V_s}{R_1 + R_2}$$


$$V_1 = R_1 \cdot I$$


$$V_1 = \frac{R_1}{R_1 + R_2} \cdot V_S$$

★

$$V_2 = \left( \frac{R_2}{R_1 + R_2} \right) V_S$$

★

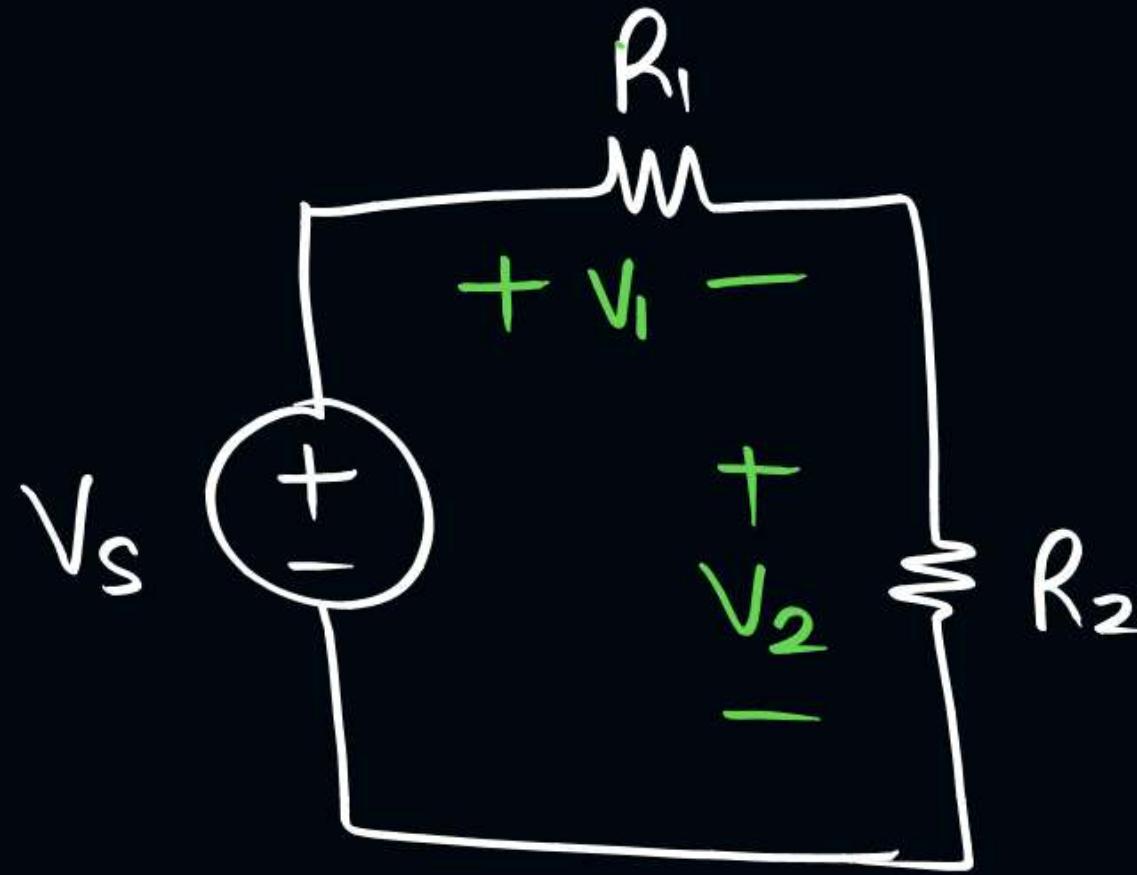

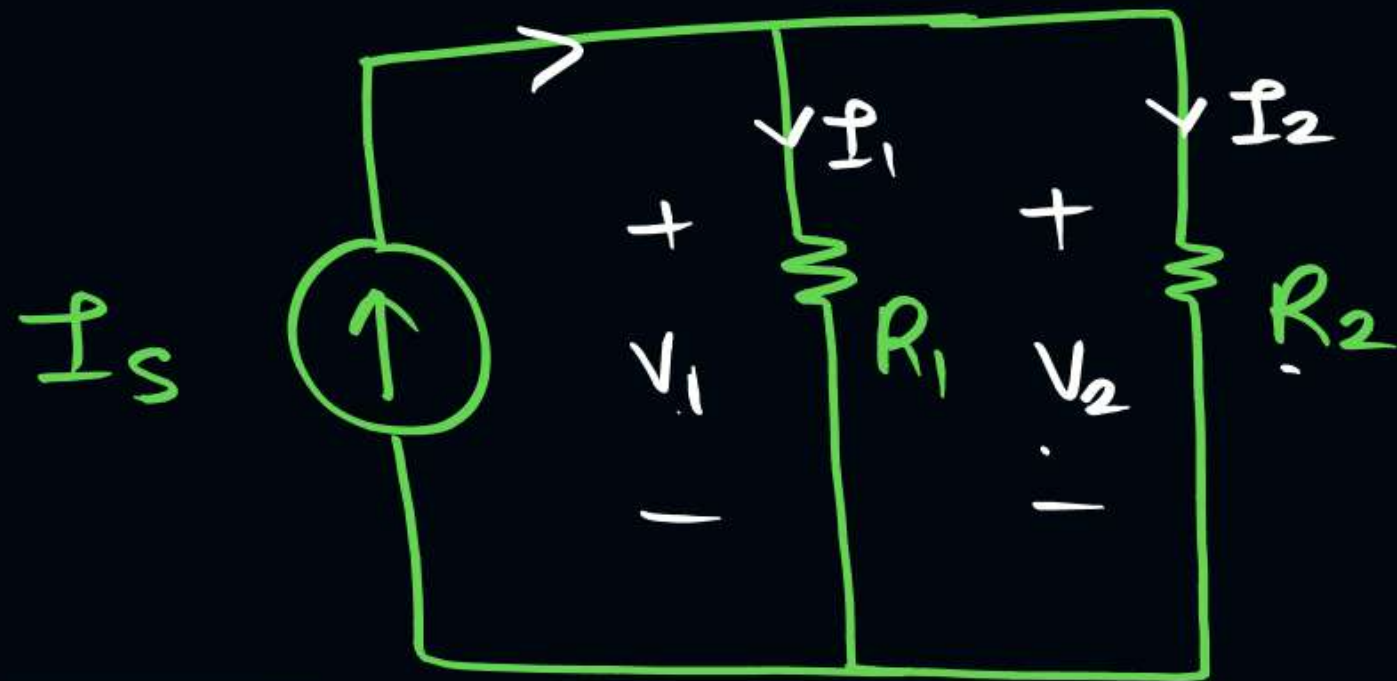


$$V_1 = V_2 = V = \frac{I_s \cdot R_1 \cdot R_2}{R_1 + R_2}$$

$V_1 = V_2$  → Parallel Connection

$$I_1 = \frac{V}{R_1} = \frac{1}{R_1} \cdot \frac{I_s \cdot R_1 \cdot R_2}{R_1 + R_2}$$

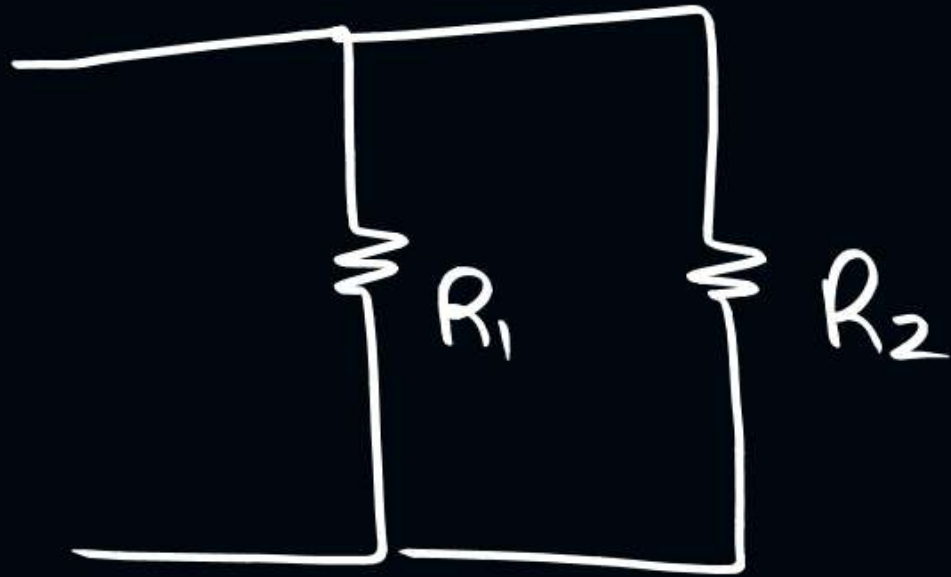
$$I_1 = \left( \frac{R_2}{R_1 + R_2} \right) I_s$$






$$R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$
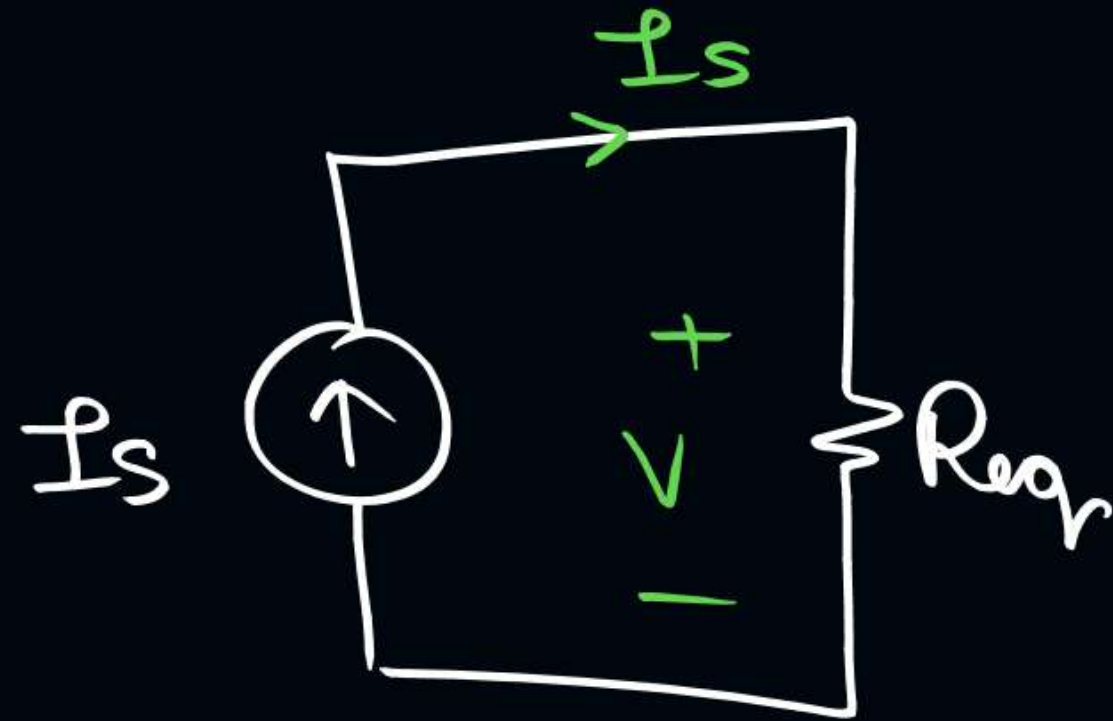
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$



$$V = I_s \cdot R_{eq}$$
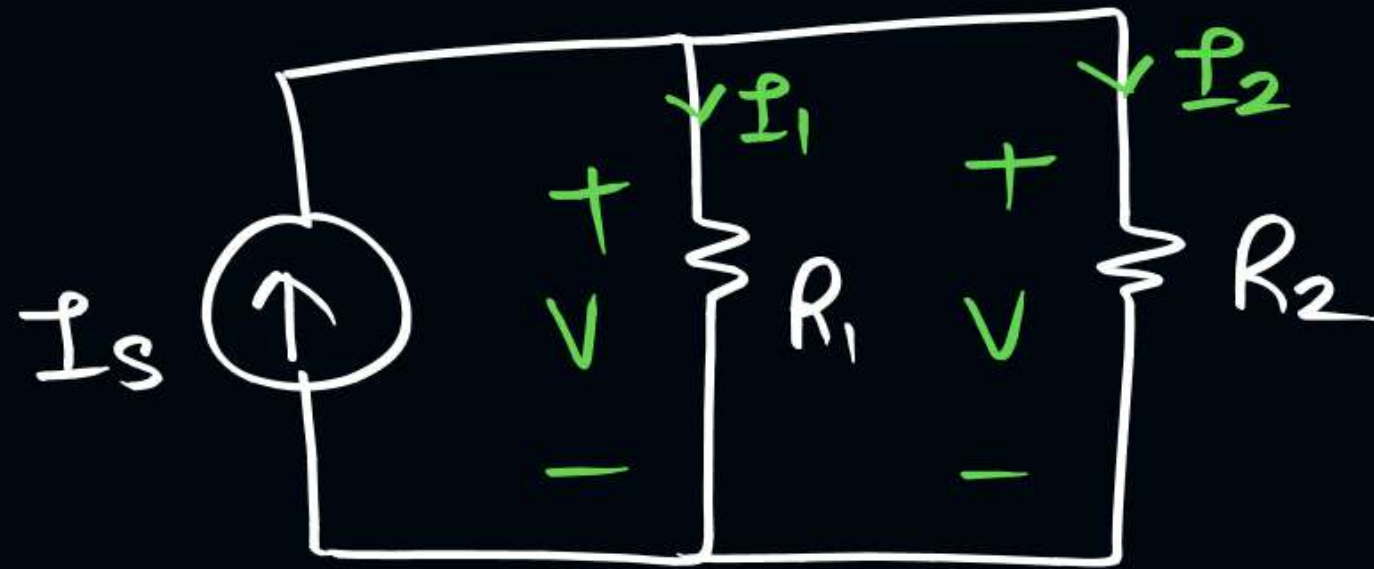
$$V = \frac{I_s \cdot R_1 R_2}{R_1 + R_2}$$




$$V = I_s \cdot \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = \frac{V}{R_1}$$

$$I_1 = \frac{I_s \cdot R_2}{R_1 + R_2}$$

$$I_2 = \frac{V}{R_2} = \frac{1}{R_2} \cdot \frac{I_s \cdot R_1 R_2}{R_1 + R_2}$$

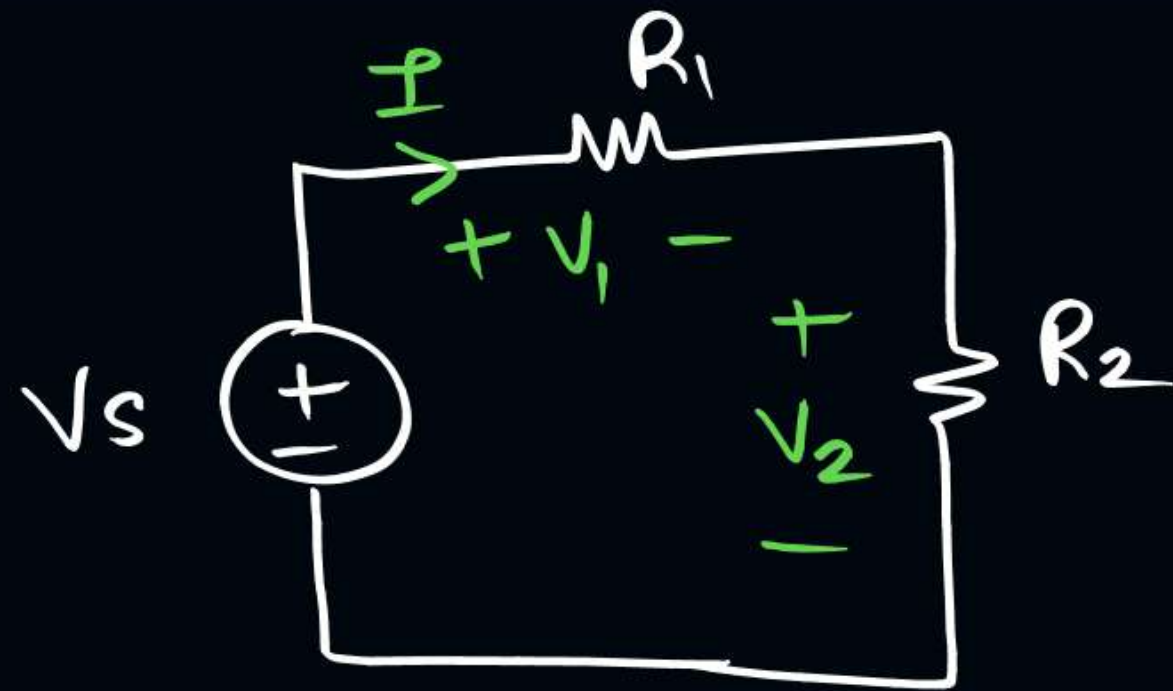
$$I_2 = \frac{I_s \cdot R_1}{R_1 + R_2}$$



$$I = \frac{V_s}{R_1 + R_2}$$

$$V_1 = V_s \cdot \frac{R_1}{R_1 + R_2}$$

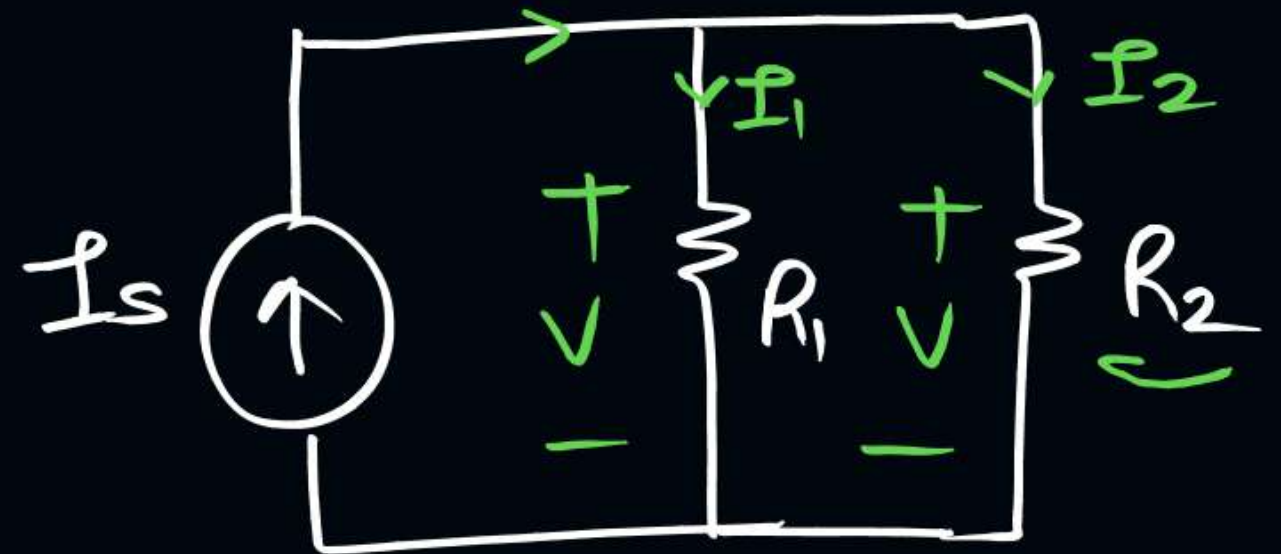
$$V_2 = \frac{V_s \cdot R_2}{R_1 + R_2}$$



$$V = I_s \cdot \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = \frac{R_2}{R_1 + R_2} \cdot I_s$$

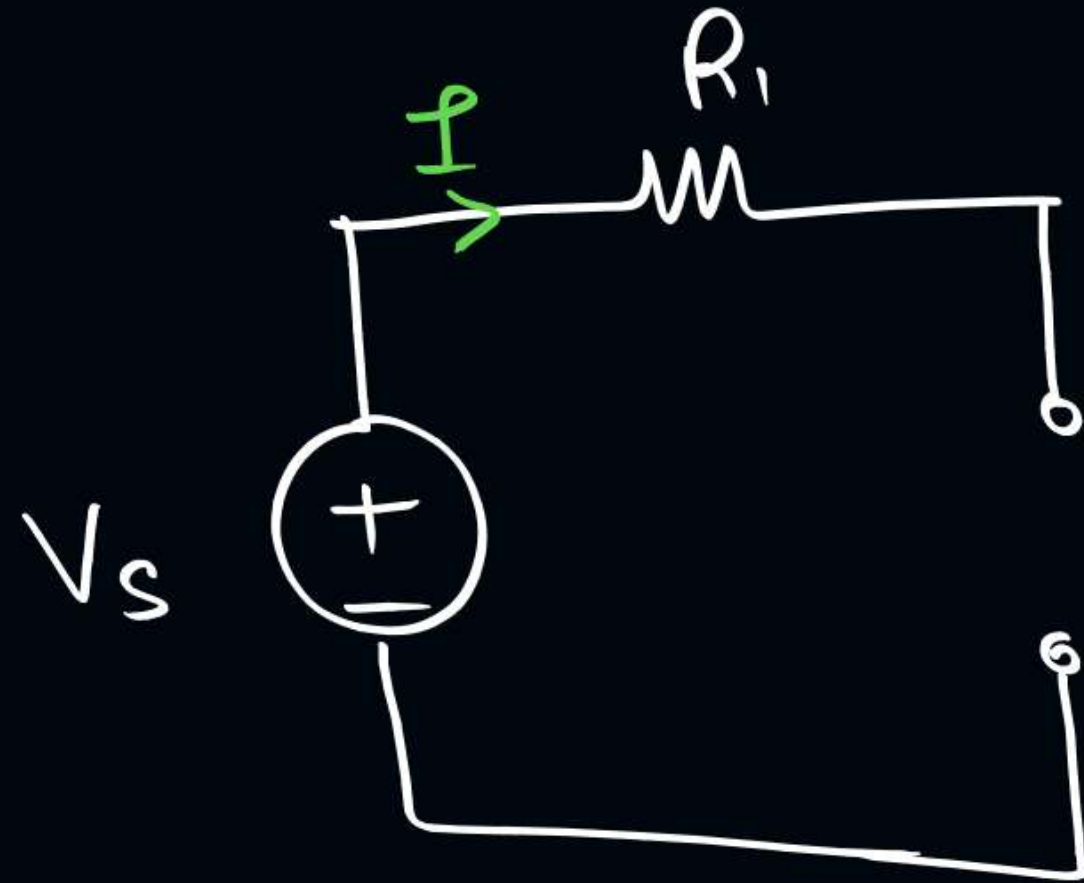
$$I_2 = \left( \frac{R_1}{R_1 + R_2} \right) I_s$$




$I = 0$  Amp

Current:

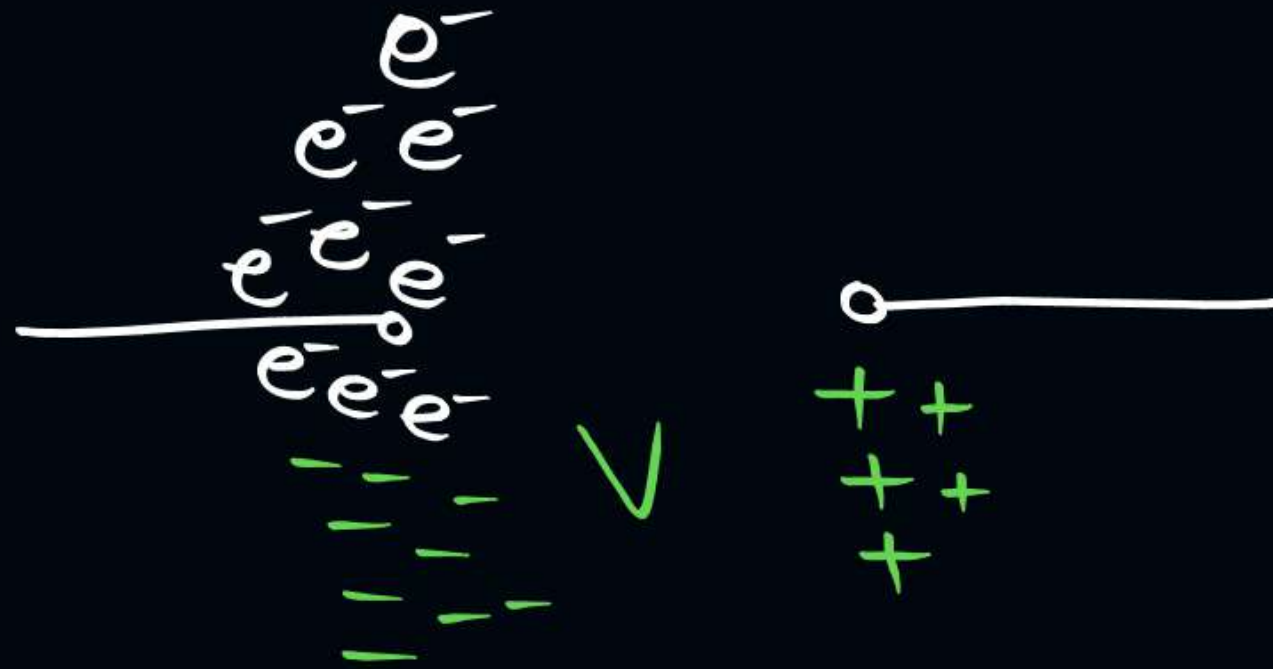Flow of  $e^-$  in particular direction is known as current.



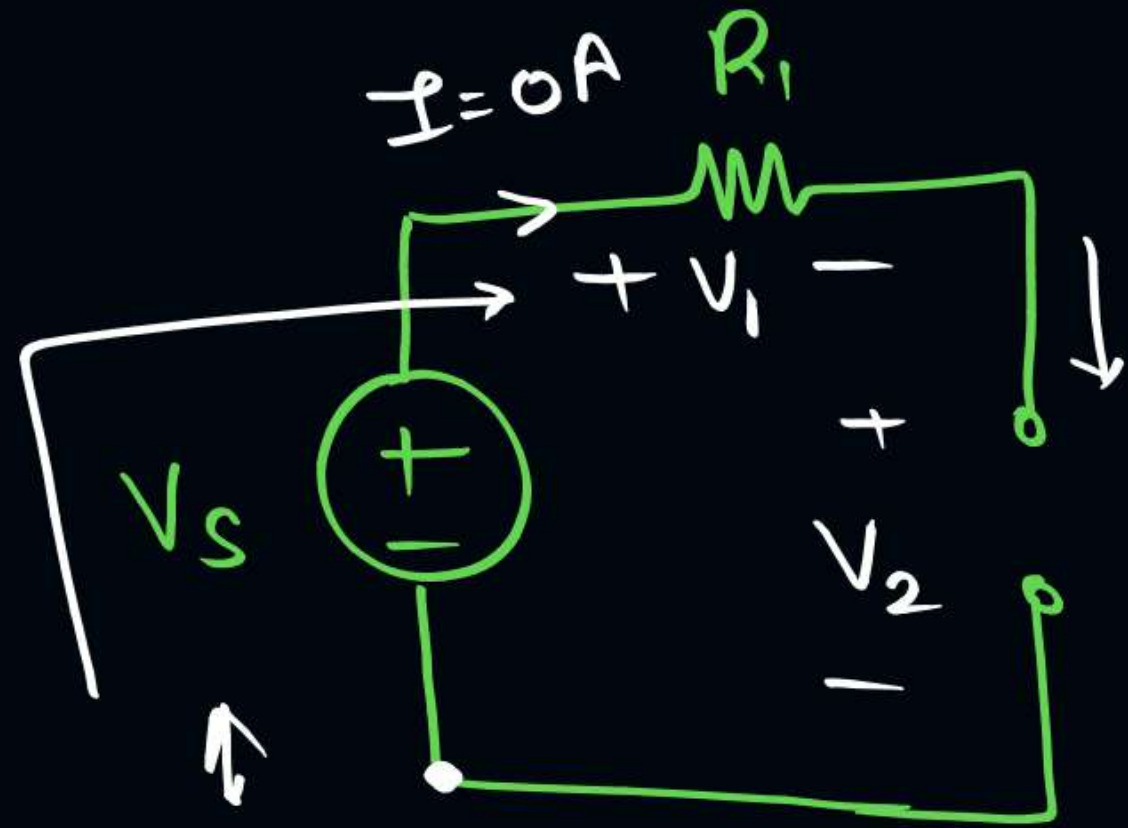Charge of  
 $e^- = -1.6 \times 10^{-19} \text{ C}$



$$-V_s + V_1 + V_2 = 0$$


$$V_1 + V_2 = V_s$$

$$V_1 = 0 \times R_1 = 0 \text{ volt}$$

KVL:

Applied on Voltage in  
a loop.

$$V_1 = 0$$
$$V_2 = V_s$$

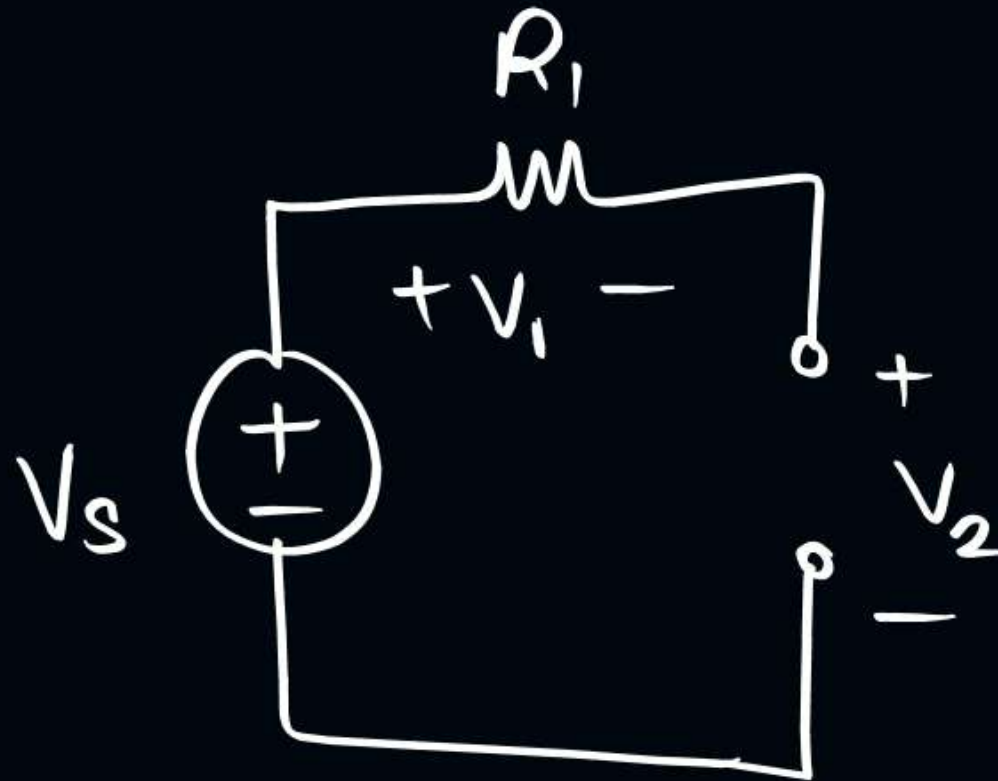

$$V_1 = 0, \quad V_2 = V_s$$



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



Y694

Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount






Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



# APP FEATURES

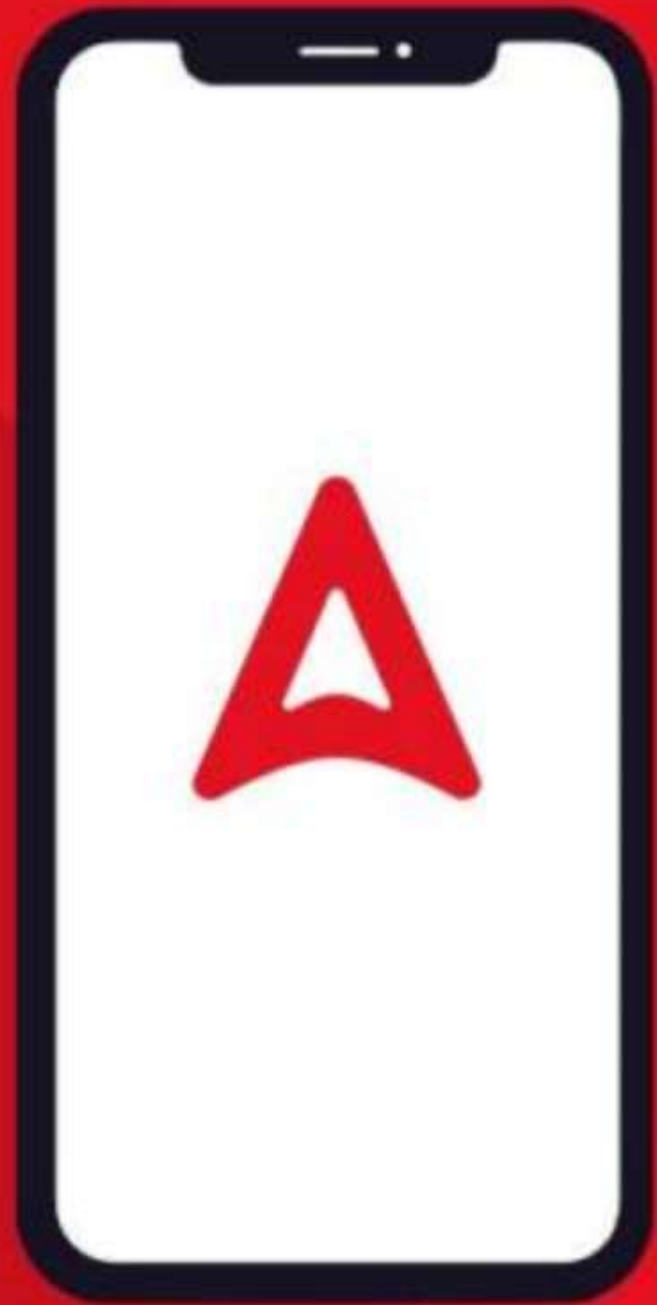

Play Store

**Download Now**

**Adda247 APP**

4694



Premium Study Material



Current Affairs



Job Alerts



Daily Quizzes



Subject-wise Quizzes



Magazines




Power Capsule



Notes & Articles



Videos

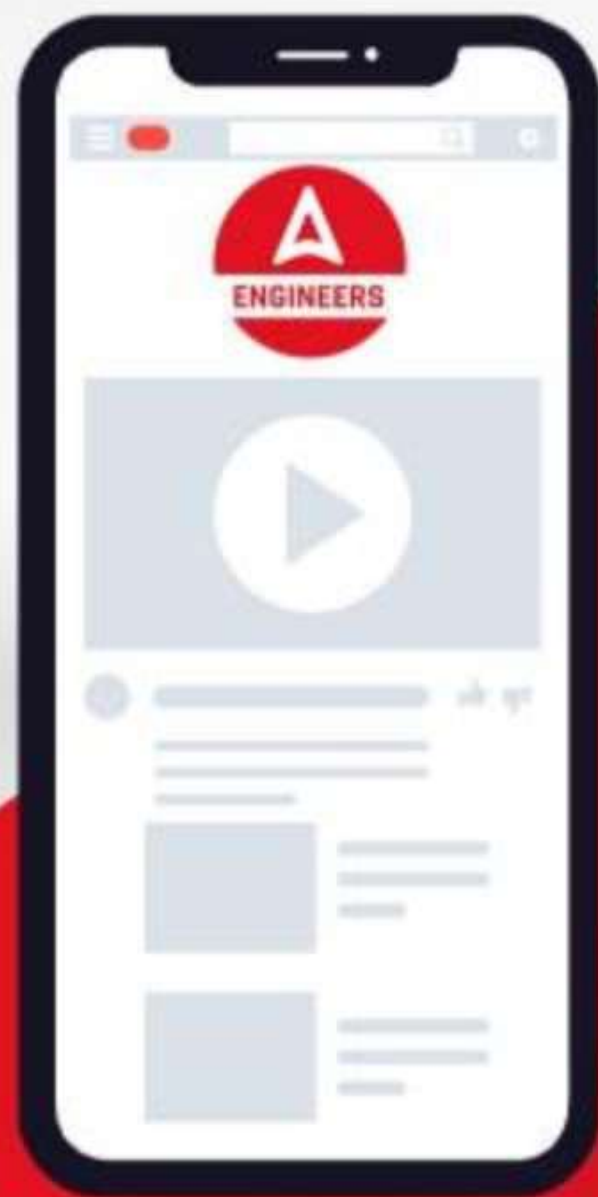

**SUBSCRIBE NOW**

**Engineers Adda247**  
YouTube Channel



THANKS FOR

# Watching

Adda247

LIKE



SHARE



COMMENT



SUBSCRIBE

