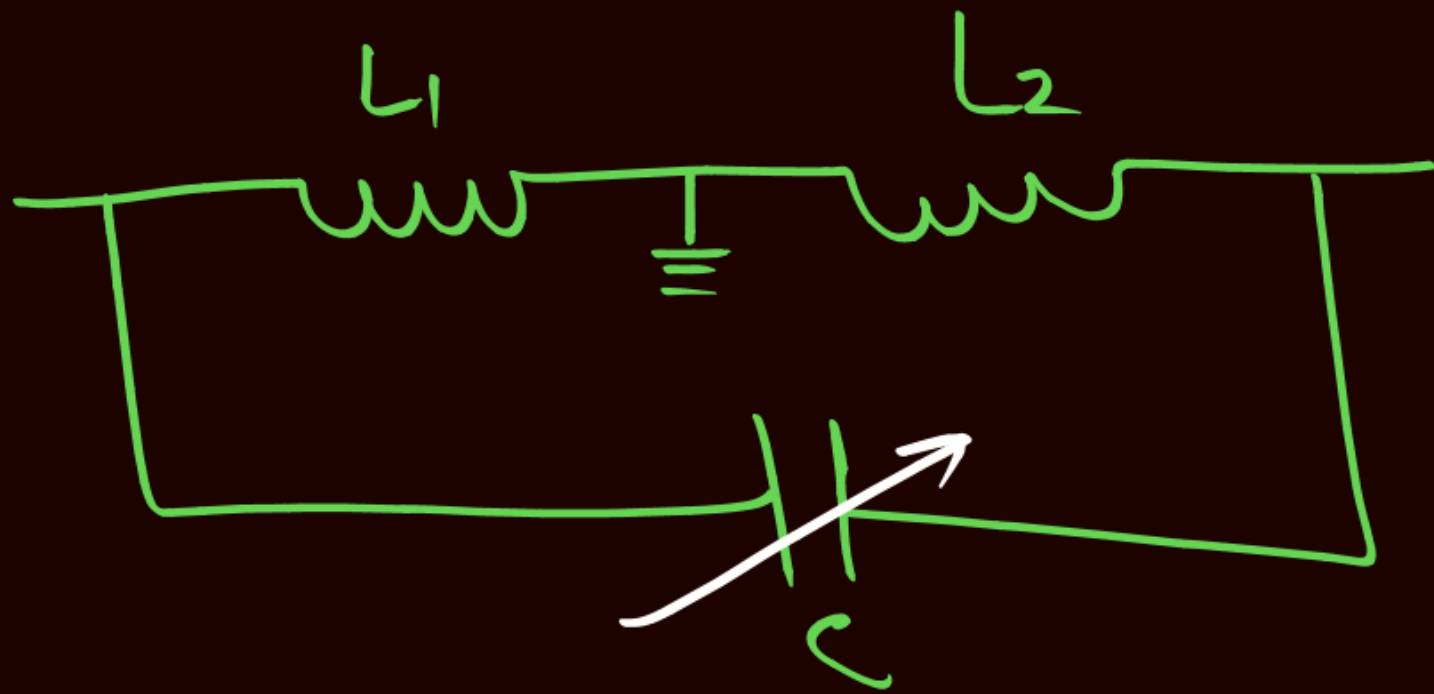


# Hartley Oscillator:

$$\omega_0 = \frac{1}{\sqrt{(L_1 + L_2)C}} \rightarrow \text{freq of Osc.}$$



Also called tapped inductor Oscillator

Working principle is parallel Resonance

Advantage:

Capacitor is used for tuning

Disadvantage:

circuit is bulky & Expensive  
due to inductor is used.


→ used as Local Oscillator at receivers.

# Colpitt Osc. :

$$Z_1 + Z_2 + Z_3 = 0$$

$$X_1 + X_2 + X_3 = 0$$
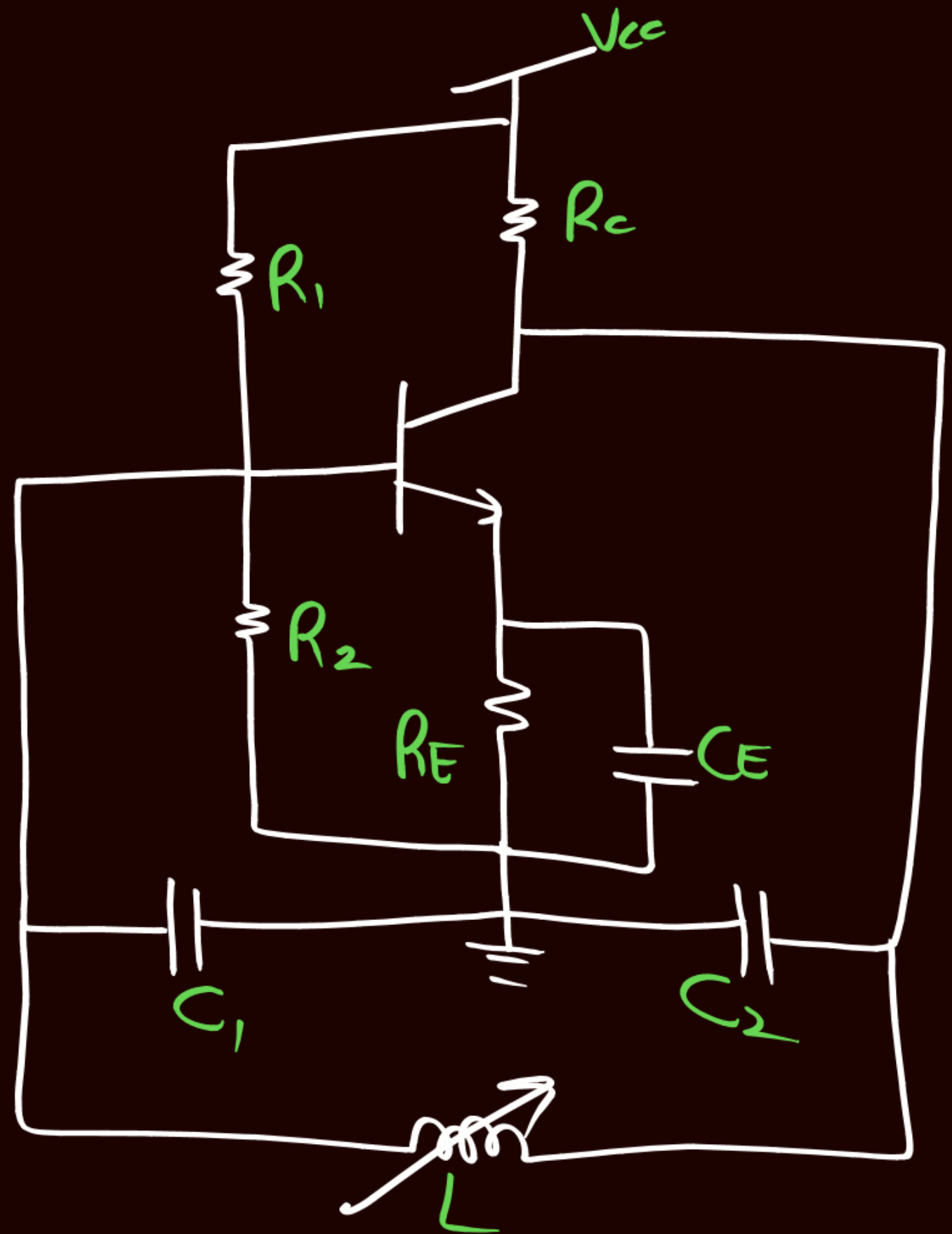
$$\frac{-1}{\omega_0 C_1} - \frac{1}{\omega_0 C_2} + \omega_0 L = 0$$



$$\omega_0 L = \frac{1}{\omega_0 C_1} + \frac{1}{\omega_0 C_2}$$


$$\omega_0 L = \frac{1}{\omega_0} \left[ \frac{1}{C_1} + \frac{1}{C_2} \right]$$

$$\omega_0^2 = \frac{1}{L} \left[ \frac{C_1 + C_2}{C_1 C_2} \right]$$

$$\omega_0 = \sqrt{\frac{1}{L} \left( \frac{C_1 + C_2}{C_1 C_2} \right)}$$

$$\omega_0 = \frac{1}{\sqrt{L \cdot \left( \frac{C_1 C_2}{C_1 + C_2} \right)}}$$
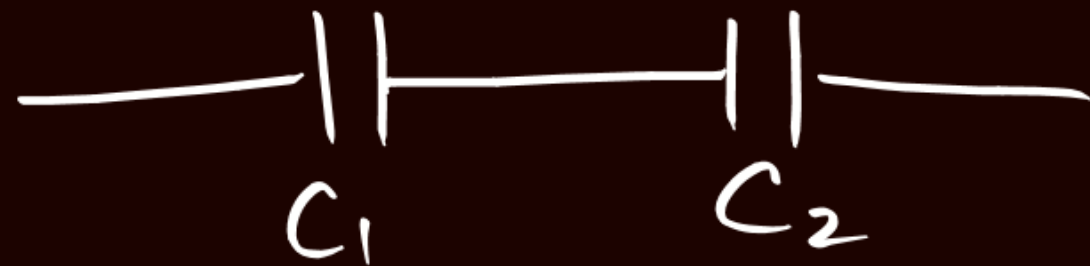
$$\omega_0 = \frac{1}{\sqrt{L \cdot C_T}}$$



$$C_T = \frac{C_1 C_2}{C_1 + C_2}$$

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2}$$

→ Working principle is Parallel Resonance.

Advantage:


→ It is smaller in size and economical

→ Better freq stability

Disadvantage:

→ Inductive tuning

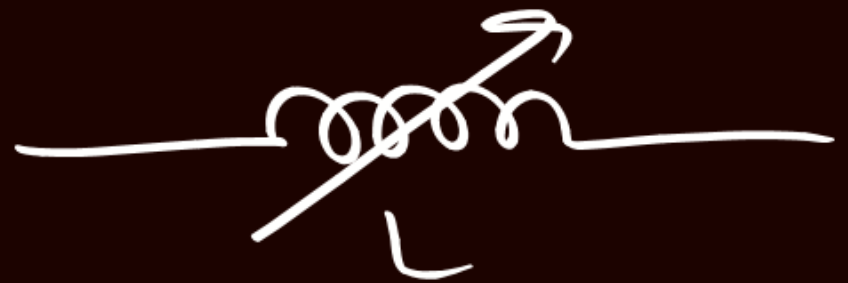
$$\omega_0 = \frac{1}{\sqrt{L \left( \frac{C_1 C_2}{C_1 + C_2} \right)}}$$





Application:

used as Local Oscillator at receiver.


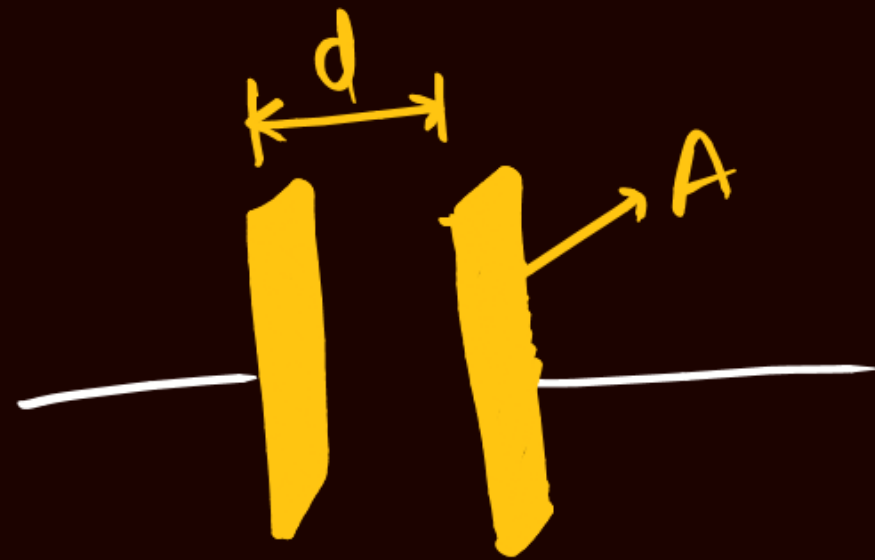


$$C = \frac{\epsilon A}{d}$$

$d \uparrow \Rightarrow C \downarrow$

$d \downarrow \Rightarrow C \uparrow$

# Clapp Oscillator:

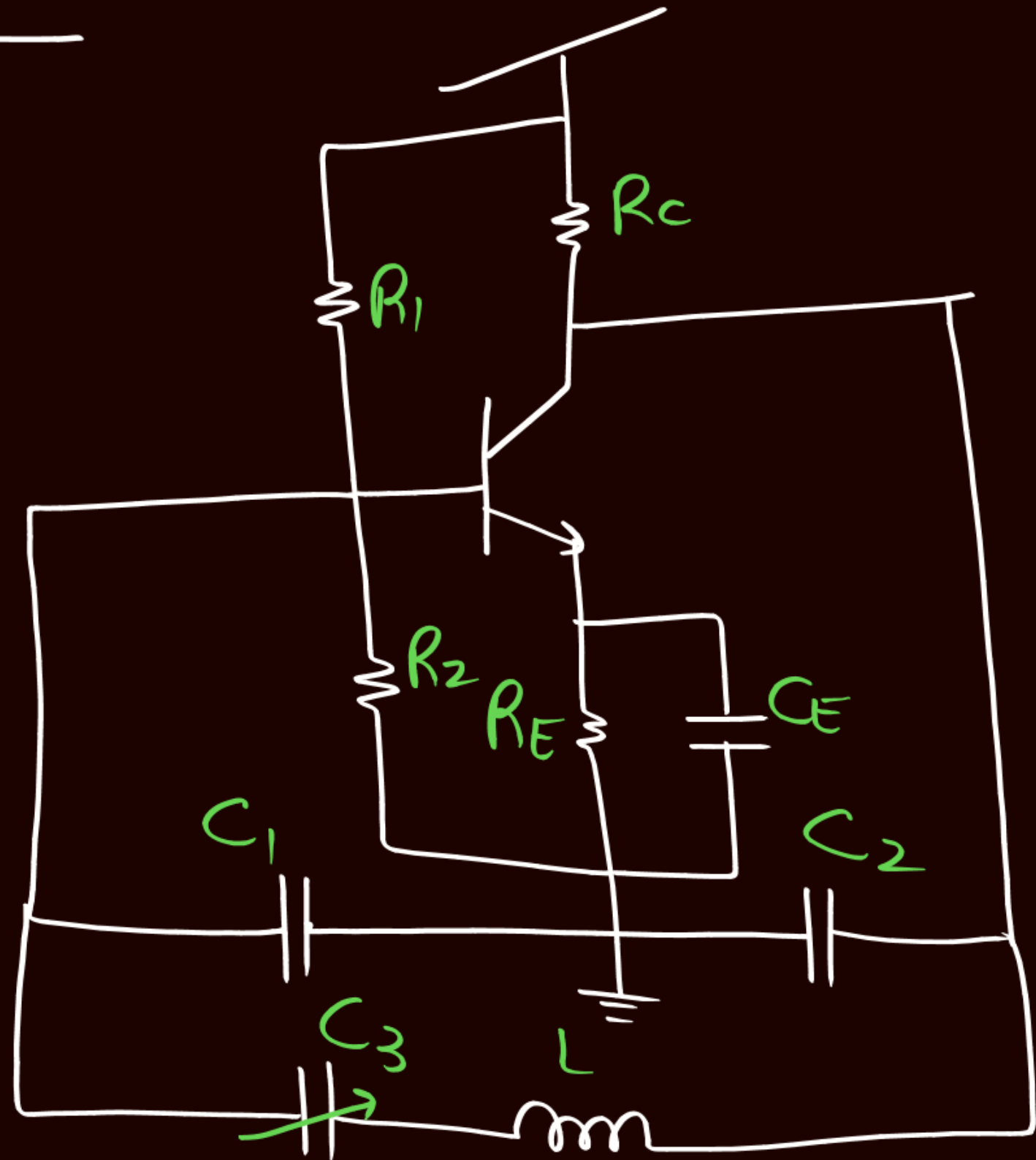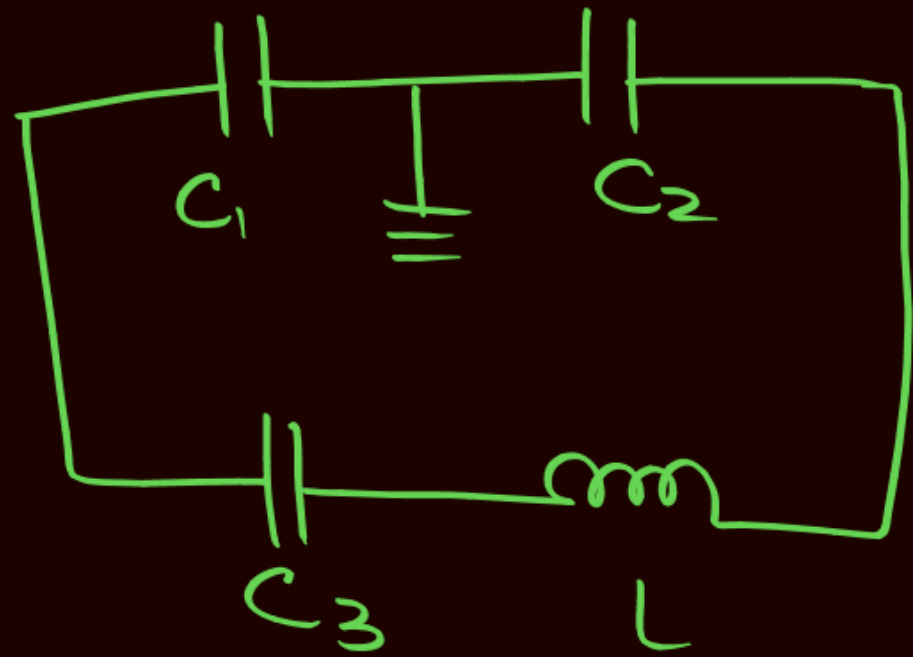

$$X_1 + X_2 + X_3 + X_4 = 0$$

$$-\frac{1}{\omega_0 C_1} - \frac{1}{\omega_0 C_2} - \frac{1}{\omega_0 C_3} + \omega_0 L = 0$$

$$\omega_0 L = \frac{1}{\omega_0} \left[ \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right]$$

\* 
$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\omega_0 L = \frac{1}{\omega_0 C_T}$$



$$\omega_0 = \frac{1}{\sqrt{L \cdot C_T}}$$

Working principle


→ Series Resonance

# Crystal Oscillator:

## Quartz crystal

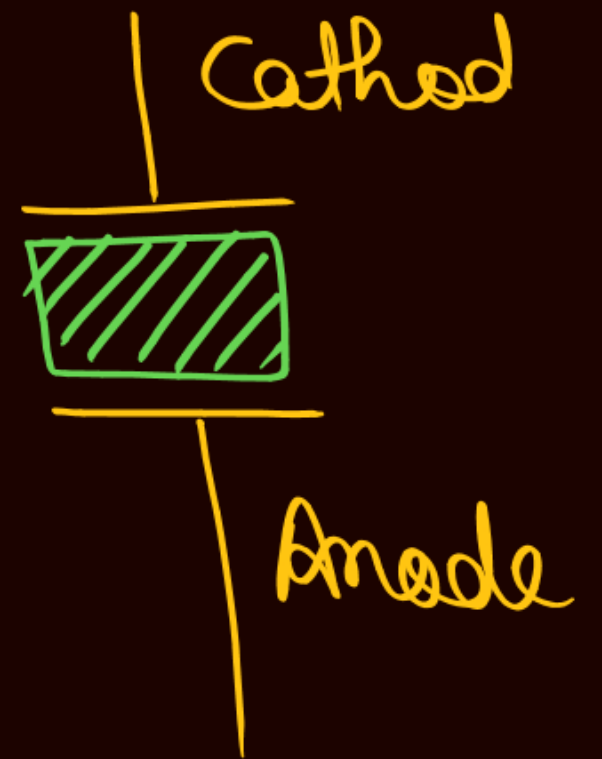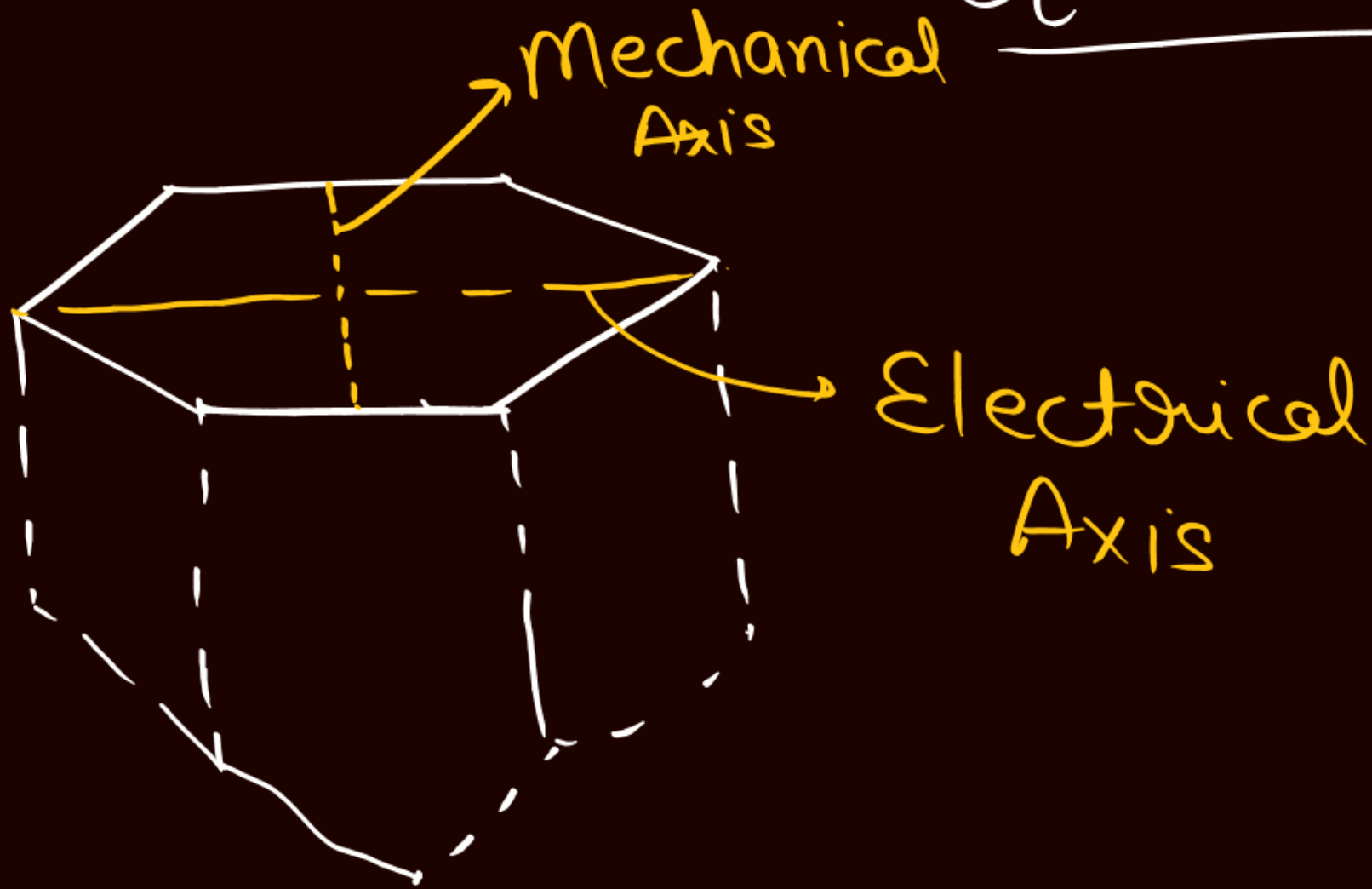

## Equivalent circuit:

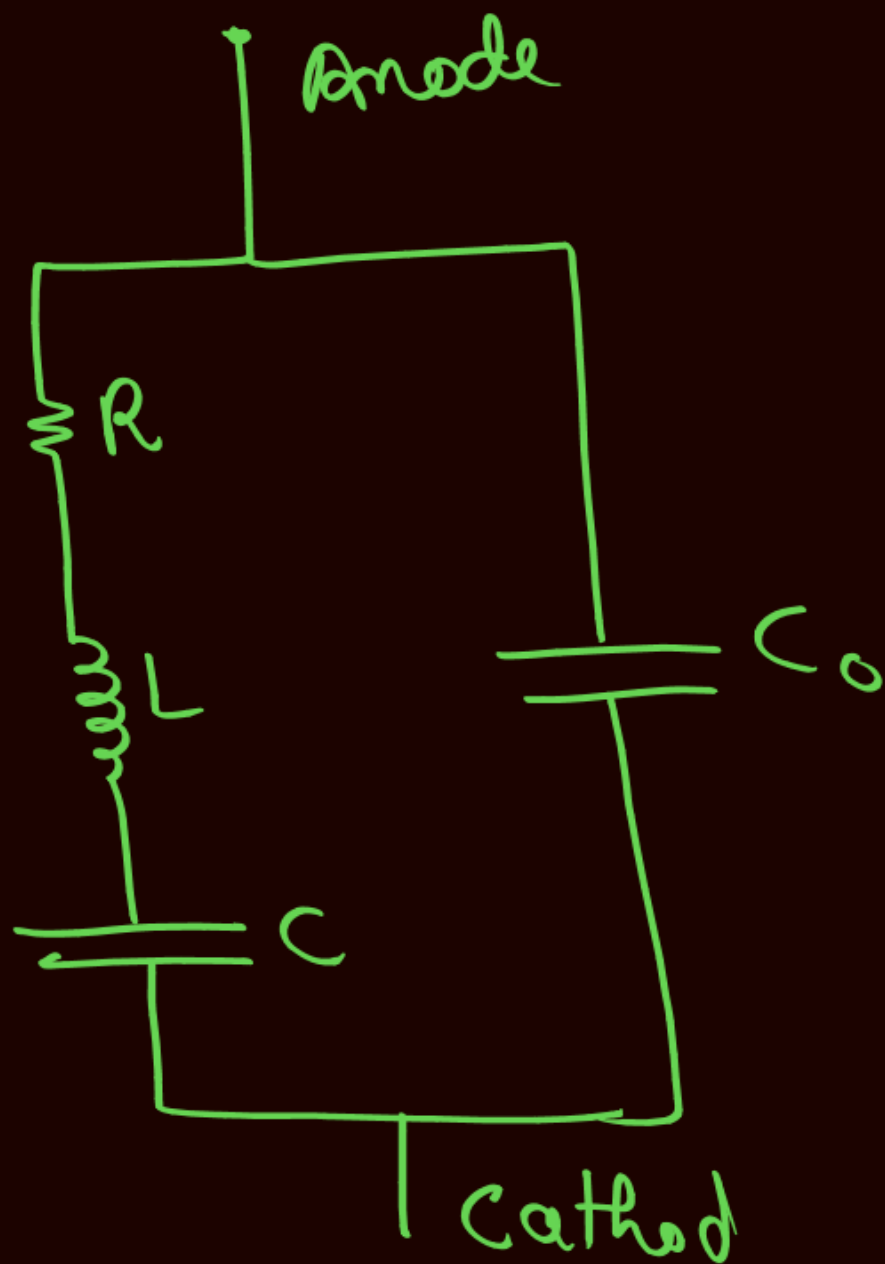

$R =$  Viscous Damping  
(circuit internal losses)

$L =$  mass of crystal

$C =$  Stiffness =  $\frac{1}{\text{Spring constant}}$

$C_0 =$  Capacitance b/w anode and Cathode

Series Resonance

$$\omega_s = \frac{1}{\sqrt{LC}}$$

Parallel Resonance

$$\omega_0 = \frac{1}{\sqrt{L \cdot C_{eq}}}$$

$$C_{eq} = \frac{C \cdot C_0}{C + C_0}$$

## Advantage:

- Excellent freq Stability
- Simplest RF Oscillator

## Disadvantage:

fixed freq type Osc.






Used as

→ to generate carrier signal in AM  
and FM transmission.

→ Designing of timer circuit.

Sinusoidal Oscillator:

The End

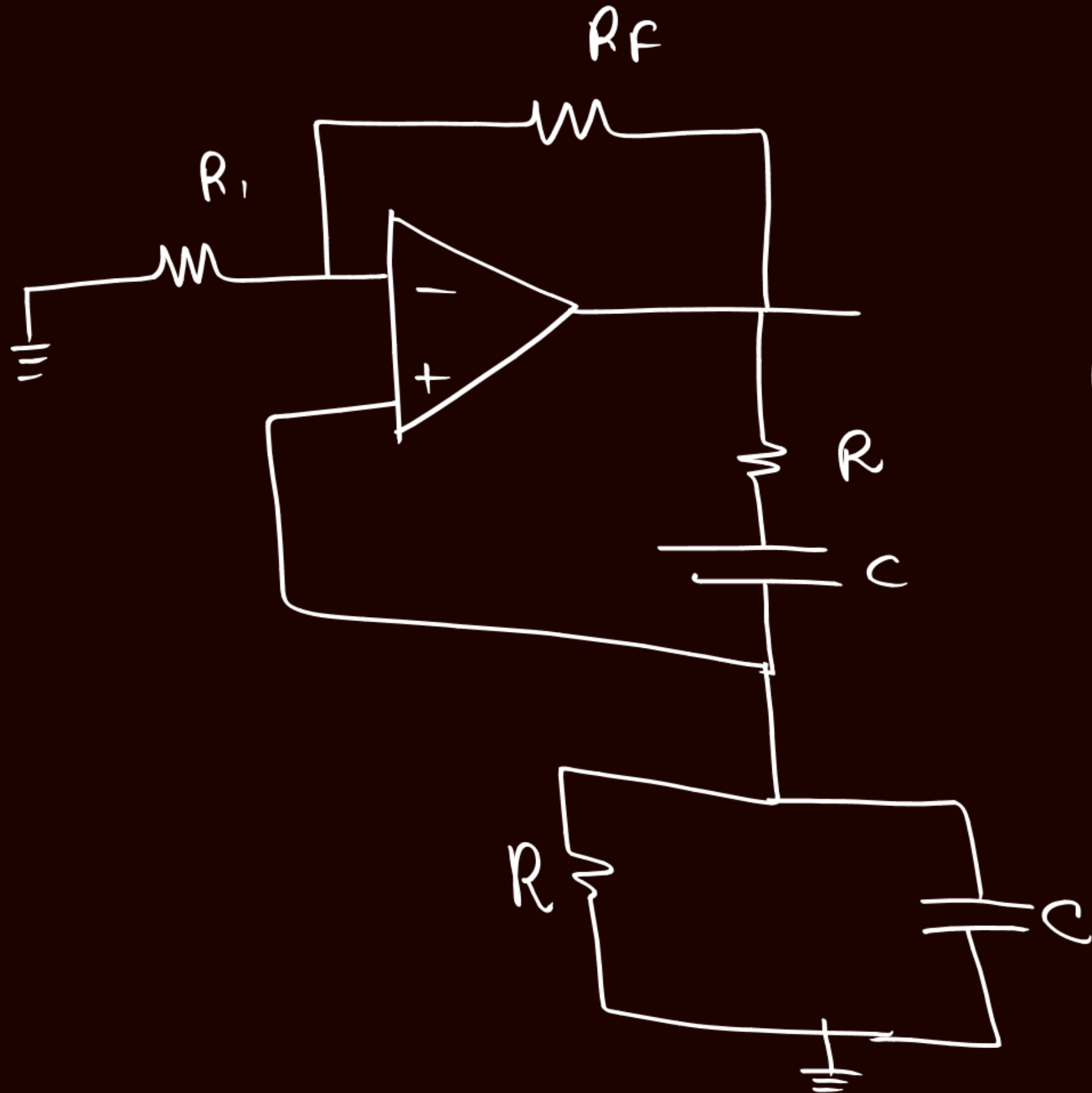

Name = Wein-Bridge  
Osc

Oscillation freq

$$\omega_0 = \frac{1}{RC}$$

Condition of Osc:

$$R_F = 2R_1$$

