
 


## GATE 2023 Electronics Engineering

 **Q1.** In a given sequential circuit initial state are  $Q_1 = 1$  and  $Q_2 = 0$ . For a clk frequency of 1 MHz, the frequency of signal  $Q_2$  in KHz is \_\_\_\_\_.



**Q2.** The switch  $S_1$  was closed and  $S_2$  was open for a long time. At  $t = 0$  switch  $S_1$  is opened and  $S_2$  is close simultaneously. The value of  $I_C(0^+)$  in amp is




- (a) -1
- (b) 0.2
- (c) 1
- (d) 0.8

**Q3.** The state equation of 2<sup>nd</sup> order system is  $\dot{x}(t) = Ax(t)$ ,  $x(0)$  is the initial condition suppose  $\lambda_1$  and  $\lambda_2$  are two distinct eigen values of A and  $V_1$  and  $V_2$  are the corresponding eigen vectors. For constant  $\alpha_1$  and  $\alpha_2$ , the solution  $x(t)$  of the state equation is


- (a)  $\sum_{i=1}^2 \alpha_i e^{4\lambda_i t} V_i$
- (b)  $\sum_{i=1}^2 \alpha_i e^{2\lambda_i t} V_i$
- (c)  $\sum_{i=1}^2 \alpha_i e^{\lambda_i t} V_i$
- (d)  $\sum_{i=1}^2 \alpha_i e^{3\lambda_i t} V_i$

 **Q4.** A closed loop system is shown in the figure where  $k > 0$  and  $\alpha > 0$ . The steady state error due to ramp input ( $R(s) > \alpha/S^2$ ) is given by



- (a)  $\frac{\alpha}{4k}$   
 (b)  $\frac{2\alpha}{k}$   
 (c)  $\frac{\alpha}{2k}$   
 (d)  $\frac{\alpha}{k}$

 
Q5. The value of the integral  $\iint xy \, dx \, dy$  over the region R, given in the figure, is \_\_\_\_.



Q6. Let  $x$  be  $n \times 1$  real column vector with length  $L = \sqrt{x^T x}$ . The trace of matrix  $P = xx^T$  is

- (a)  $L^2/2$   
 (b)  $L^2$   
 (c)  $L^2/4$   
 (d)  $L$

 
Q7. In the full block diagram  $R(s)$  and  $D(S)$  are 2 inputs. The opposite  $Y(S)$  is expressed as  $T(S) = G_1(S) R(S) + G_2(S) D(S)$ ,  $G_1(S)$  and  $G_2(S)$  are given by



- (a)  $G_1(S) = \frac{G(S)}{1+G(S)+G(S)H(S)}$  and  $G_2(S) = \frac{G(S)}{1+G(S)+G(S)H(S)}$   
 (b)  $G_1 = \frac{G}{1+G+GH}$   $G_2 = \frac{G}{1+G+H}$   
 (c)  $G_1 = \frac{G}{1+G+H}$   $G_2 = \frac{G}{1+G+H}$   
 (d)  $G_1 = \frac{G}{H+G+H}$   $G_2 = \frac{G}{1+G+GH}$

Q8. A sample and hold circuit is complemented using a resistive RAT switch and a capacitor with time constant of  $1 \mu s$ . The time 2 m for the sampling switch to stay closed to charge a capacitor adequately to a full scale voltage of 1 V with 12-bit accuracy is \_\_\_\_\_  $\mu s$ .

 **Q9.** In the circuit shown below  $D_1$  and  $D_2$  are silicon diodes with cut in voltage of 0.7V  $V_{IN}$  and  $V_{OUT}$  are input and output voltage in volt. The T.C. is




- (a)
- (b)
- (c)
- (d)




**Q10.** The value of line integral  $\int_P^Q (Z^2 dx + 3y^2 dy + 2xz dz)$  along the straight line joined the points  $P(1, 1, 2)$  and  $Q(2, 3, 1)$  is

- (a) 20
- (b) -5
- (c) 29
- (d) 24

 
**Q11.** The asymptotic magnitude Bode plot of a minimum phase system is shown in the figure. The T.F of the system is  $G(S) = \frac{K(S+Z)^a}{S^b(S+P)^c}$  where  $K, Z, p, a, b$  and  $c$  are positive constants. The value of  $(a + b + c)$  is



 
**Q12.** In the circuit below, the voltage  $V_C$  is \_\_\_\_\_ V.



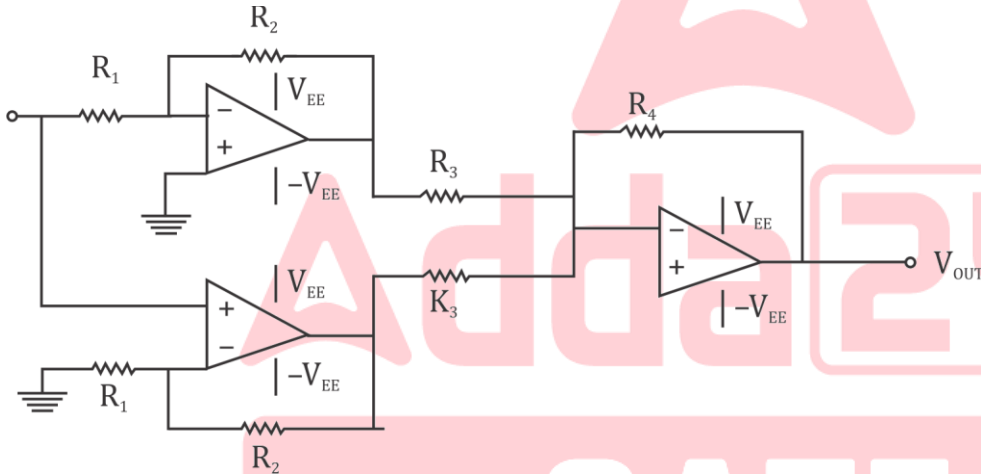**Q13.** The  $\frac{V_{OUT}}{V_{IN}}$  of the circuit shown below is




 **Q14.** The synchronous sequential circuit shown below works at a circuit frequency of 1 GHz. The through put in M bitts, and the latency in nS respectively are




- (a) 333.333, 1
- (b) 333.33, 3
- (c) 2000, 3
- (d) 1000, 3

 **Q15.** For the circuit shown below, the propagation delay of each NAND Gate is 1 ns. The critical path delay, in ns is –




 **Q16.** In the circuit shown below, P and Q are the inputs. The logical function realized by the circuit shown below is




- (a)  $Y = P + Q$
- (b)  $Y = \overline{P + Q}$
- (c)  $Y = \overline{PQ}$
- (d)  $Y = PQ$

 **Q17.** In the circuit shown below, the current  $i$  flowing through  $200 \Omega$  resistor is \_\_\_\_\_.



 **Q18.** In the circuit shown below, switch  $S$  was closed for a long time. If switch is opened at  $t = 0$  the maximum magnitude of the voltage  $V_R$  in volt is \_\_\_\_\_.



**Q19.** The voltage of contour integral  $\oint_c \left( \frac{z+z}{z^2+2z+z} \right) dt$ , where the contour  $C$  is  $\left\{ Z: \left| Z + 1 - \frac{3}{2}i \right| = 1 \right\}$ , taken in the counter clockwise direction is

- (a)  $\pi(1 - j)$
- (b)  $-\pi(1 - j)$
- (c)  $-\pi(1 + j)$
- (d)  $\pi(1 + j)$

**Q20.** The open loop T.F of a unity negative f/b system is  $G(S) = \frac{K}{S(1+ST_1)(1+ST_2)}$  where,  $K, T_1, T_2$  are positive constants. The phase cross over frequency in rad/sec.

- (a)  $\frac{1}{T_2\sqrt{T_1}}$
- (b)  $\frac{1}{\sqrt{T_1T_2}}$
- (c)  $\frac{1}{T_1\sqrt{T_2}}$
- (d)  $\frac{1}{T_1T_2}$

**Q21.** Let  $V_1 = \begin{bmatrix} 1 \\ 2 \\ 0 \end{bmatrix}$  and  $V_2 = \begin{bmatrix} 2 \\ 1 \\ 3 \end{bmatrix}$  be two vectors. The value of coefficient  $\alpha$  is the expression  $V_1 = \alpha V_2 + e$ .

Which minimizes the length of error vector is,

- (a)  $-\frac{2}{7}$
- (b)  $\frac{7}{2}$
- (c)  $-\frac{7}{2}$
- (d)  $\frac{2}{7}$


**Q22.** A series RLC circuit has a Quality factor  $Q$  of 1000 at a centre frequency of  $10^6$  rad/sec. The possible value of RLC are

- (a)  $R = 0.001 \Omega, L = 1\mu H$  and  $C = 1 \mu F$
- (b)  $R = 1\Omega, L = 1\mu H$  and  $C = 1\mu H$
- (c)  $R = 0.01 \Omega, L = 1 \mu H$  and  $C = 1\mu F$
- (d)  $R = 0.1 \Omega, L = 1 \mu H$  and  $C = 1 \mu F$

**Q23.** Let the given vector of the matrix  $B$  be  $\{\lambda_K | 1 \leq K \leq n\}$  and  $\{V_K | 1 \leq K \leq n\}$ , respectively. For any invertible matrix  $P$ , the sets of eigen value and eigen vector of matrix  $A$ , where  $B = P^{-1}AP$ , respectively are

- (a)  $\{\lambda_K | 1 \leq K \leq n\}$  and  $\{V_K | 1 \leq K \leq n\}$
- (b)  $\{\lambda_K \det(A) | 1 \leq K \leq n\}$  and  $\{Pv_K | 1 \leq K \leq n\}$
- (c)  $\{\lambda_K | 1 \leq K \leq n\}$  and  $\{PV_K | 1 \leq K \leq n\}$
- (d)  $\{\lambda_K | 1 \leq K \leq n\}$  and  $\{P^+V_K | 1 \leq K \leq n\}$

 **Q24.** In the circuit shown below  $V_1$  and  $V_2$  are bias voltage. Based on input and output impedance the circuit behave as



- (a) Voltage control source
- (b) VCCS
- (c) CCCS
- (d) CCVS

**Q25.** For the 2-port network shown below, the  $[Y]$  – parameter is given as  $[Y] = \frac{1}{100} \begin{bmatrix} 2 & -1 \\ -1 & 4/3 \end{bmatrix} S$

The value of load impedance in  $\Omega$ , for maximum power transfer will be \_\_\_\_\_.



**Q26.** A cascade of common source amplifier in a unity gain feedback configuration oscillate when

- (a) Closed loop gain is greater than 1 and phase shift is less than  $180^\circ$
- (b) Closed loop gain is less than 1 and phase shift is greater than  $180^\circ$
- (c) Closed loop gain is less than 1 and phase shift is less than  $180^\circ$
- (d) Closed loop gain is greater than 1 and phase shift is greater than  $180^\circ$