



RRB JE | SSE 2023

Foundation Batch

Analog Electronics

Day-2

> LIVE

1 PM

LAWRENCE Sir



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount

Adda247

WELCOME
TO Adda247

We are limitless

APP FEATURES



4694

Playstore

Download Now
Adda247 APP



Premium Study Material



Current Affairs



Job Alerts



Daily Quizzes



Subject-wise Quizzes



Magazines




Power Capsule



Notes & Articles




Videos

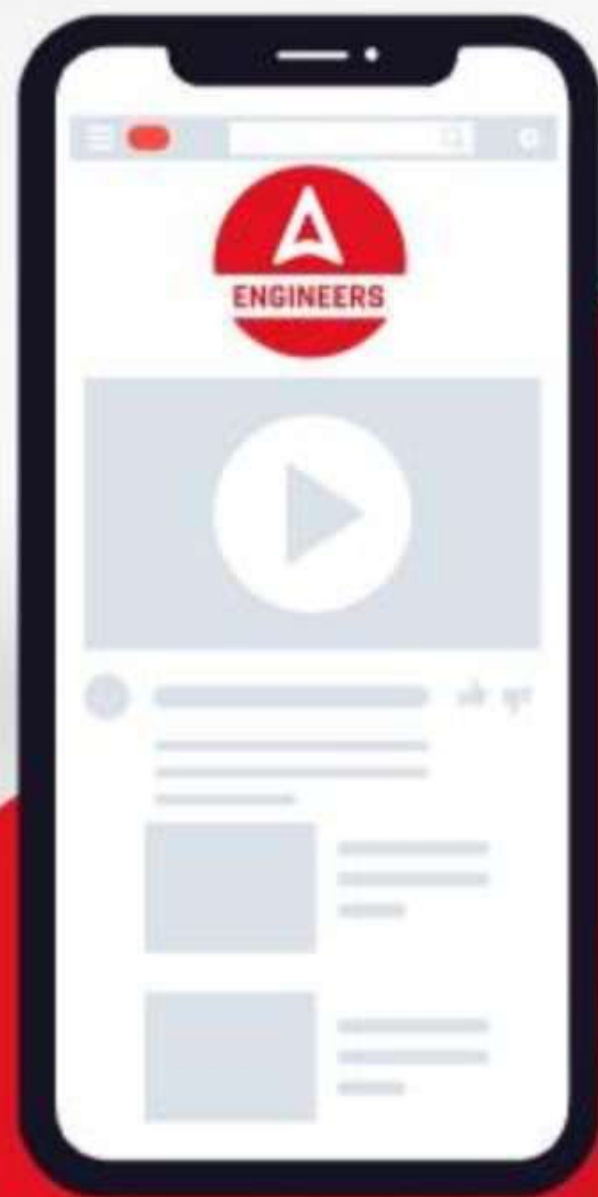


SUBSCRIBE NOW

Engineers Adda247
YouTube Channel

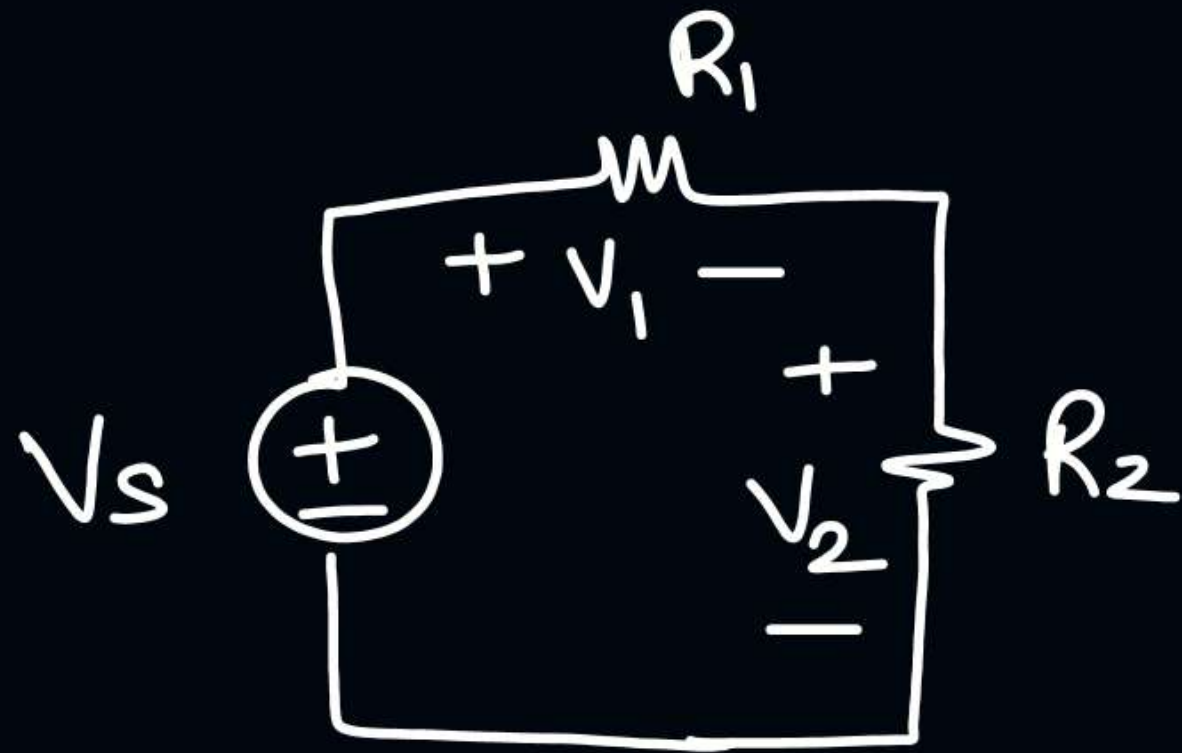

$$V_2 = \frac{R_2}{R_1 + R_2} \cdot V_s$$

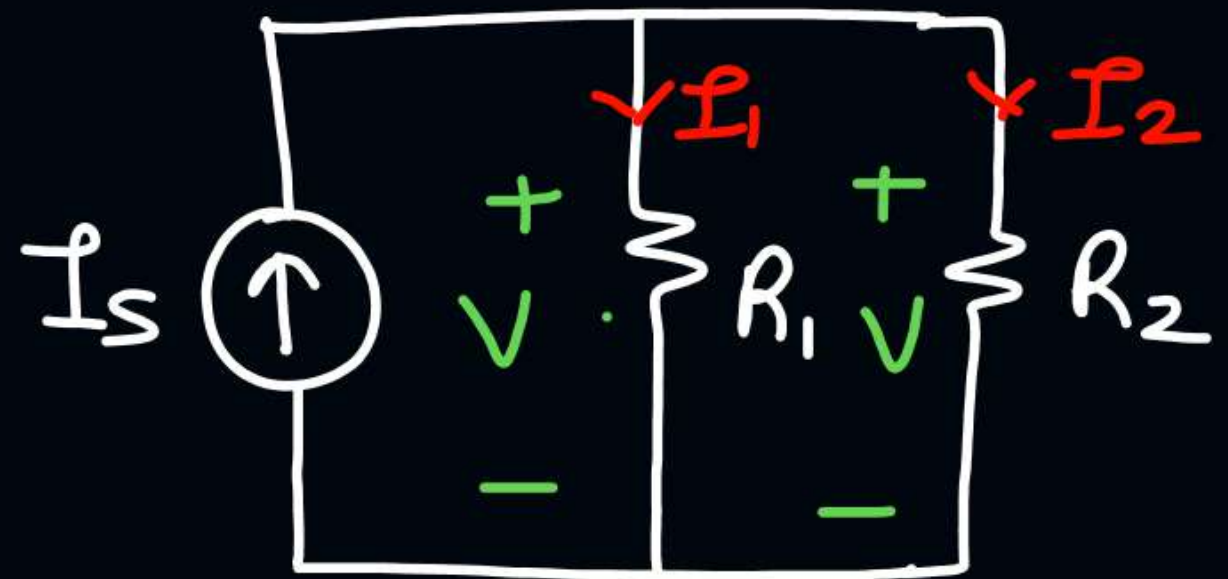
$$V_1 = \frac{R_1}{R_1 + R_2} \cdot V_s$$



$$I_1 = \frac{R_2}{R_1 + R_2} \cdot I_s$$

$$I_2 = \frac{R_1}{R_1 + R_2} \cdot I_s$$

Type of Amplifier:

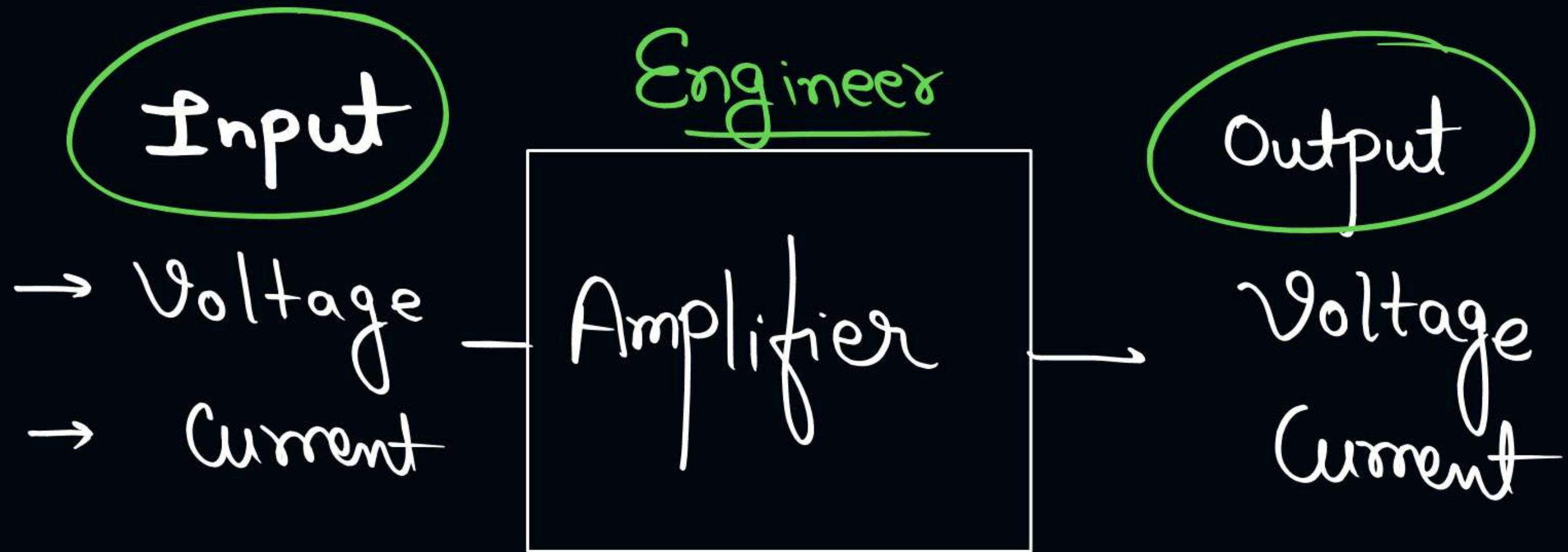

①

Input \rightarrow Voltage

Output \rightarrow Voltage



① Voltage Amplifier

$$\text{Gain} = \frac{\text{Output}}{\text{Input}} = \frac{V_o}{V_i} \quad \frac{\text{volt}}{\text{volt}}$$

$$\text{Gain} = \frac{V_o}{V_i} \quad (\text{unit less})$$

Input \rightarrow Current
Output \rightarrow Voltage



$$\text{Gain} = \frac{\text{Output}}{\text{Input}}$$

$$\text{Gain} = \frac{V_o}{I_i} \quad \frac{\text{volt}}{\text{amp}} \quad \text{or} \quad \Omega$$

$$R_m = \frac{V_o}{I_i} \quad \Omega$$

Resistor

transistor
Amplifier

3: Input = Voltage

Output = Current



$$\text{Gain} = \frac{\text{Output}}{\text{Input}}$$

$$\text{Gain} = \frac{I_o}{V_i} \quad \frac{\text{amp}}{\text{volt}}$$

or Ω $\xrightarrow{\text{Conductance}}$ $G = \frac{1}{R}$

$$G_m = \frac{I_o}{V_i} \quad \Omega$$


Trans conductance
Amplifier

Input \rightarrow current
Output \rightarrow current



$$\text{Gain} = \frac{P_o}{P_i} \frac{\text{amp}}{\text{amp}} \quad (\text{unit less})$$

∴ Current Amplifier

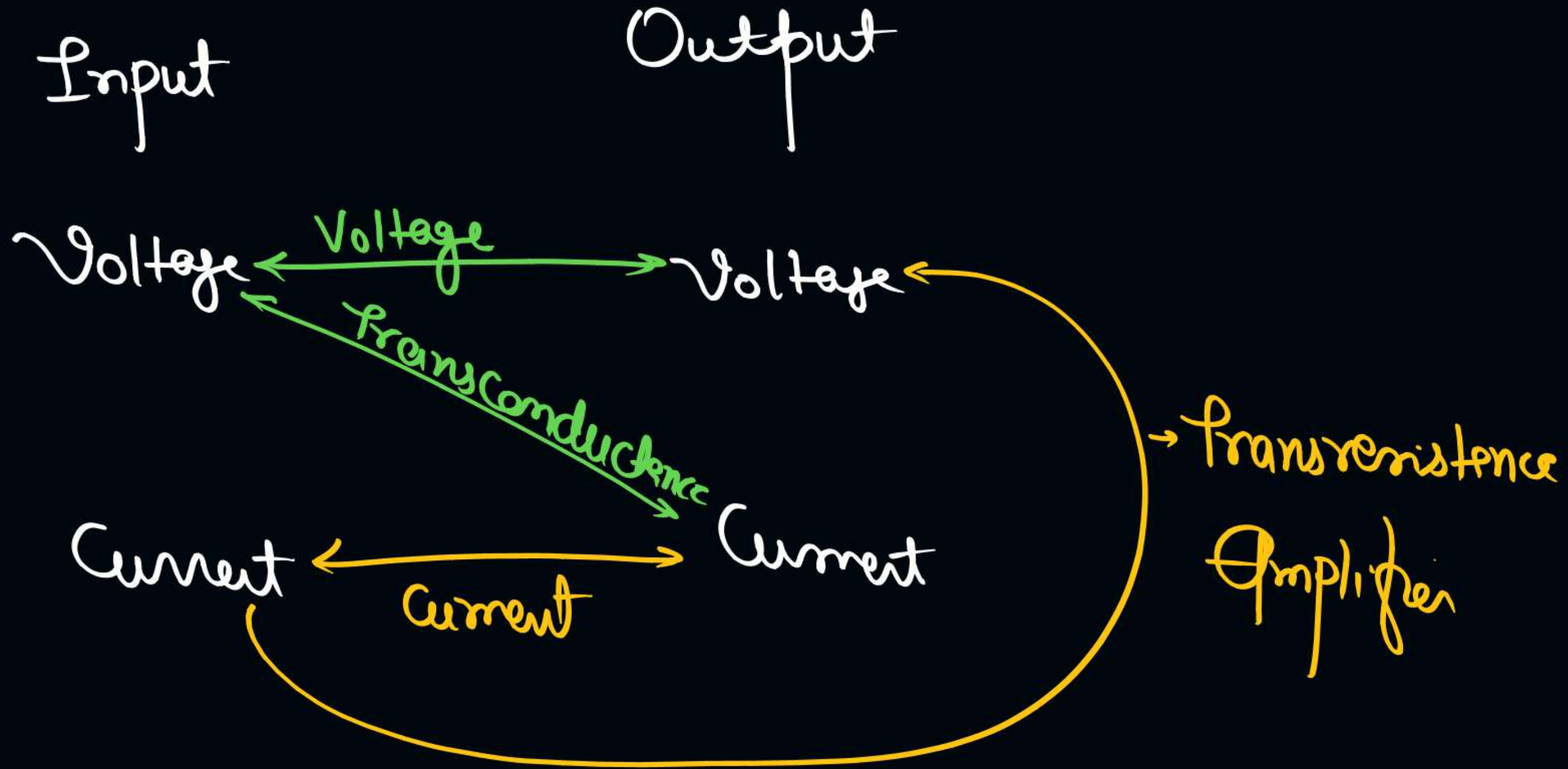

Amplifier	Input	Output	Gain
Voltage	v_i	v_o	$\frac{v_o}{v_i}$ (unit less)
Transconductance $G = (\Omega^{-1})$	v_i	i_o	$\frac{i_o}{v_i}$ (Ω^{-1})
Transresistance $R (\Omega)$	i_i	v_o	$\frac{v_o}{i_i}$ (Ω)
Current	i_i	i_o	$\frac{i_o}{i_i}$ (unit less)

Q: The unit of Transconductance Amplifier is

a) Ω (ohm)


b) unit less

c) Ω (mho)


d) amp



Voltage Source

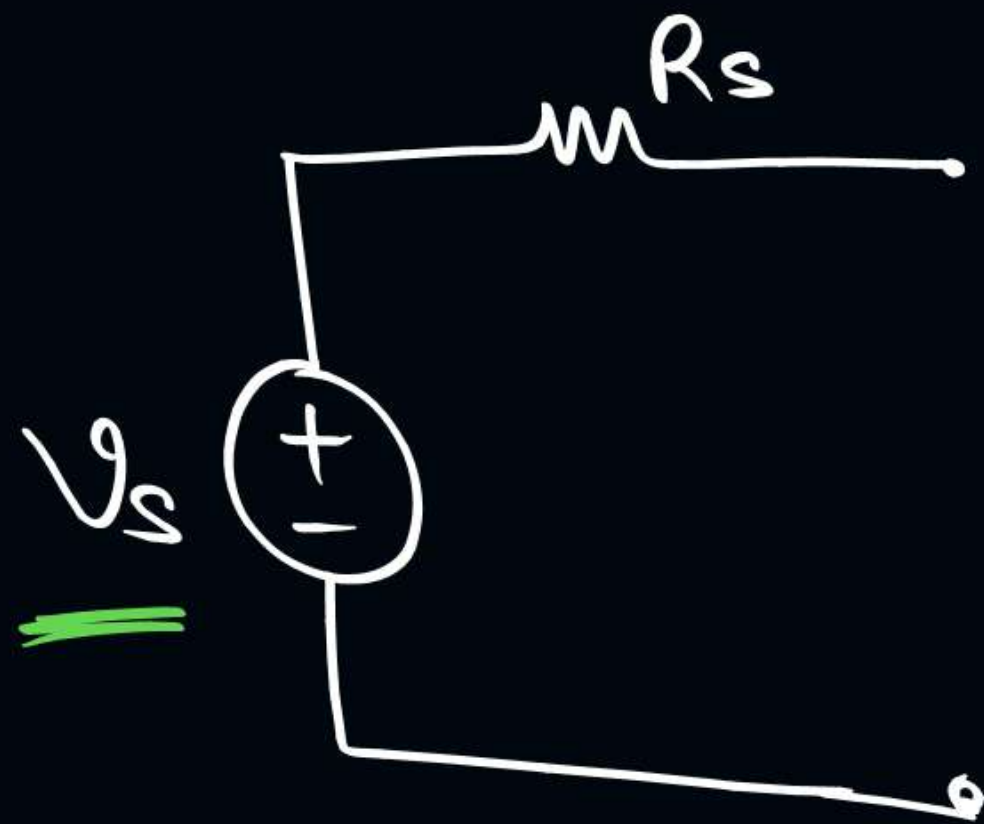


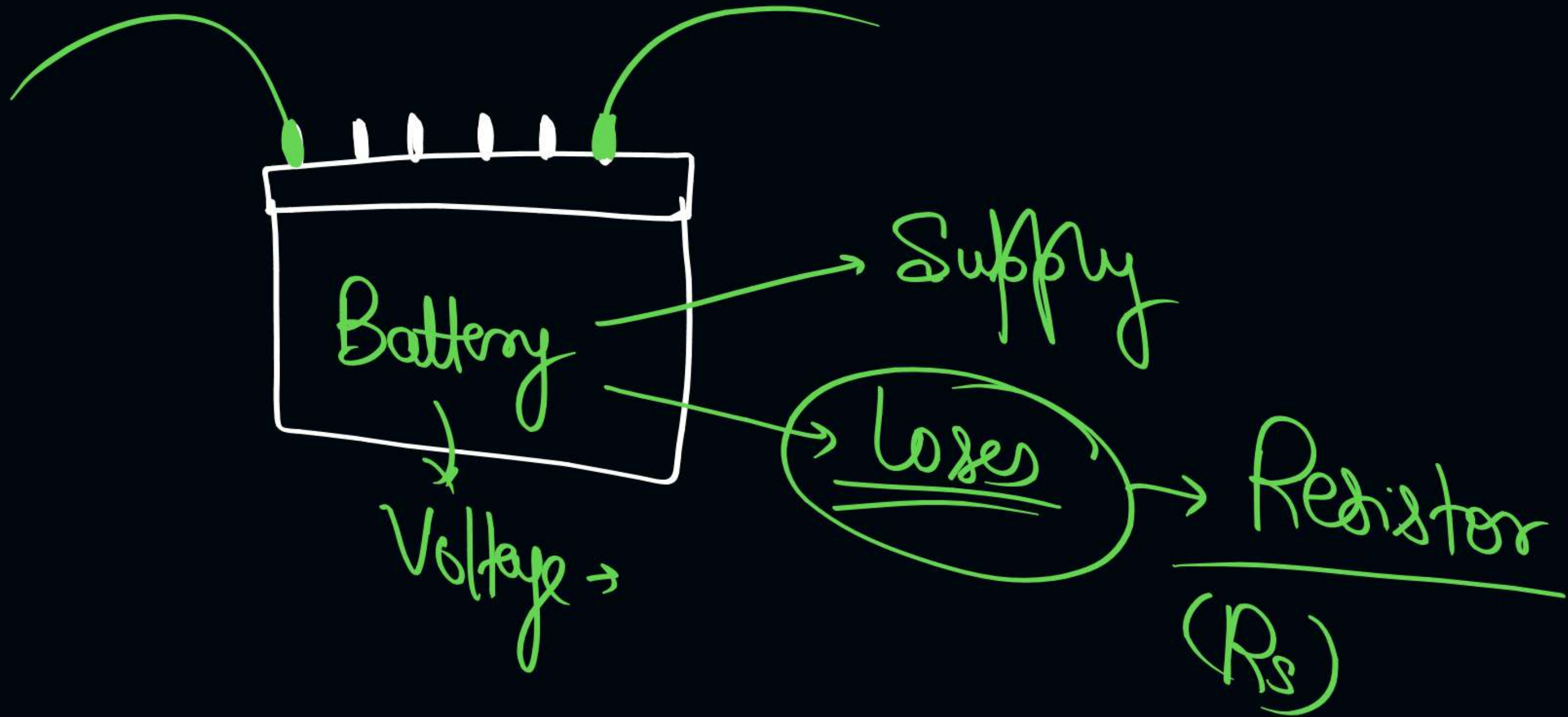When, $R_s \rightarrow$ Internal Resistance of Voltage Source.
 \rightarrow Practical Voltage Source




Ideal Voltage Source:

$$R_s = 0$$

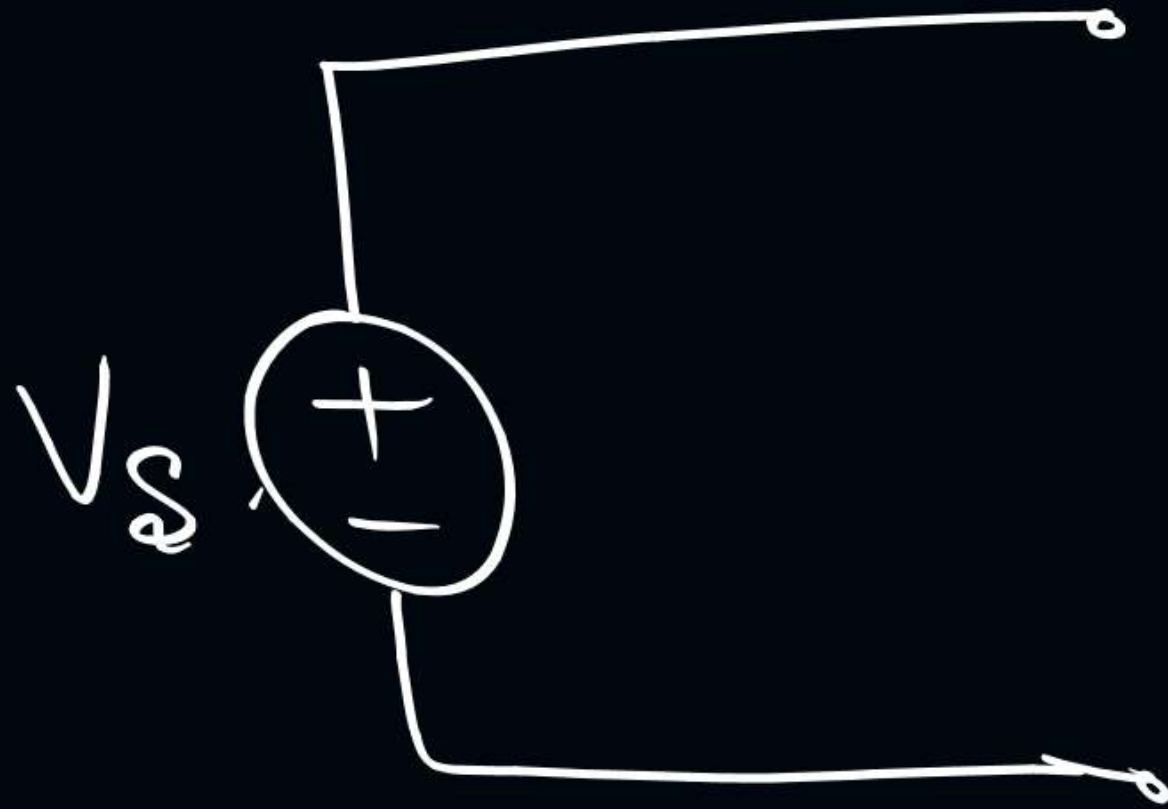


Ideal Voltage
Source

Current Source: → Current

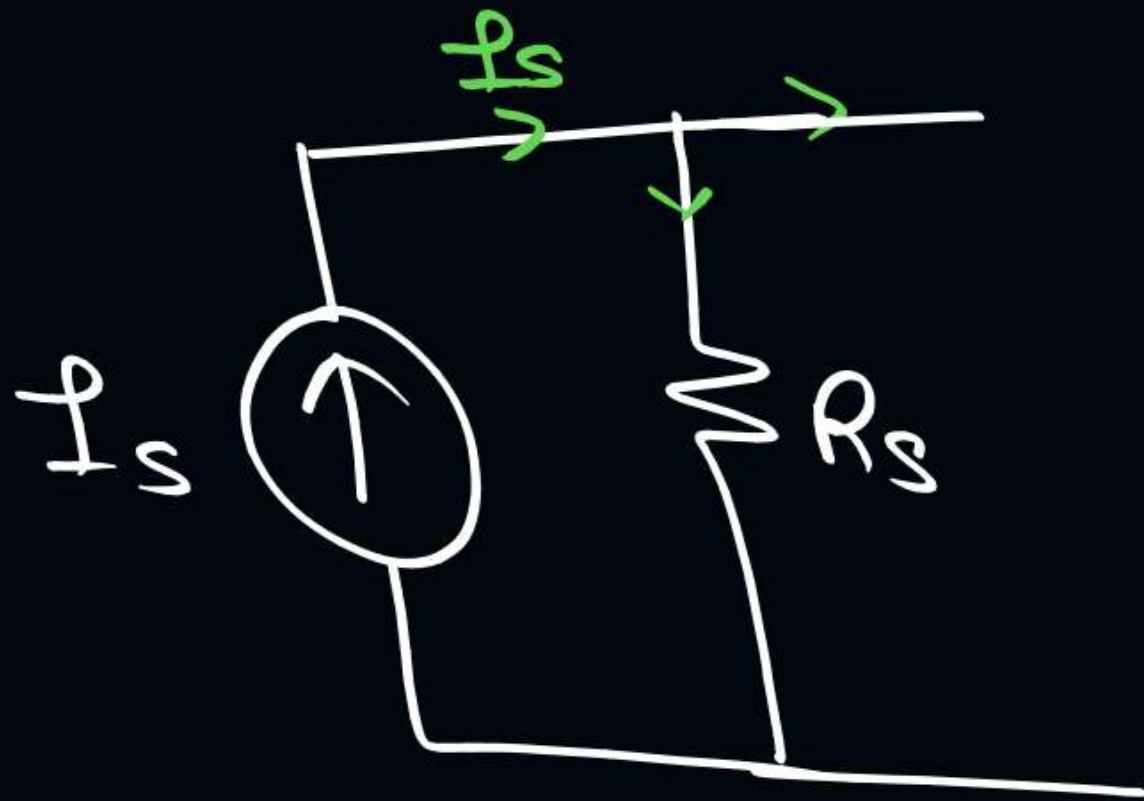

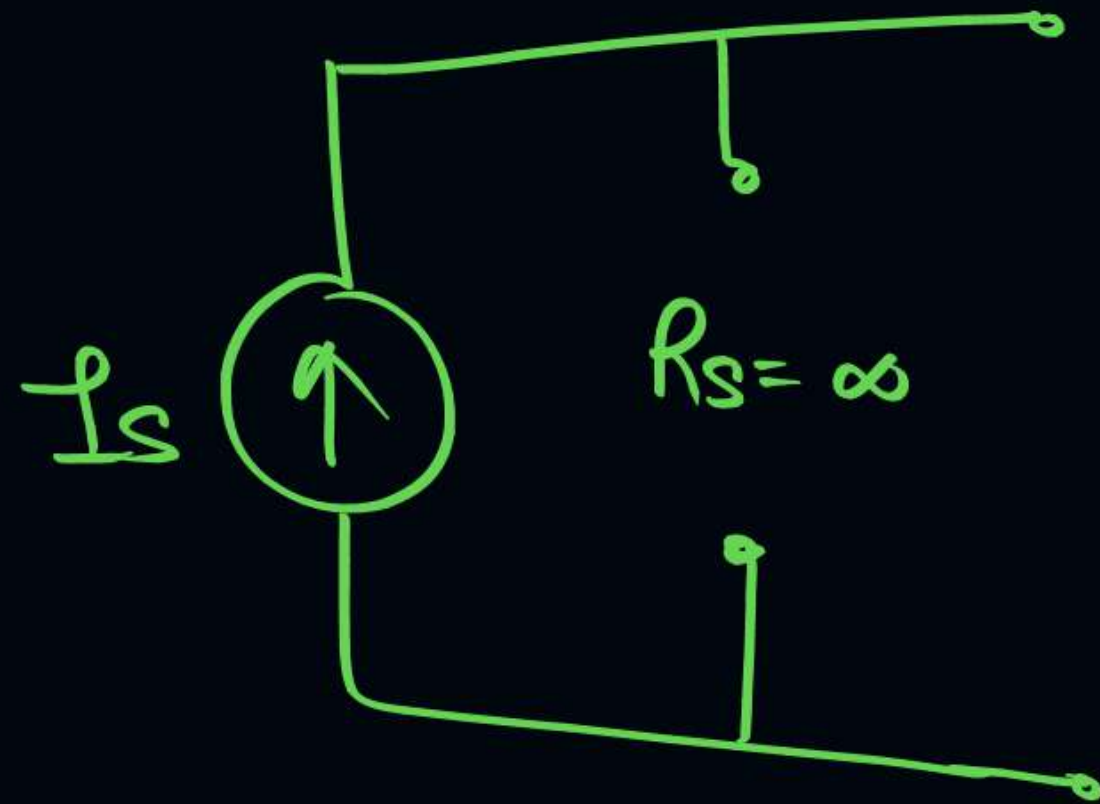
R_s → Internal Resistance
of Current Source



→ Ideal Current Source


$$R_s = \infty \Omega$$

Ideal Voltage

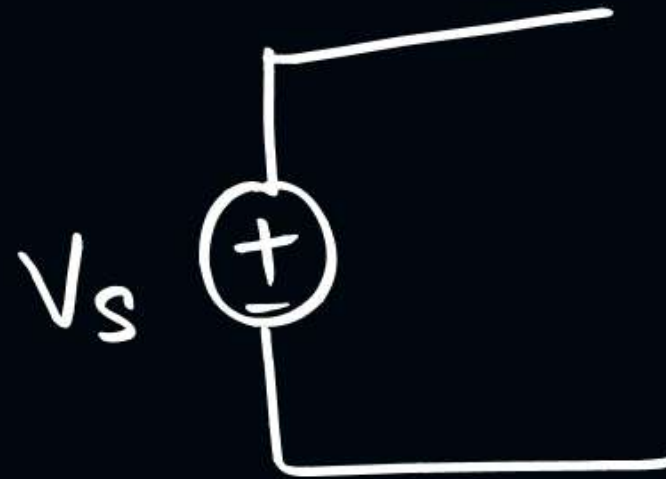


$$R_s = 0$$

Practical Voltage Source

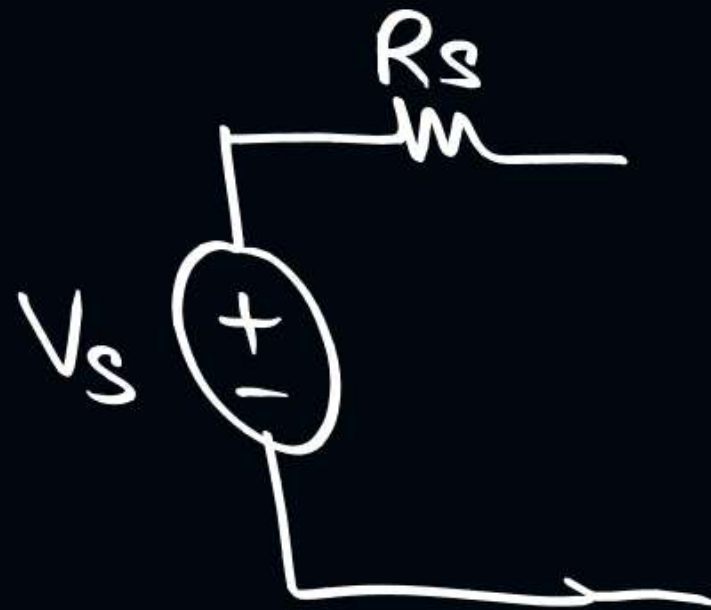

$$\underline{R_s = v.v. \text{ low}}$$


Ideal Current

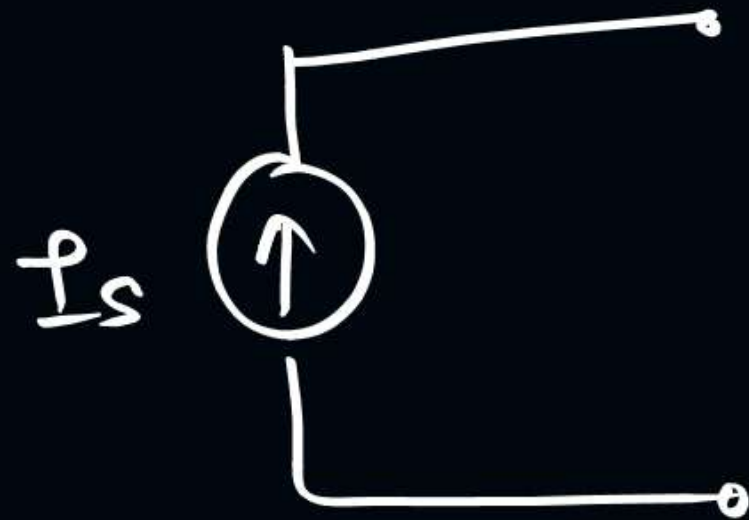

Internal Resistance

$$R_s = \infty$$

Practical
Current
Source

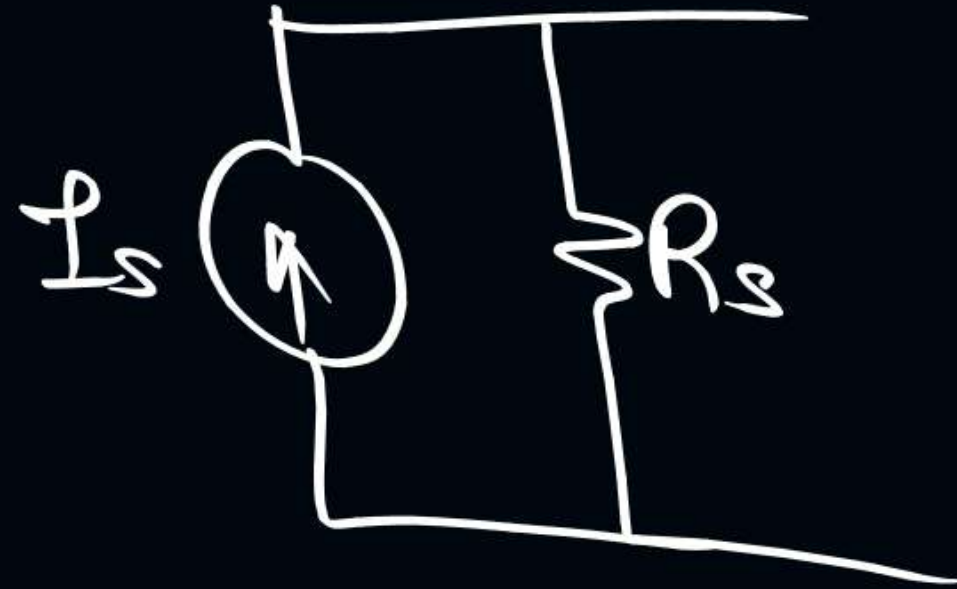

$$R_s = v.v. \text{ high}$$

Q: The internal Resistance of Practical Voltage Source is

(Kilo-ohm)

a) ~~∞~~

b) 10Ω

c) ~~0Ω~~

~~d) $100K \Omega$~~

Input Resistance \uparrow
Output Resistance of
Voltage Amplifier

||

Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount




Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



APP FEATURES

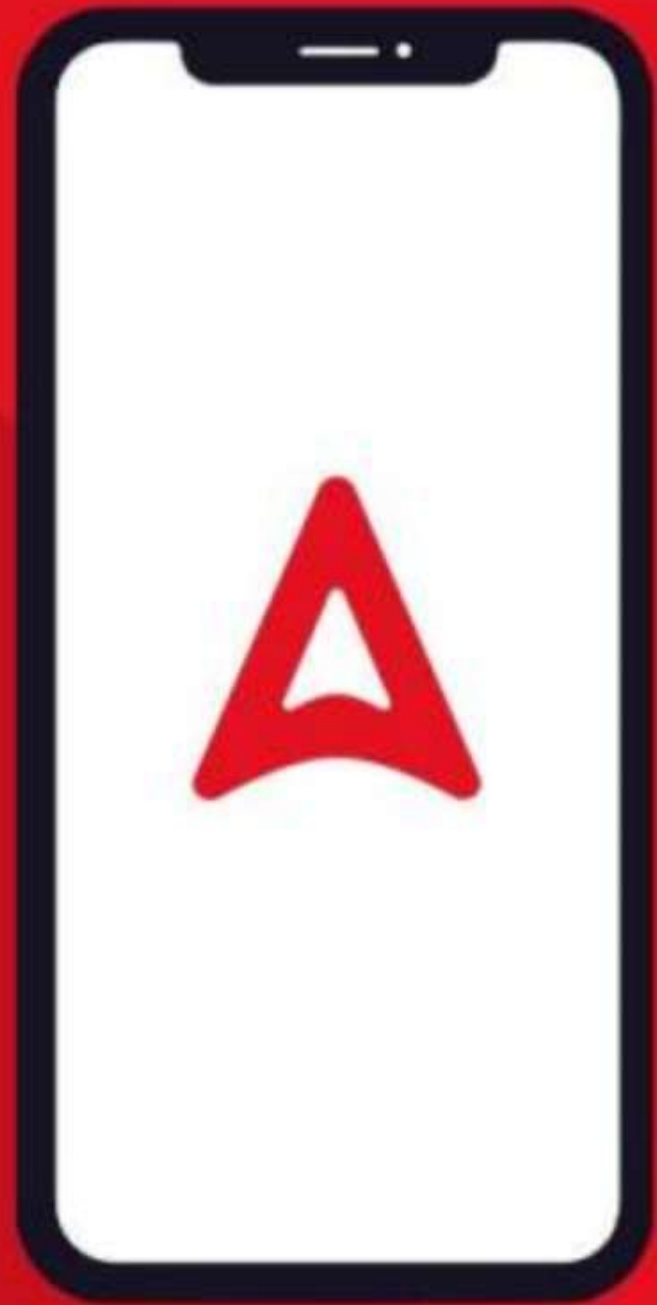

Download Now
Adda247 APP

PlayStore




Premium Study Material



Current Affairs



Job Alerts



Daily Quizzes



Subject-wise Quizzes



Magazines




Power Capsule



Notes & Articles



Videos

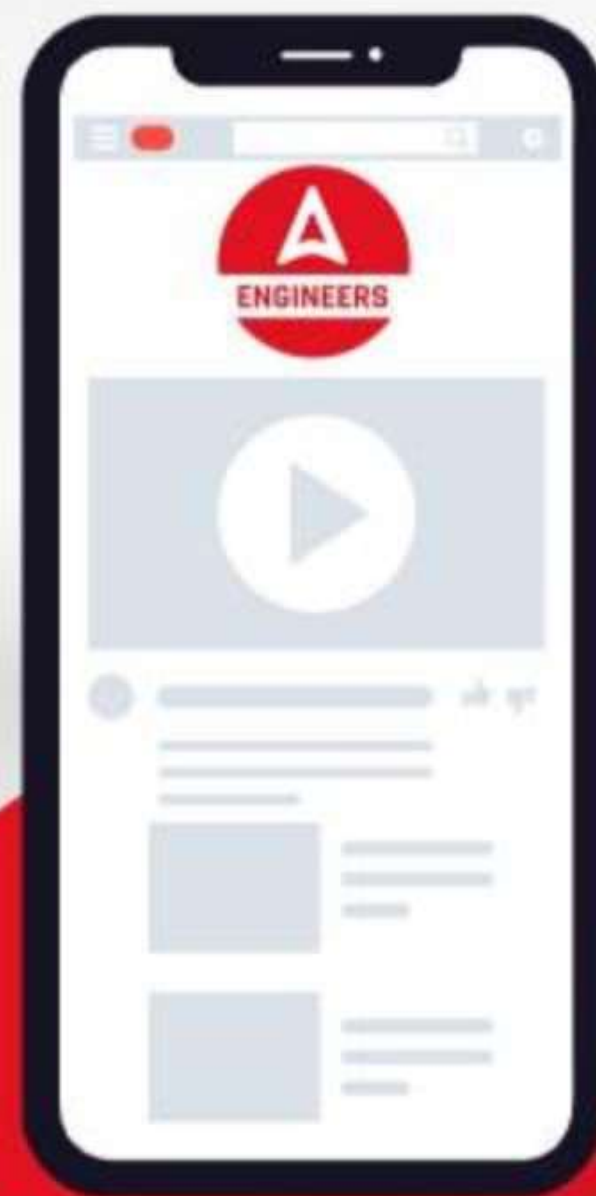

SUBSCRIBE NOW

Engineers Adda247

YouTube Channel

THANKS FOR

Watching

Adda247

LIKE



SHARE

COMMENT



SUBSCRIBE

