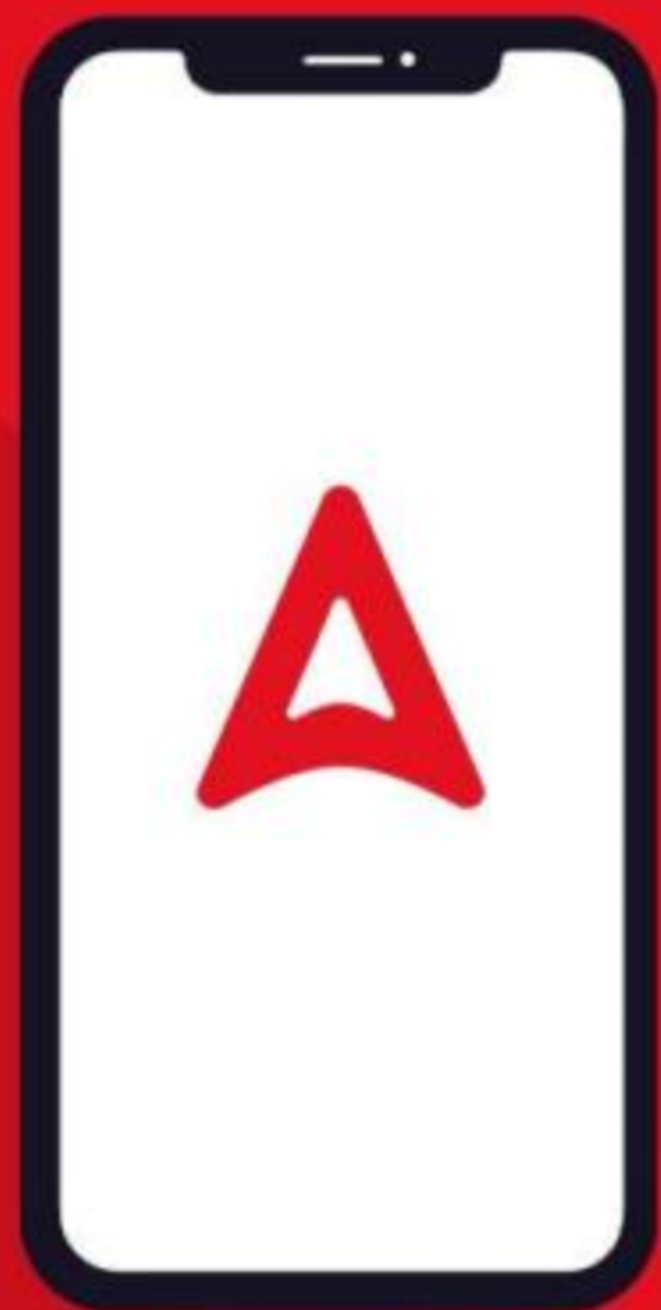


WELCOME
TO Adda247

Belief creates the
actual fact

APP FEATURES



Download Now
Adda247 APP



Premium Study Material



Current Affairs



Job Alerts



Daily Quizzes



Subject-wise Quizzes



Magazines



Power Capsule



Notes & Articles



Videos



SUBSCRIBE NOW

Engineers Adda247
YouTube Channel



Control system

V.V.I →

transfer function

$$TF = \frac{L[o/p]}{L[I/p]}$$

$$TF = \frac{K(s+z_1)(s+z_2) \dots}{s^n(s+p_1)(s+p_2) \dots}$$

Use
Y642
Max Discount

Use
Y642
Max Discount

eg: \rightarrow

$$G(s) = \frac{100}{(s+2)}$$

$$\text{pole} \rightarrow s = -2$$

$$\text{zero} \rightarrow s = \infty$$

$$\frac{100}{\infty+2} = \frac{100}{\infty} = 0$$

Use
Y642
Max Discount

eq. \rightarrow

$$G(s) = \left\{ \frac{100(s+1)}{s(s+2)} \right\}$$

$$\text{poles} = 0, -2$$


$$\text{zero} = -1, \infty$$

$$G(s) = \frac{100(s+1)}{s(s+2)(s+3)}$$

$$\begin{aligned} \text{No. of zeroes at } \infty \\ = \underline{\underline{2}} \end{aligned}$$

Transfer function: →
 ~~~~~

Use  
**Y642**  
 Max Discount

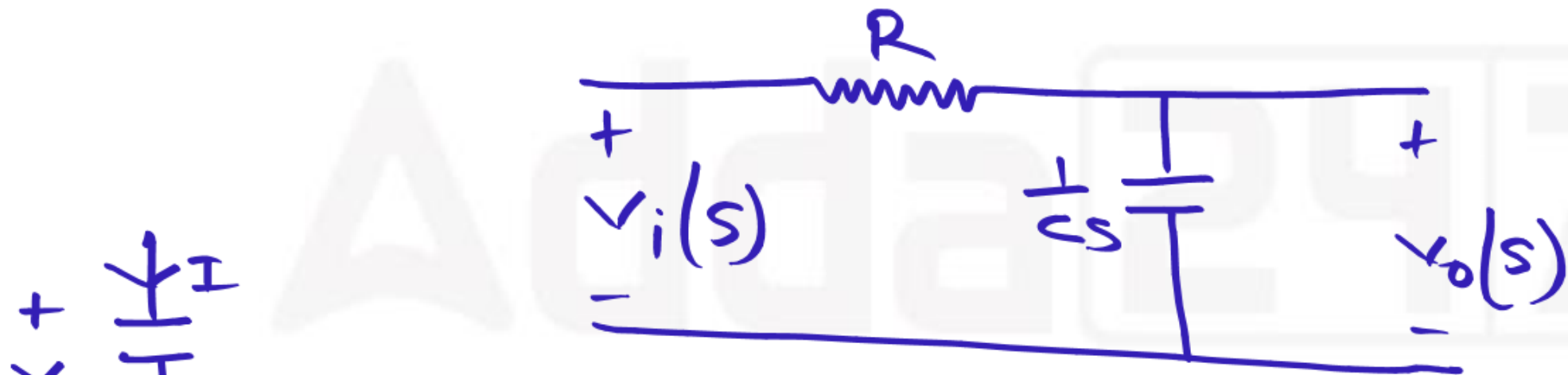

$$TF = \frac{v_o(s)}{v_i(s)}$$


$R \rightarrow R \checkmark$   
 $C \rightarrow \frac{1}{Cs}$   
 $L \rightarrow sL$

$$I = C \frac{dv}{dt}$$

$$I(s) = Cs \cdot v(s) \Rightarrow \boxed{v(s) = \frac{1}{Cs} \cdot I(s)}$$



Use  
**Y642**  
Max Discount

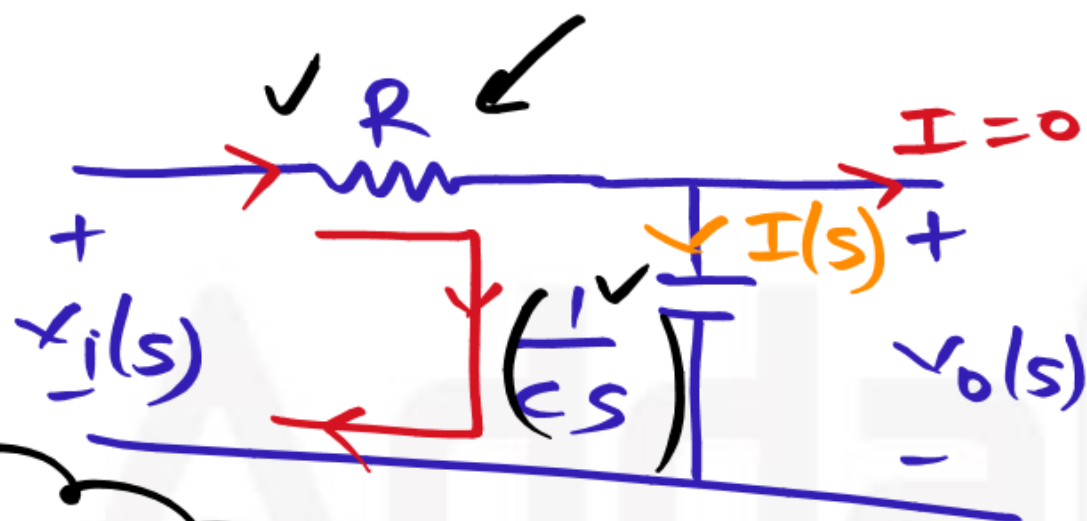


$$v_o(s) = \frac{1}{cS} \times I(s)$$

$$\frac{v_o(s)}{v_i(s)} = \frac{z_{oe}}{z_{ie} + z_{oe}}$$

$$I(s) = \frac{v_i(s)}{R + \frac{1}{cS}}$$

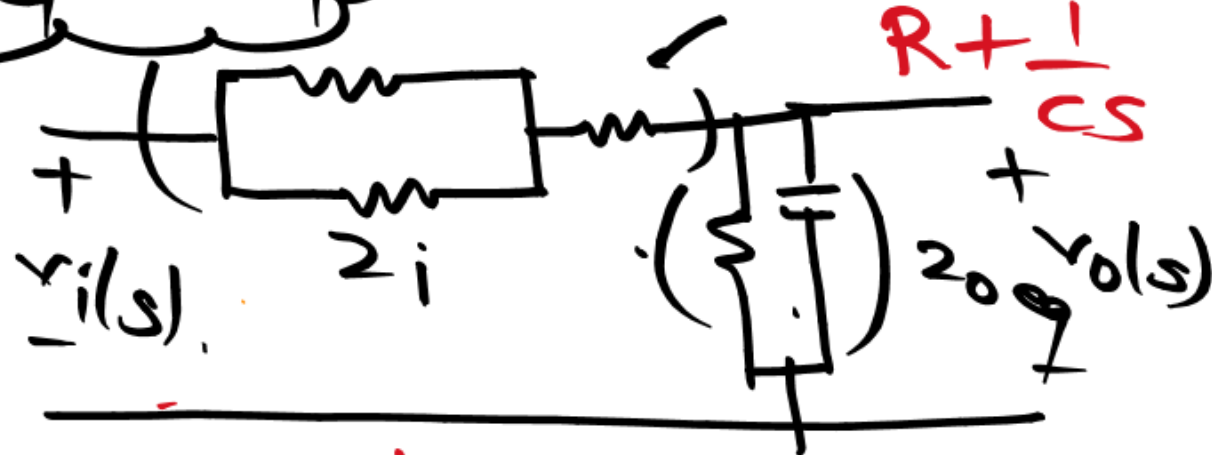
$$v_o(s) = \frac{1}{cS} \times \frac{v_i(s)}{R + \frac{1}{cS}}$$



$$\Rightarrow \frac{v_o(s)}{v_i(s)} = \frac{\left(\frac{1}{cS}\right)}{R + \frac{1}{cS}}$$


Use  
**Y642**  
Max Discount

eg:

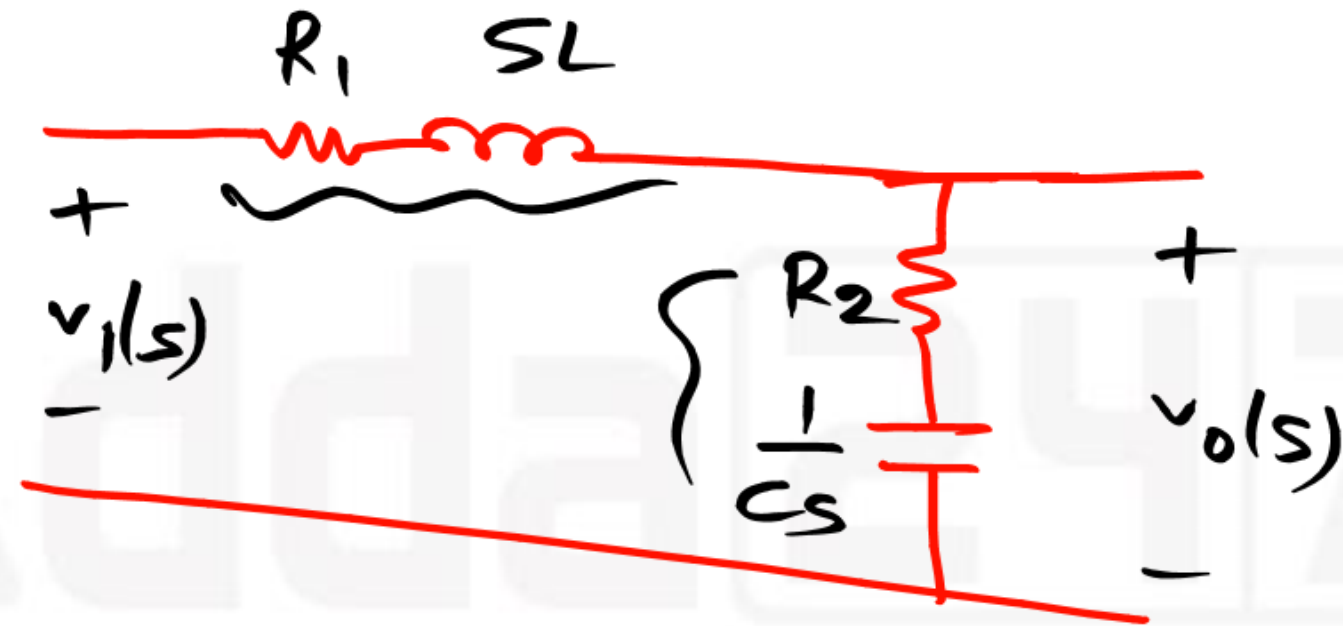


$$\checkmark \frac{v_o(s)}{v_i(s)} = \frac{R_2 + \frac{1}{c_s}}{R_1 + SL + R_2 + \frac{1}{c_s}}$$

Use  
**Y642**  
Max Discount

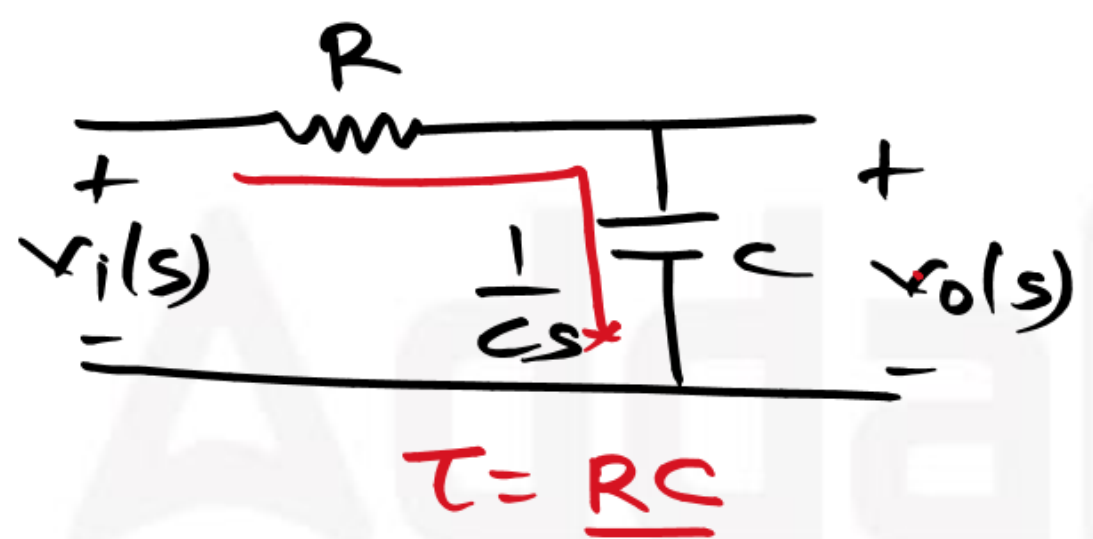


$$\frac{v_o(s)}{v_i(s)} = \frac{\frac{1}{Cs}}{R + \frac{1}{Cs}} = \frac{\frac{1}{Cs}}{\frac{RCs + 1}{Cs}} = \left( \frac{1}{RCs + 1} \right)$$

time constant →

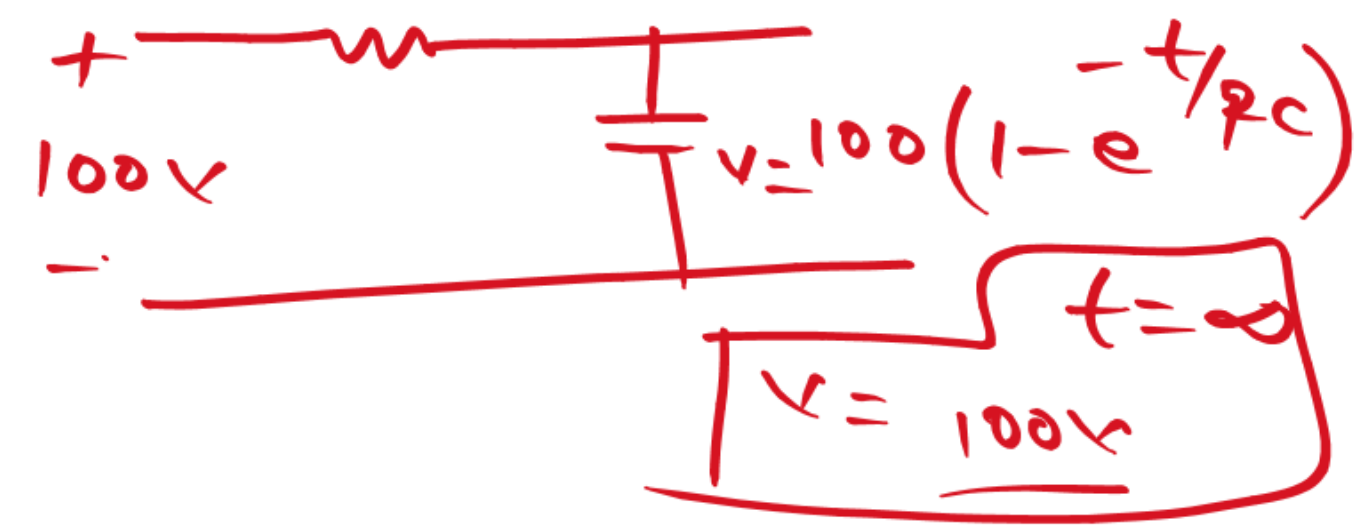

$$e^{-\infty} = \frac{1}{e^{\infty}} = \frac{1}{\infty} = 0$$

Use  
**Y642**  
Max Discount

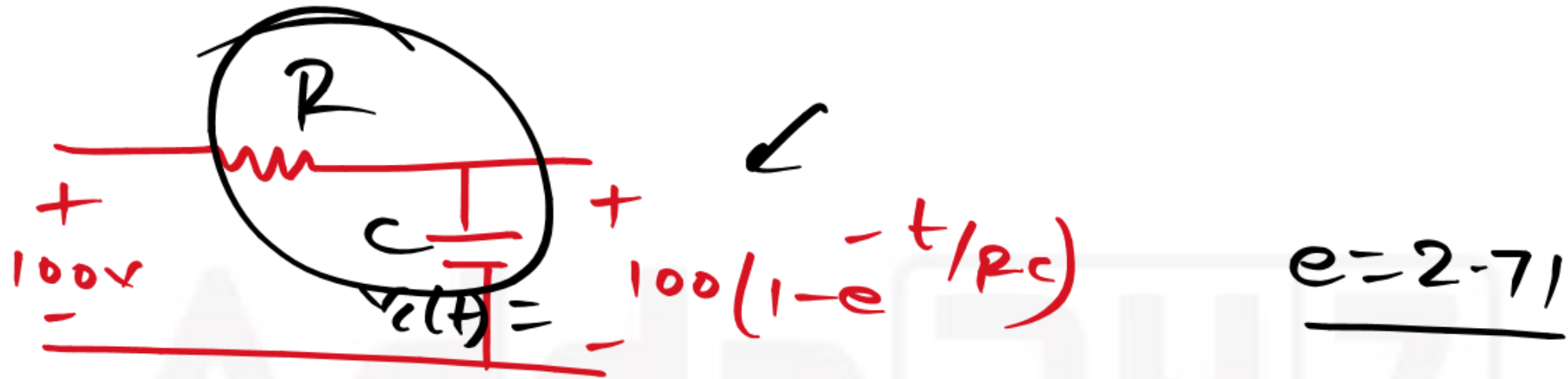

5.  $t = \infty, v_c(t) = 100V$

1.  $t = 0, v_c(t) = 0V$


63.2%  
↓

→ 2.  $t = RC$ ,  $v_c(t) = 100(1 - e^{-1}) = 100V \cdot 63.2$   
= 63.2V

Setting time.

3.  $t = 4RC$ ,  $v_c(t) = 100(1 - e^{-4}) = 100V \cdot 98$   
4.  $t = 5RC$ ,  $v_c(t) = 99V$  = 98V


Use  
**Y642**  
Max Discount

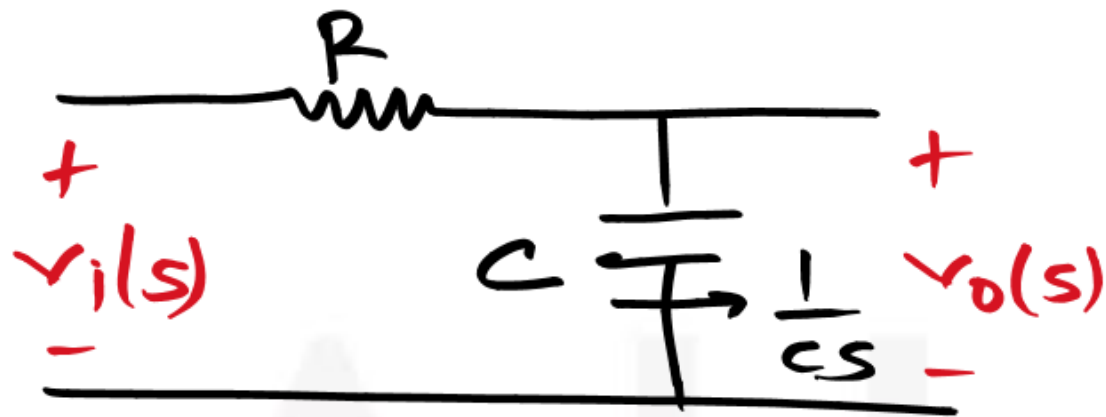


$s = \sigma + j\omega$

$$\frac{v_o(s)}{v_i(s)} = \frac{1}{s \cdot RC + 1} = \frac{1}{s\tau + 1}$$

Q1

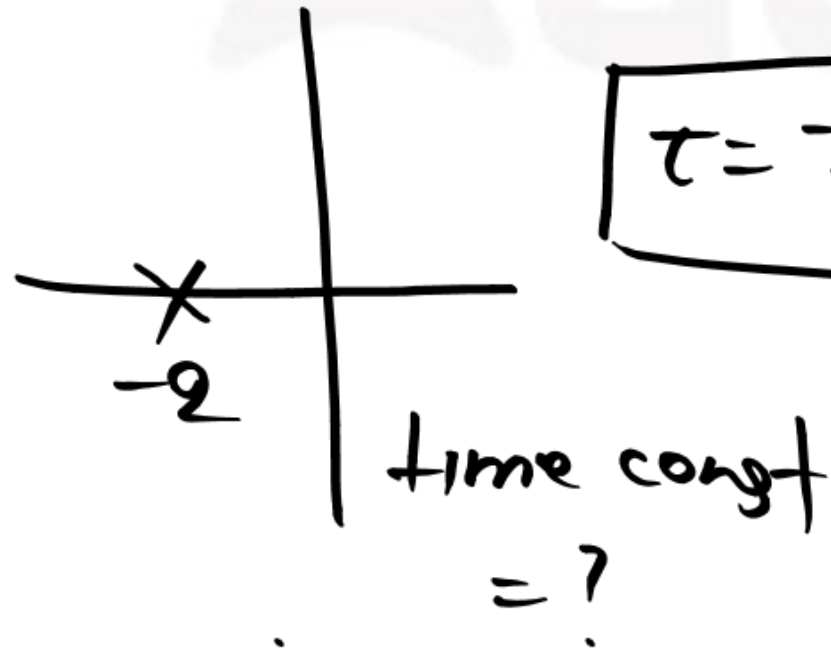


$\tau = -\frac{1}{s}$

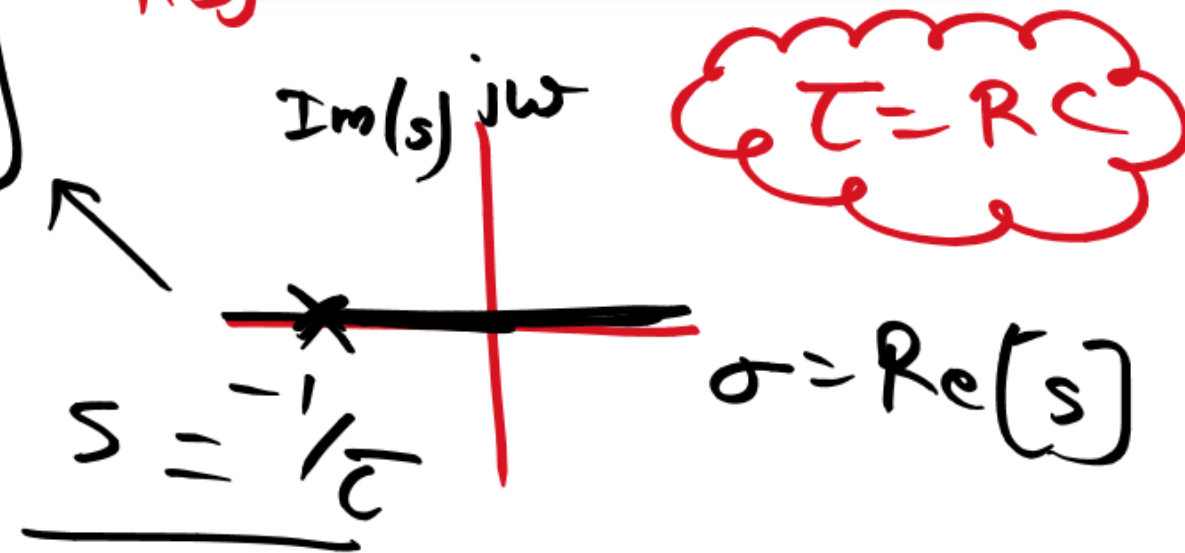


$s = -\frac{1}{\tau}$   
↓  
pole

Use  
**Y642**  
Max Discount

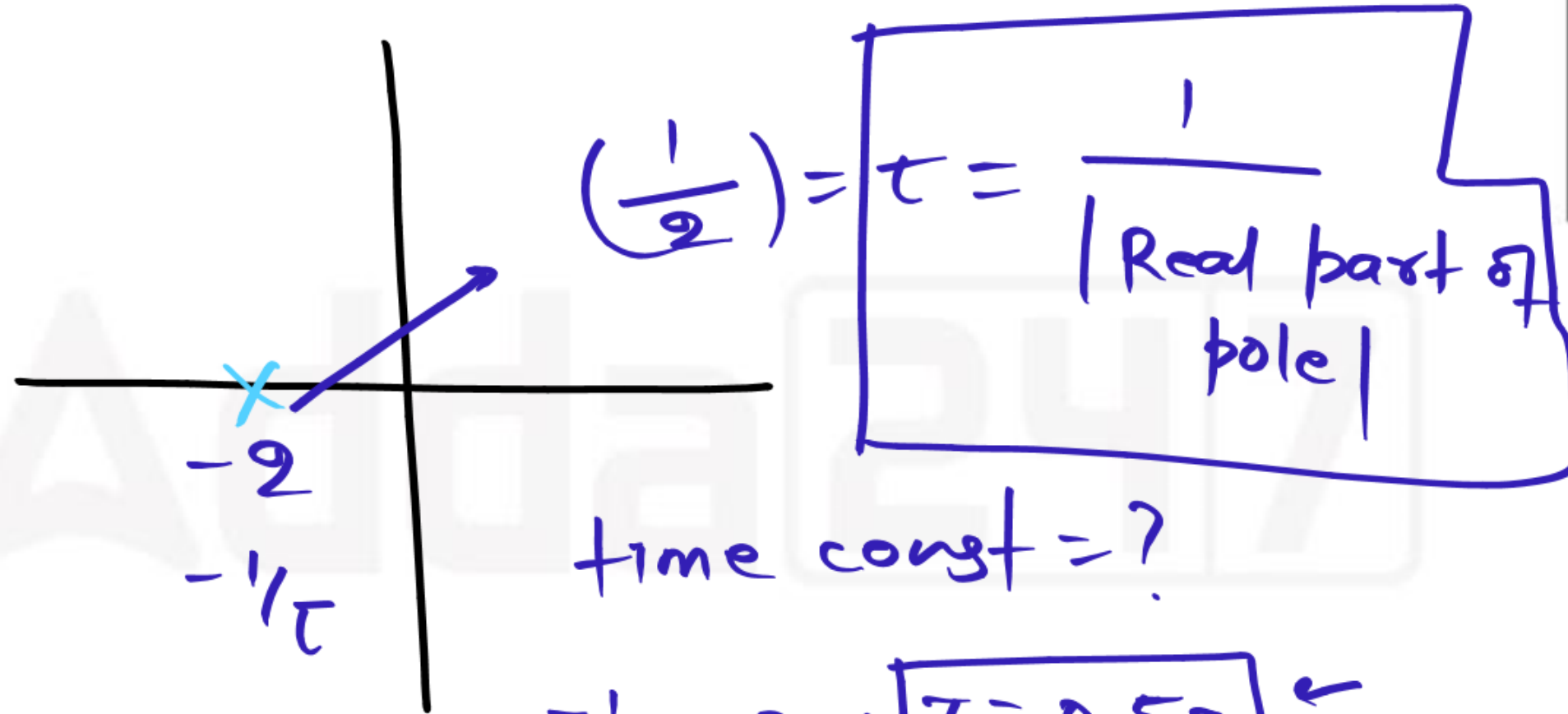

$-\frac{1}{\tau} = -2 \Rightarrow \tau = 0.5s$

$\tau = \frac{1}{2}$

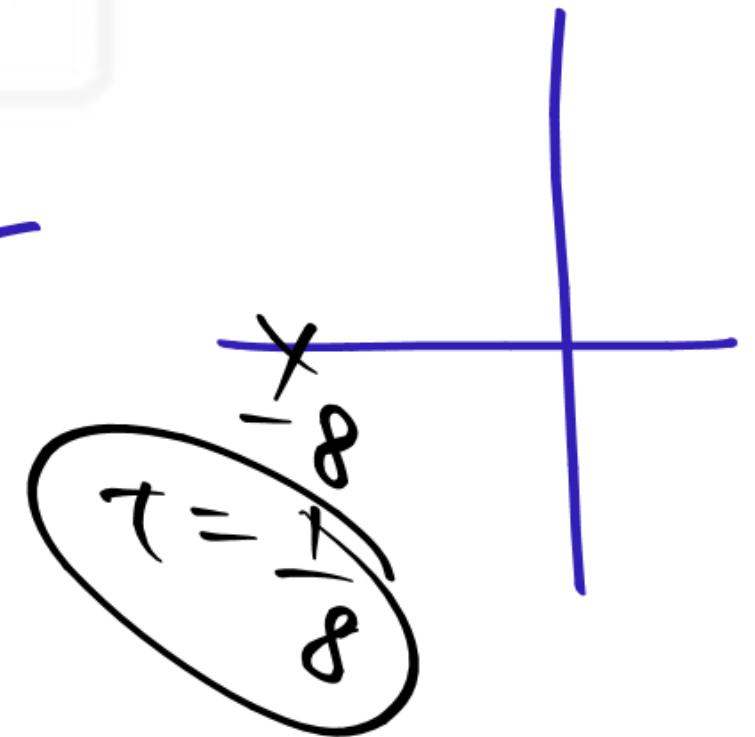

Use  
**Y642**  
Max Discount



$$\tau = \frac{1}{|\text{Real part of pole}|}$$

$$\tau = \frac{1}{|-1|} = 1$$

Y642

order and types of the control system

Use  
**Y642**  
Max Discount

R L C  
~~~~~  
dissipates stores energy



order of the control system → No. of energy storing elements in a system.

USE MAX DISCOUNT **CODE Y642**

Adda247

Use
Y642
Max Discount

Adda247

THANKS FOR

Watching

Adda247

LIKE



SHARE



COMMENT



SUBSCRIBE

