



RRB JE | SSE 2023

Foundation Batch

Analog Electronics

Day-5

> LIVE

2 PM

LAWRENCE Sir



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount

Adda247


WELCOME

TO Adda247

We are limitless

APP FEATURES

4694

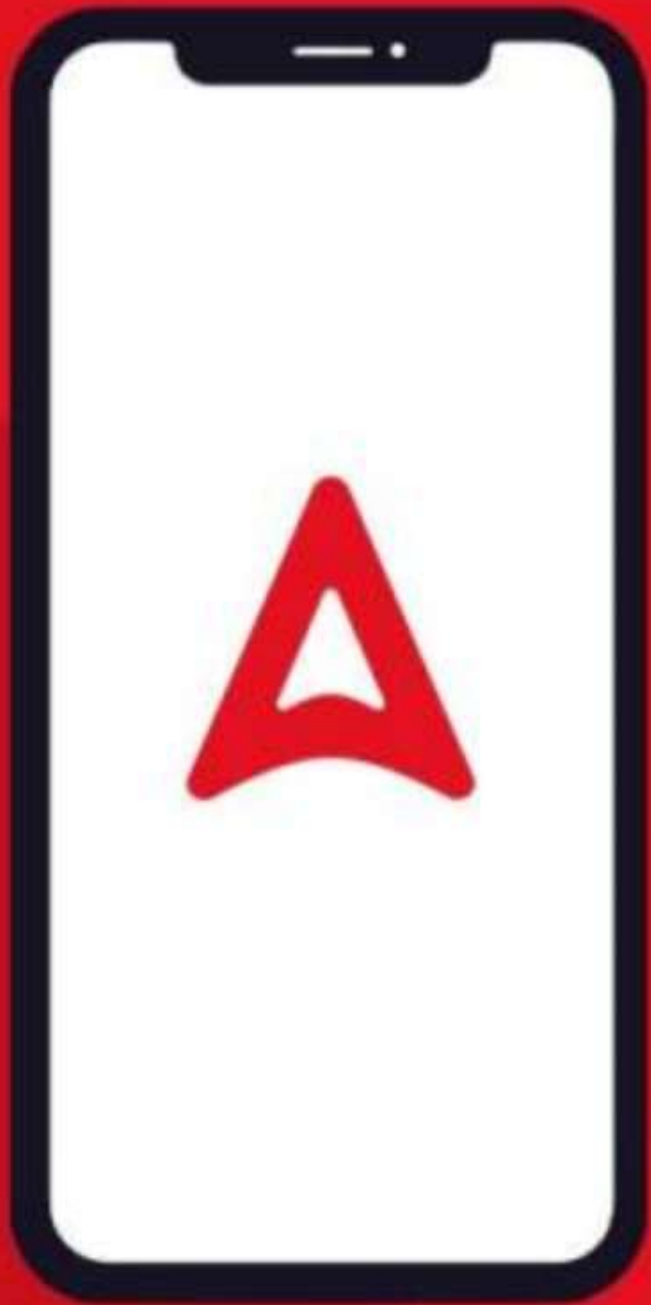

PlayStore

Download Now

Adda247 APP



Premium Study Material



Current Affairs



Job Alerts



Daily Quizzes



Subject-wise Quizzes



Magazines




Power Capsule



Notes & Articles



Videos

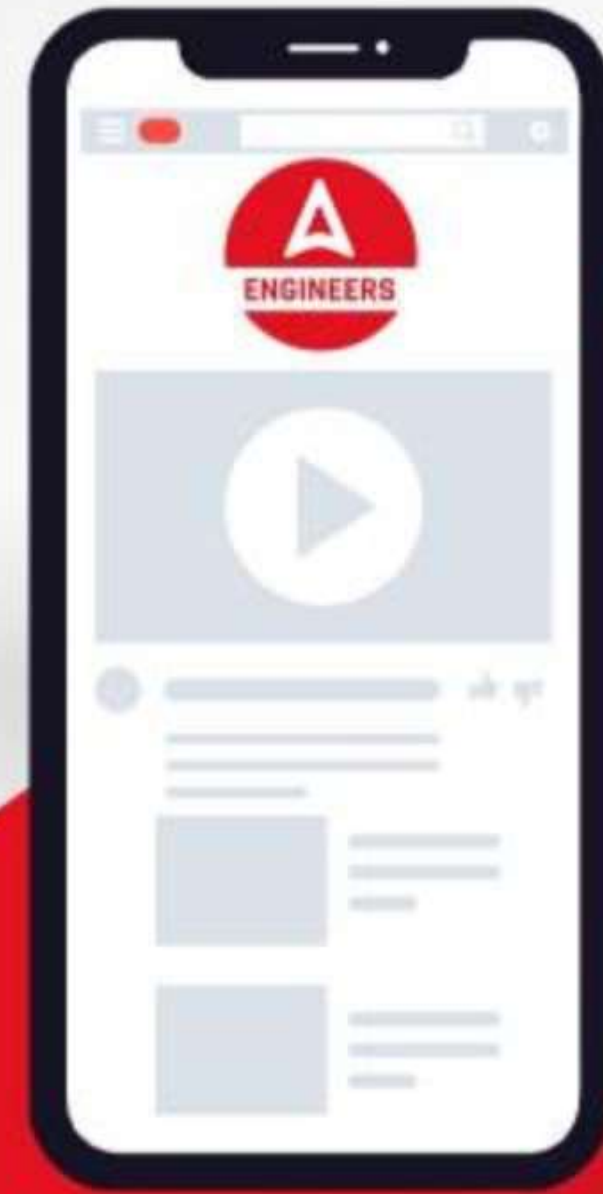

SUBSCRIBE NOW


Engineers Adda247
YouTube Channel

Mode of operation:

→ Inverting Mode

→ Non-Inverting Mode


→ Differential Mode

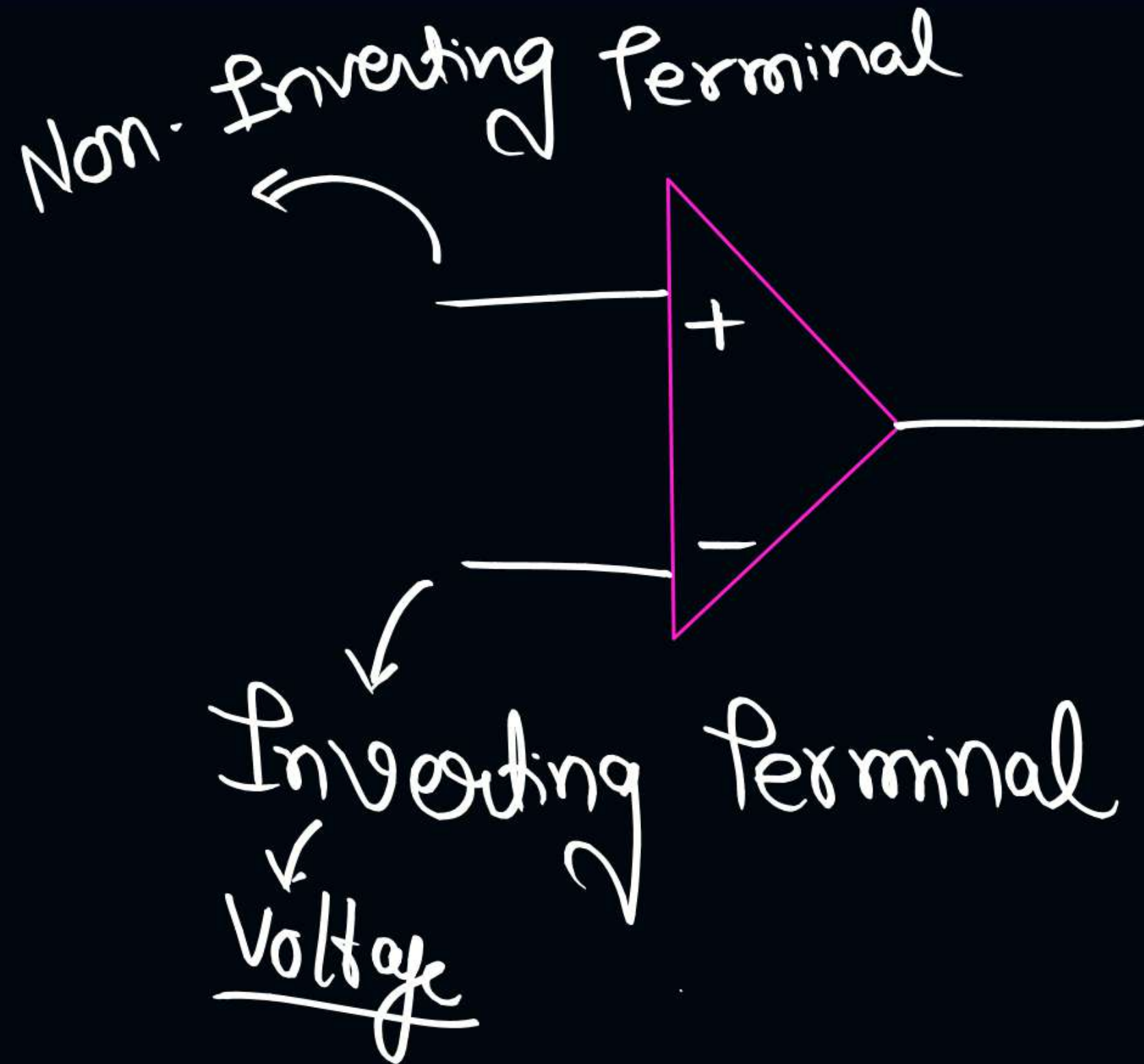

Convert:

+	→	-
-	→	+

Inverting Mode:

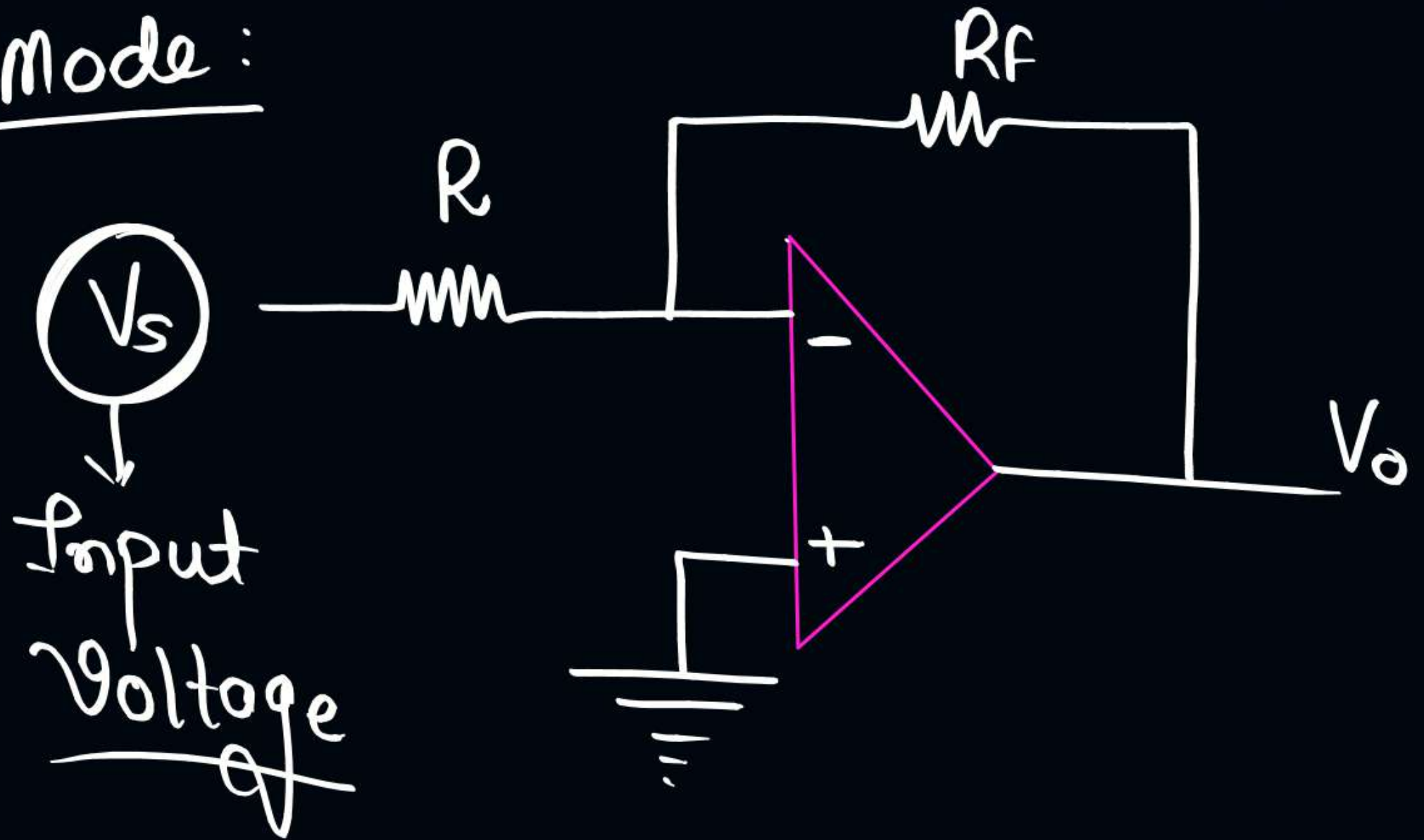


☺ V_p : AMP
is Ideal:


$$V_p = V_n$$

Virtual Short
Concept

$$V_p = 0 = V_n$$

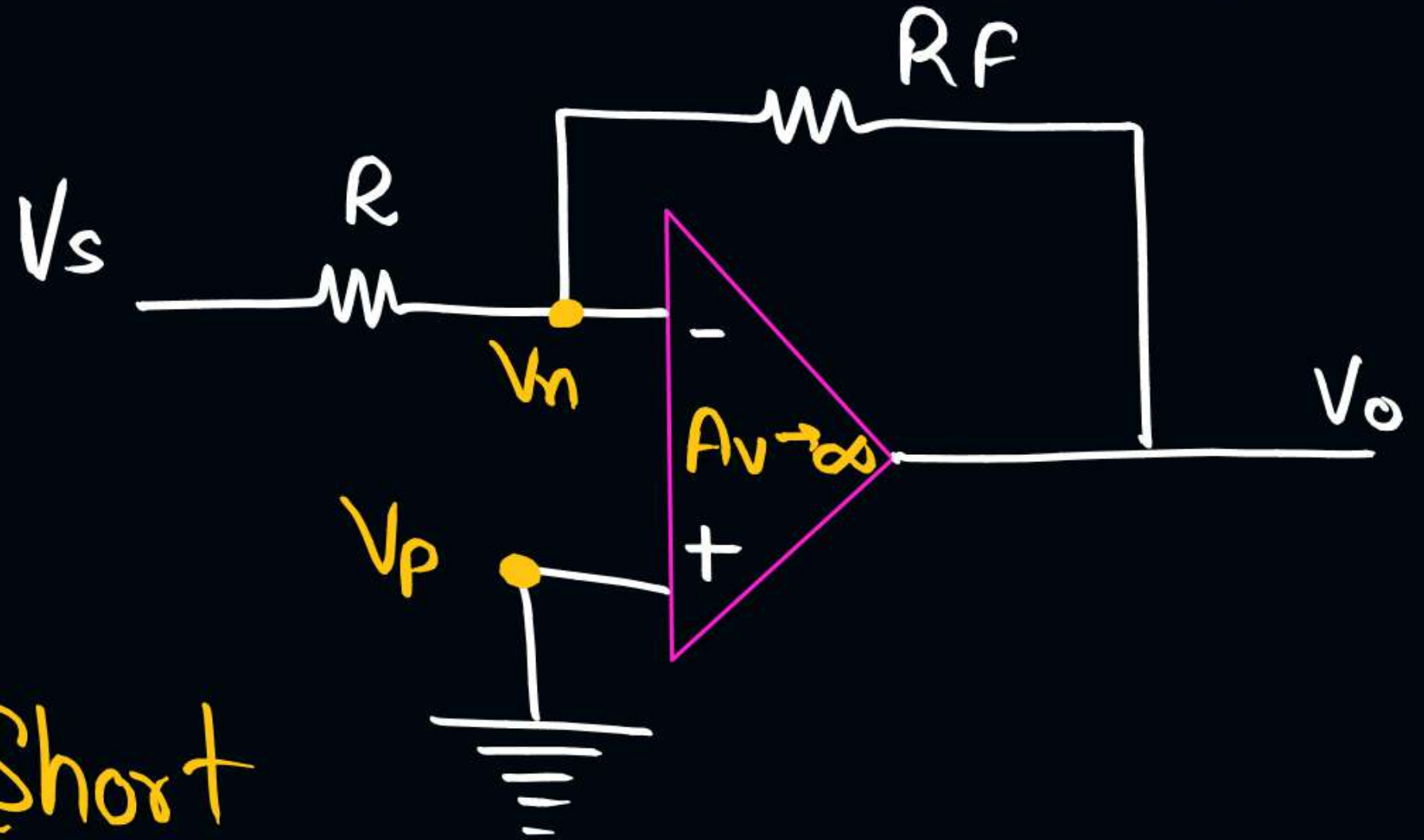

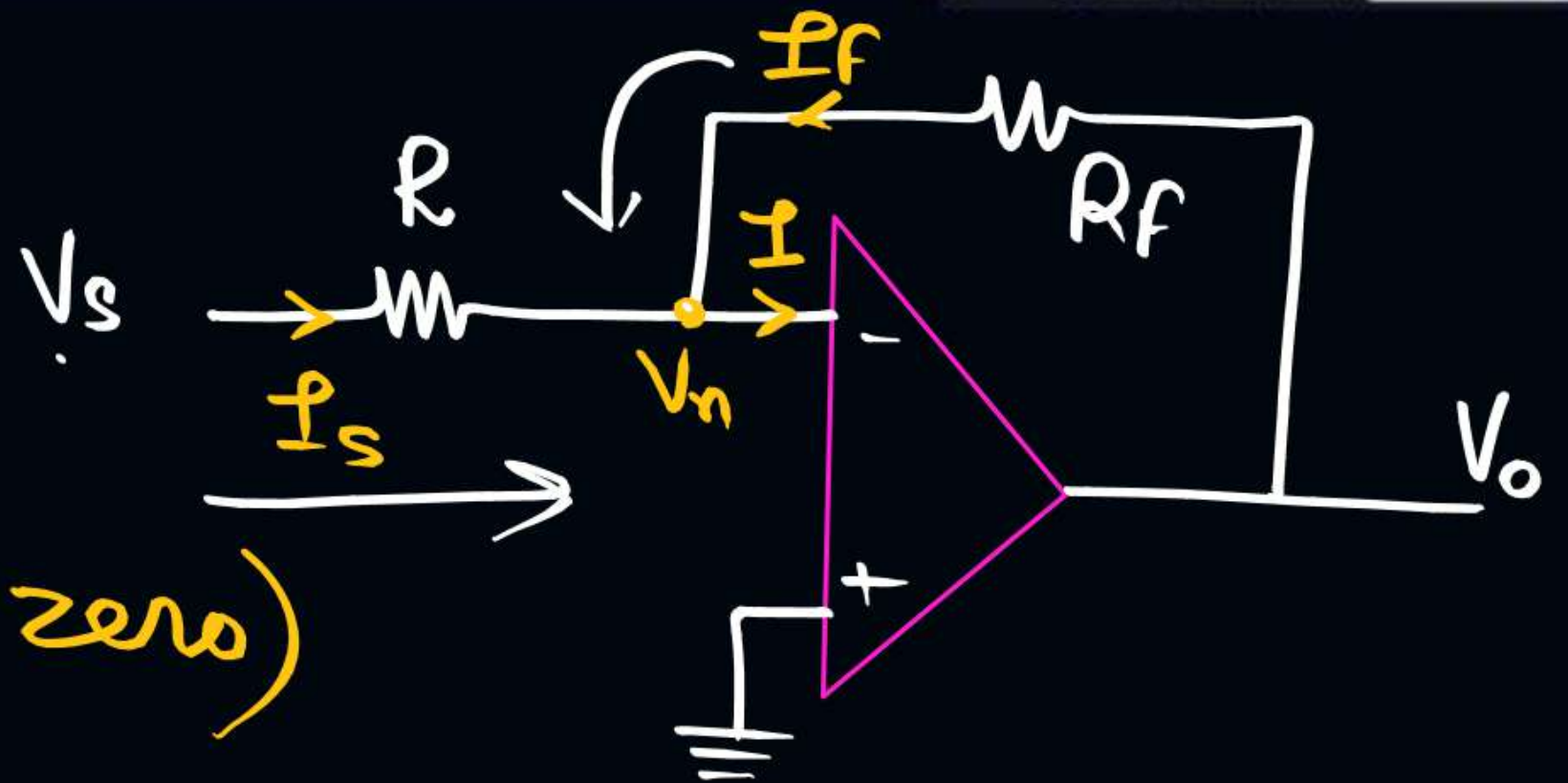
$\therefore I = 0$ (current enters at OP-Amp is zero)




Apply KCL @ V_n :

$$I_f + I_s = I = 0$$

$$I_f + I_s = 0$$

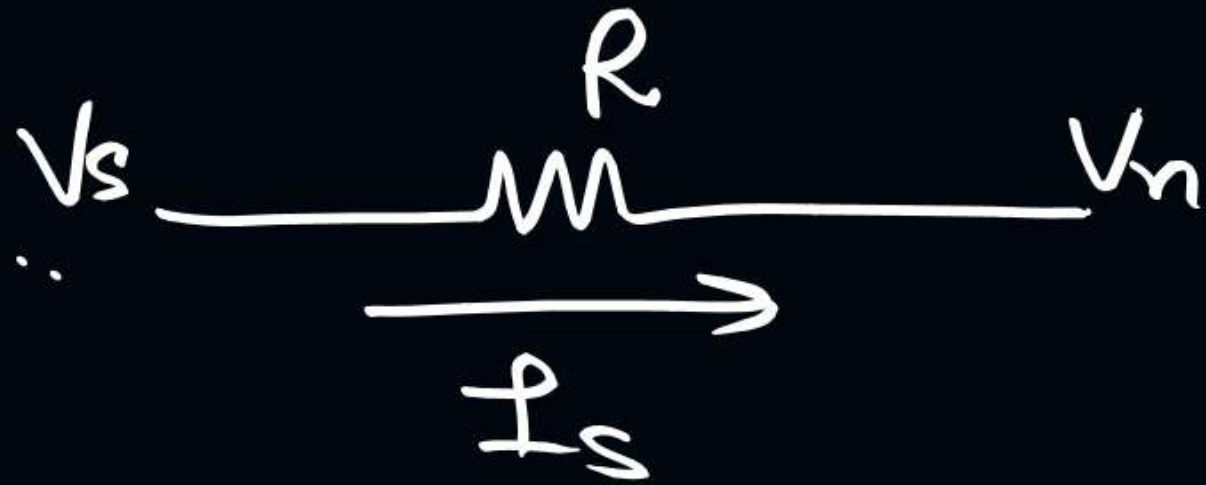

$$I_s = \frac{V_s - V_n}{R}$$

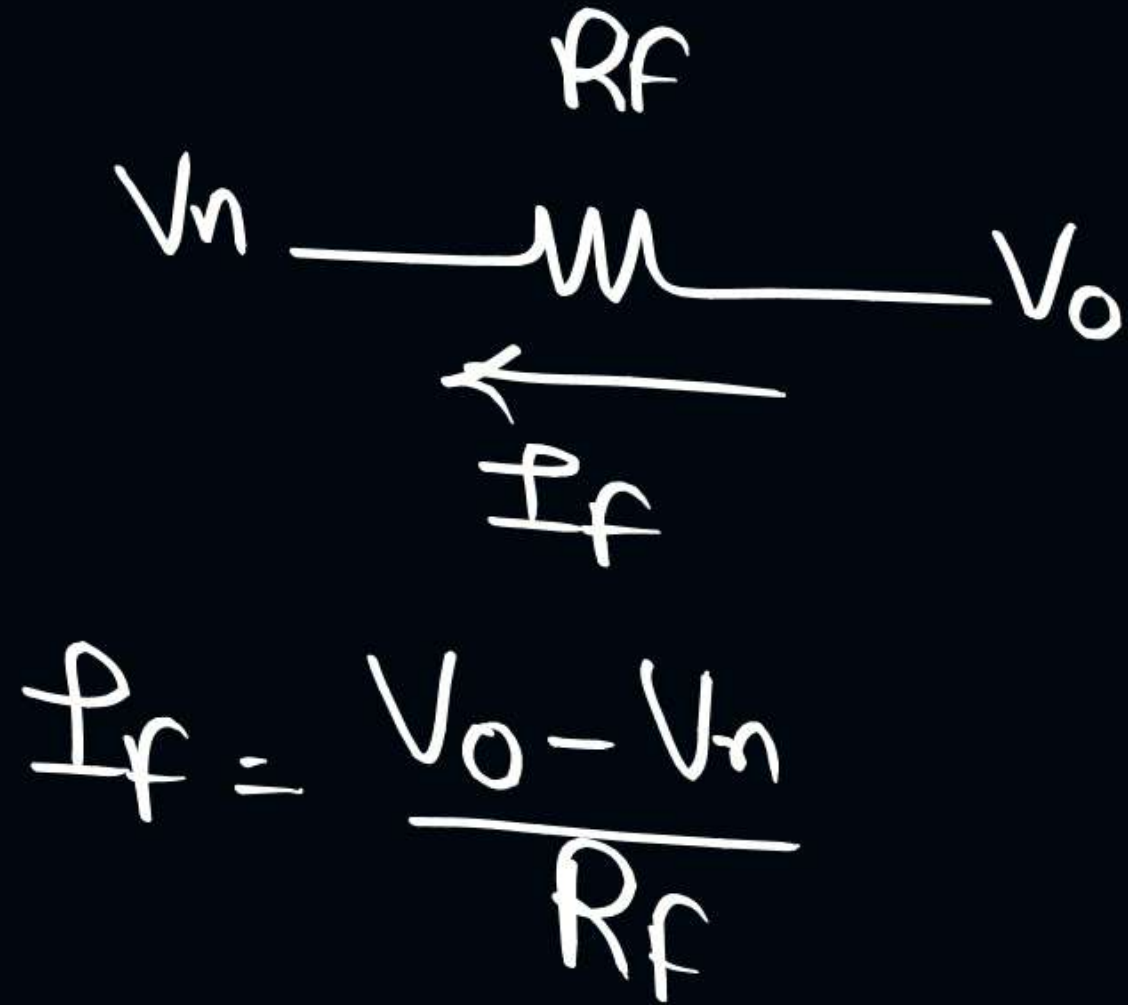

$$I_f = \frac{V_o - V_n}{R_f}$$

$$\frac{V_o - V_n}{R_f} + \frac{V_s - V_n}{R} = 0$$

$\therefore V_n = 0 = V_p$ (Virtual Short Concept)

$$\frac{V_o}{R_f} + \frac{V_s}{R} = 0$$

$$\frac{V_o}{R_f} = -\frac{V_s}{R}$$

$$V_o = \left(-\frac{R_f}{R}\right) \cdot V_s$$

→ Output of Inverting Mode OP-Amp


$$\frac{V_o}{V_s} = -\frac{R_f}{R}$$

→ Gain of Inverting Mode

$$V_o = -\frac{R_f}{R} \cdot V_s$$


$$\therefore R_f = 2\text{K}\Omega, R = 1\text{K}\Omega, \underline{V_s = 1\text{V}}$$
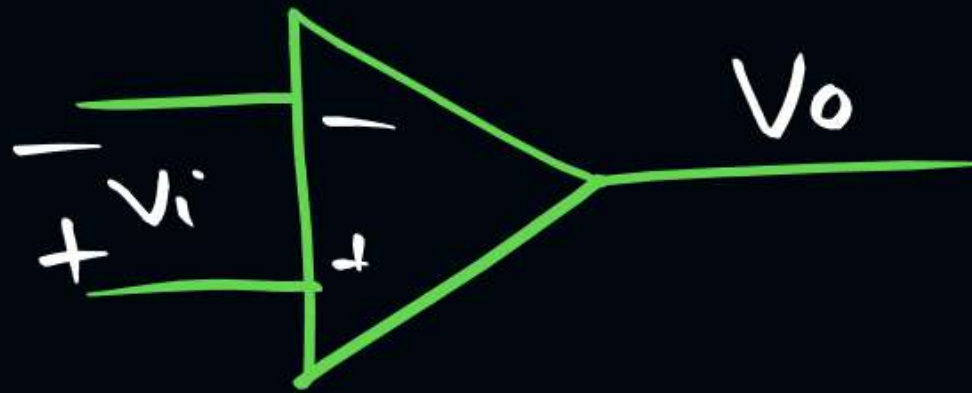
$$V_o = \frac{-2}{1} \cdot 1 = \underline{-2\text{V}} \quad (\text{Inverting Mode})$$



$$A_v = \infty \text{ (Ideal)}$$

$$\frac{V_o}{V_i} = \infty$$

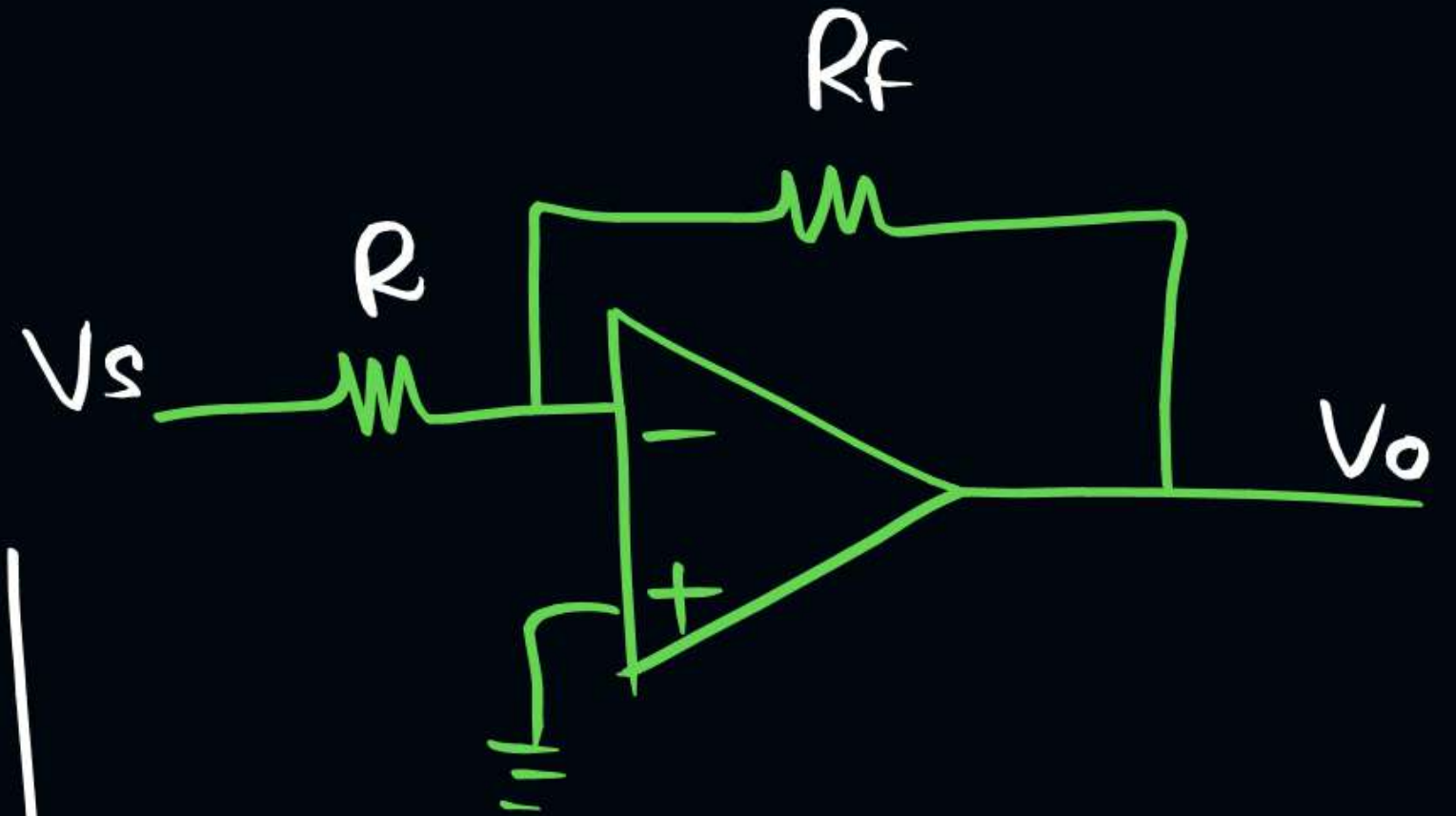

$$\frac{V_o}{V_s} = -\frac{R_f}{R}$$


BW \uparrow ∞

Ques:

Find

$$V_o = ?$$


$$I_f = ?$$

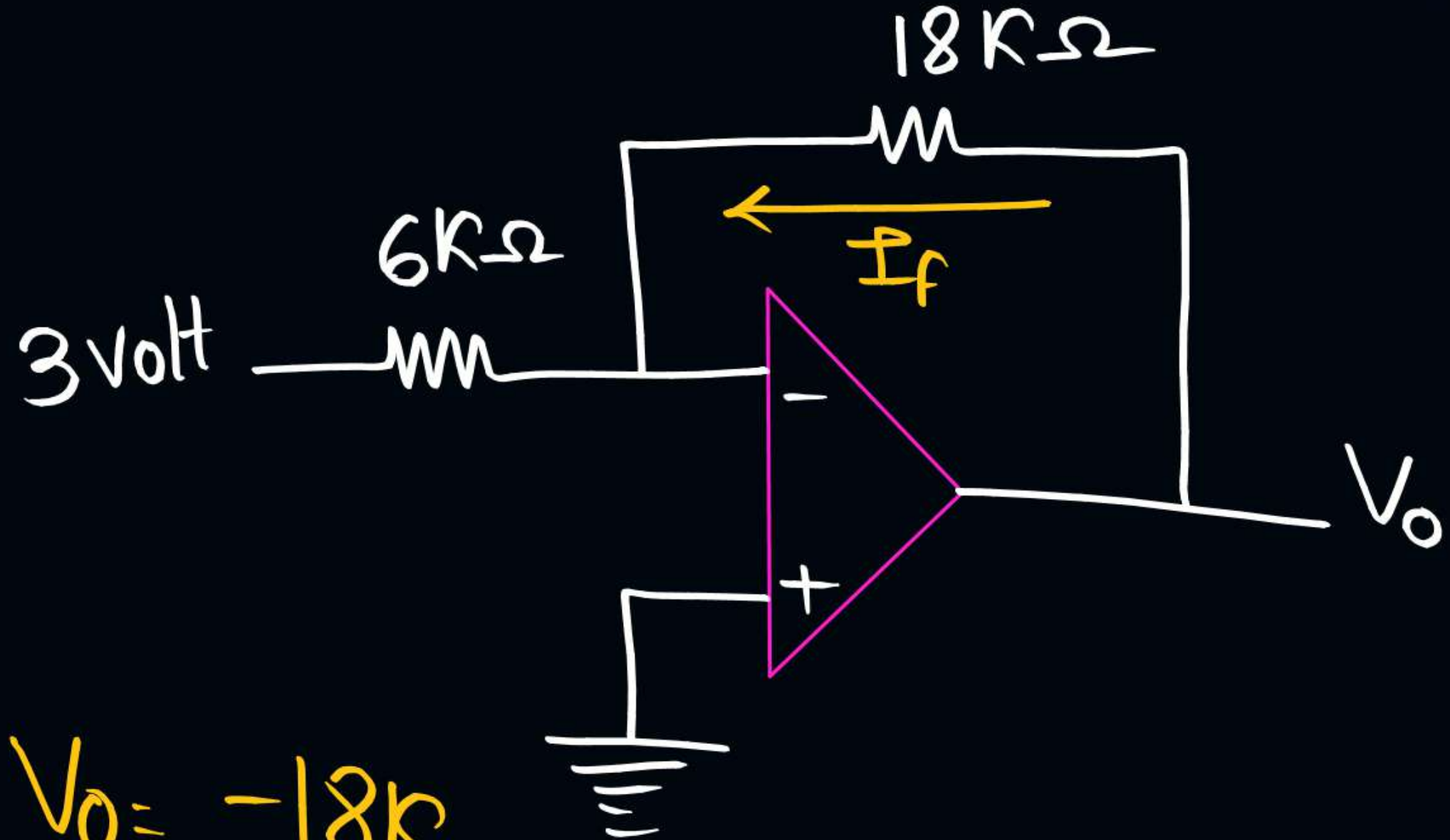

$$V_o = -\frac{18k}{6k} \times 3v = \underline{\underline{-9 \text{ volt}}}$$

$$I_f = \frac{V_o - V_n}{18k}$$

$$I_f = \frac{-9 - 0}{18k}$$

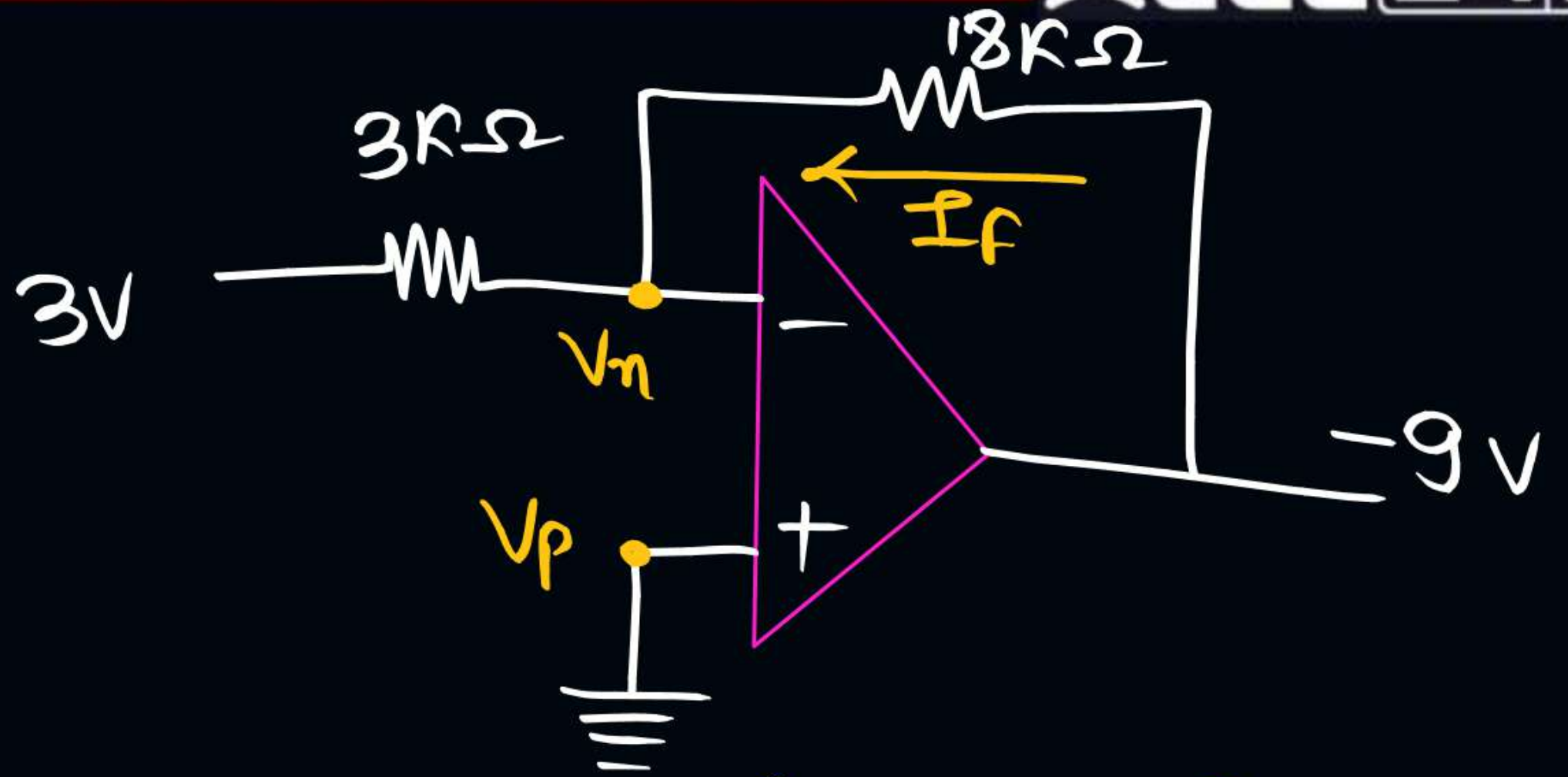

$$V_p = 0 = V_n \text{ (Virtual Short Concept)}$$

$$I_f = \frac{-9}{18 \text{ k}}$$

$$= -\frac{1}{2} \text{ mA} = -0.5 \text{ mA}$$


Q:

Find


$$I_1 = ?$$

$$I_2 = ?$$

$$V_o = ?$$

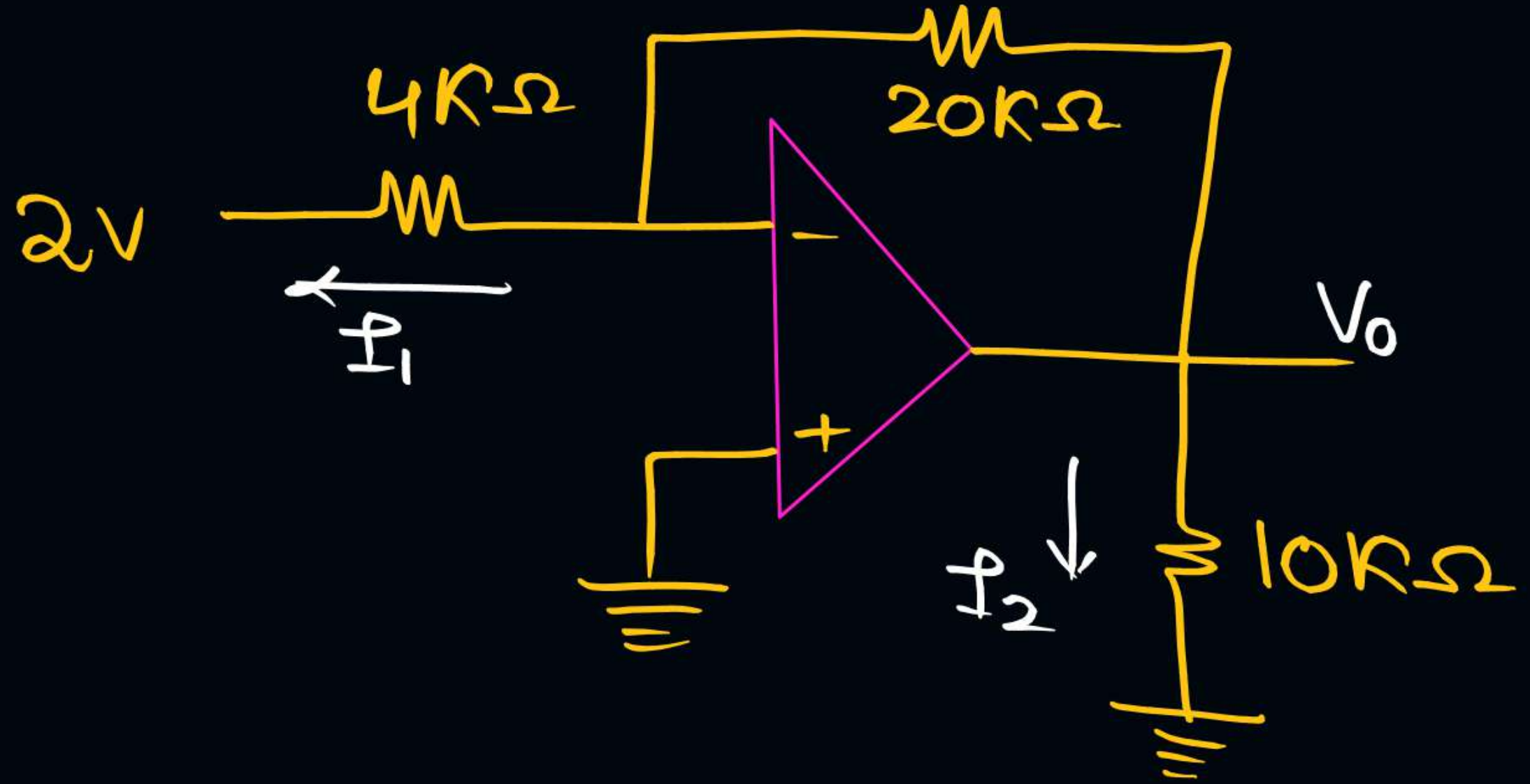

$V_p = 0 = V_n$ (Virtual Short concept)

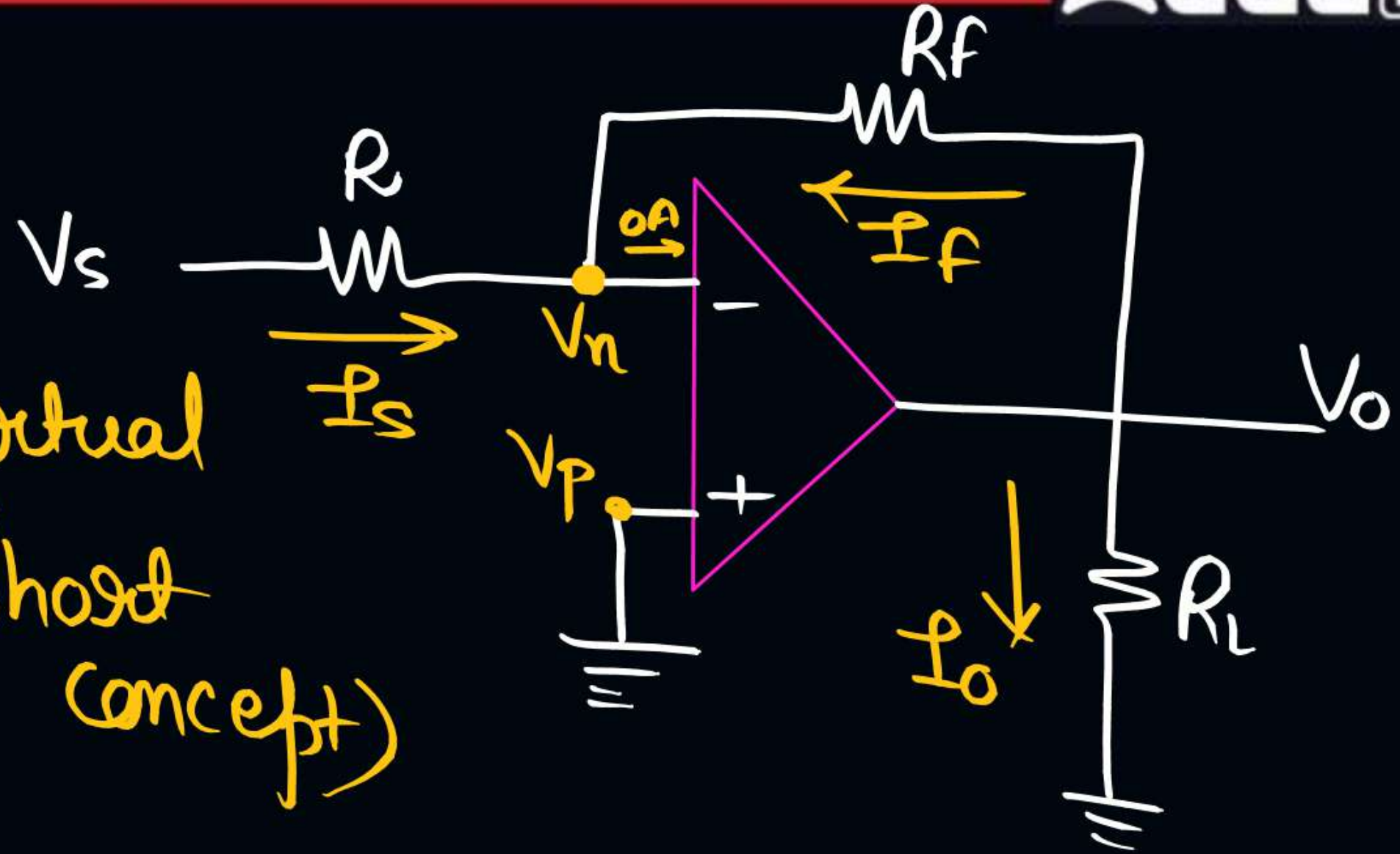

Apply KCL @ V_n :

$$I_s + I_f = 0$$


$$\frac{V_s - V_n}{R} + \frac{V_o - V_n}{R_f} = 0$$

$$\boxed{V_n = 0}$$

$$\Rightarrow \boxed{V_o = -\frac{R_f}{R} V_s}$$

$$V_o = -\frac{5}{4k} (2v)$$

$$V_o = -10 \text{ Volt}$$

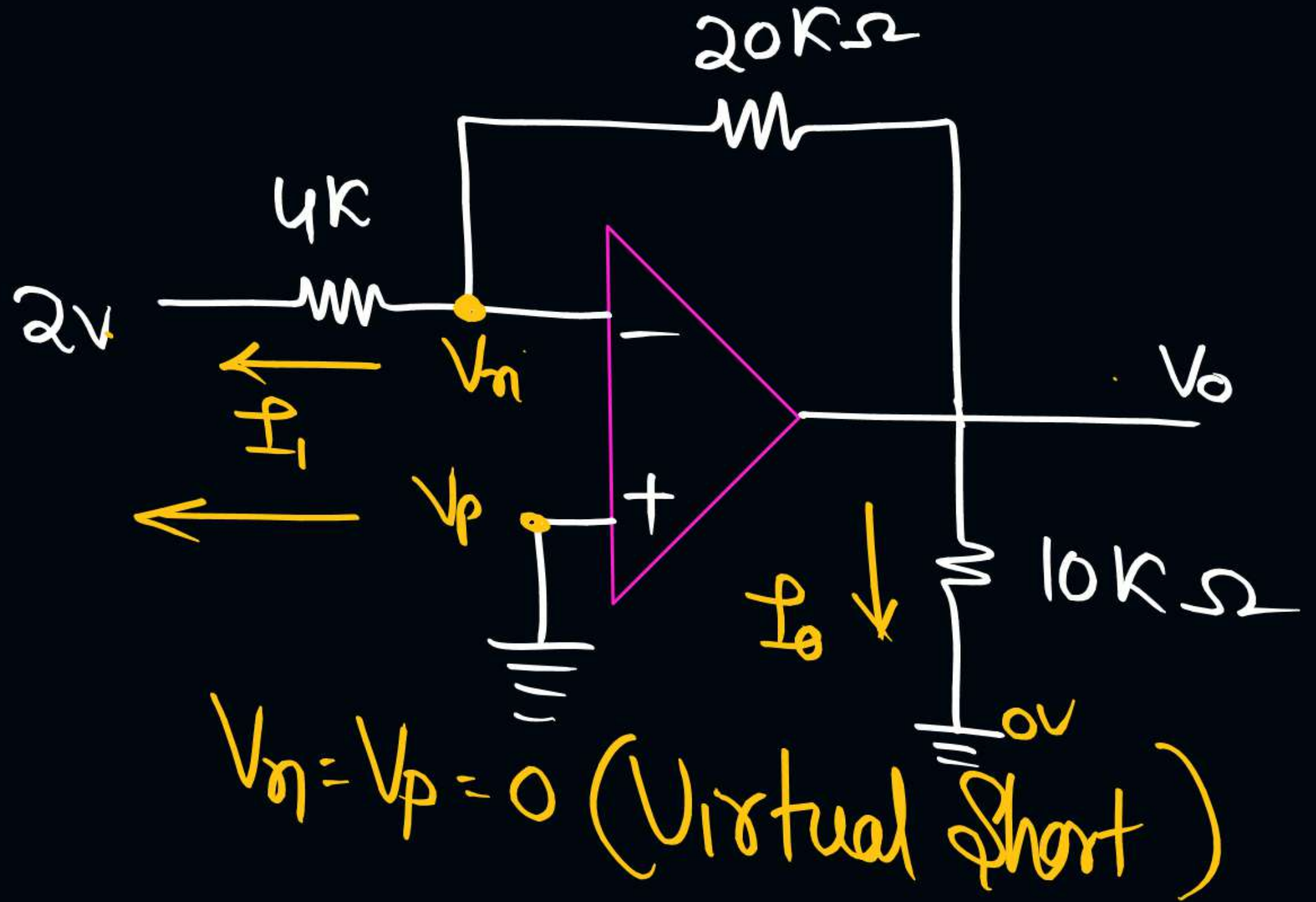

$$I_1 = \frac{V_n - 2}{4k}$$


$$I_1 = \frac{0 - 2}{4k}$$

$$I_1 = -\frac{2}{4} \text{ mA} = -0.5 \text{ mA}$$

$$I_o = \frac{V_o - 0}{10k\Omega}$$

$$I_o = \frac{-10V}{10k\Omega}$$

$$I_o = -1 \text{ mA}$$

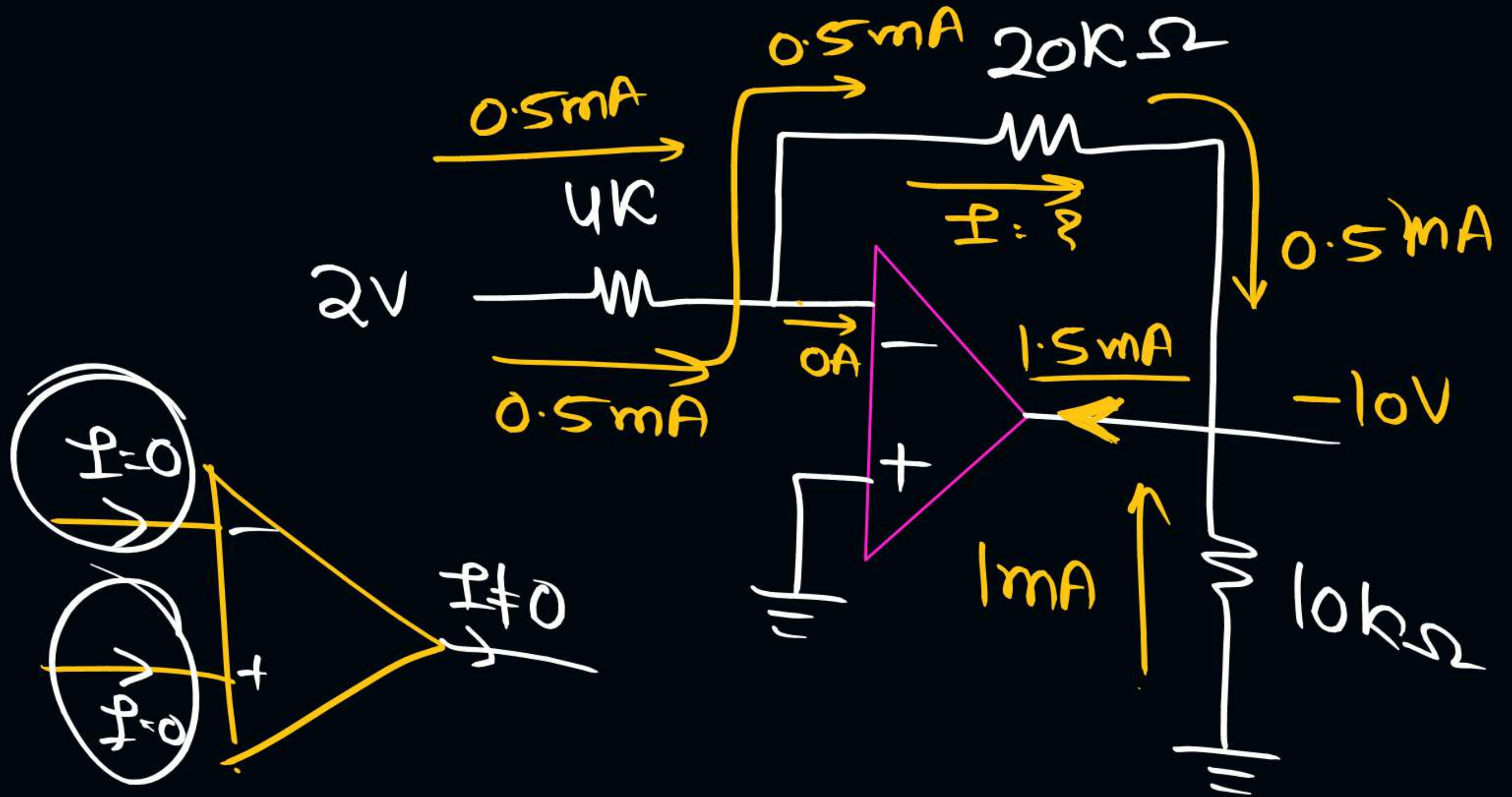

Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount




Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



Join ADDA247 GATE GURUKUL BATCH using code Y694 to get maximum discount



APP FEATURES

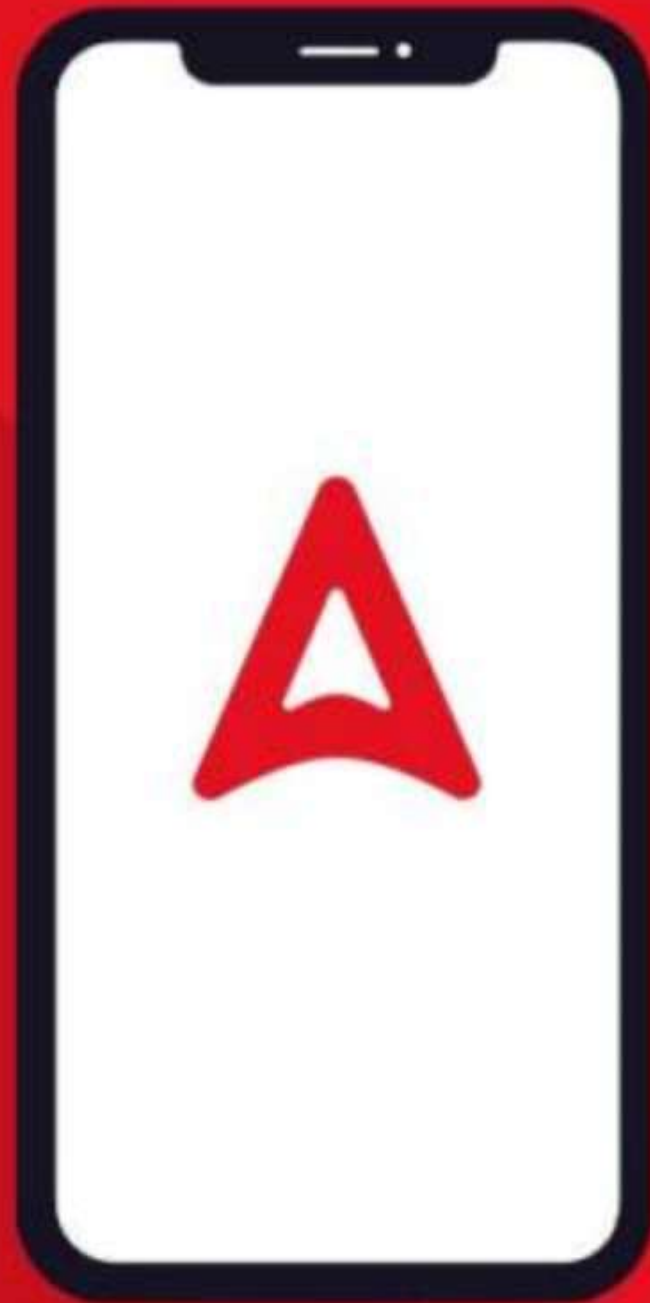

PDF

Play Store

Download Now
Adda247 APP



Premium Study Material



Current Affairs



Job Alerts



Daily Quizzes



Subject-wise Quizzes



Magazines




Power Capsule



Notes & Articles



Videos

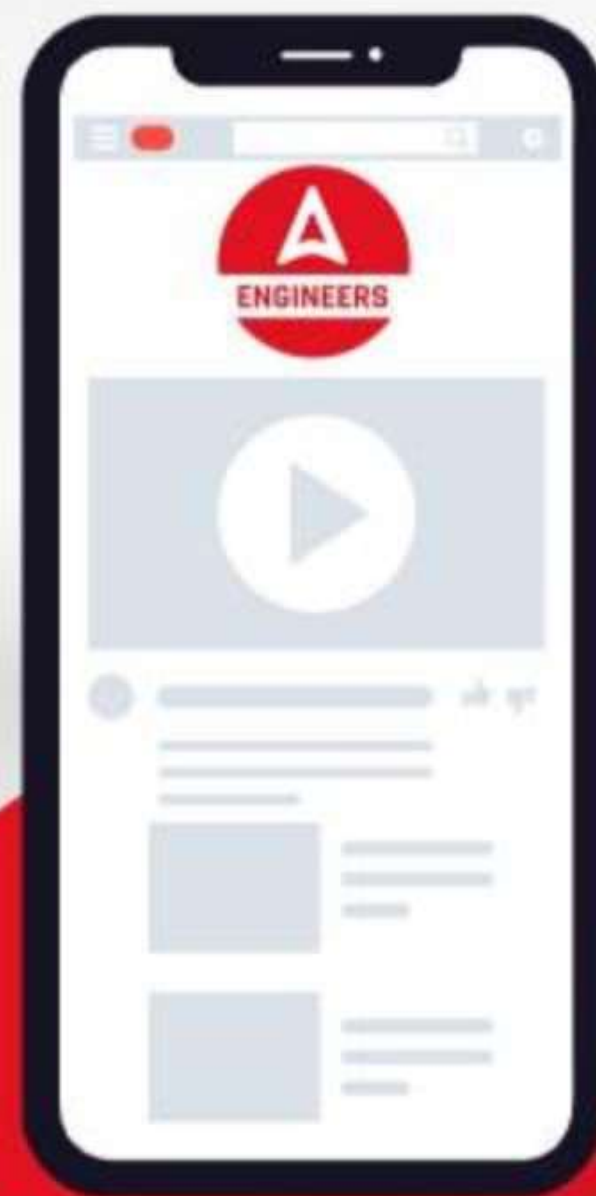

SUBSCRIBE NOW

Engineers Adda247
YouTube Channel

THANKS FOR

Watching

Adda247

LIKE



SHARE



COMMENT



SUBSCRIBE

