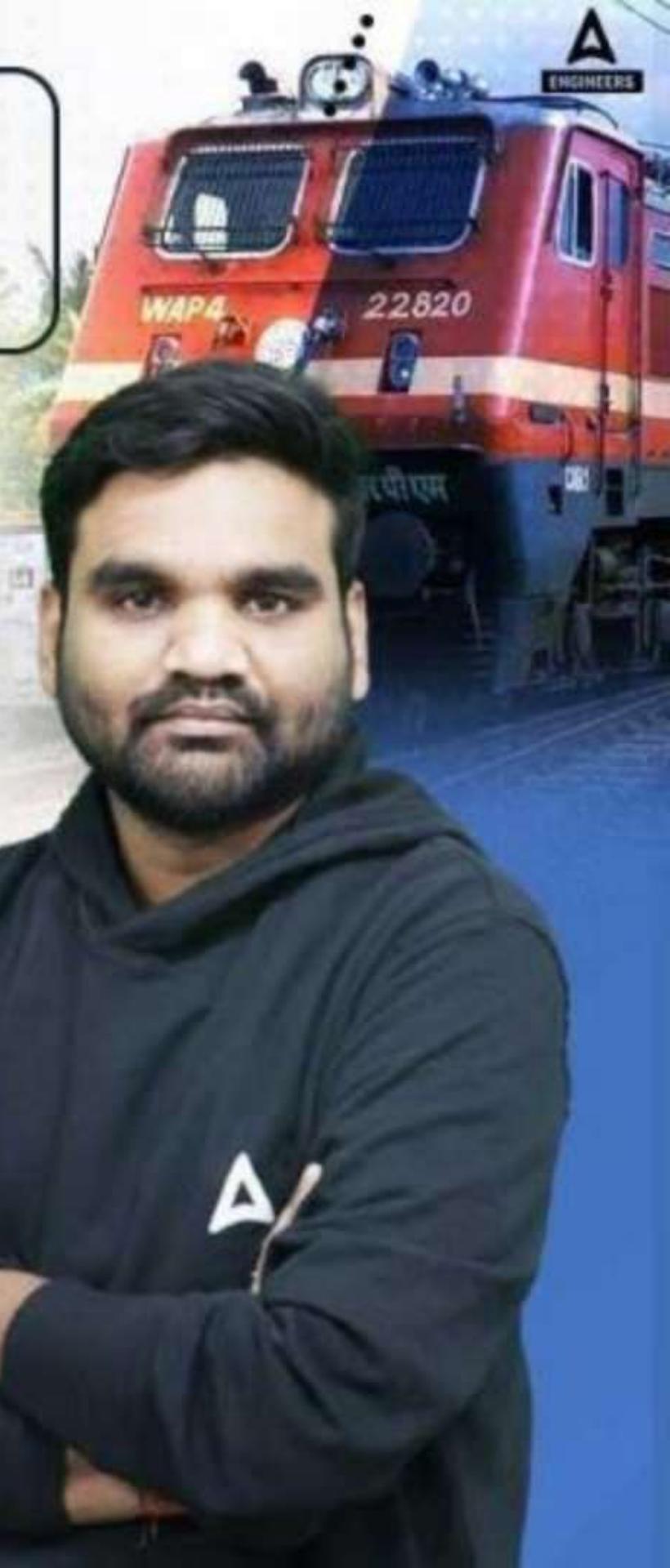




RRB JE | SSE 2023



Foundation Batch

Analog Electronics

Day-7

› LIVE

2PM

LAWRENCE Sir




Join ADDA247 MAHAPACK using code Y694 to get maximum discount



WELCOME
TO **Adda247**

We are limitless

APP FEATURES

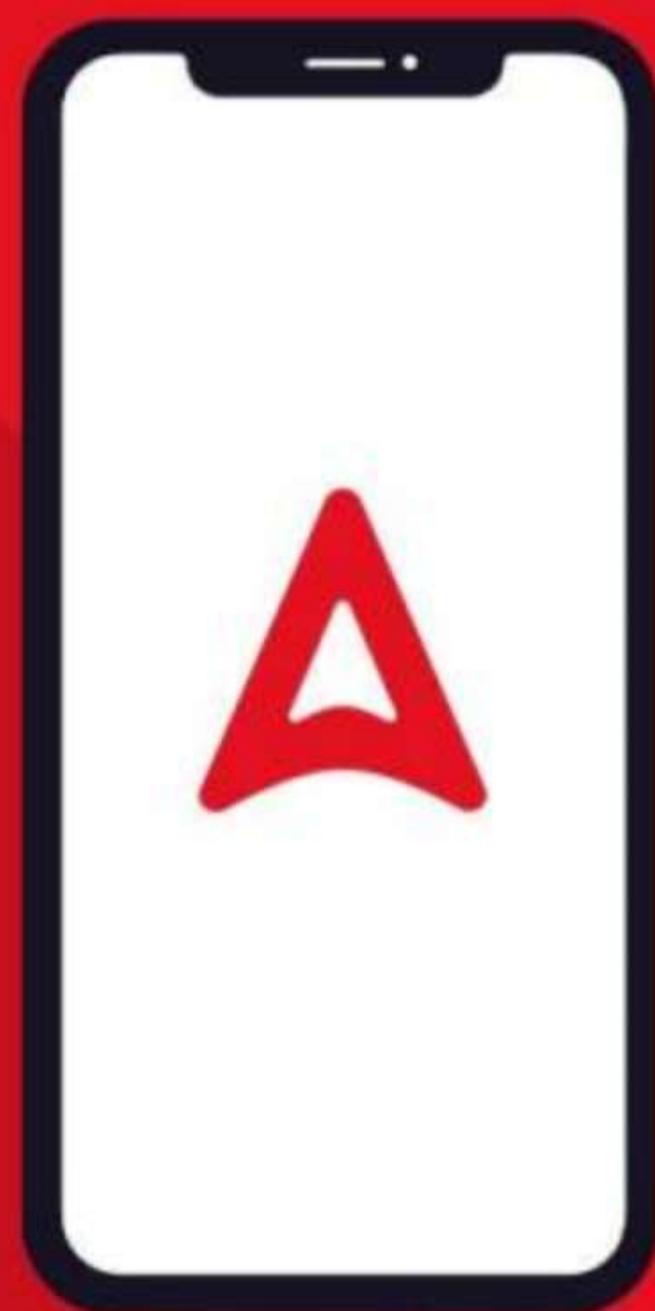

Download Now
Adda247 APP



Premium Study Material



Current Affairs



Job Alerts



Daily Quizzes



Subject-wise Quizzes



Magazines



Power Capsule



Notes & Articles



Videos

Adda247

Presents

► BIGGEST ◄

Birthday
Party
of the Year

14 Years of Success
Celebrating

Double Validity +

FLAT
77 % OFF

On All Mahapacks

₹694

USE CODE

₹694


BUY NOW ON ADDA247 APP

Offer Ending Soon



SUBSCRIBE NOW

Engineers Adda247
YouTube Channel

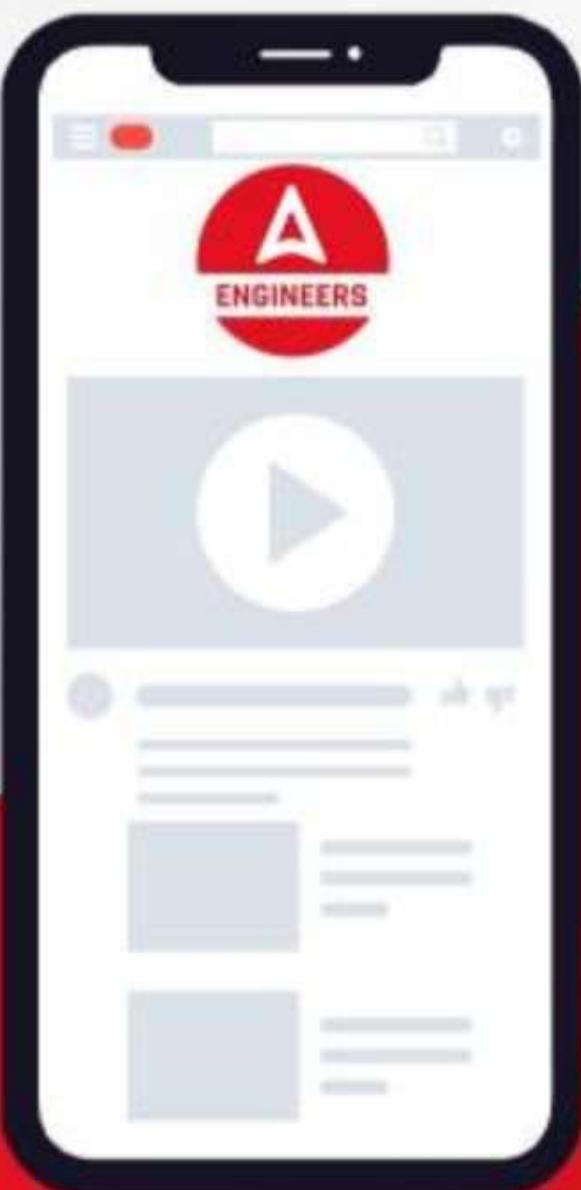



Non-Inverting Mode:

i) OP-Amp

is Ideal:

$A_V \rightarrow \infty$

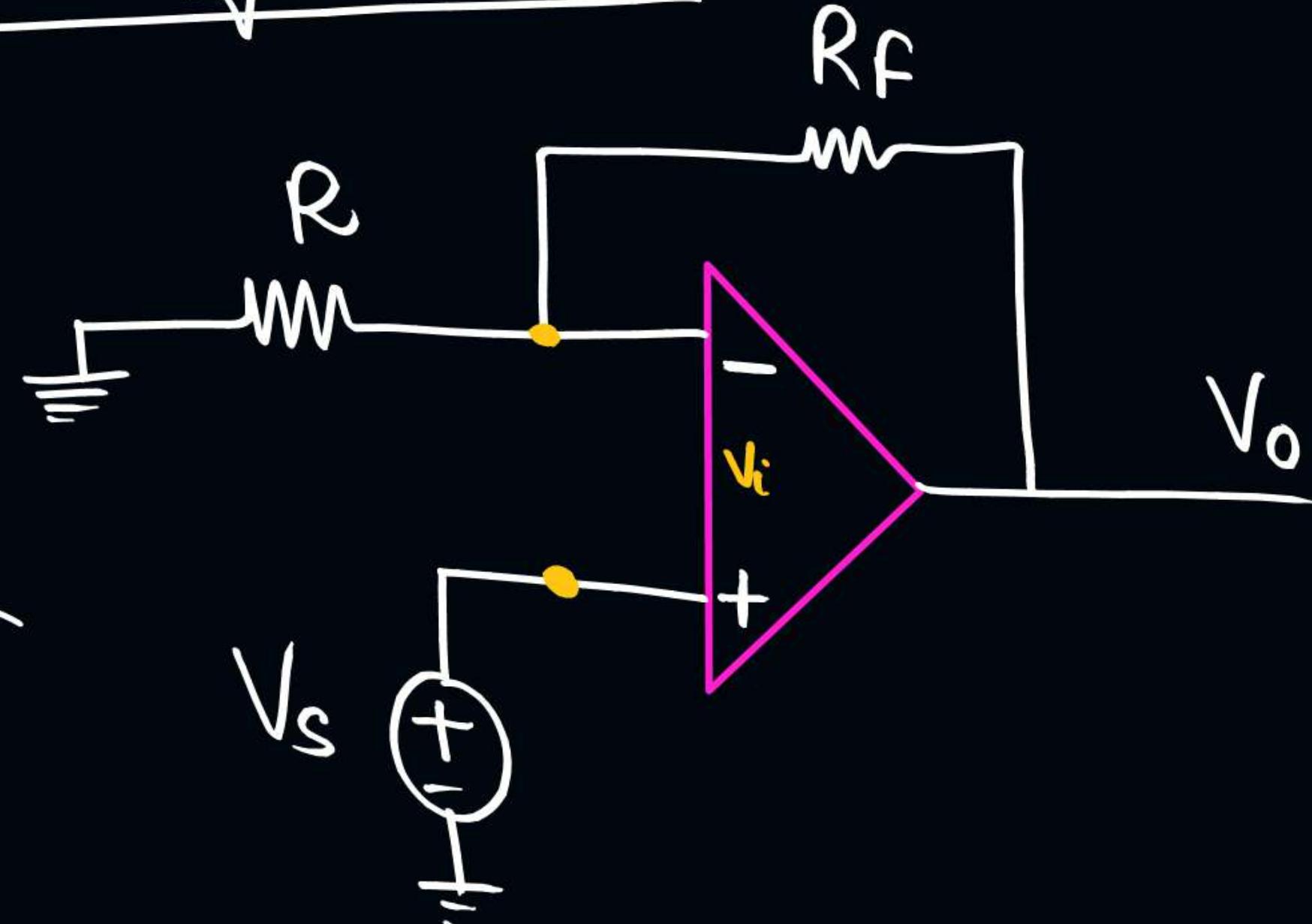

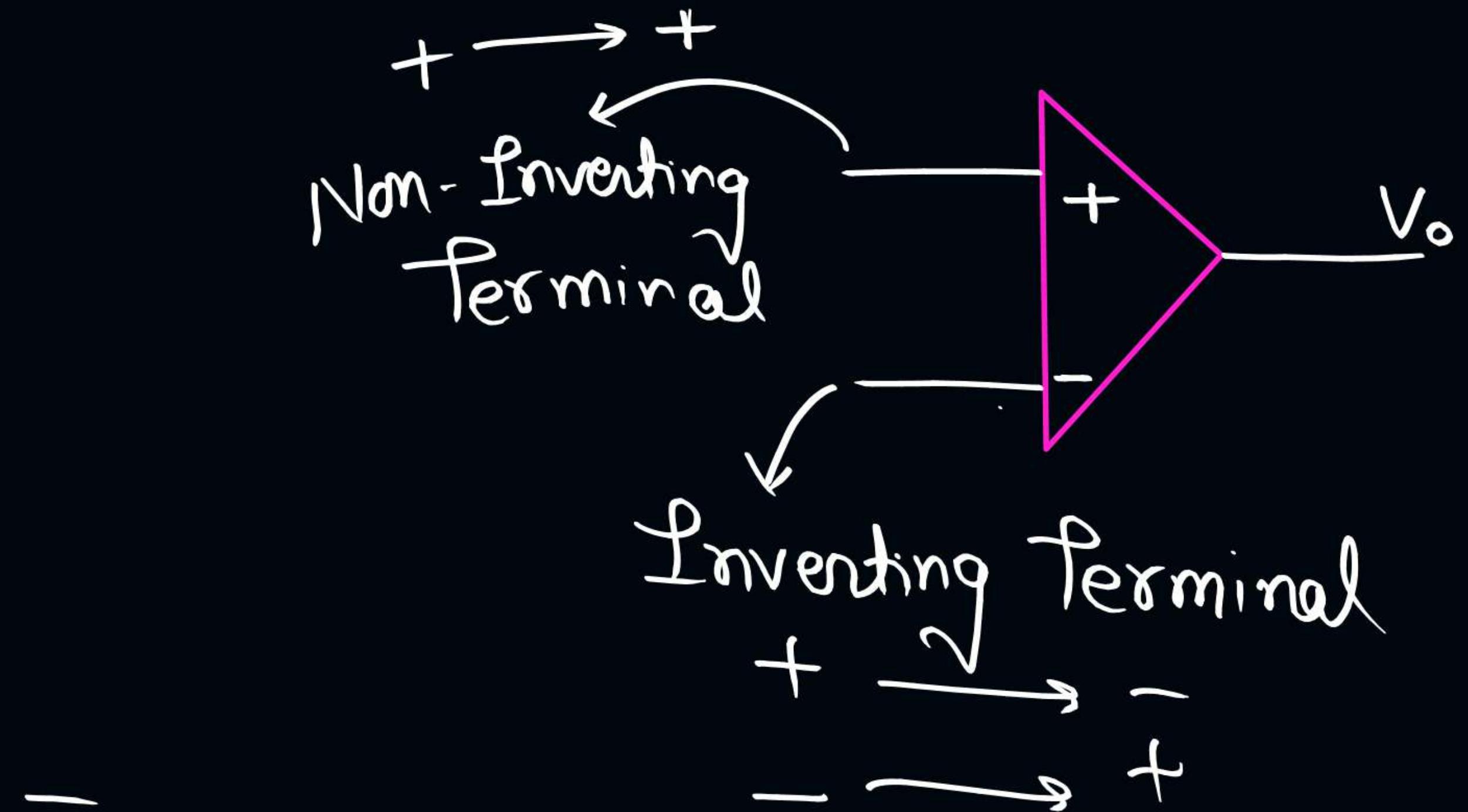


Virtual Short

Concept :


$$V_P = V_n$$

$$\rightarrow V_P = V_S = V_n$$

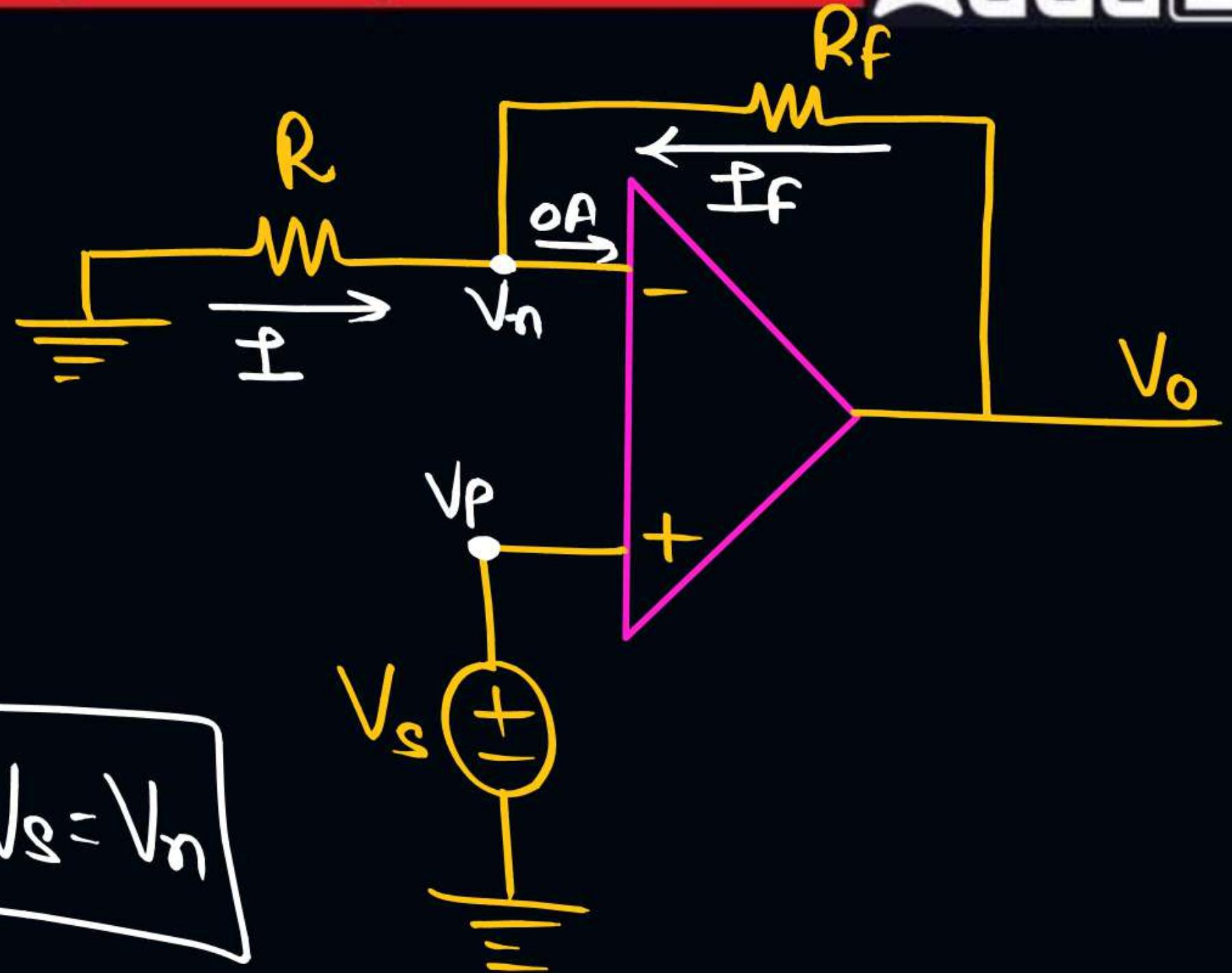


Apply KCL @ V_n :

$$I + I_f = 0$$

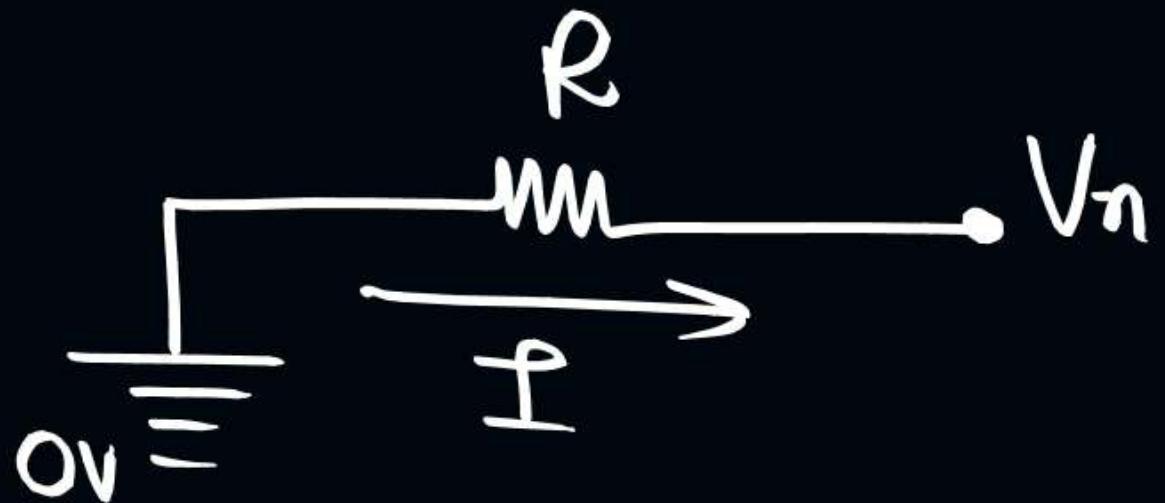

$$I = \frac{o - V_n}{R} = -\frac{V_n}{R}$$

$$I_f = \frac{V_o - V_n}{R_f}$$

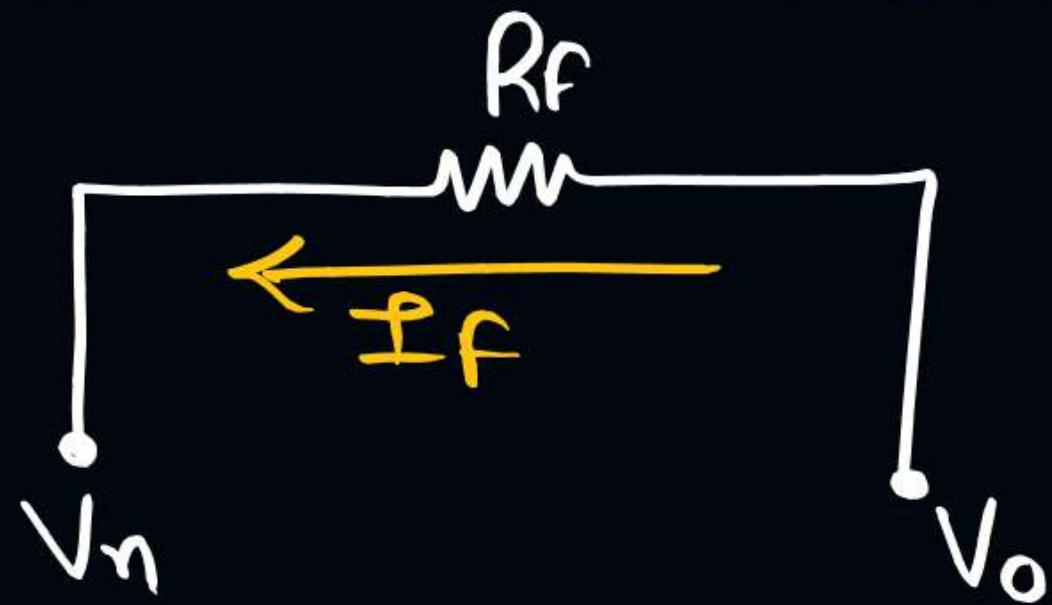

$$I + I_f = 0$$

$$-\frac{V_n}{R} + \frac{V_o - V_n}{R_f} = 0$$

Put $V_n = V_s$ (Virtual Short concept)

$$-\frac{V_s}{R} + \frac{V_o - V_s}{R_F} = 0$$

$$\frac{V_o}{R_F} - \frac{V_s}{R_F} = \frac{V_s}{R}$$

$$\frac{V_o}{R_f} = \frac{V_s}{R} + \frac{V_s}{R_f}$$

Multiply ' R_f ' both side

$$V_o = V_s \cdot \frac{R_f}{R} + V_s = V_s \left(1 + \frac{R_f}{R} \right)$$

$$\frac{V_o}{V_s} = 1 + \frac{R_f}{R}$$


$$V_o = \left(1 + \frac{R_f}{R}\right) V_s$$

If $V_s = 1V$, $R_f = R = 1K\Omega$

$$V_o = \left(1 + \frac{1K}{1K}\right) 1 \text{ volt}$$


$$V_o = 2 \text{ volt}$$

Inverting Mode

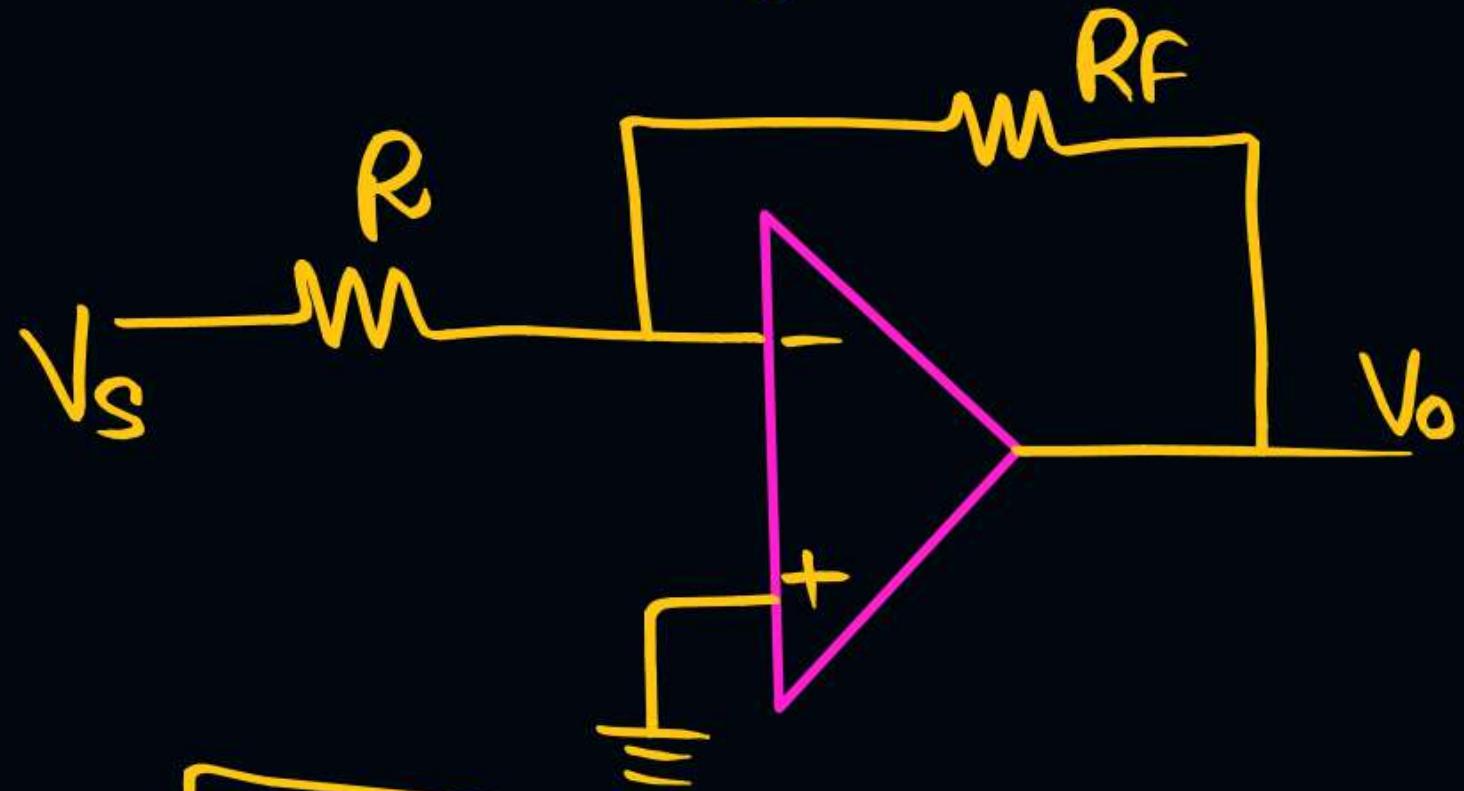

$$V_o = -\frac{R_F}{R} \cdot V_s$$

Non-Inverting Mode

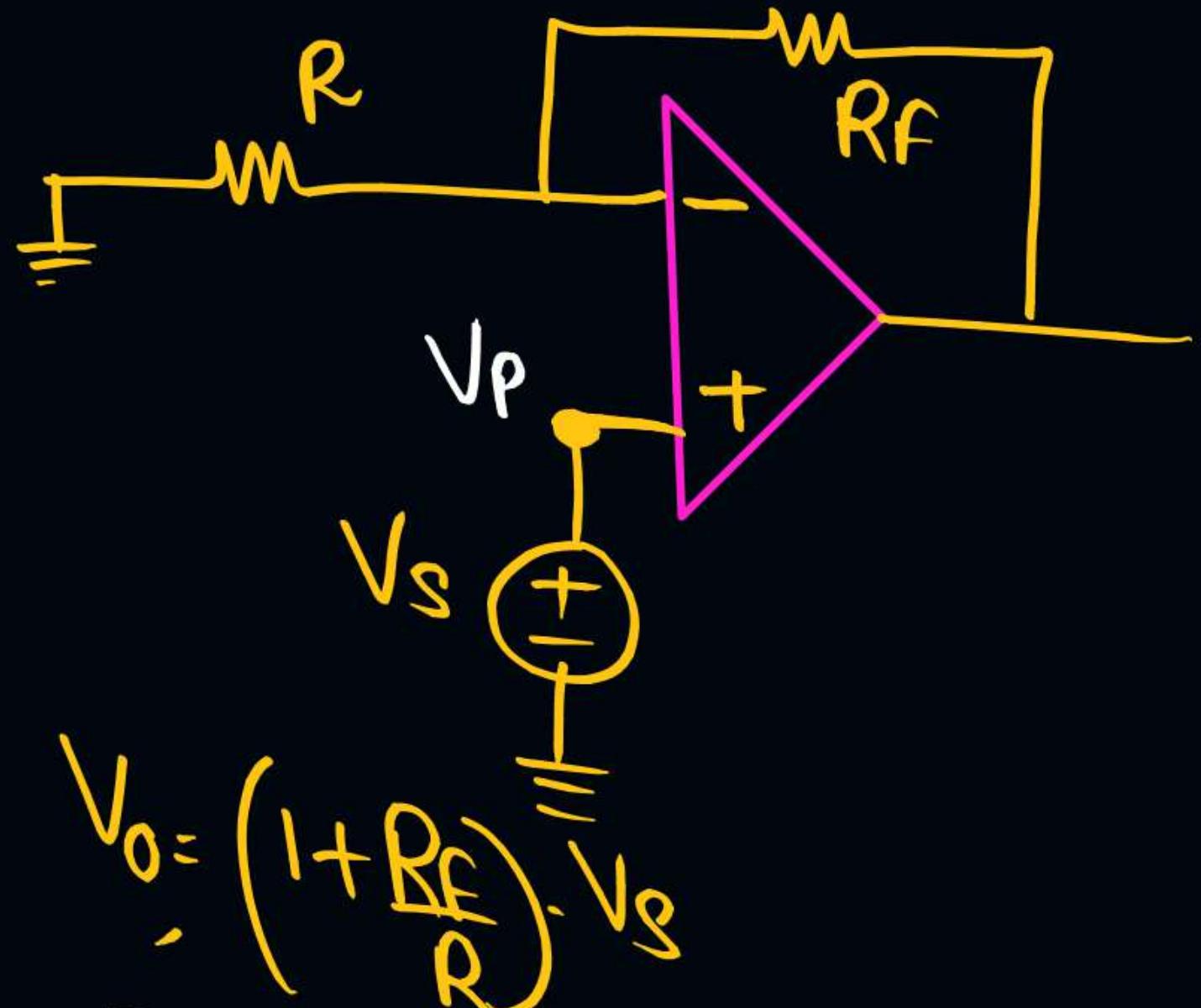


$$V_o = \left(1 + \frac{R_F}{R}\right) \cdot V_s$$

Find the value
of V_o and $\underline{P} - \underline{Q}$

Solution :

$$V_p = V_n = 4 \text{ volt}$$

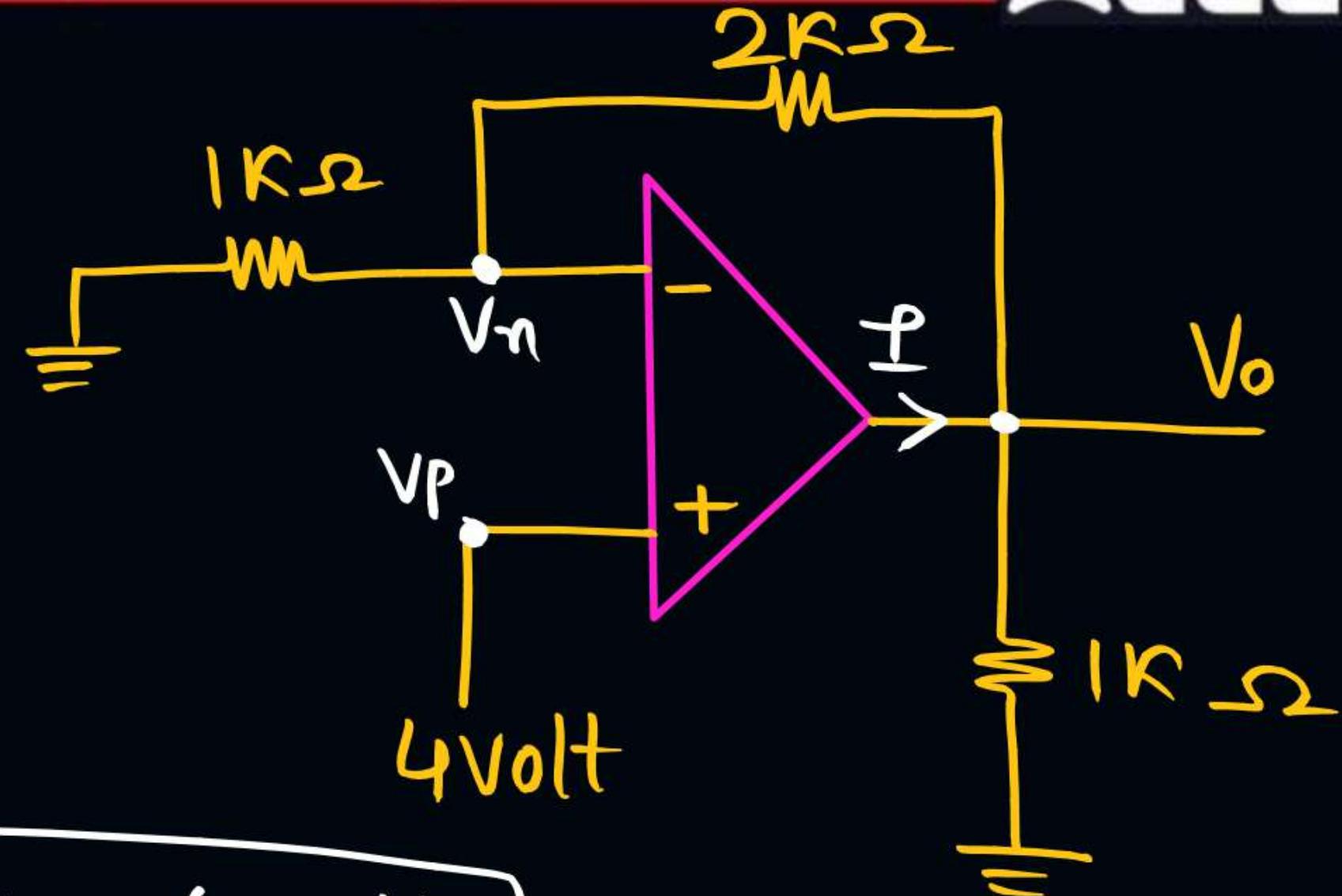


$$V_n = 4V$$

KCL @ V_n :

$$I_f = I_o + 0$$
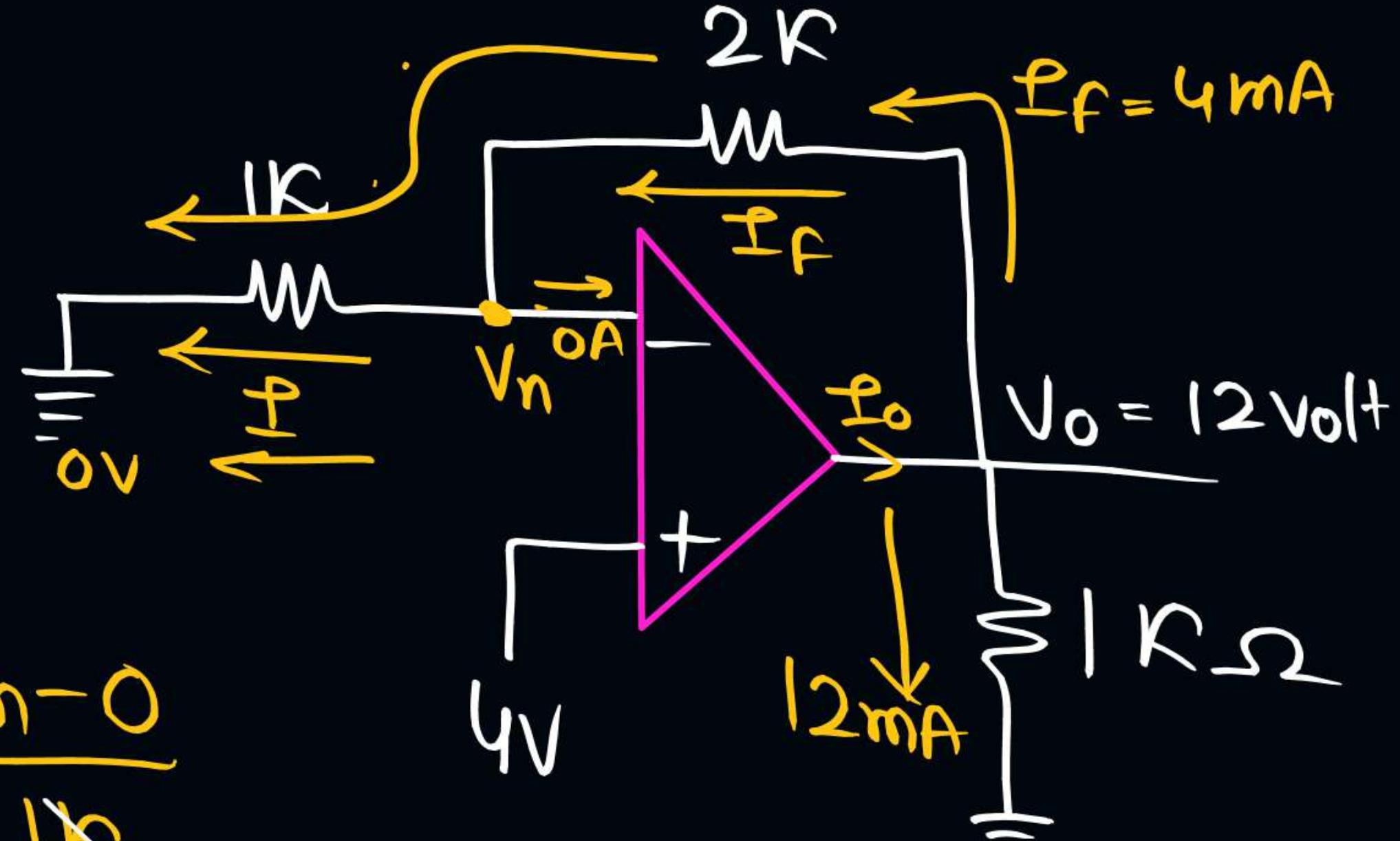
$$\frac{V_o - V_n}{2k} = \frac{V_n - 0}{1k}$$



$$\frac{V_o - 4}{2} = \frac{4}{1}$$

$$V_o - 4 = 8$$

$$V_o = 12 \text{ Volt}$$

$$V_o = \left(1 + \frac{R_f}{R}\right) \cdot V_s$$


$$= \left(1 + \frac{2k}{k}\right) \cdot 4$$


$$V_o = 12 \text{ Volt}$$

$$I = \frac{V_n - 0}{1K} = \frac{4}{1K} = 4mA$$

Find $V_o = ?$
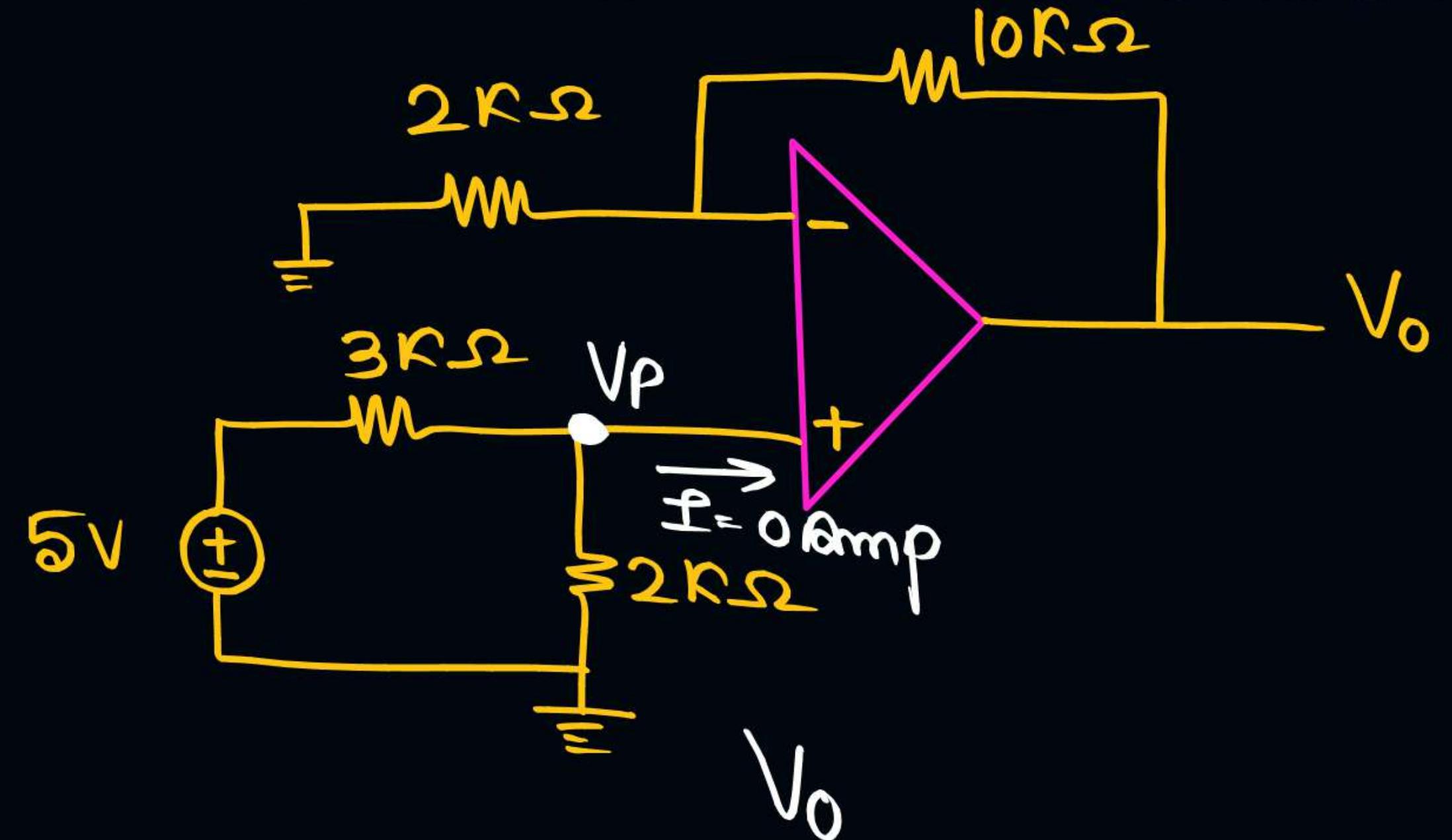
$$V_o = \left(1 + \frac{R_f}{R}\right) V_p$$



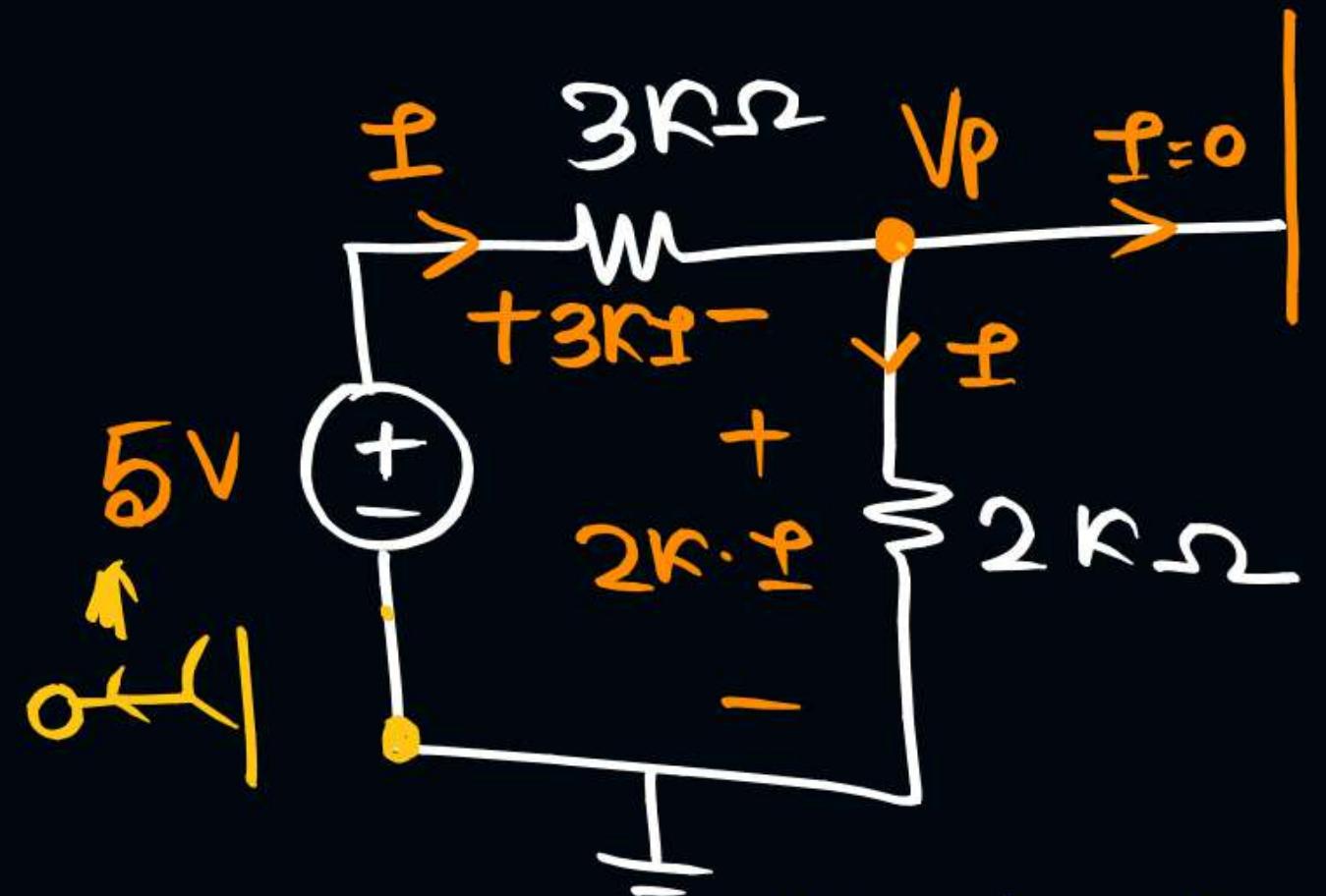

$$V_p = (2k) \cdot I$$

$$V_p = 2 \text{ Volt}$$


RVL

$$-5 + 3k \cdot I + 2k \cdot I = 0$$

$$5k \cdot I = 5$$

$$I = \frac{5}{5k}$$

$$I = 1 \text{ mA}$$

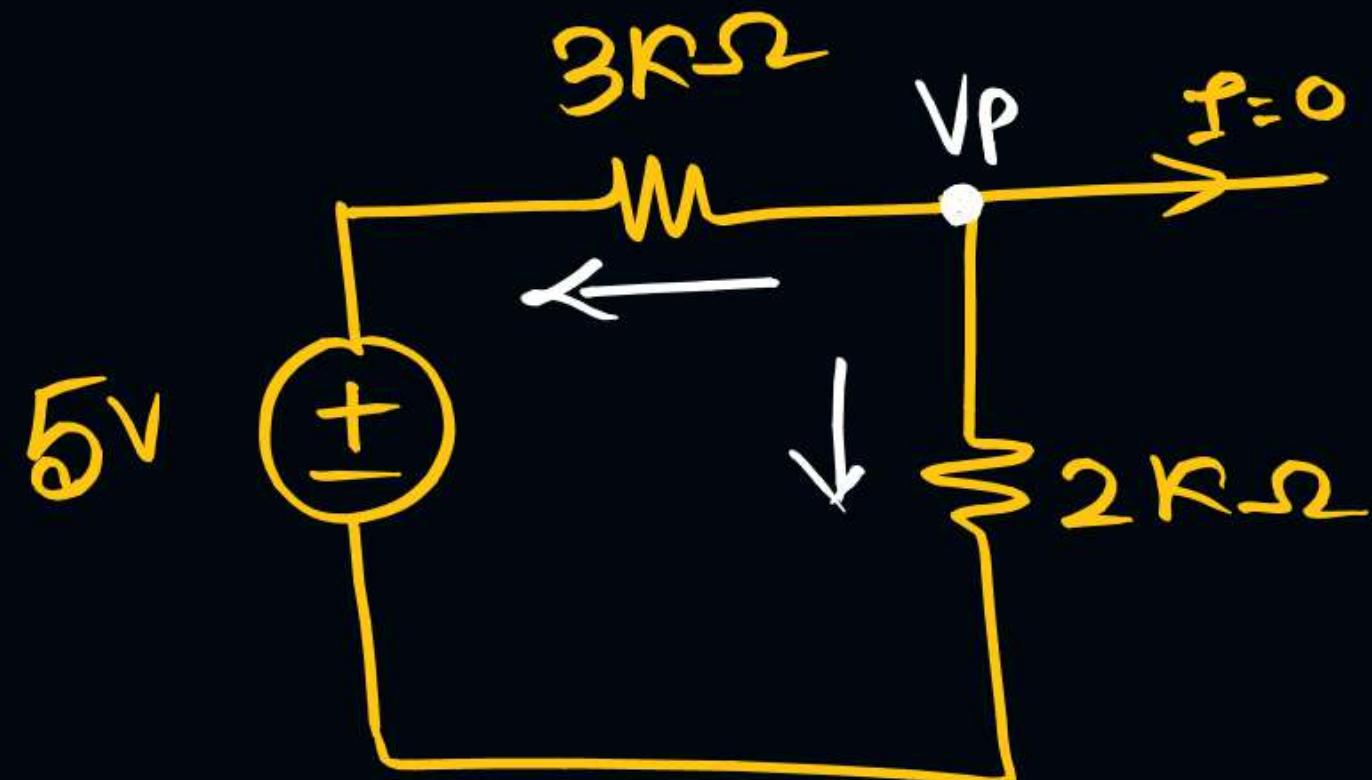

Nodal @ V_p :

$$\frac{V_p - 5}{3k} + \frac{V_p}{2k} + 0 = 0$$

$$V_p = 2 \text{ Volt}$$

$$V_o = \left(1 + \frac{10k}{2k}\right) \cdot V_p$$

$$V_o = (1 + 5)^2 = 12 \text{ Volt}$$

Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Adda247

Presents

► BIGGEST ◄

Birthday
Party
of the Year

14 Years of Success
Celebrating

Double Validity +

FLAT
77 % OFF

On All Mahapacks

Y694

USE CODE

Y694

BUY NOW ON ADDA247 APP

Offer Ending Soon

APP FEATURES



Premium Study Material



Current Affairs



Daily Quizzes



Magazines



Notes & Articles



Job Alerts



Subject-wise Quizzes



Power Capsule




Videos



SUBSCRIBE NOW

Engineers Adda247
YouTube Channel

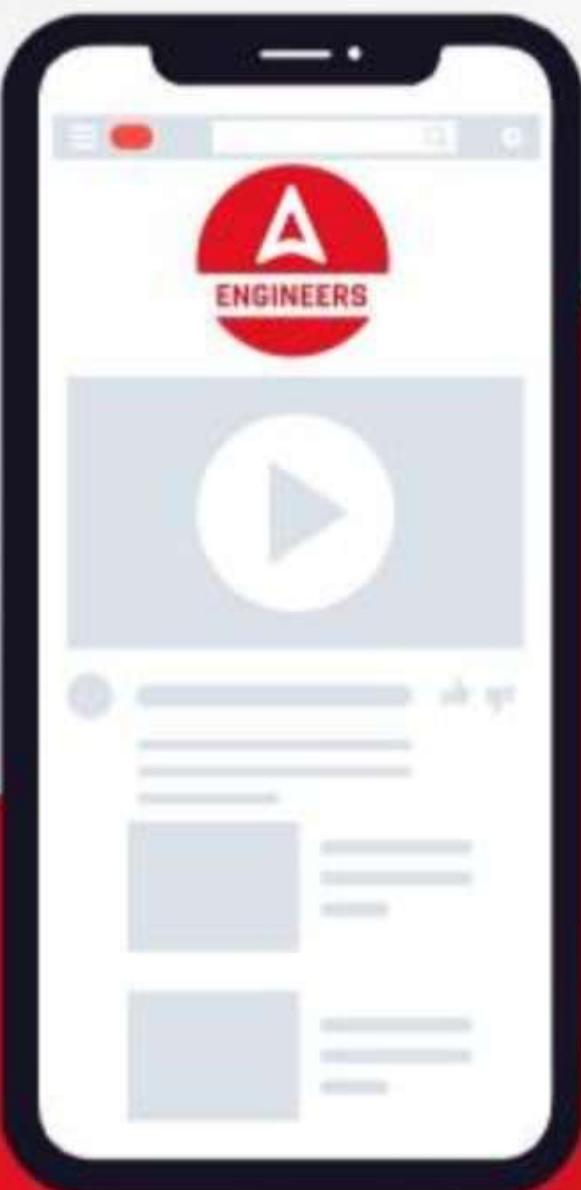

THANKS FOR

Watching
Adda247

