





# RRB JE | SSE 2023

## Foundation Batch

### Analog Electronics

### Day-11

> LIVE

2PM

LAWRENCE Sir



Join ADDA247 MAHAPACK using code Y694 to get maximum discount

**Adda247**

**WELCOME**  
**TO Adda247**

**We are limitless**

# APP FEATURES



**Download Now**  
**Adda247 APP**



Premium Study Material



Current Affairs



Job Alerts



Daily Quizzes



Subject-wise Quizzes



Magazines



Power Capsule



Notes & Articles



Videos

Adda247

Presents

▶ BIGGEST ◀

Birthday  
Party

of the Year

Celebrating  
**14**  
Years of  
**Success**

**Double Validity +**

FLAT  
**77** % OFF


On All Mahapacks

USE CODE

**Y694**

BUY NOW ON ADDA247 APP

Offer Ending Soon

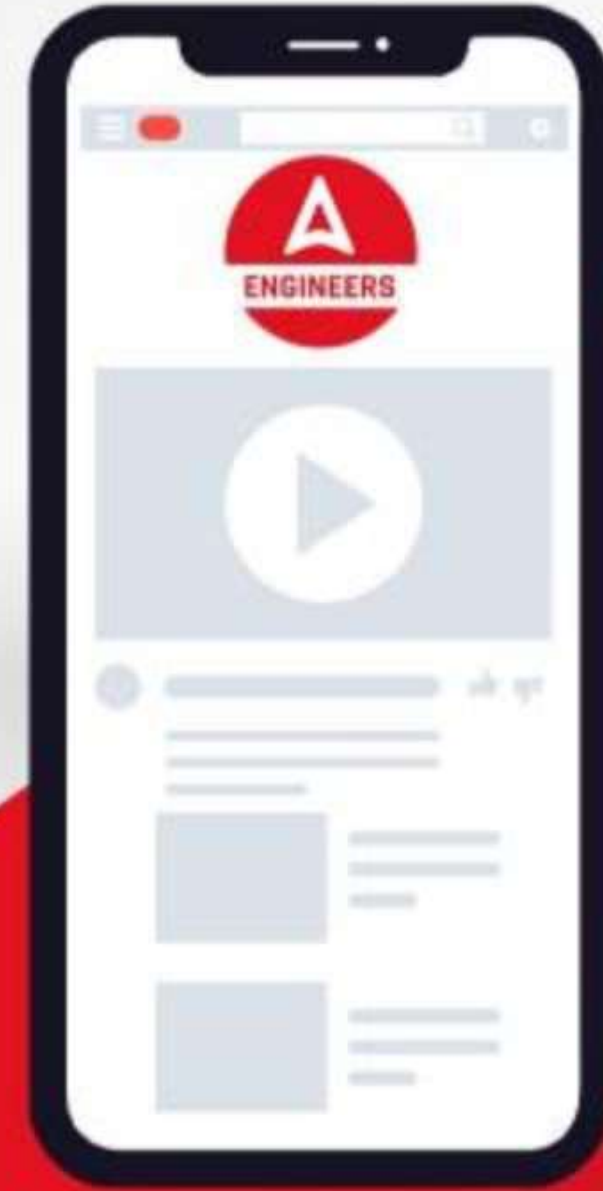

**SUBSCRIBE NOW**

↗ **Engineers Adda247**  
YouTube Channel

Application of OP-Amp :

→ Summer :

→ Inverting Summer

→ Non-Inverting Summer

Voltage  $\rightarrow$   $\underline{V_1 = 2V}$   $\underline{V_2 = 5V}$

Inverting Summer Output =  $-7$

Non-Inverting Summer Output =  $7$




Inverting Summer:

2 Input Inverting Summer:

①  $V_1$

②  $V_2$

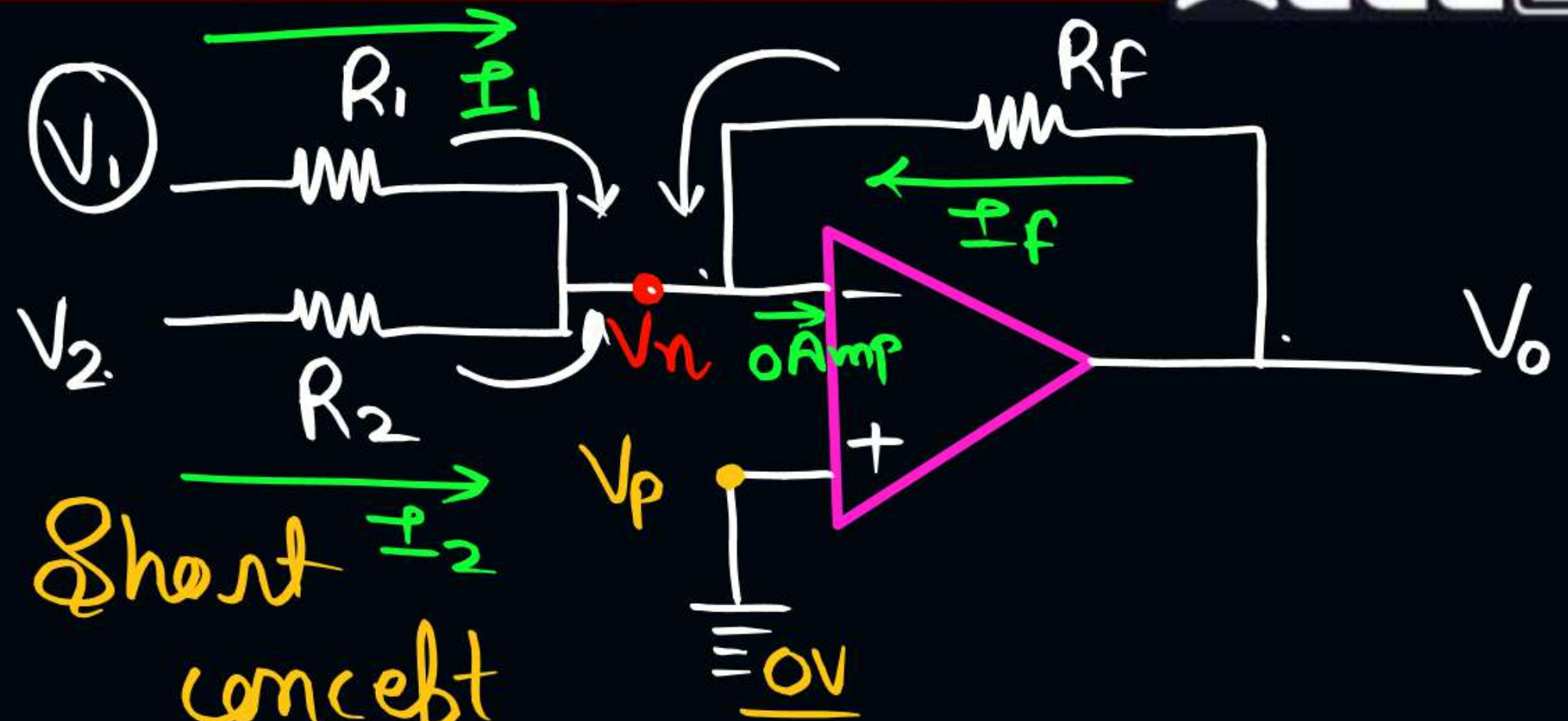

$V_p = 0 = V_n$

Virtual Short concept

Apply KCL @  $V_n$ :

$$I_1 + I_2 + I_f = 0$$

$$\frac{V_1 - V_m}{R_1} + \frac{V_2 - V_m}{R_2} + \frac{V_0 - V_m}{R_f} = 0$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_0}{R_f} = 0$$

$$\frac{V_0}{R_f} = -\frac{V_1}{R_1} - \frac{V_2}{R_2}$$

$$V_0 = \left(-\frac{R_f}{R_1}\right)V_1 + \left(-\frac{R_f}{R_2}\right)V_2$$


If  $R_1 = R_2 = R_f = R$

$$V_0 = -\frac{R}{R} \cdot V_1 + \left(-\frac{R}{R}\right) \cdot V_2$$

$$V_0 = -V_1 - V_2$$

$$V_0 = -(V_1 + V_2) \rightarrow$$

2 Input Inverting Summer:

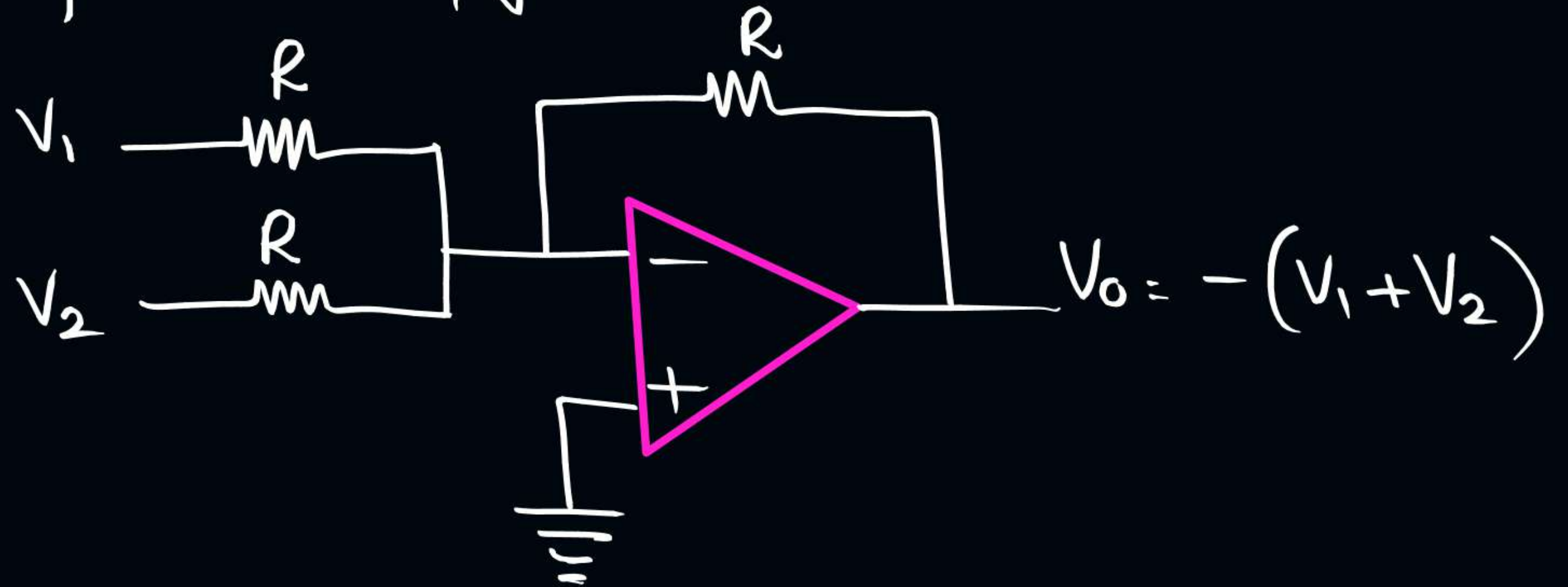


Ques: Design Three input Inverting  
Summer and write the  
condition for  $R_1, R_2, R_3$  and  $R_F$   
for Inverting Summer?

$$V_p = 0 = V_n$$



Virtual Short concept

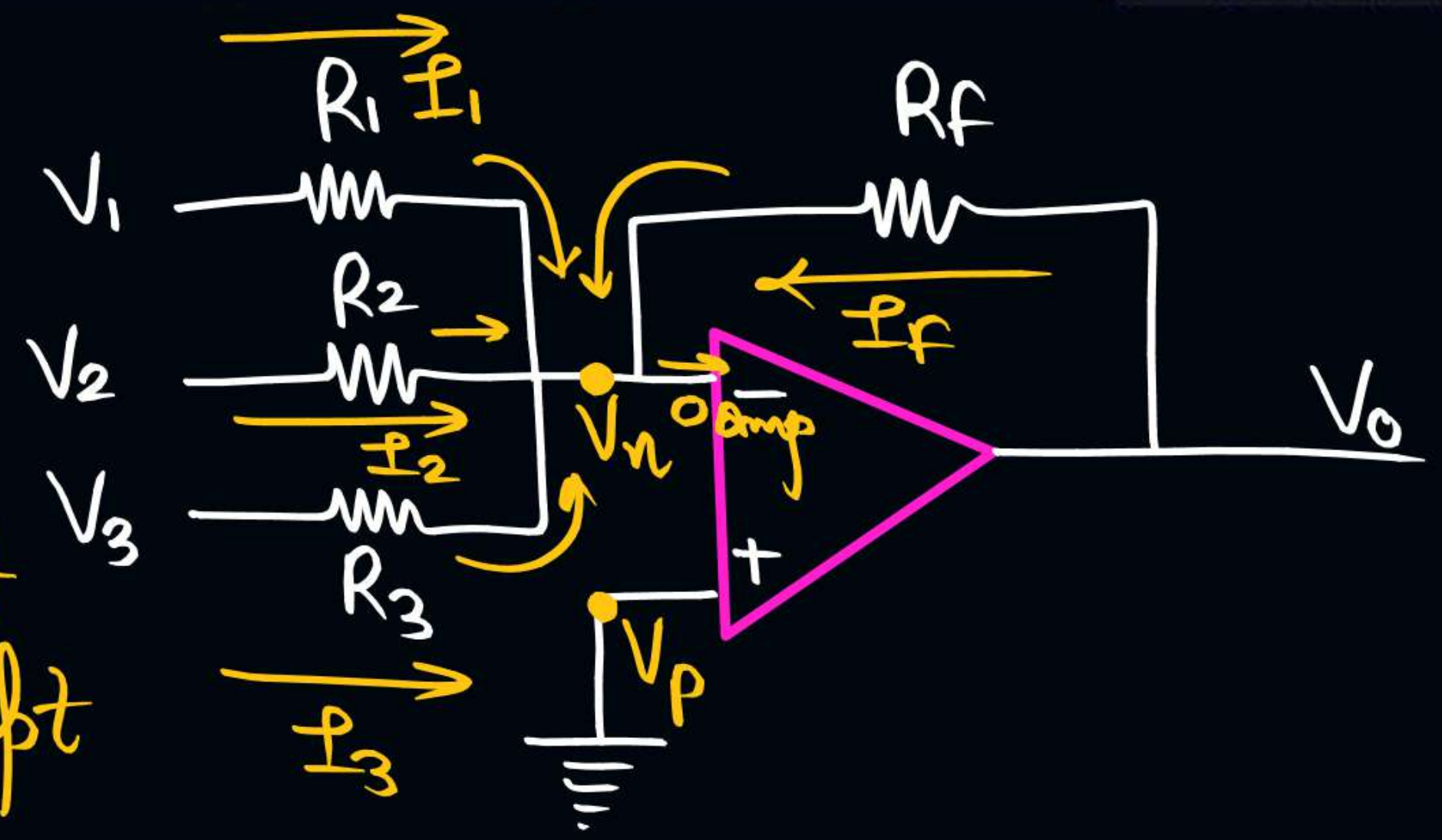



Apply KCL @  $V_n$ :

$$I_1 + I_2 + I_3 + I_f = 0$$

$$\frac{V_1 - V_n}{R_1} + \frac{V_2 - V_n}{R_2} + \frac{V_3 - V_n}{R_3} + \frac{V_0 - V_n}{R_f} = 0$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_0}{R_f} = 0$$


$$\frac{V_0}{R_f} = -\frac{V_1}{R_1} - \frac{V_2}{R_2} - \frac{V_3}{R_3}$$

★ 
$$V_0 = \left(-\frac{R_f}{R_1}\right)V_1 + \left(-\frac{R_f}{R_2}\right)V_2 + \left(-\frac{R_f}{R_3}\right)V_3$$


Condition for Summer:

$$R_f = R_1 = R_2 = R_3 = R$$

$$V_0 = -(V_1 + V_2 + V_3)$$

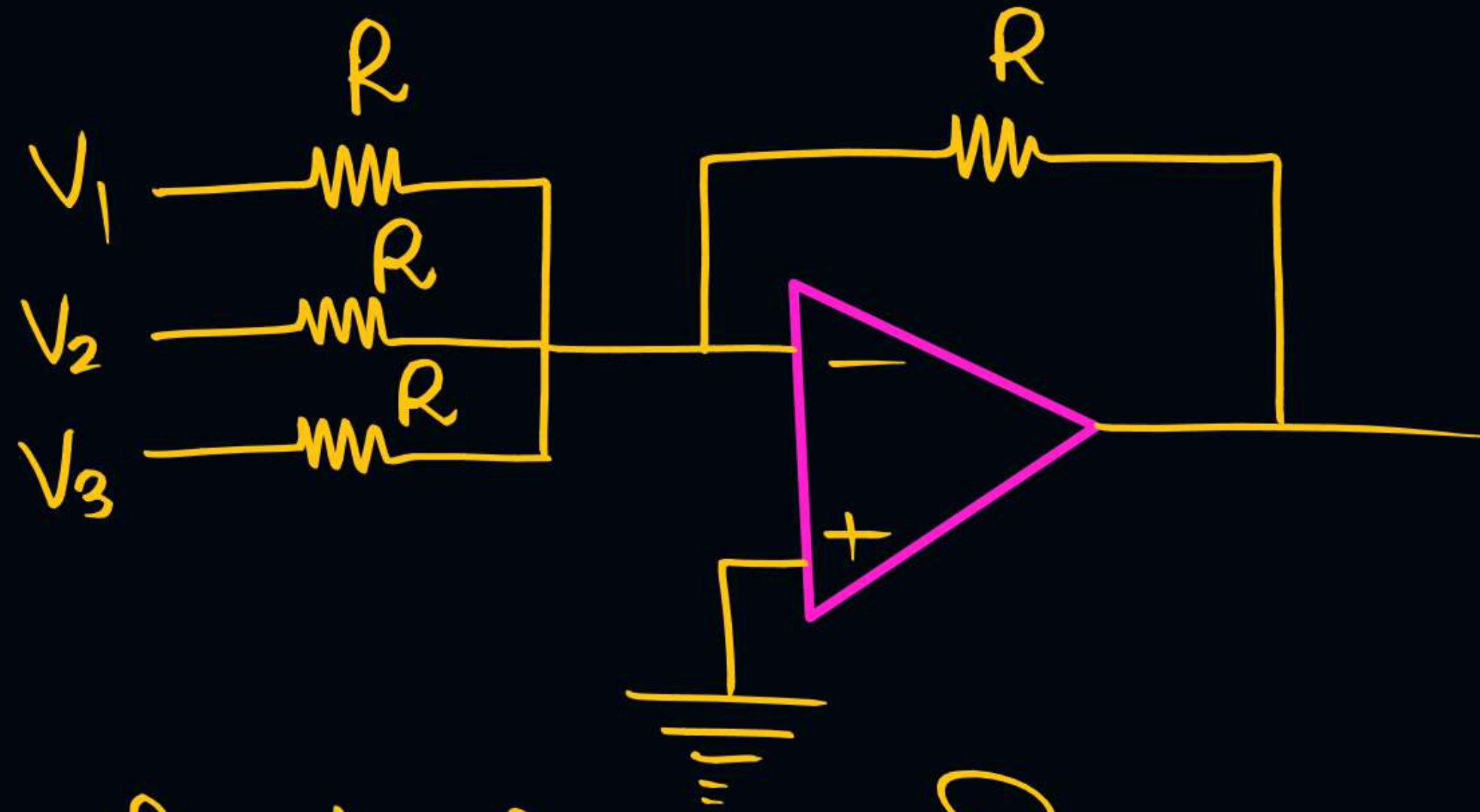

3 - Input Inverting Summer:

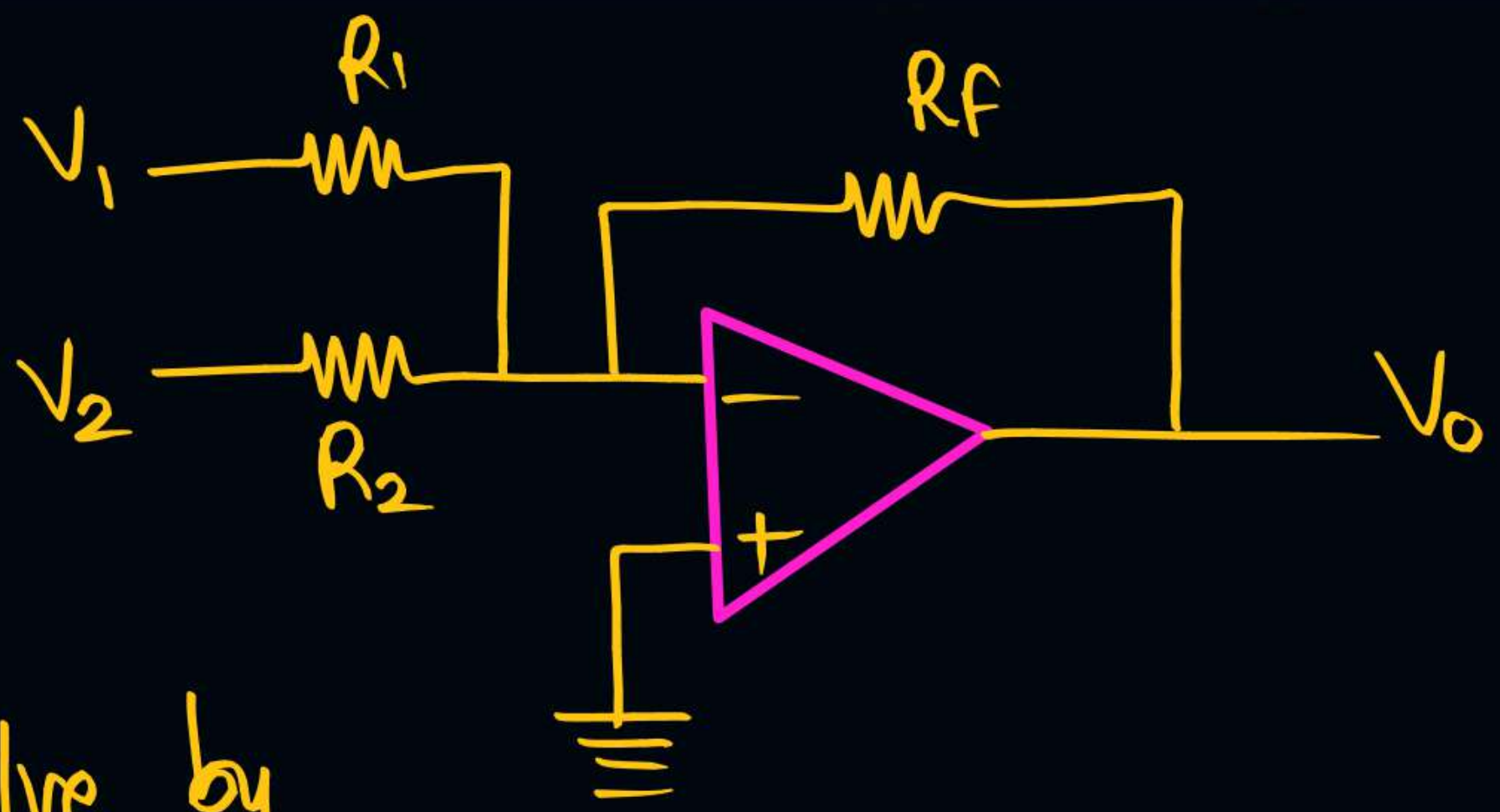


Solve by

Super-Position theorem

$V_1 \rightarrow \text{Active}$   
 $V_2 \rightarrow 0$

find  $V_0' = ?$

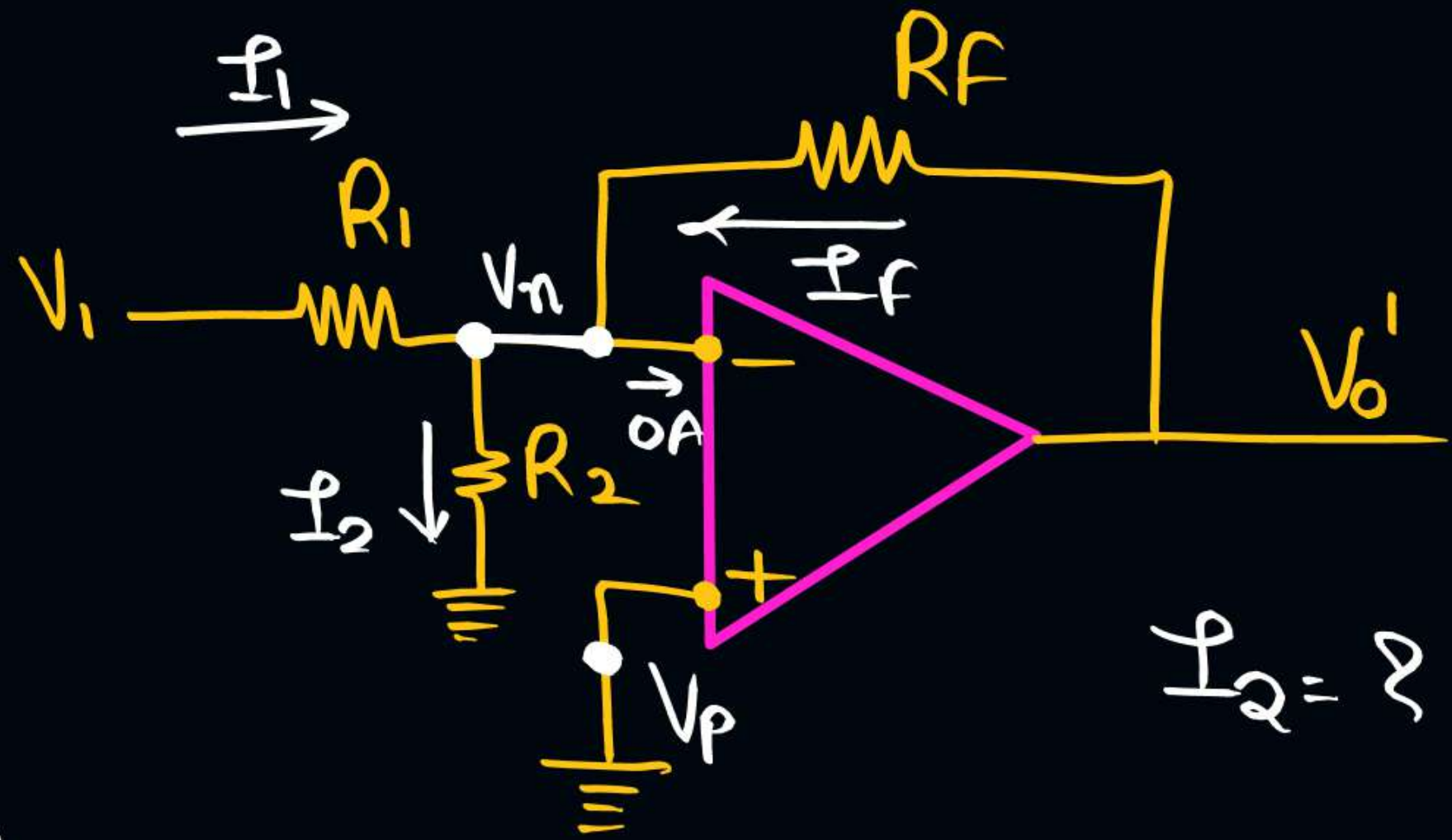

$V_p = 0 = V_n$

Virtual Short Concept


$$I_2 = ? = \frac{V_n - 0}{R_2} = 0 \text{ Amp}$$

KCL @  $V_n$ :

$$I_1 + I_f = 0$$

$$\frac{V_1 - V_n}{R_1} + \frac{V_o - V_n}{R_f} = 0$$


$$V_o = -\frac{R_f}{R_1} V_1$$

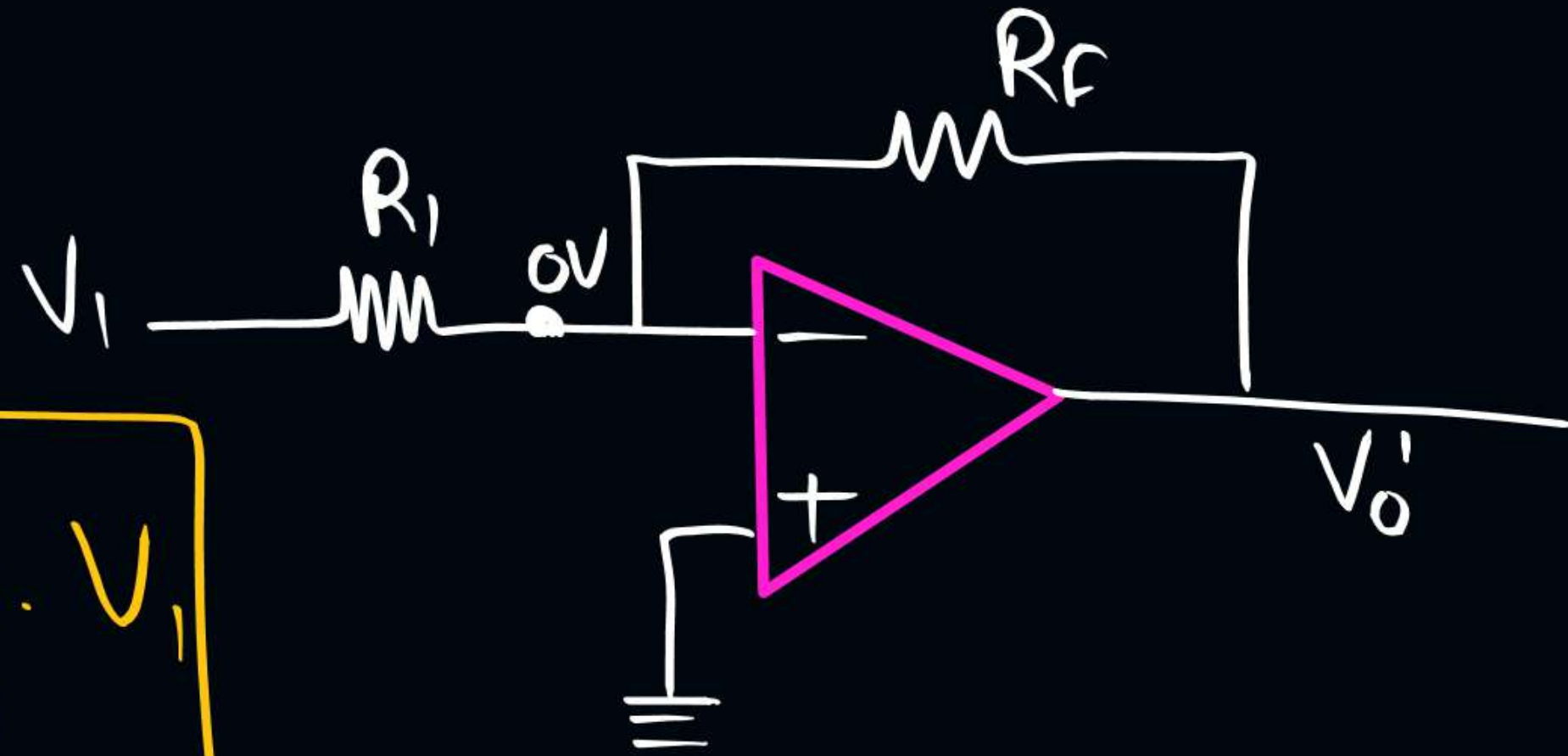

$$V_0' = -\frac{R_f}{R_1} \cdot V_1$$




$V_2$  - Active  
 $V_1$  → Inactive

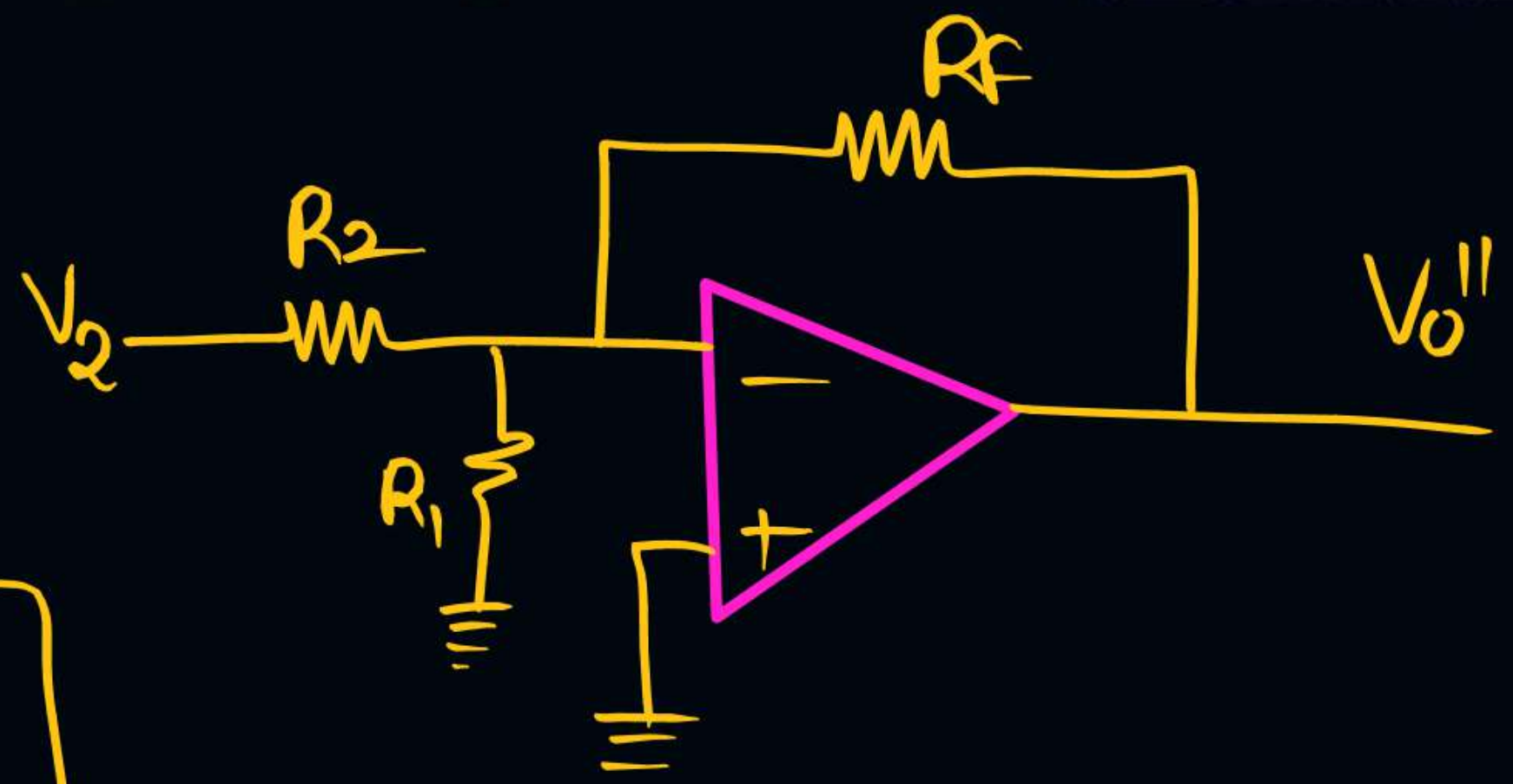

$$V_{o''} = -\frac{R_f}{R_2} \cdot V_2$$

$$V_o = V_o' + V_o''$$
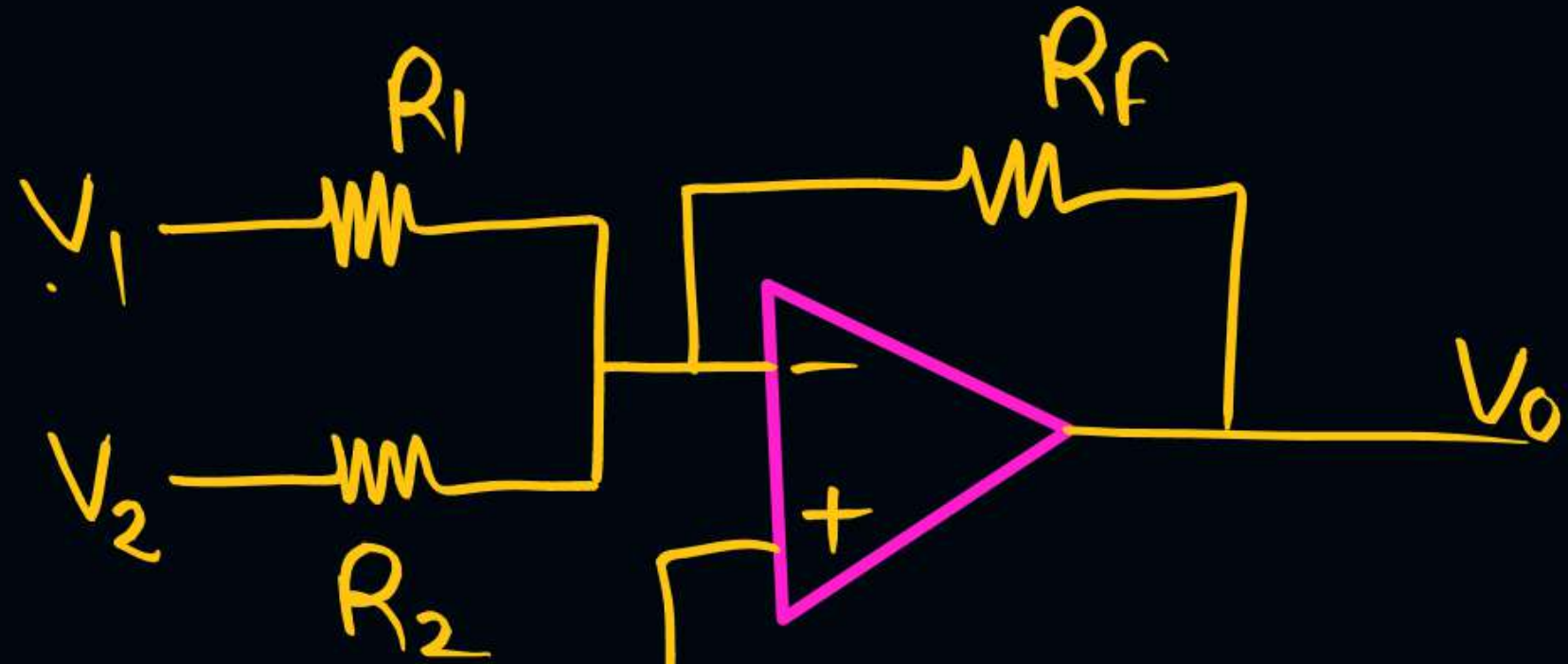
$$V_o = -\frac{R_f}{R_1} V_1 + \left(-\frac{R_f}{R_2}\right) V_2$$



★ 
$$V_o = -\frac{R_f}{R_1} (V_1) + \left( -\frac{R_f}{R_2} \right) V_2$$

Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount





Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount





Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount





Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Adda247

Presents

▶ BIGGEST ◀

Birthday  
Party

of the Year

Celebrating  
**14**  
Years of  
**Success**

**Double Validity +**

FLAT  
**77** % OFF

On All Mahapacks

USE CODE

**Y694**

BUY NOW ON ADDA247 APP

Offer Ending Soon

# APP FEATURES



**Download Now**  
**Adda247 APP**



Premium Study Material



Current Affairs



Job Alerts



Daily Quizzes



Subject-wise Quizzes



Magazines




Power Capsule



Notes & Articles



Videos

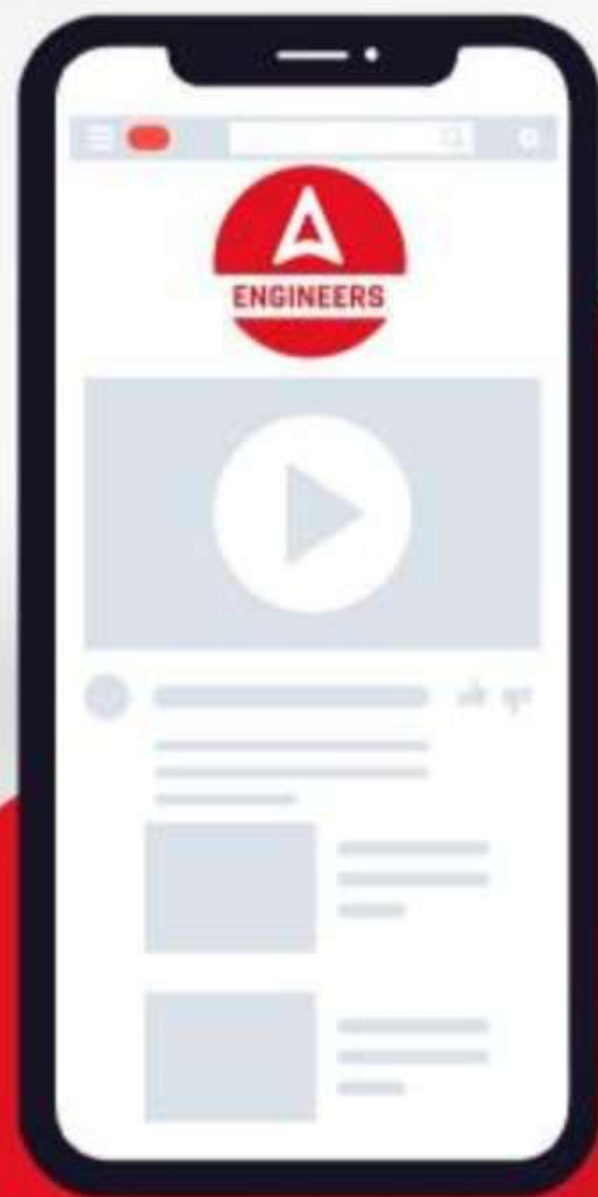

**SUBSCRIBE NOW**

**Engineers Adda247**  
YouTube Channel

THANKS FOR

# Watching

Adda247

LIKE



SHARE



COMMENT



SUBSCRIBE

