



RRB JE | SSE 2023

Foundation Batch

Analog Electronics

Day-12

> LIVE

2PM

LAWRENCE Sir



Join ADDA247 MAHAPACK using code Y694 to get maximum discount

Adda247

WELCOME
TO Adda247

We are limitless

APP FEATURES



Download Now
Adda247 APP



Premium Study Material



Current Affairs



Job Alerts



Daily Quizzes



Subject-wise Quizzes



Magazines



Power Capsule



Notes & Articles



Videos

Adda247

Presents

▶ BIGGEST ◀

Birthday
Party

of the Year

Celebrating
14
Years of
Success

Double Validity +

FLAT
77 % OFF


On All Mahapacks

USE CODE

Y694

BUY NOW ON ADDA247 APP

Offer Ending Soon

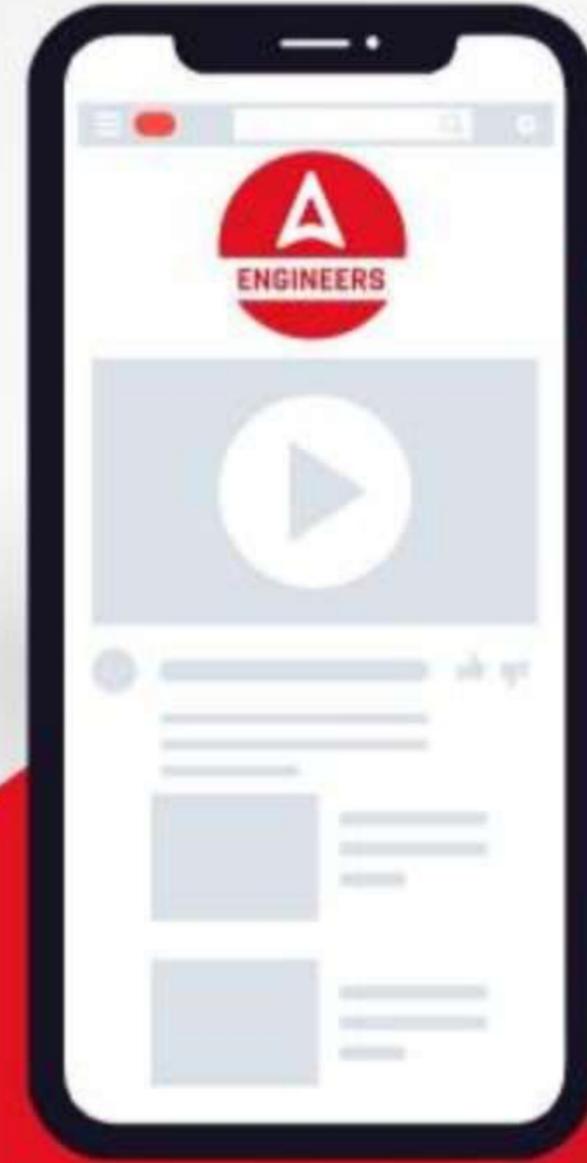

SUBSCRIBE NOW

Engineers Adda247

YouTube Channel


Non Inverting Summer:

$$V_1 = 4V \quad \& \quad V_2 = 3 \text{ volt}$$

$$\text{Non-Inverting Summer o/p} = 4 + 3 \\ = 7 \text{ volt}$$

Two Input Non-Inverting Summer:

Find $V_o = ?$

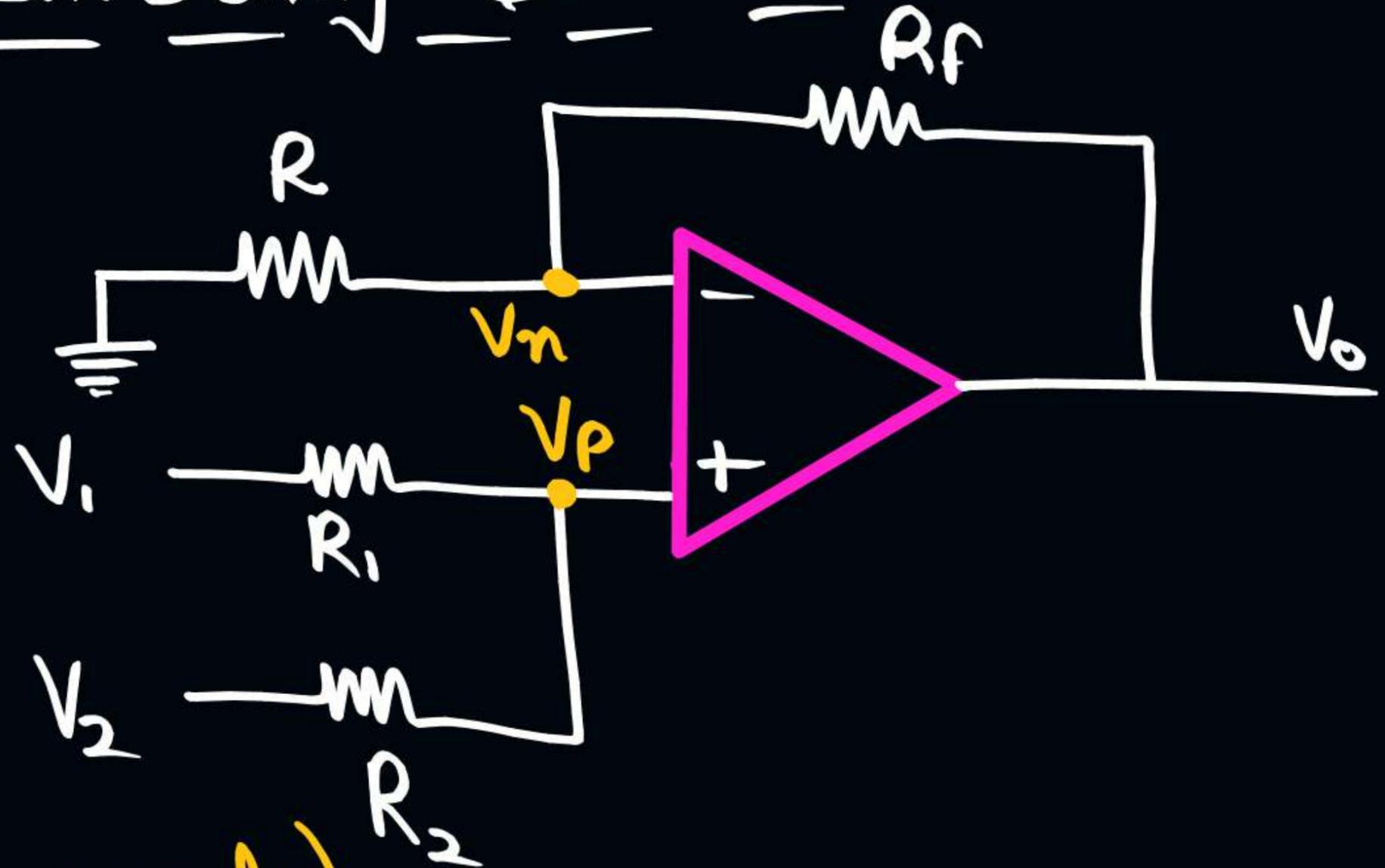


$V_n = V_p$ (Virtual Short concept)

KCL @ V_p :

$$I_1 + I_2 = 0$$
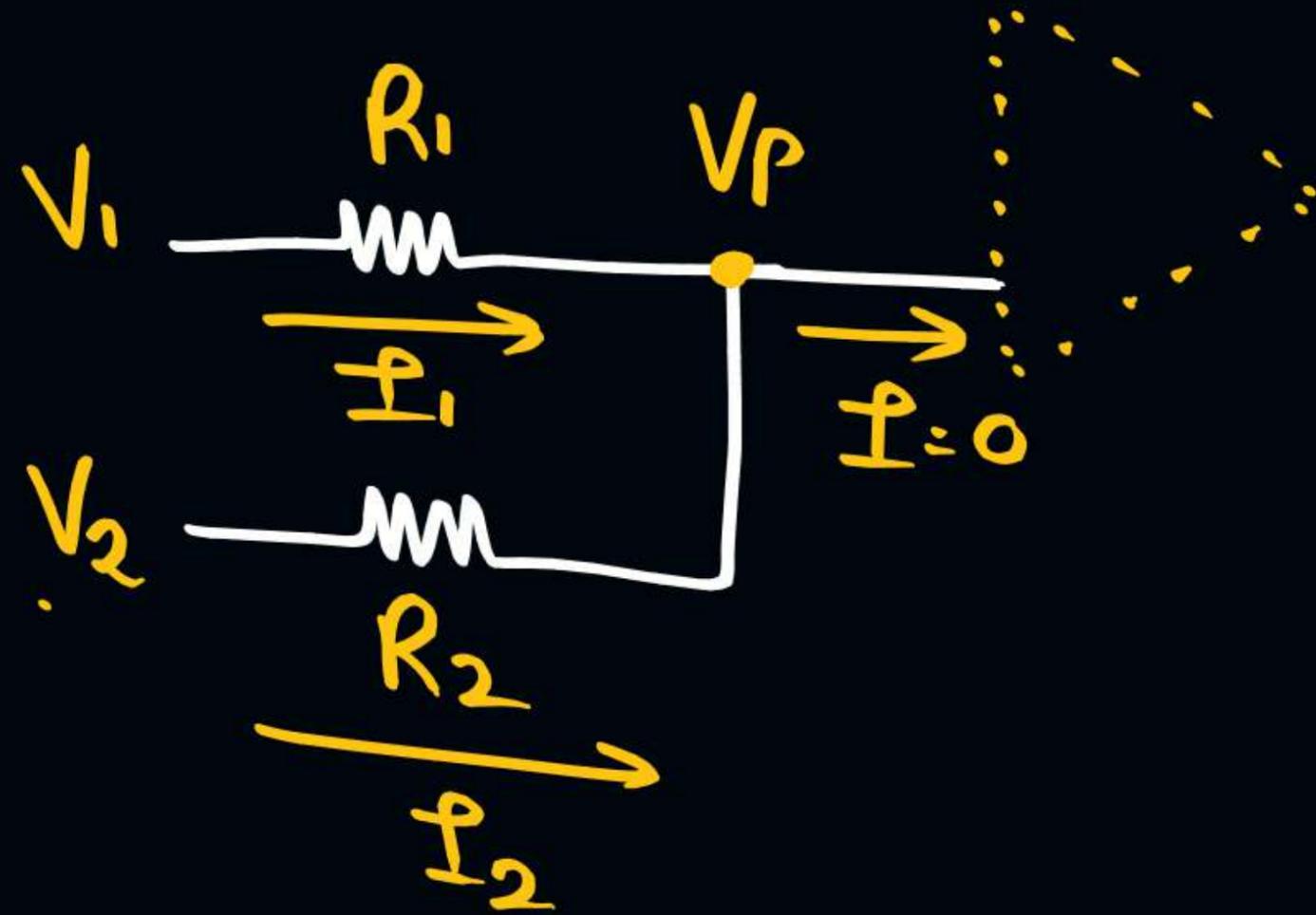
$$\frac{V_1 - V_p}{R_1} + \frac{V_2 - V_p}{R_2} = 0$$



$$\frac{V_1 - V_P}{R_1} + \frac{V_2 - V_P}{R_2} = 0$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} - \frac{V_P}{R_1} - \frac{V_P}{R_2} = 0$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{V_P}{R_1} + \frac{V_P}{R_2}$$

$$\frac{V_1 \cdot R_2 + V_2 \cdot R_1}{\cancel{R_1 R_2}} = \frac{V_p R_2 + V_p \cdot R_1}{\cancel{R_1 R_2}}$$


$$V_p (R_1 + R_2) = V_1 R_2 + V_2 \cdot R_1$$

$$\star \quad V_p = \frac{V_1 \cdot R_1}{R_1 + R_2} + \frac{V_2 \cdot R_1}{R_1 + R_2}$$

$$V_p = \frac{V_1 \cdot R_2 + V_2 \cdot R_1}{R_1 + R_2}$$


Q.: $R_1 = R_2 = R'$
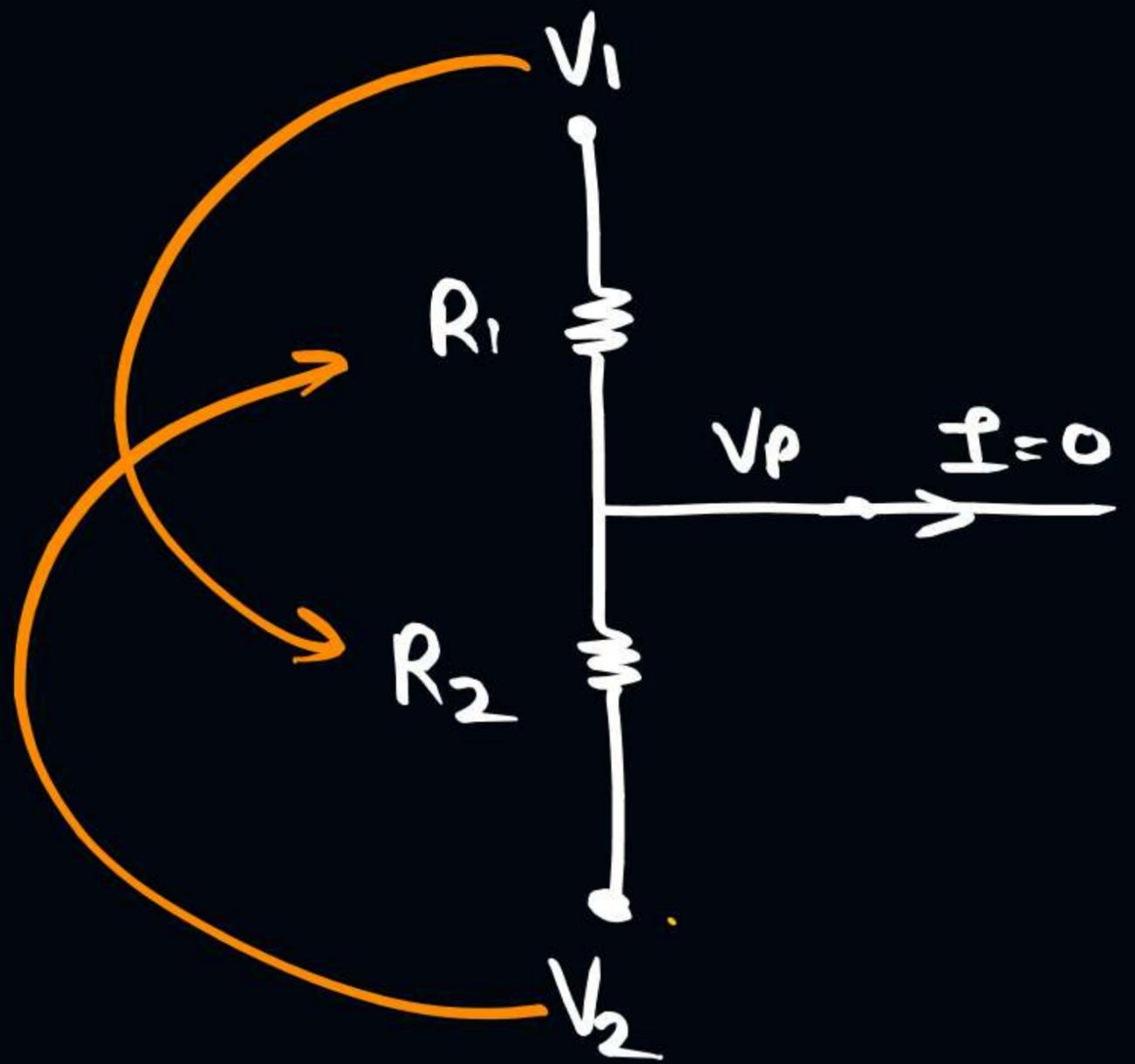
$$V_p = \frac{V_1 \cdot R' + V_2 \cdot R'}{2R'}$$



$$V_p = \frac{V_1 + V_2}{2}$$
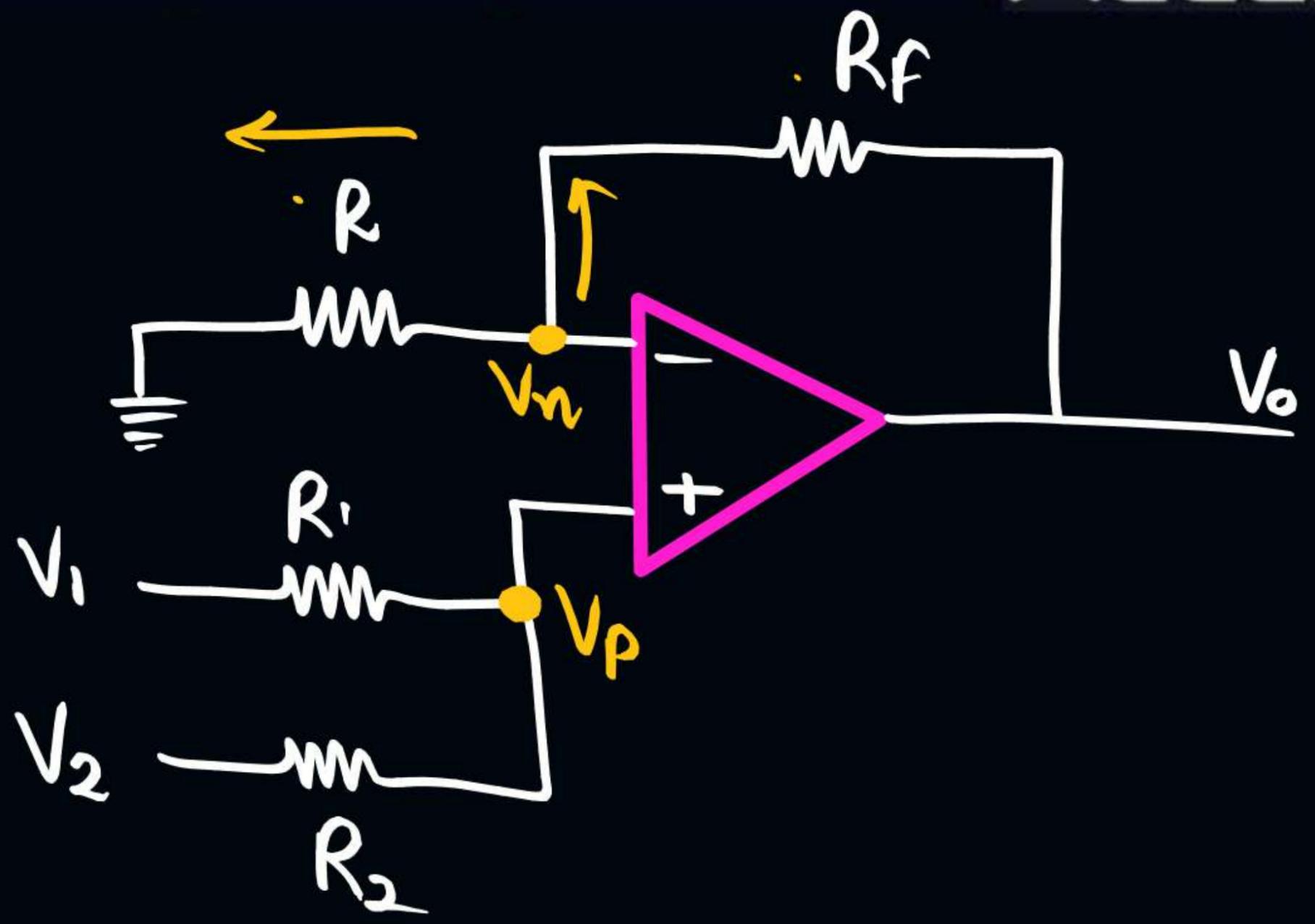
$$V_o = \left(1 + \frac{R_f}{R}\right) \cdot V_p$$



Nodal @ V_n :

$$\frac{V_n - 0}{R} + \frac{V_n - V_o}{R_f} = 0$$

$$\frac{V_n}{R} + \frac{V_n}{R_f} - \frac{V_o}{R_f} = 0$$

$$\frac{V_o}{R_f} = V_n \left(\frac{1}{R} + \frac{1}{R_f} \right)$$

$$V_o = V_n \left(1 + \frac{R_f}{R} \right)$$

$$\therefore V_n = V_p$$

$$V_o = V_p \left(1 + \frac{R_f}{R} \right)$$


$$V_0 = \frac{V_1 + V_2}{2} \left(1 + \frac{R_f}{R} \right)$$

if $R_f = R = R''$


$$V_0 = \frac{V_1 + V_2}{2} \left(1 + \frac{R''}{R''} \right) = V_1 + V_2$$

Two Input Non-Inverting Summer:

$$V_o = V_1 + V_2$$

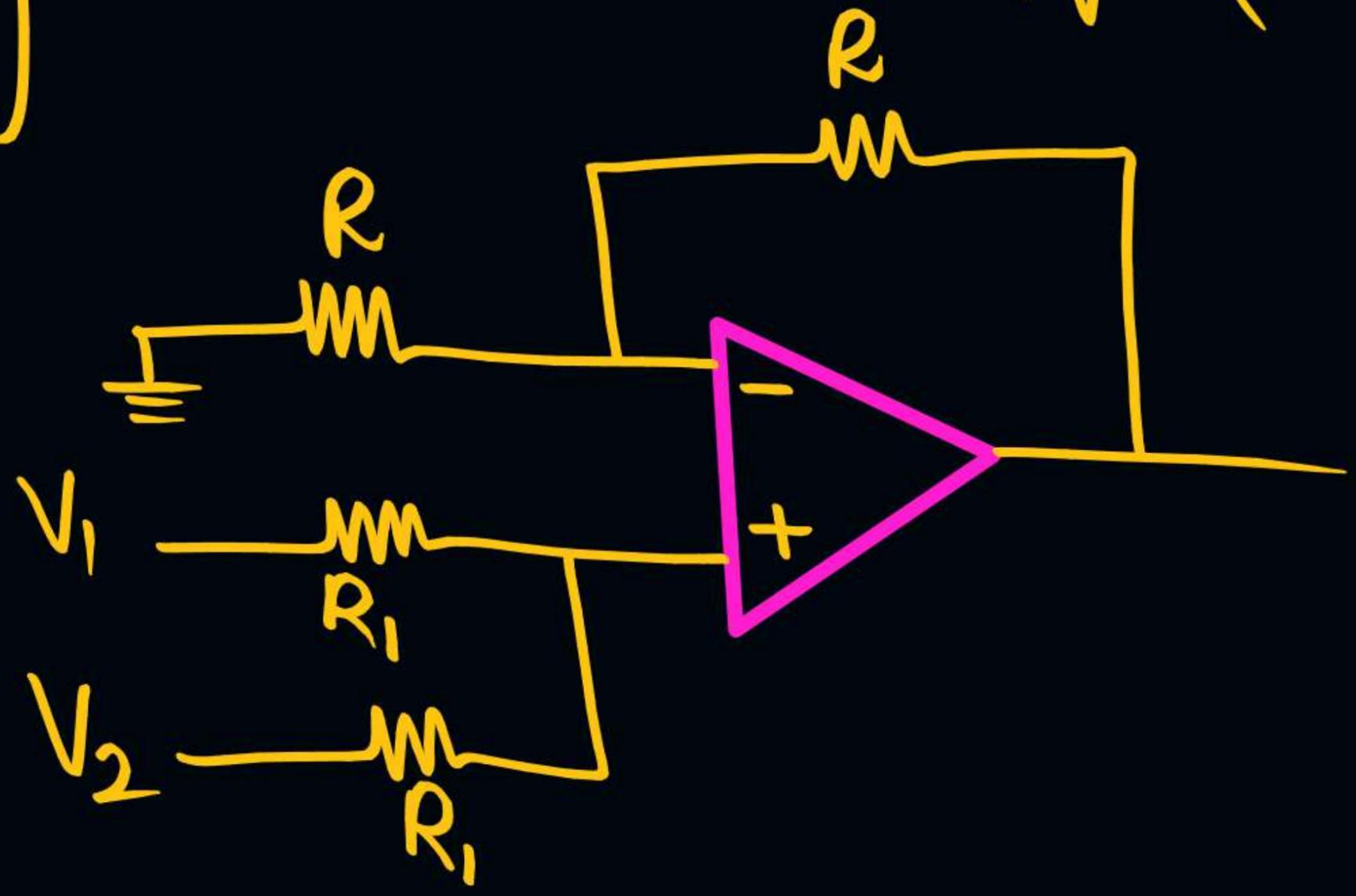

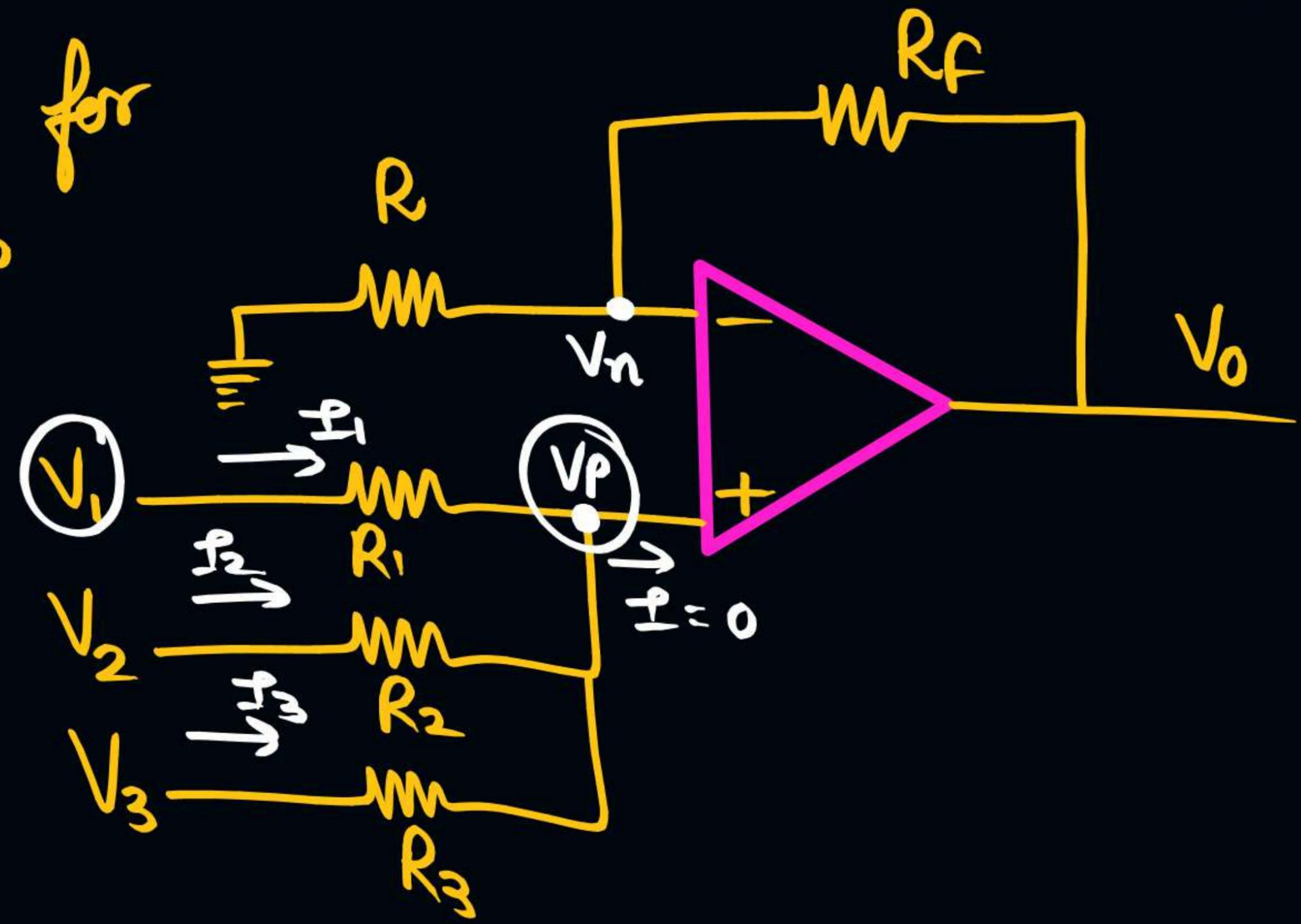find condition for
Resistance to
get output
Voltage
 $V_0 = V_1 + V_2 + V_3$



KCL @ V_p :

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_1 - V_p}{R_1} + \frac{V_2 - V_p}{R_2} + \frac{V_3 - V_p}{R_3} = 0$$

If $R_1 = R_2 = R_3 = R'$

$$\frac{V_1 - V_p}{R'} + \frac{V_2 - V_p}{R'} + \frac{V_3 - V_p}{R'} = 0$$

$$\frac{V_1 - V_p + V_2 - V_p + V_3 - V_p}{R'} = 0$$


$$V_1 + V_2 + V_3 - 3V_p = 0$$

$$3V_p = V_1 + V_2 + V_3$$

$$V_p = \frac{V_1 + V_2 + V_3}{3}$$

$$V_o = V_p \left(1 + \frac{R_f}{R} \right)$$
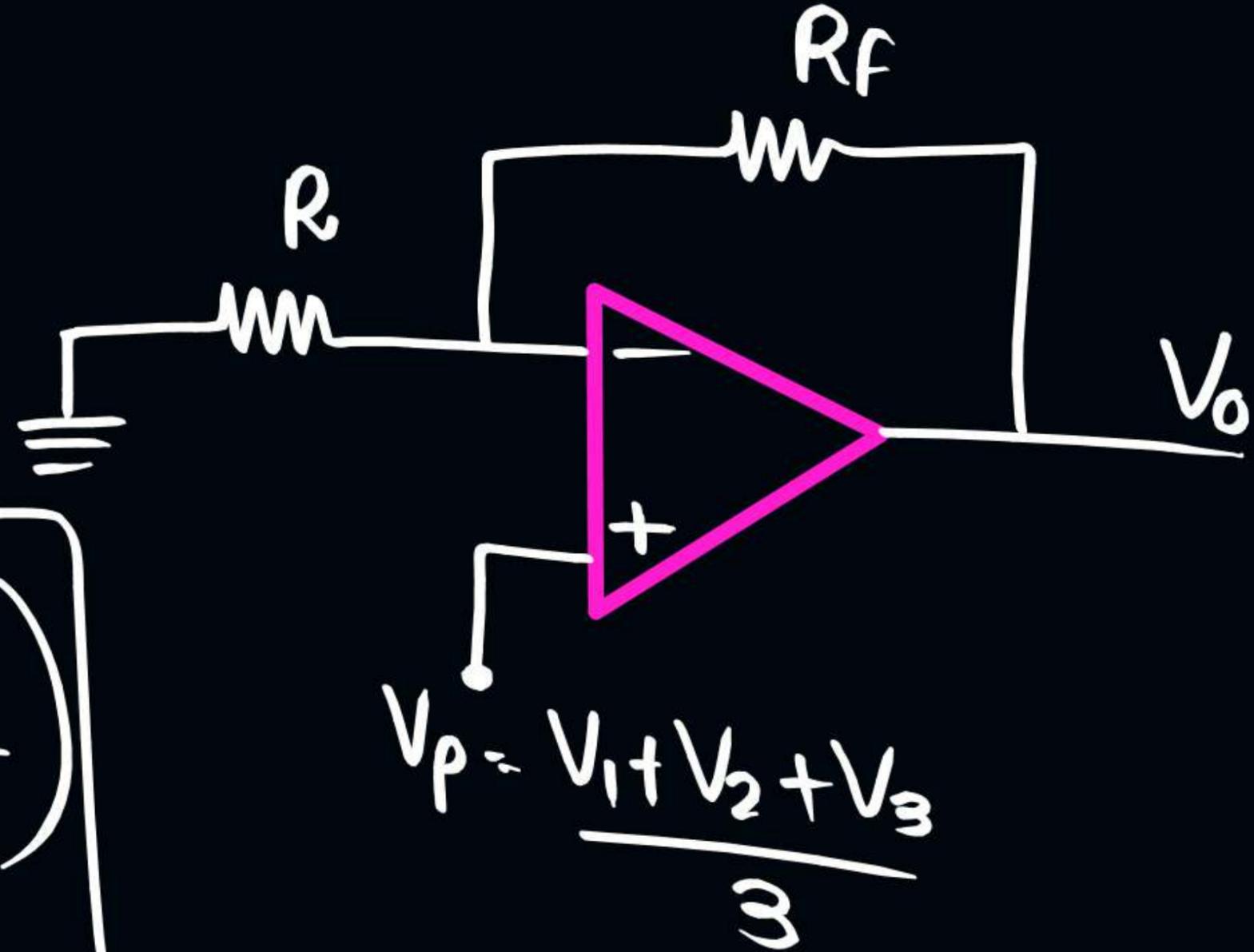
$$V_o = \frac{V_1 + V_2 + V_3}{3} \left(1 + \frac{R_f}{R} \right)$$



$$V_p = \frac{V_1 + V_2 + V_3}{3}$$


for Summer: $R_f = 2R$



$$V_0 = \frac{V_1 + V_2 + V_3}{3} \left(1 + \frac{2R}{R} \right)$$

$$V_0 = V_1 + V_2 + V_3 \rightarrow$$

Ques:

Find
 $V_o = ?$
 $I_o = ?$
 $I' = ?$

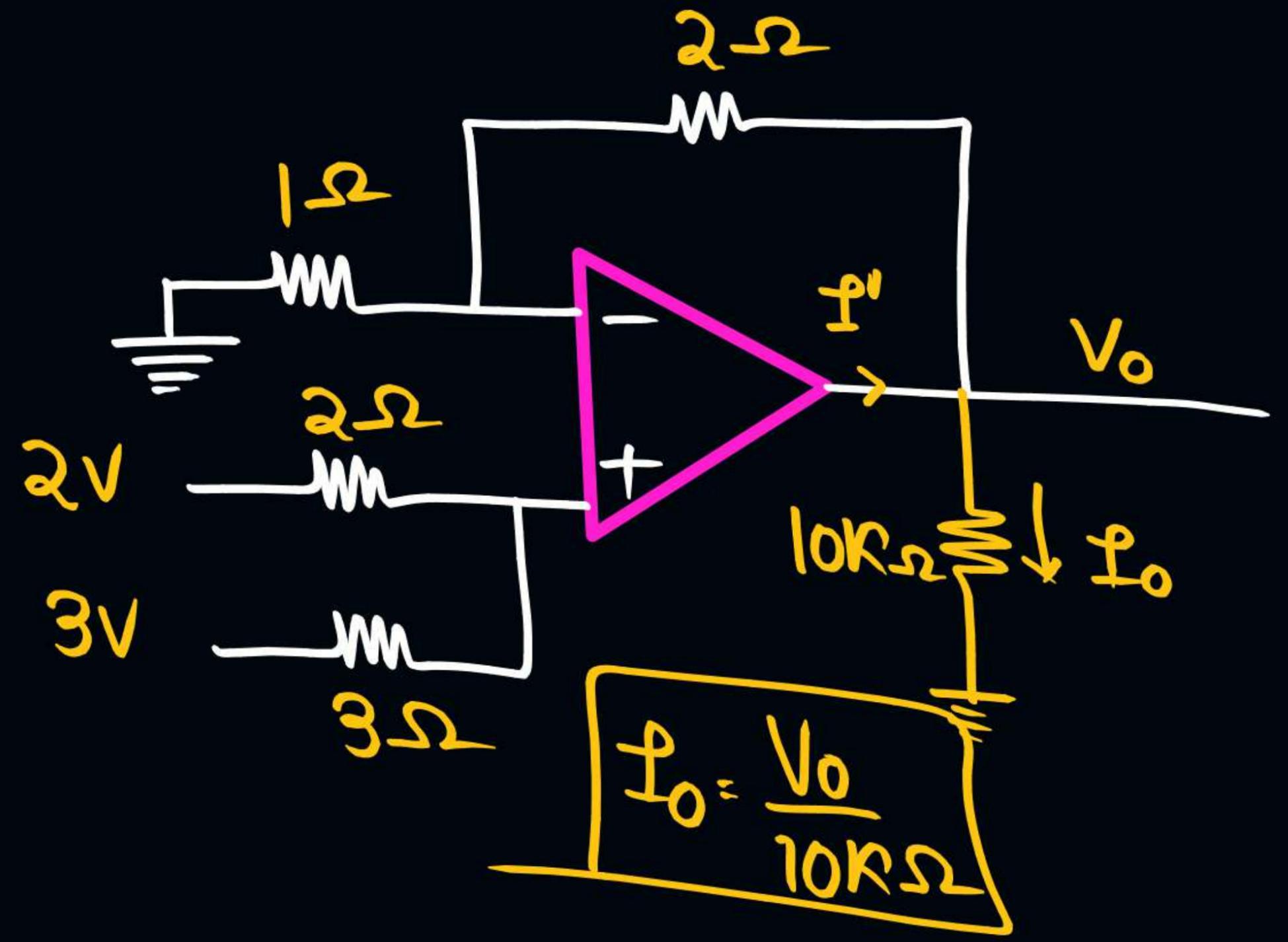

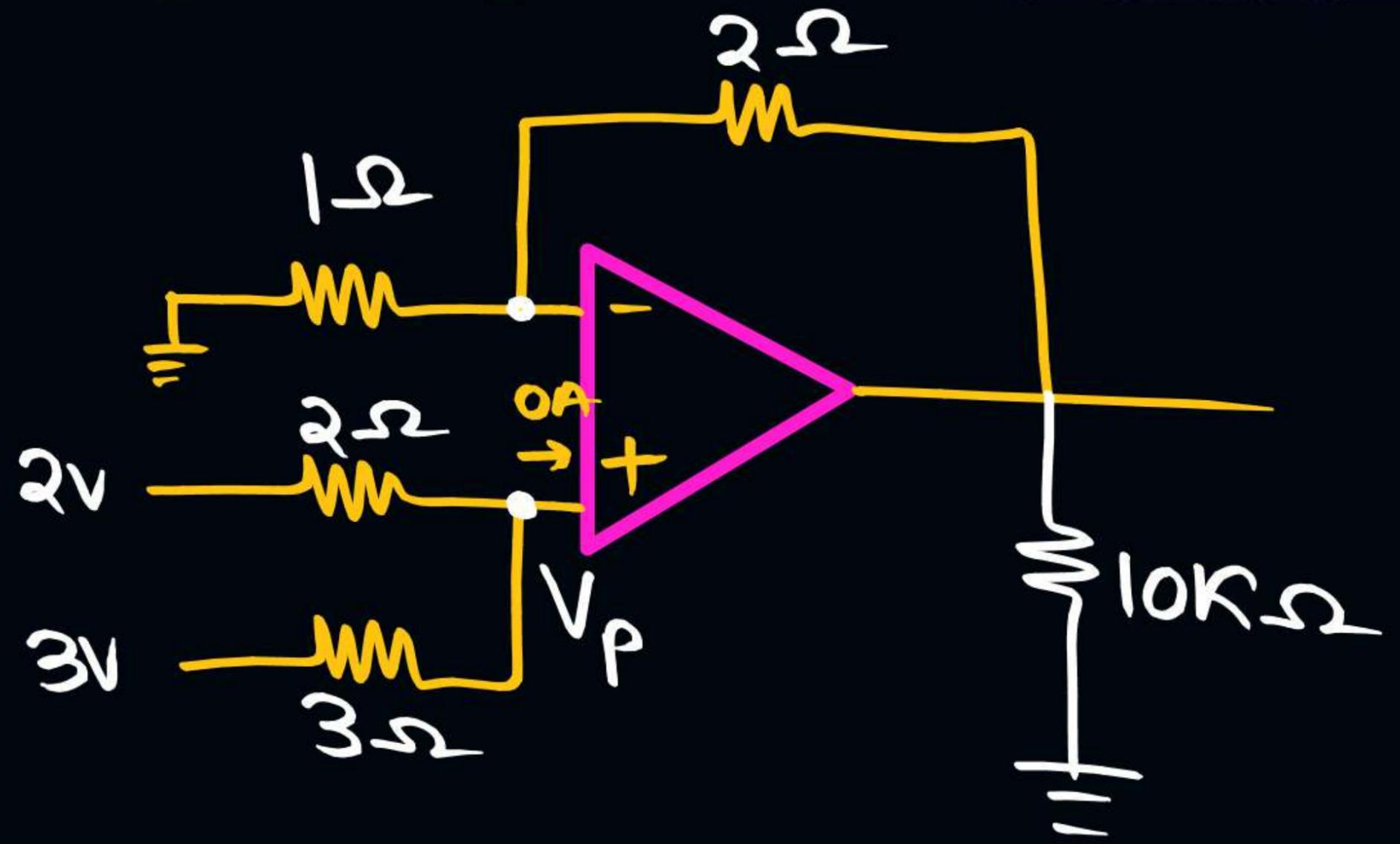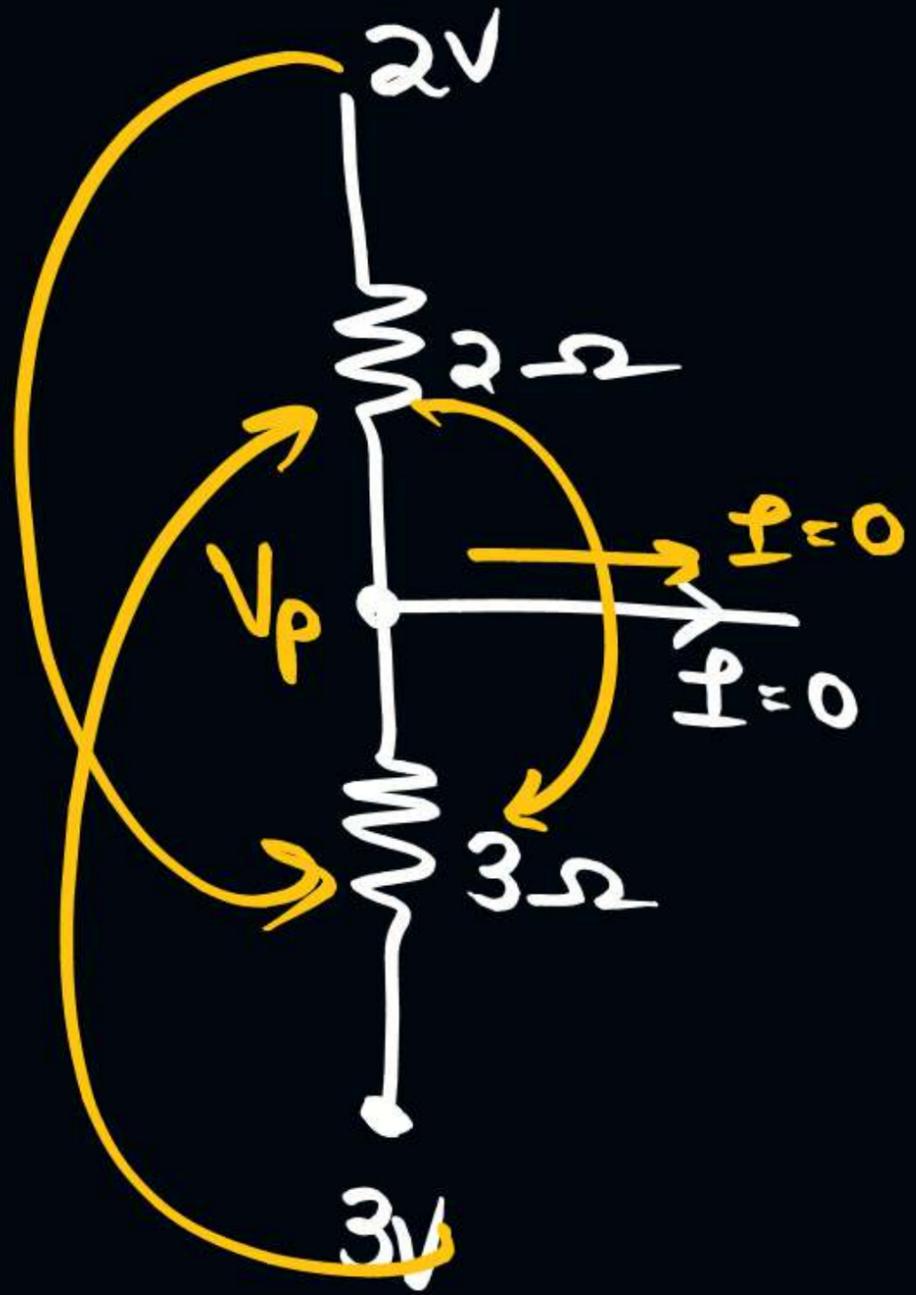


$$V_p = \frac{2 \times 3 + 3 \times 2}{2 + 3}$$

$$V_p = \frac{6 + 6}{5} = \frac{12}{5} = 2.4 \text{ volt}$$

$V_n = V_p = 2.4$
↓
Virtual Short
concept :

Nodal @ V_n :
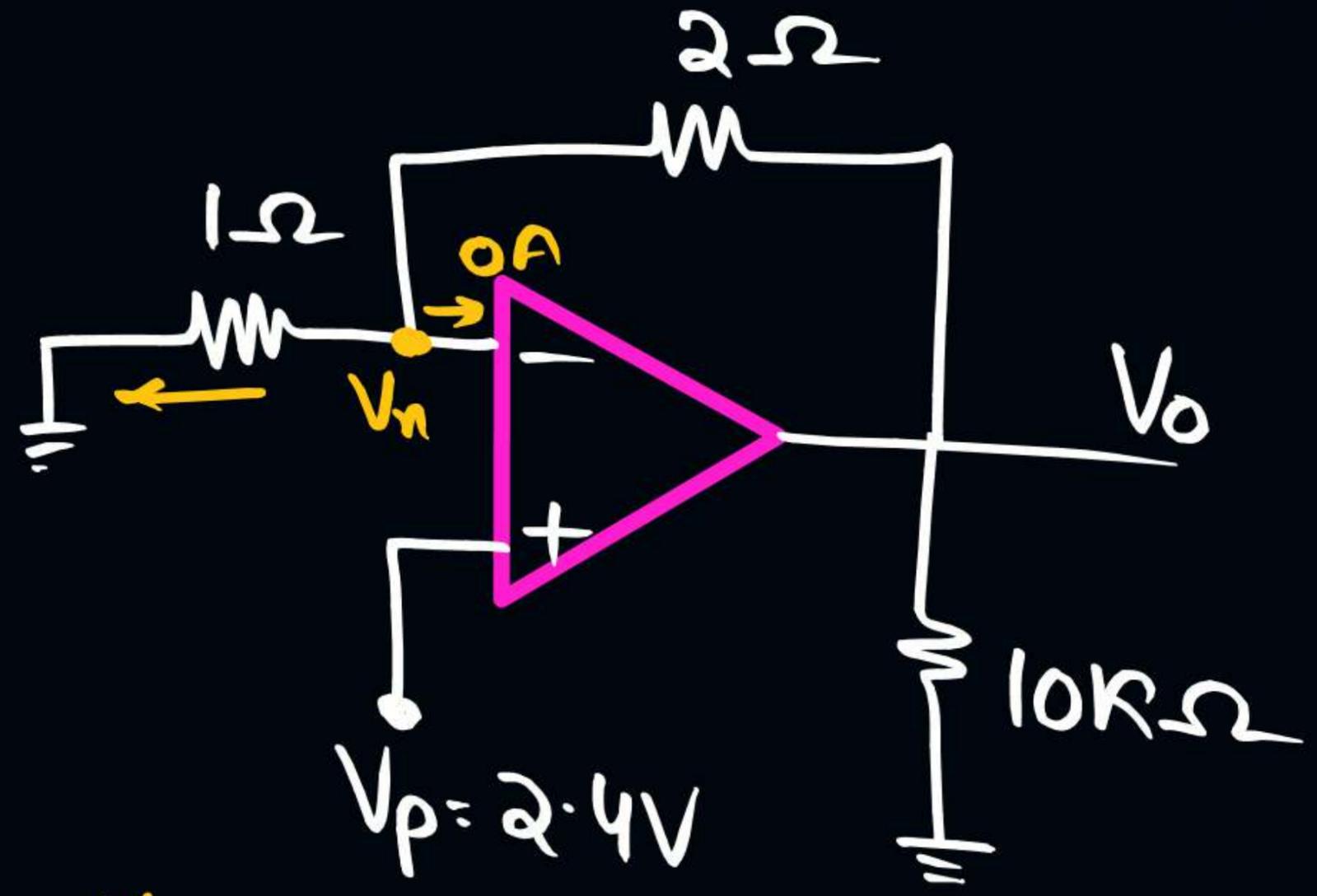
$$\frac{V_n - 0}{1} + \frac{V_n - V_o}{2} = 0$$




$$\frac{2.4}{1} + \frac{2.4 - V_0}{2} = 0$$

$$\frac{4.8 + 2.4 - V_0}{2} = 0$$


$$V_0 = 7.2 \text{ Volt}$$

$$I_0 = \frac{7.2}{10K}$$

$$I_0 = 0.72 \text{ mA}$$

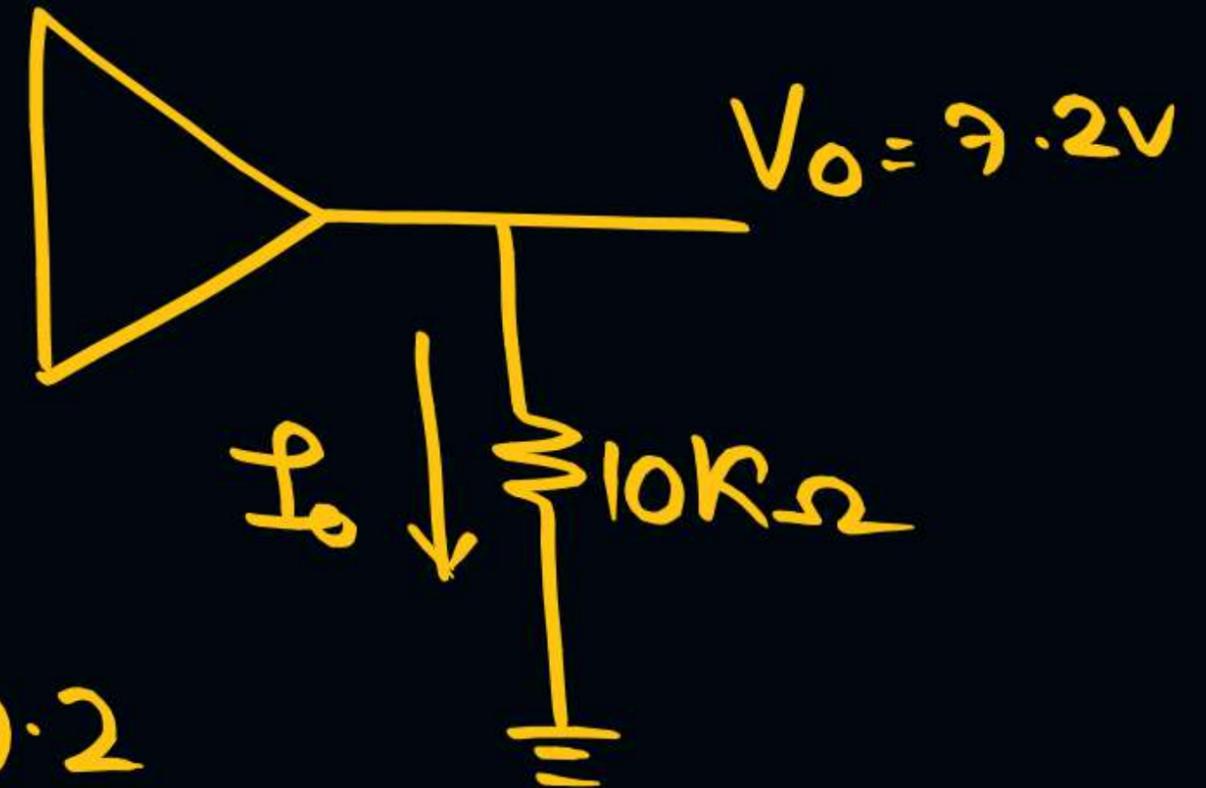
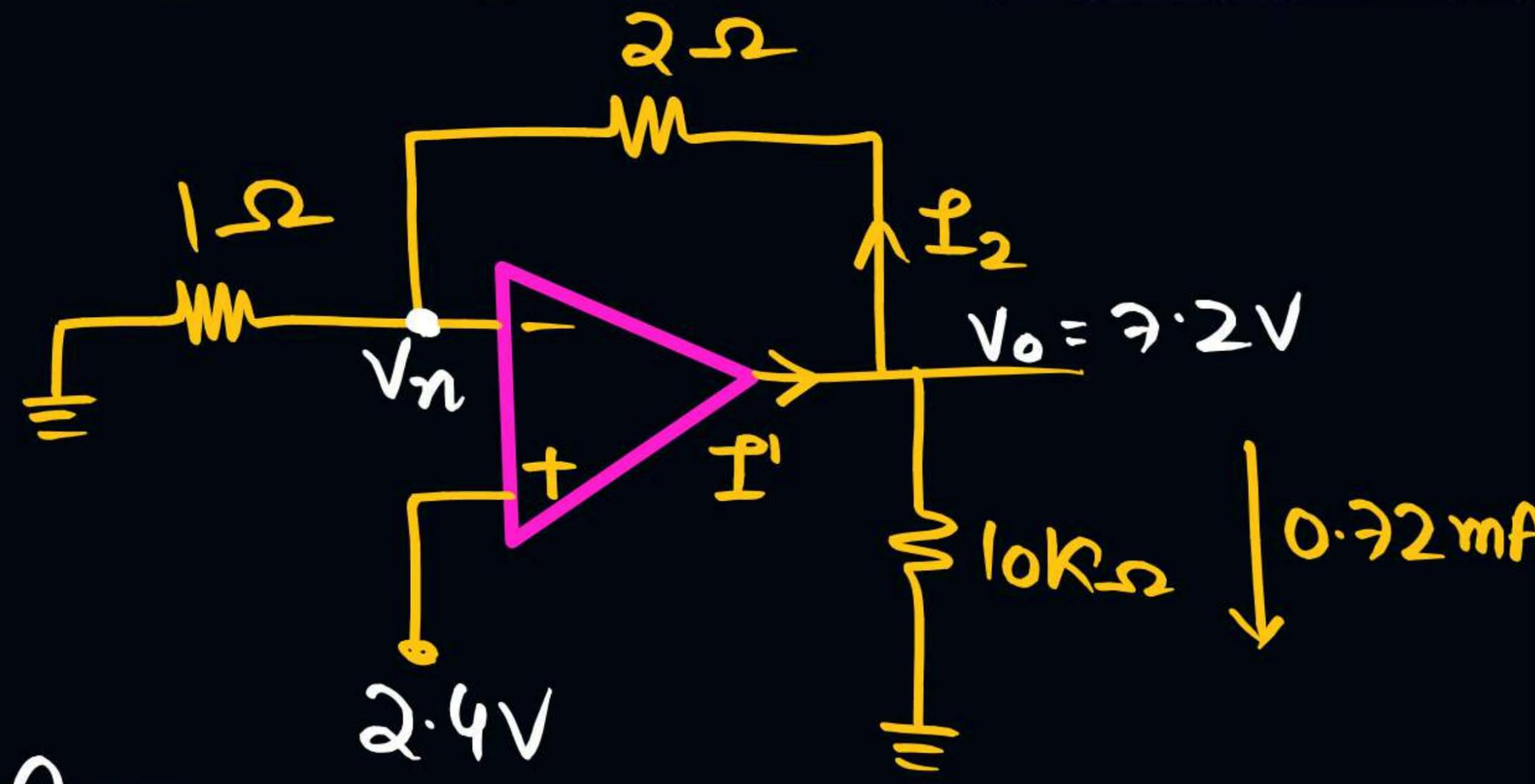
$$I_2 = \frac{V_o - V_n}{2\Omega}$$
$$= \frac{7.2 - 2.4}{2}$$
$$= \frac{4.8}{2} = 2.4 \text{ Amp}$$



$$I' = I_2 + I_0$$

$$= 2.4 + 0.72 \text{ mA}$$

$$= 2.4 + 0.00072 \text{ Amp}$$

$$I' = 2.40072 \text{ Amp}$$

Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Join ADDA247 ENGINEERING MAHAPACK using code Y694 to get maximum discount



Adda247

Presents

▶ BIGGEST ◀

Birthday
Party

of the Year

Celebrating
14
Years of
Success

Double Validity +

FLAT
77 % OFF

On All Mahapacks

USE CODE

Y694

BUY NOW ON ADDA247 APP

Offer Ending Soon

APP FEATURES



Download Now
Adda247 APP



Premium Study Material



Current Affairs



Job Alerts



Daily Quizzes



Subject-wise Quizzes



Magazines




Power Capsule



Notes & Articles



Videos

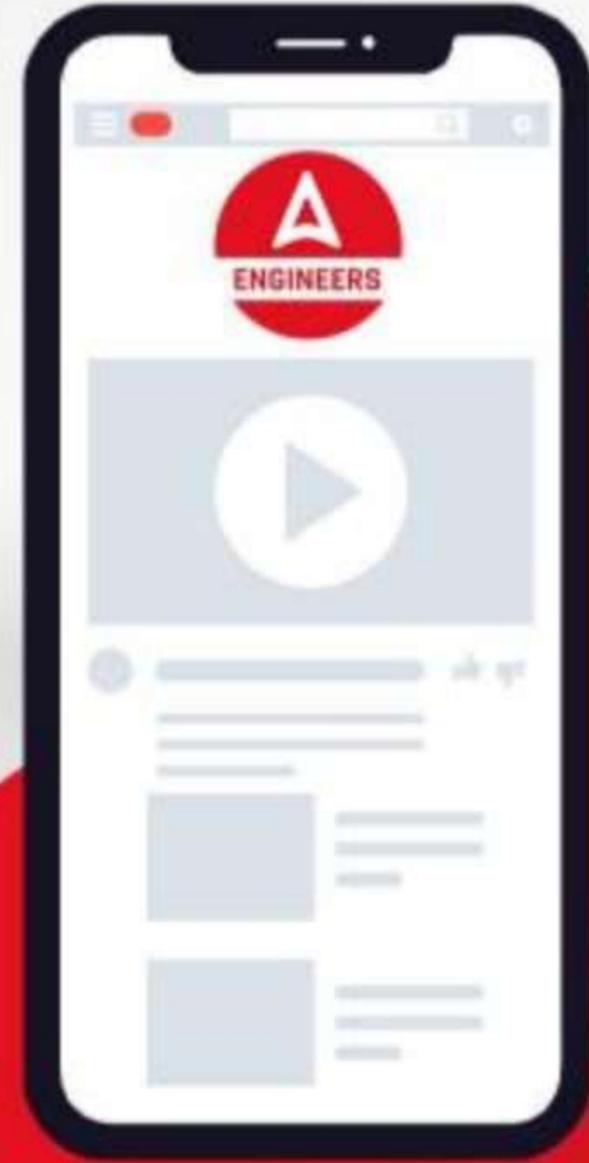

SUBSCRIBE NOW ✓

Engineers Adda247
YouTube Channel

THANKS FOR

Watching

Adda247

LIKE



SHARE



COMMENT



SUBSCRIBE

