

WELCOME
TO Adda247

Hard work matters!


ARE YOU READY?
EE & EC GUYS

GATE 2024
GURUKUL BATCH



POWER SYSTEM ANALYSIS

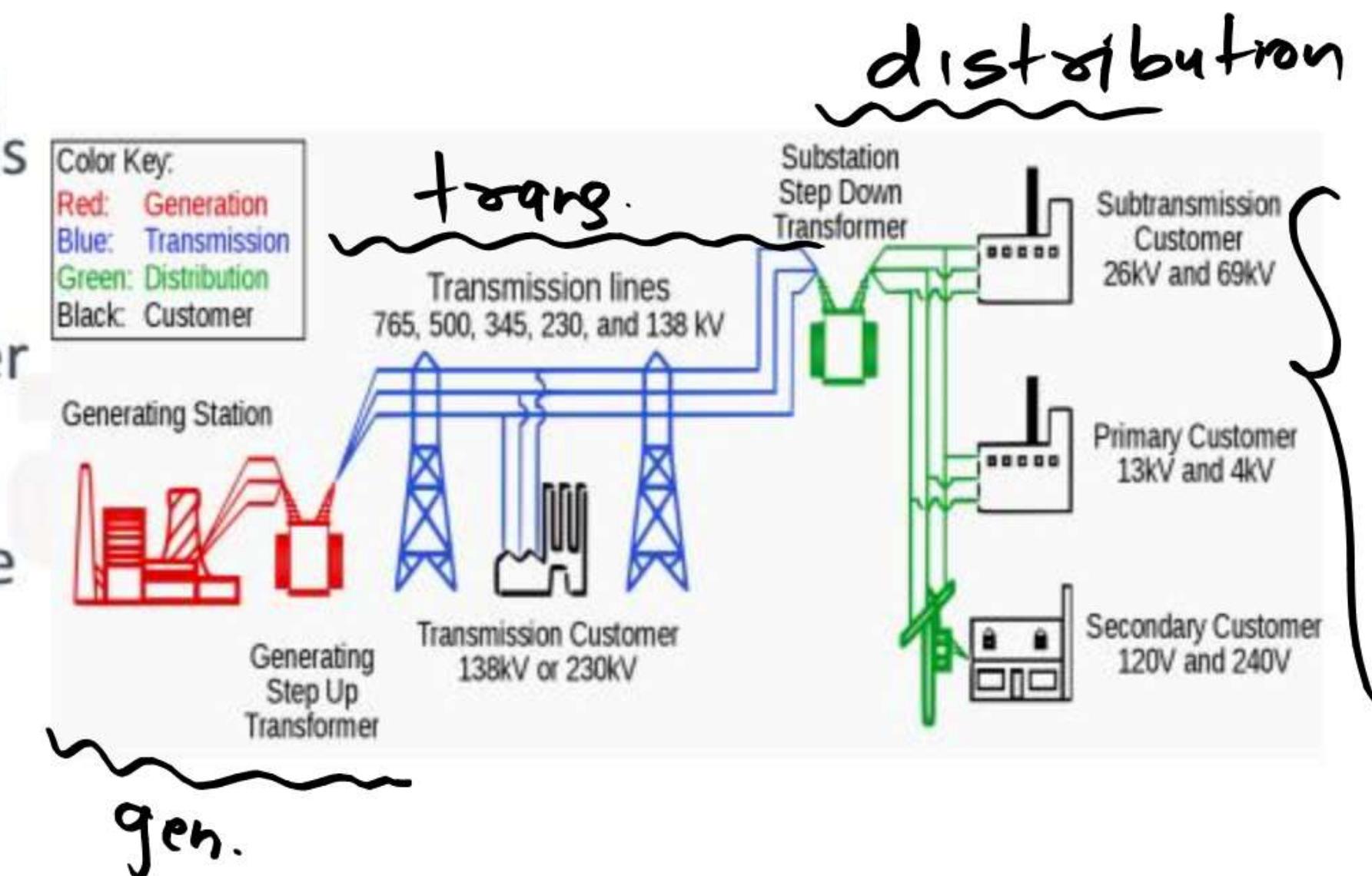- Power system analysis is a branch of electrical engineering that deals with the analysis and design of power systems, which are networks of interconnected power components that generate, transmit, and distribute electrical power to consumers. The purpose of power system analysis is to ensure the safe, reliable, and efficient operation of power systems.




RECENT TRENDS OF PSA IN GATE::

YEAR	PERCENTAGE OF MARKS
2023	9
2022	8
2021	12
2020	11
2019	11

TODAY'S TOPIC: BASICS OF 3 PHASE

The Generator

3-phase output

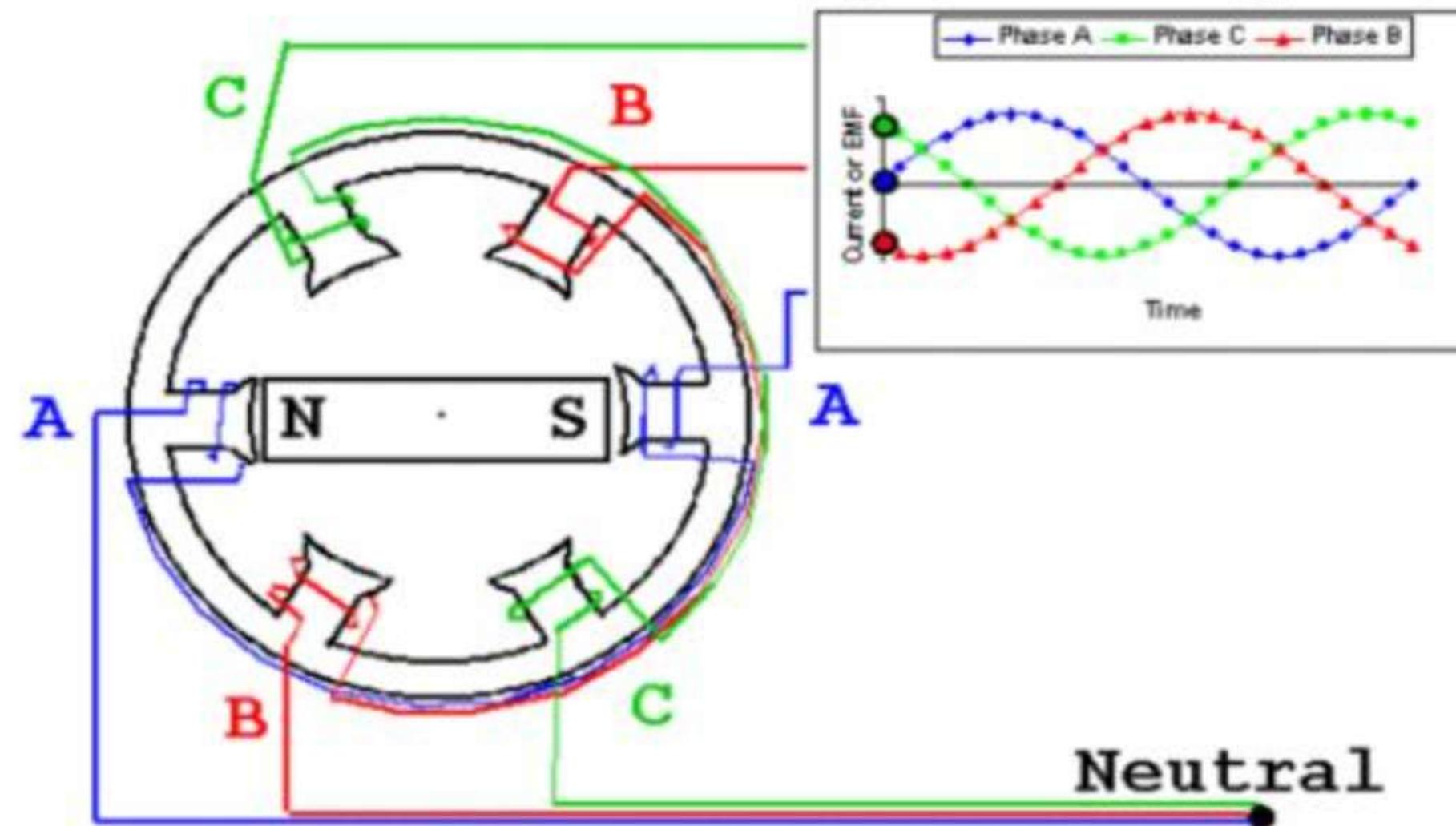

WHY ONLY 3 PHASE CIRCUITS ARE USED FOR GENERATION AND TRANSMISSION?




$$P = \frac{V_P I_P \cos\theta}{}$$

$$P_{3\phi} = 3 \frac{V_P I_P \cos\theta}{}$$

$V_P \uparrow \rightarrow$ insulation $\uparrow \rightarrow$ cost \uparrow


$I_P \uparrow$ cross sectional \uparrow \rightarrow cost \uparrow
area

2 PHASE SYSTEM Imp.

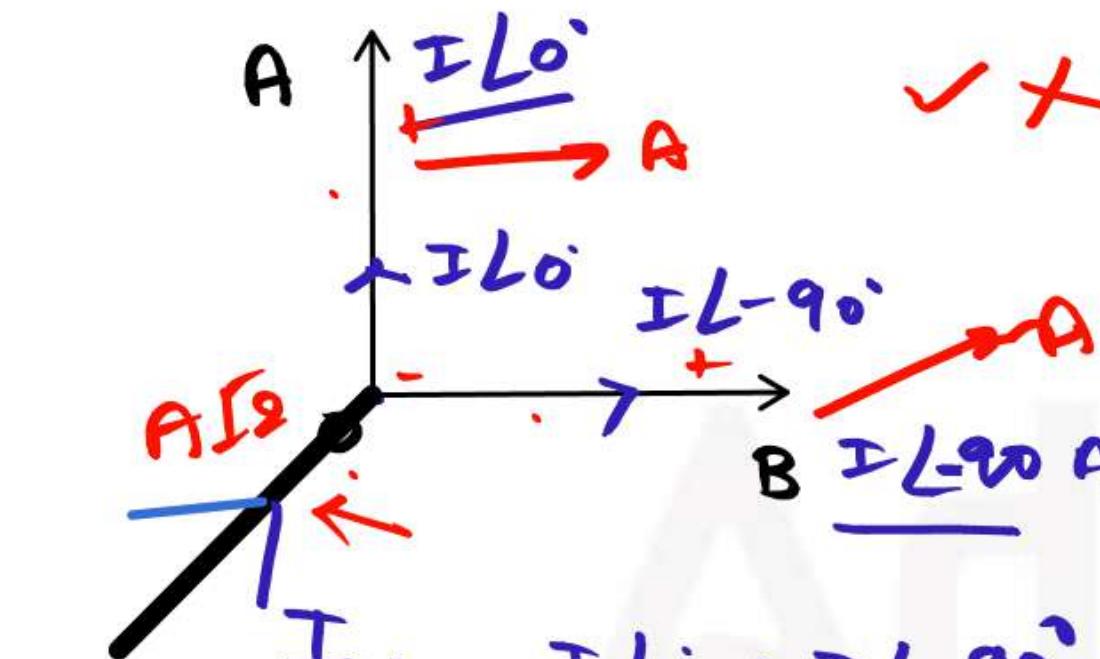

$$I_N = IL_0 + IL - 90^\circ$$

$$I_N = I\sqrt{2}L - 45^\circ$$

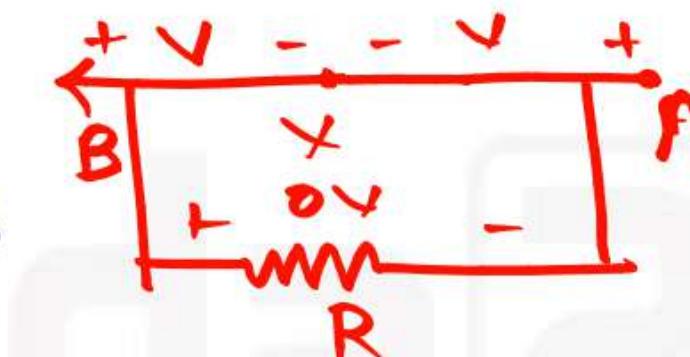

balanced system

Peak/rms value of $\sqrt{3}V_g$ or current of all the phases must be same.

$$\text{angle} \rightarrow \theta_n = \frac{360^\circ}{n} \quad n > 2$$

GATE

(PQ)

b/w two
phase


$$= 90^\circ \quad n = 2$$

2 phase system


$$V_A = V_m \cos \omega t$$

$$V_B = V_m \sin(\omega t + \delta_1) \quad \underline{\delta_1 = ?}$$


GENERATION OF 3 PHASE:

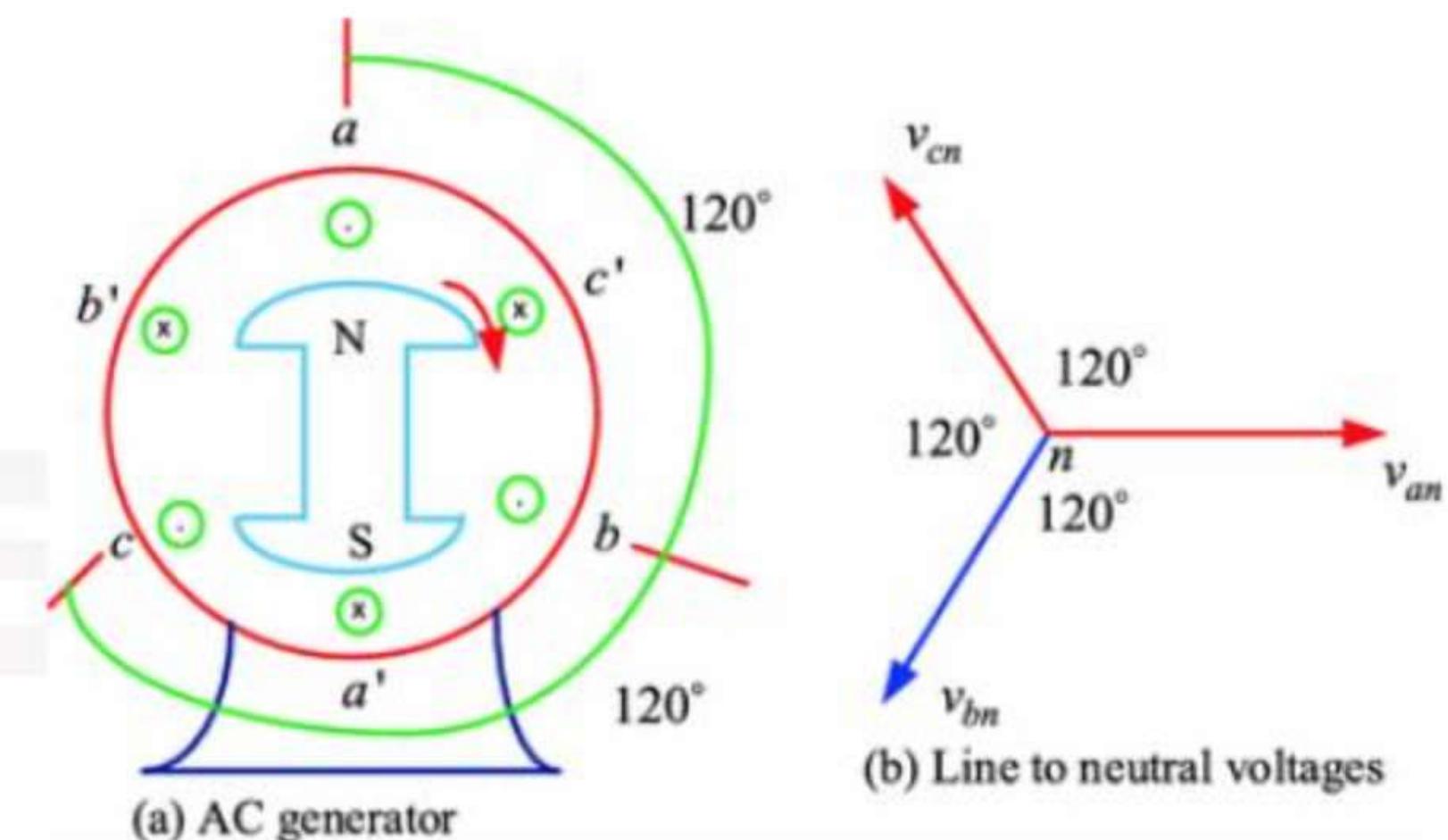


Generation of 3 phase: →

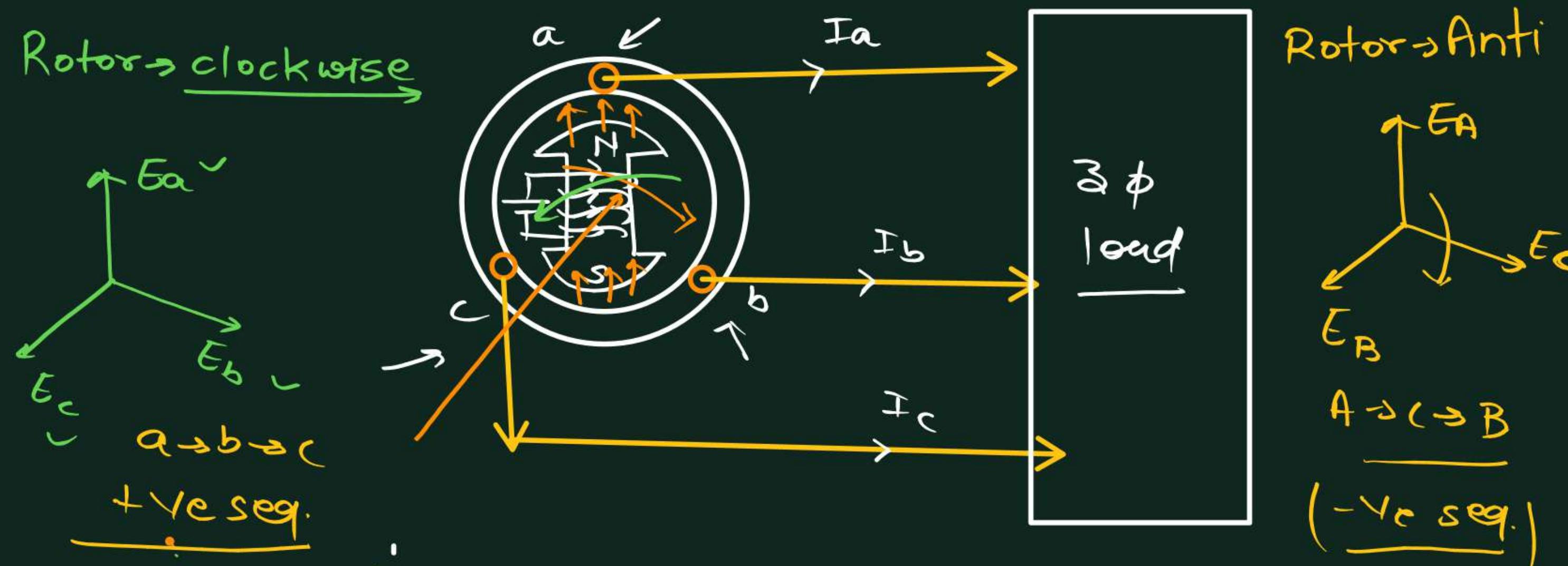

SEQUENCE OF 3 PHASE:

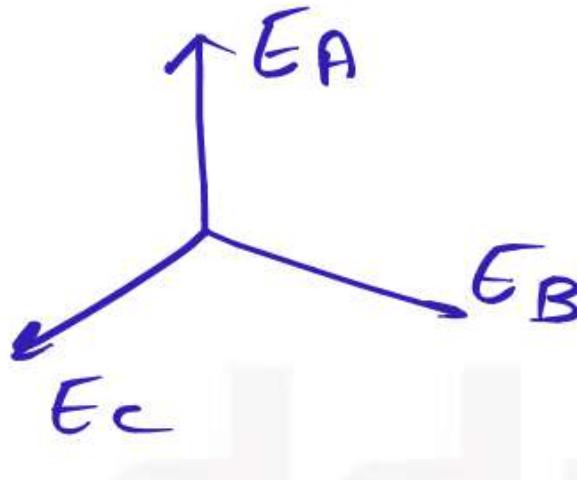

+ve seq

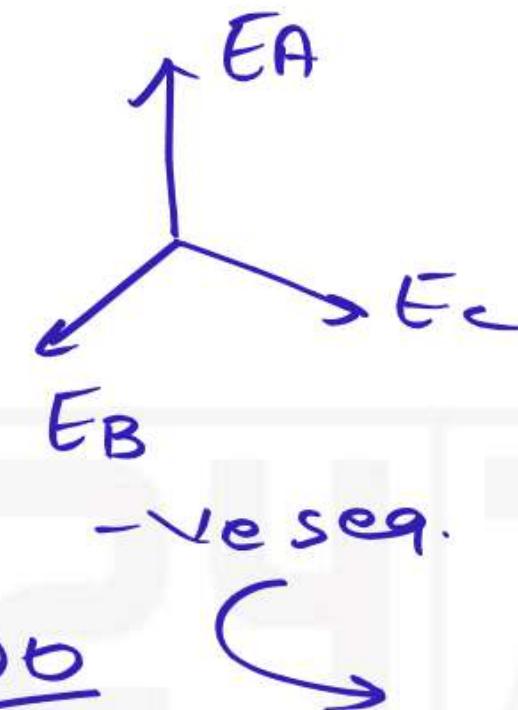


-ve seq.

DRDO


$$\text{eg. } E_A = E L 0^\circ \quad E_B = E L -120^\circ$$

$$E_C = E L -73^\circ$$

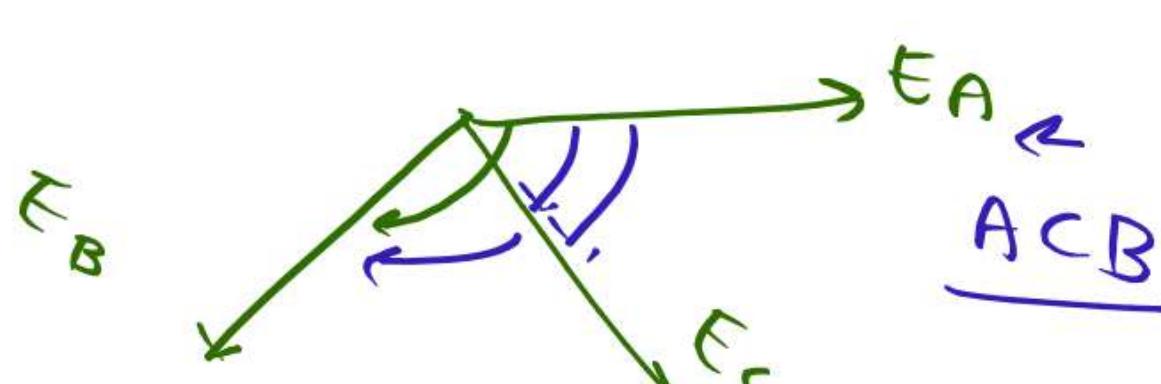


seq \rightarrow the order
in which
max^m emf
appears.



TYPES OF 3 PHASE CONNECTIONS:

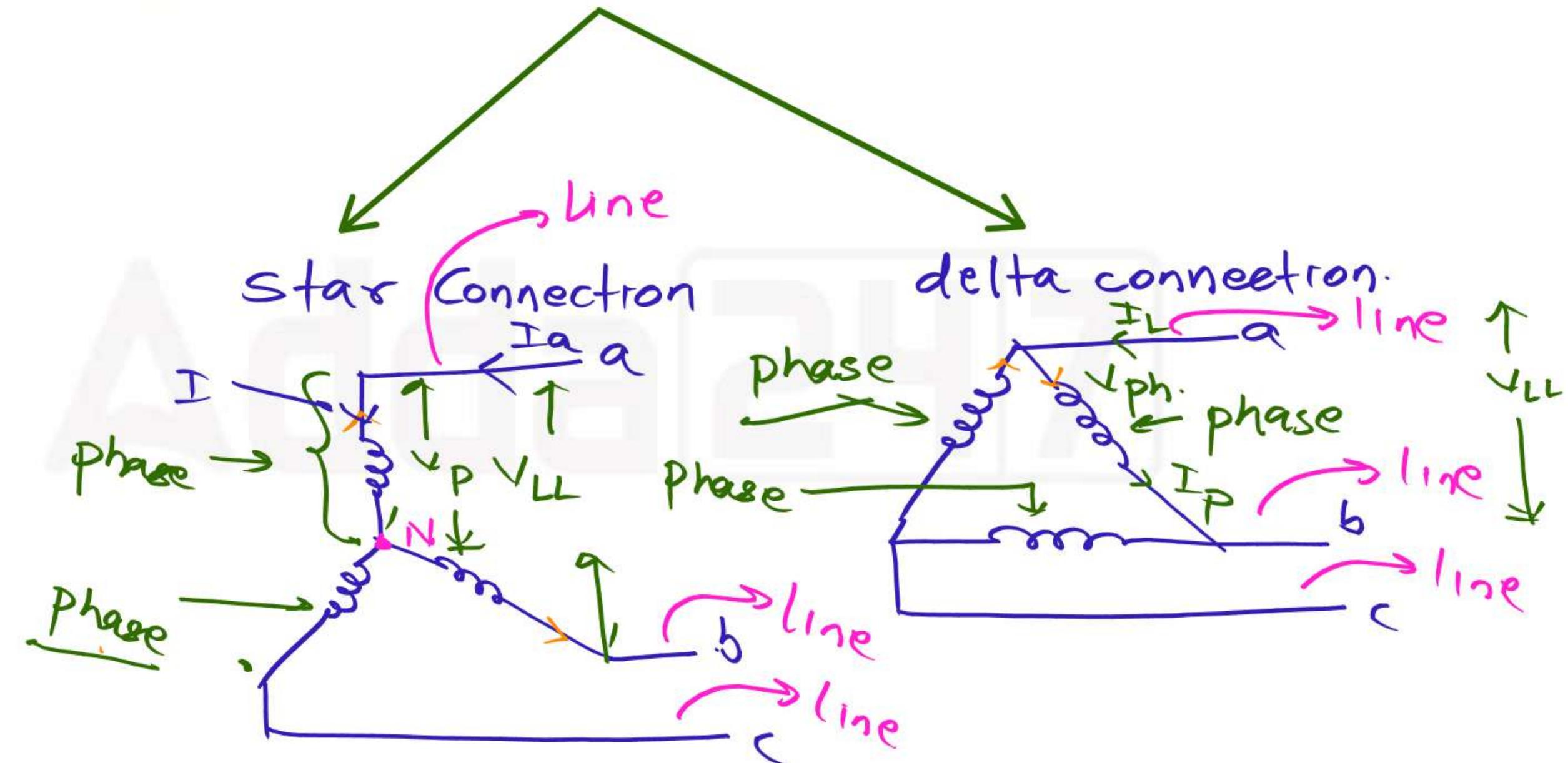


BALANCED SYSTEM:

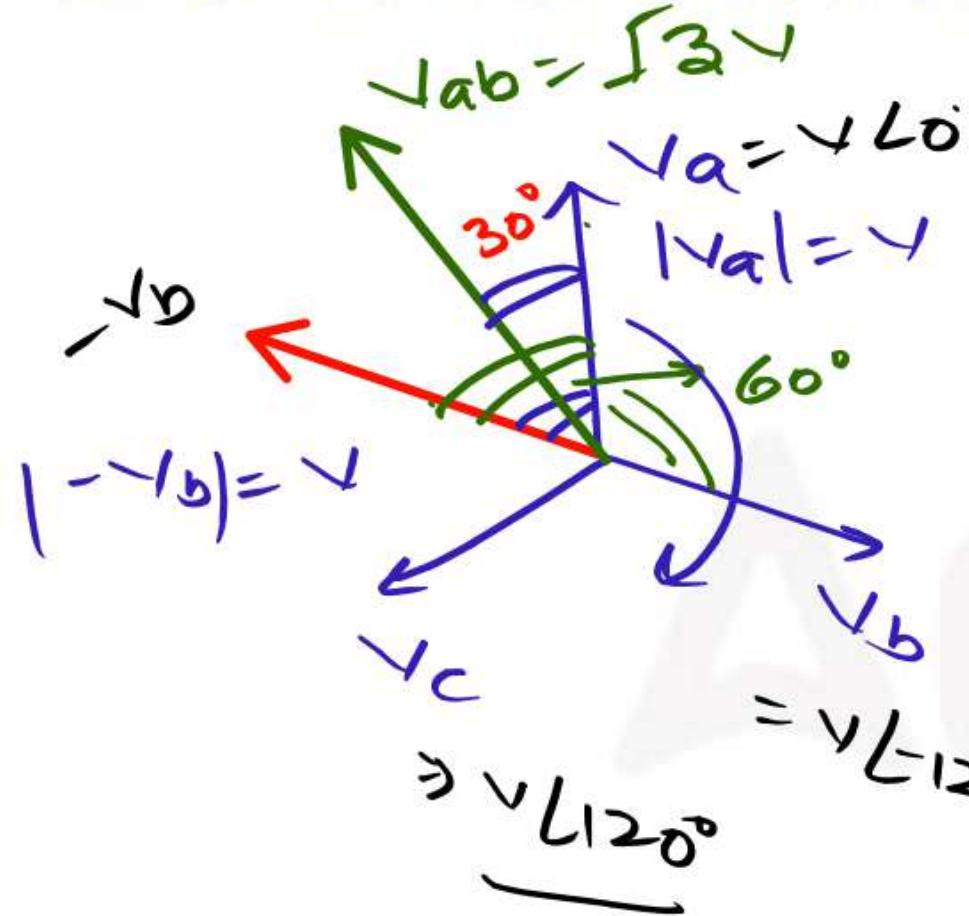

+ve seq (λ connection)

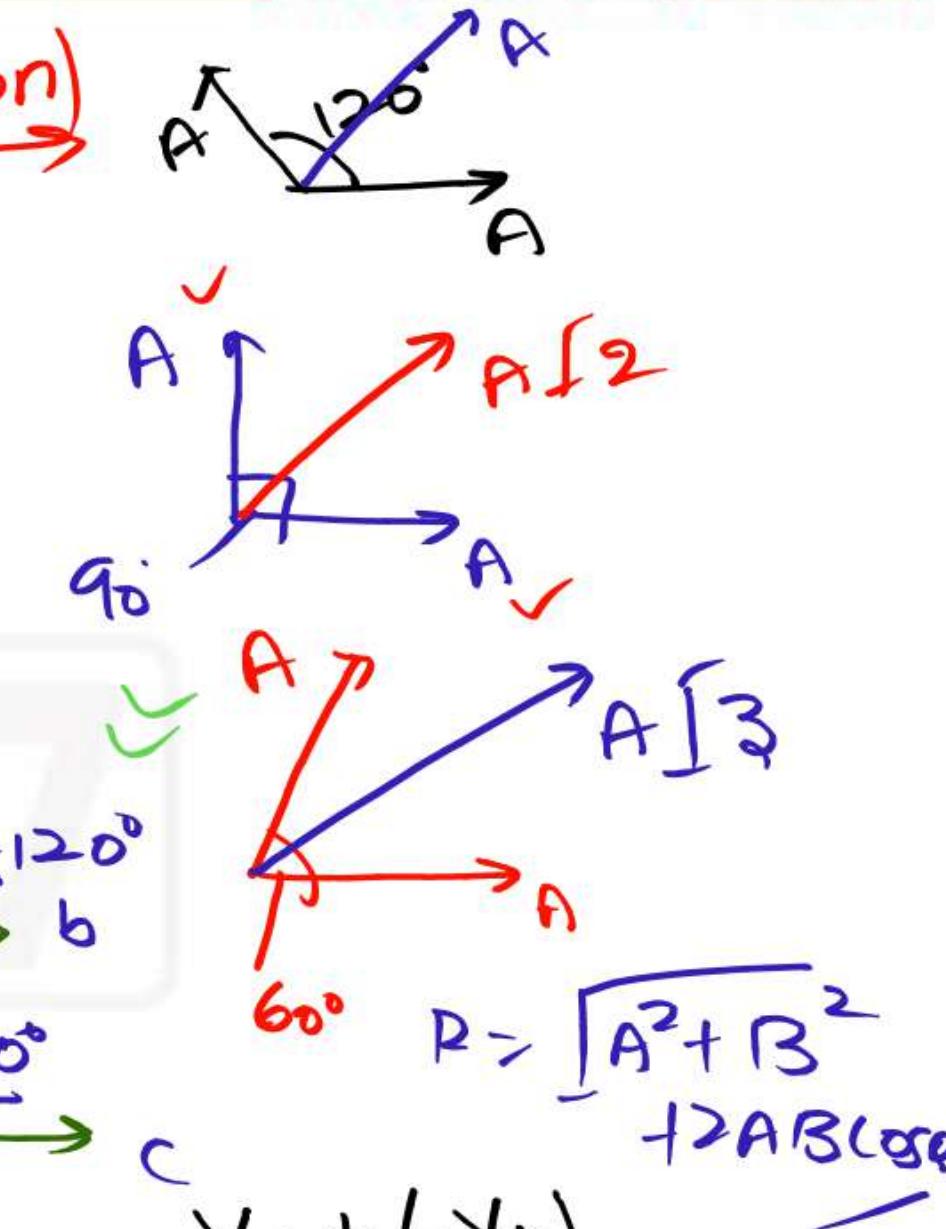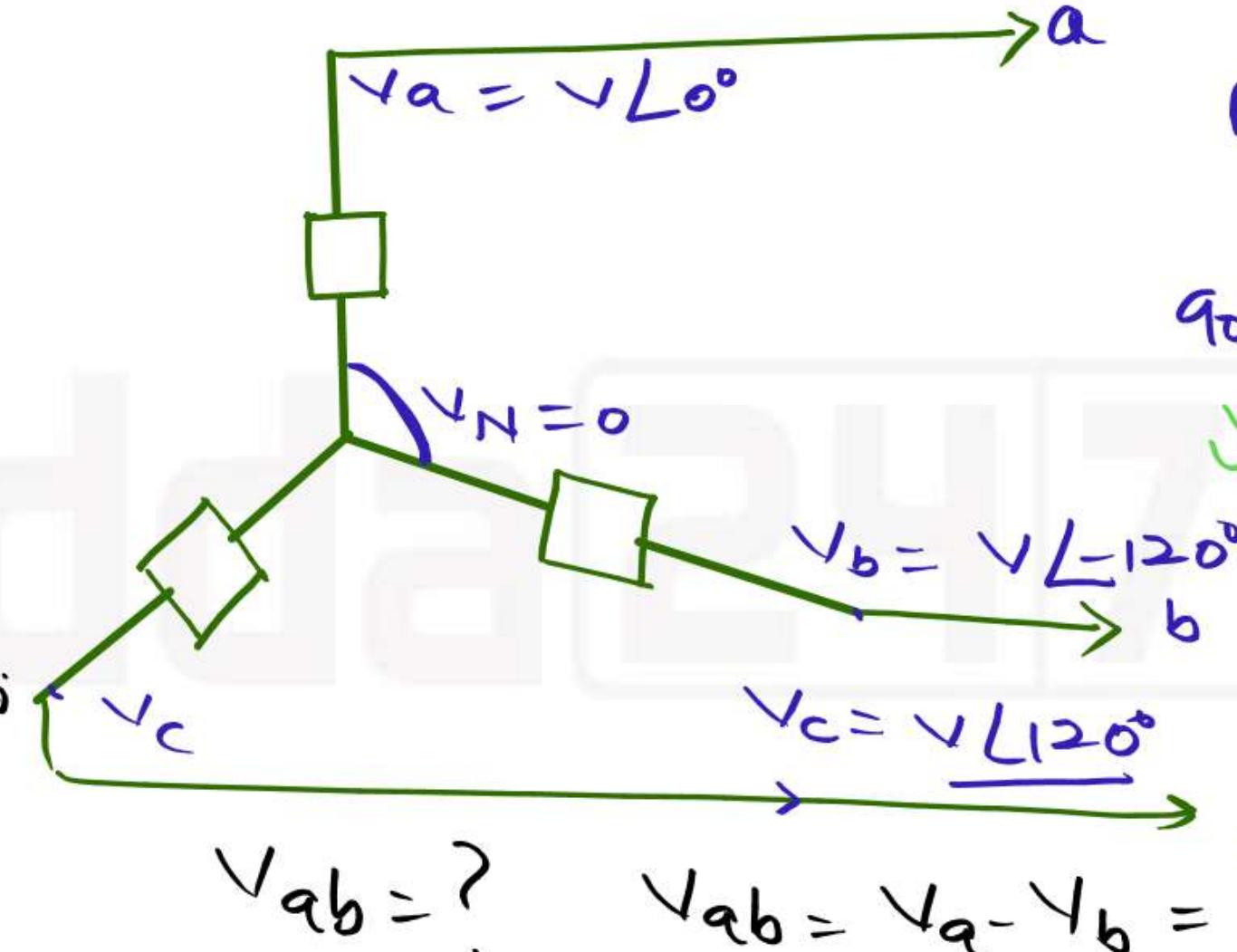

RELATIONS BETWEEN LINE AND PHASE VALUE:

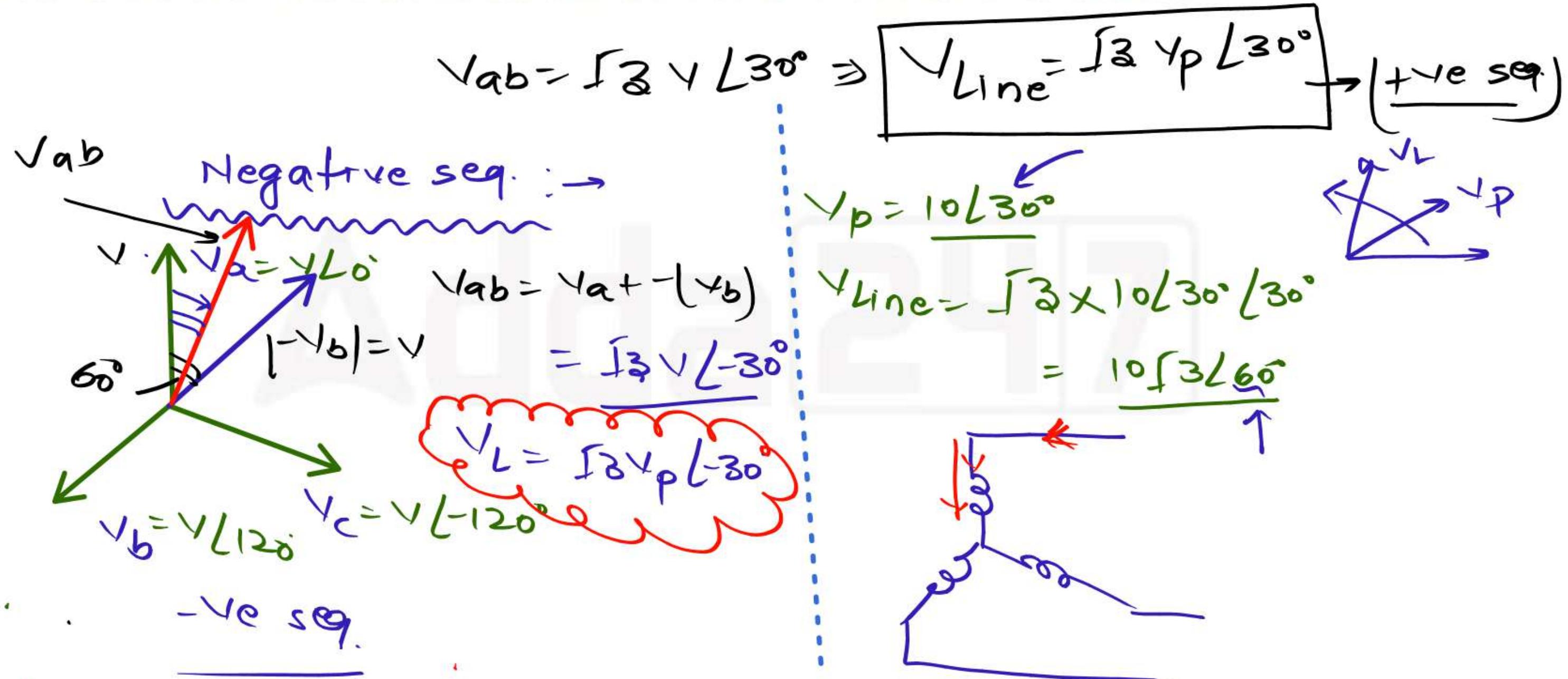

RELATIONS BETWEEN LINE AND PHASE VALUE:



+ve seq. $V_L = \sqrt{3} V_p / 30^\circ \quad I_L = I_p$

-ve seq. $V_L = \sqrt{3} V_p / -30^\circ \quad I_L = I_p$


→ Actual

input $\left\{ \begin{array}{l} V_L = V_p / 30^\circ \text{ (+ve seq.)} \\ V_L = V_p / -30^\circ \text{ (-ve seq.)} \end{array} \right\} (Y)$

RELATIONS BETWEEN LINE AND PHASE VALUE:

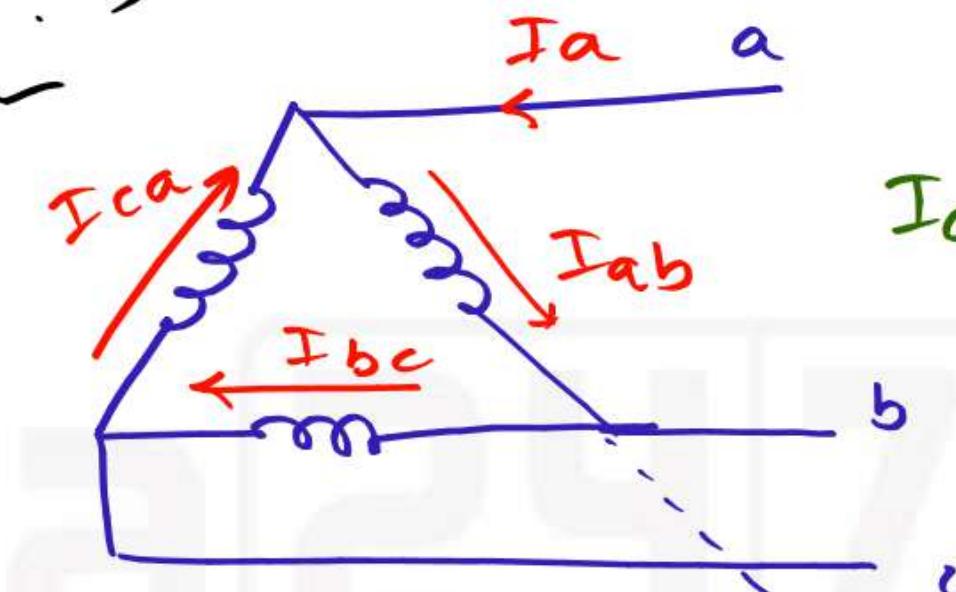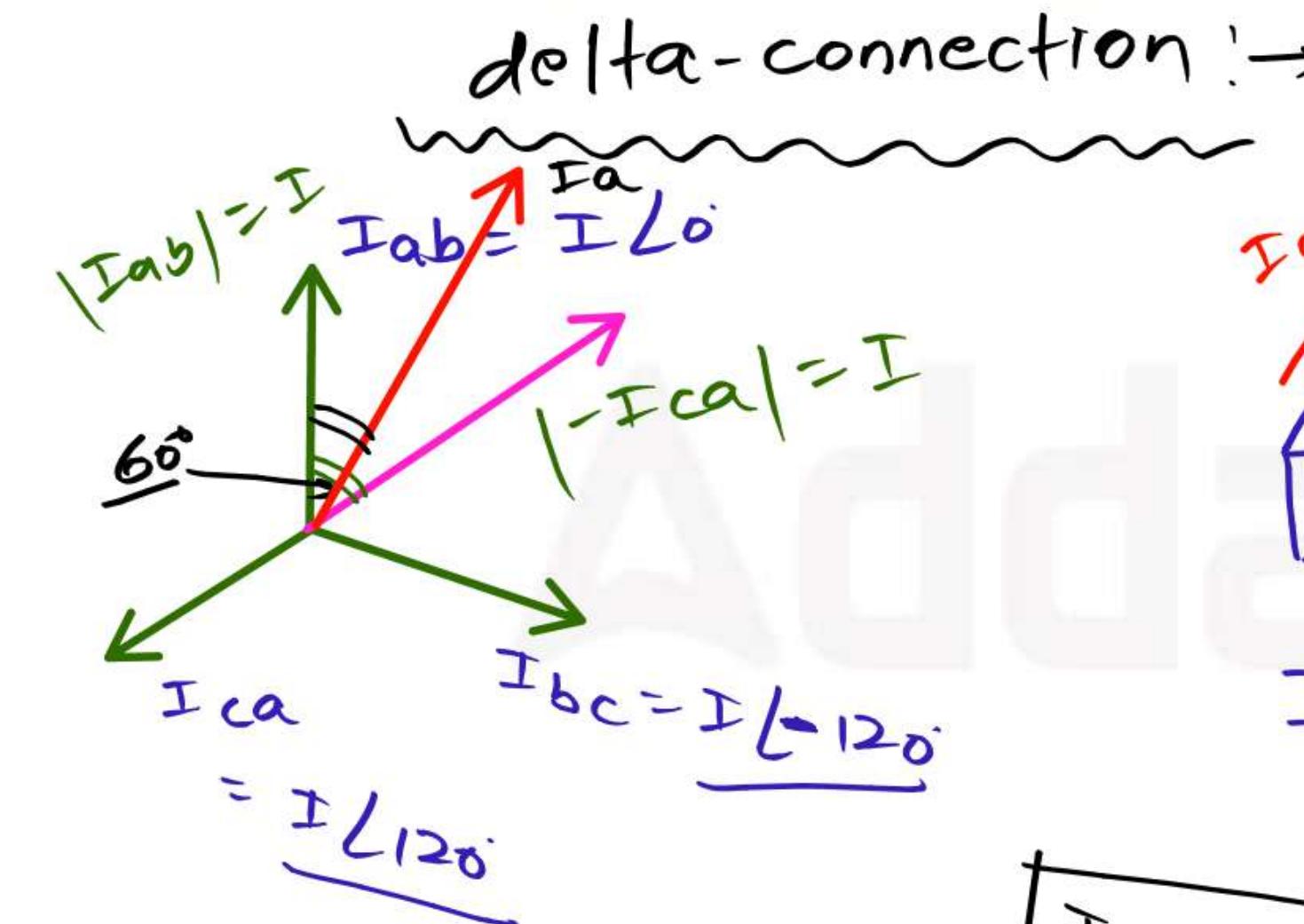
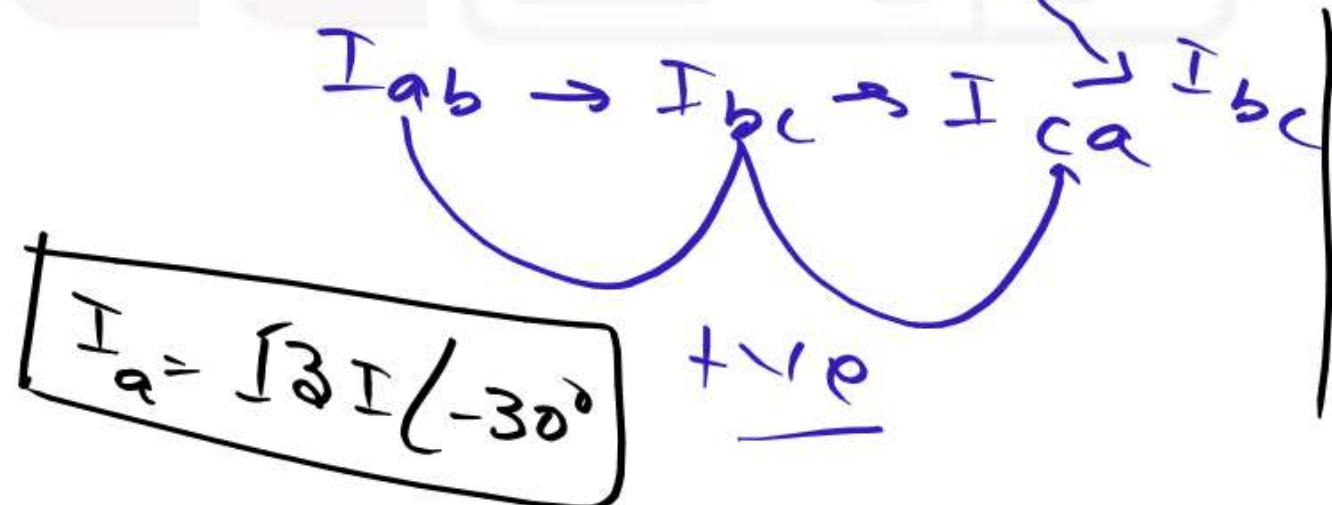
$$\begin{aligned} I_a + I_{ca} &= I_{ab} \\ \Rightarrow I_a &= I_{ab} - I_{ca} \\ &= I_{ab} + (-I_{ca}) \end{aligned}$$



$$I_L = \sqrt{3} I_p \angle -30^\circ$$

+ve seq.

SOME TRICKS:

$$I_L = \sqrt{3} I_P L - 30^\circ$$

↓

△-conn. (+ve seq.)

+ve seq.

$$V_L = \sqrt{3} V_P L + 30^\circ$$


↓



△ conn (+ve)

(-ve seq.)


Δ	$V_L = \sqrt{3} V_P L / 30^\circ$ $I_L = I_P$	$V_L = \sqrt{3} V_P L - 30^\circ$ $I_L = I_P$
\perp	$I_L = \sqrt{3} I_P L / -30^\circ$ $V_L = V_P$	$I_L = \sqrt{3} I_P L + 30^\circ$ $V_L = V_P$

Selection of 3 φ connections

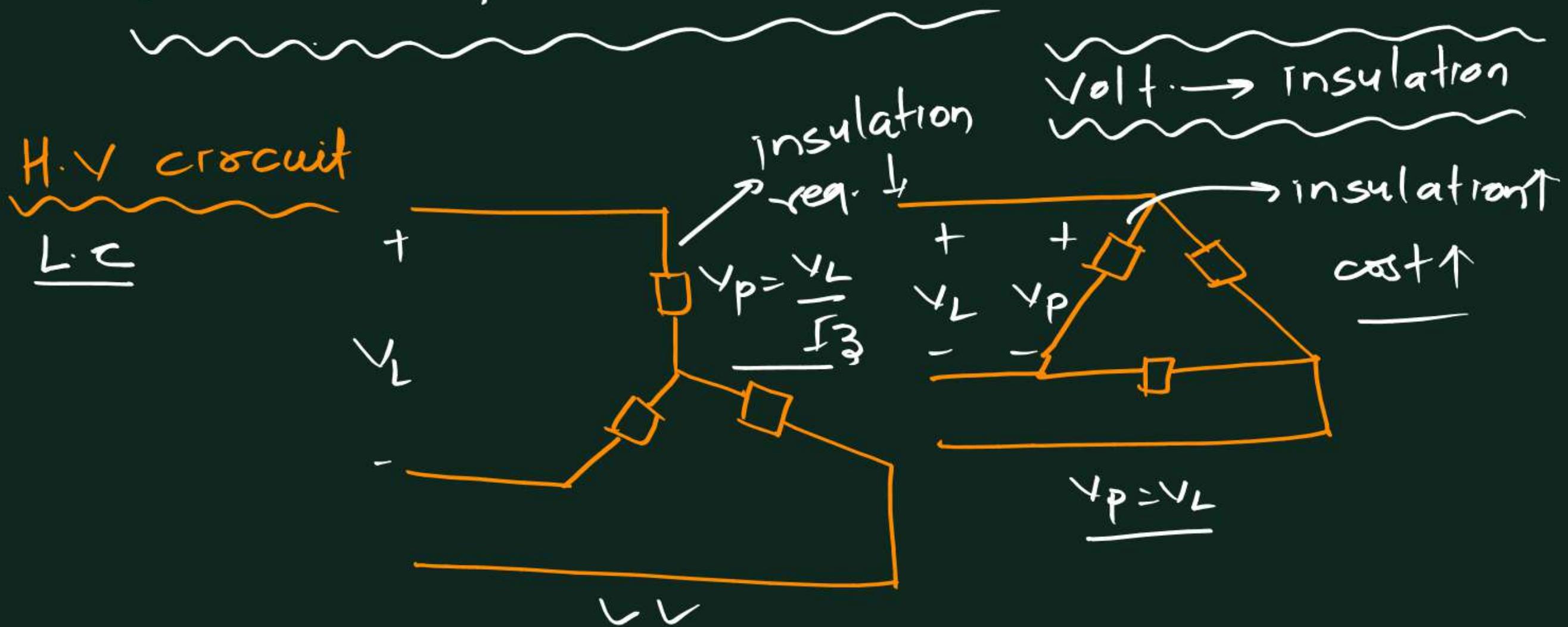


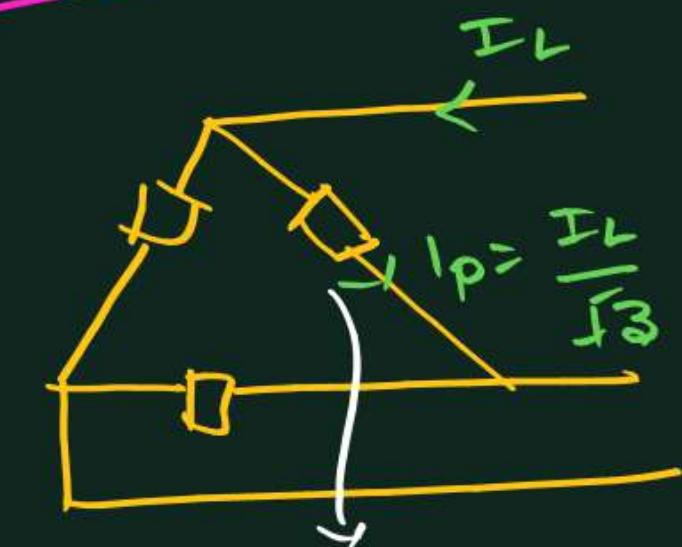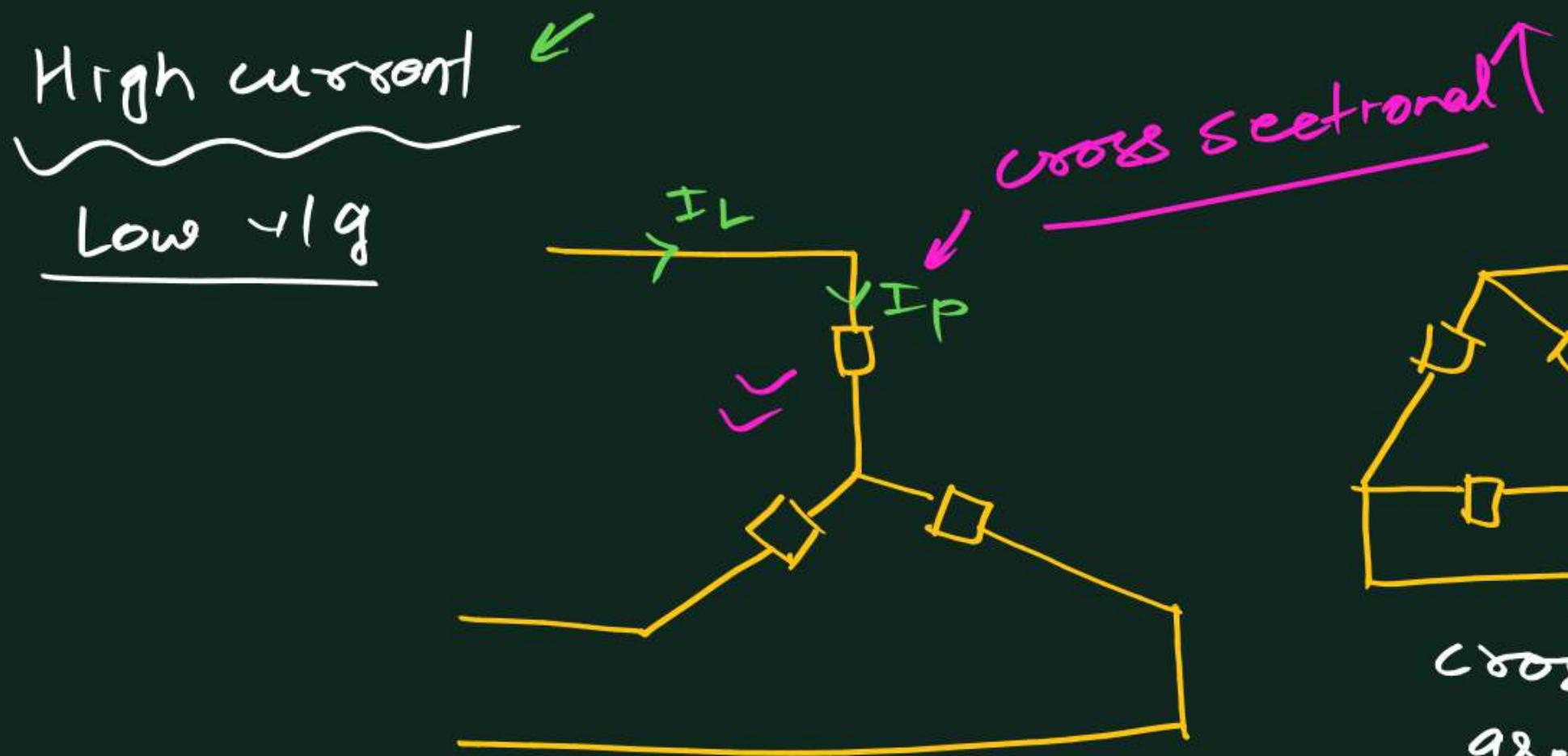

cross-sectional area ↓
 Cost ↓

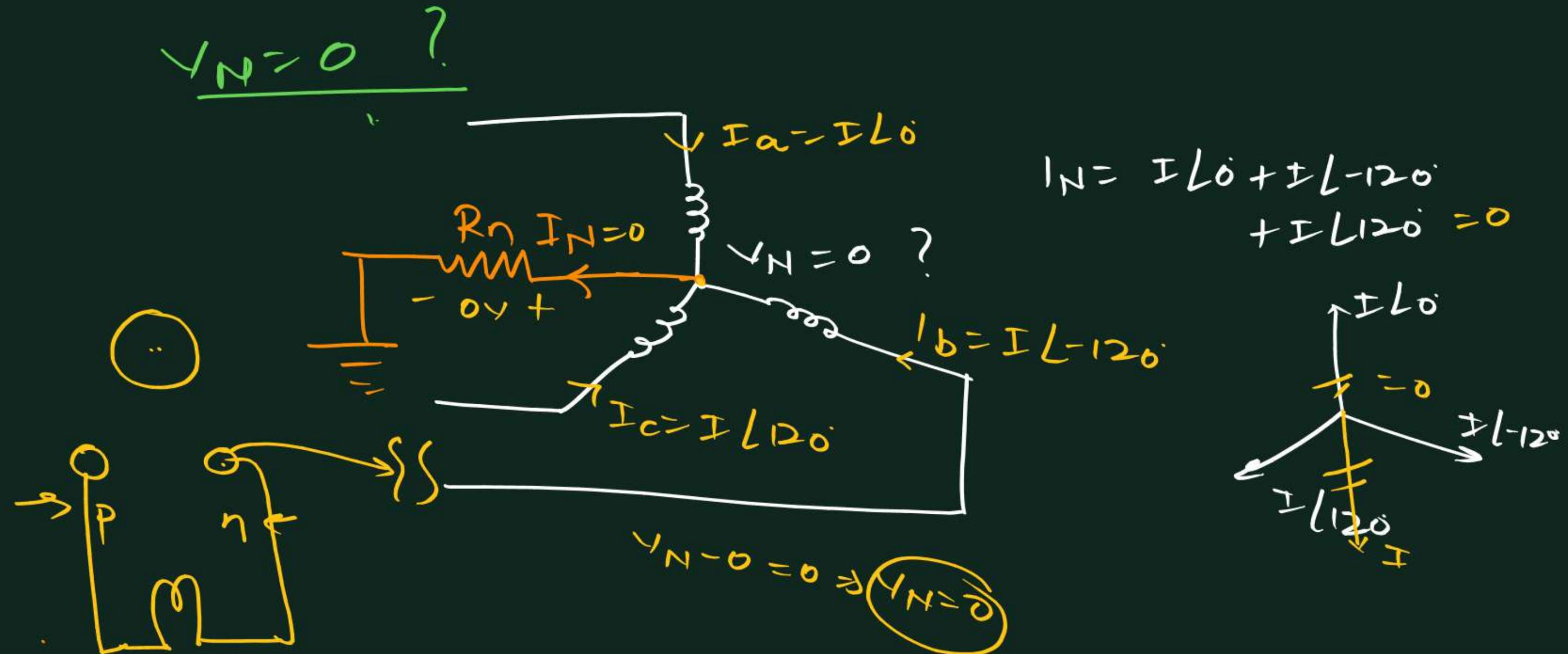

eq:

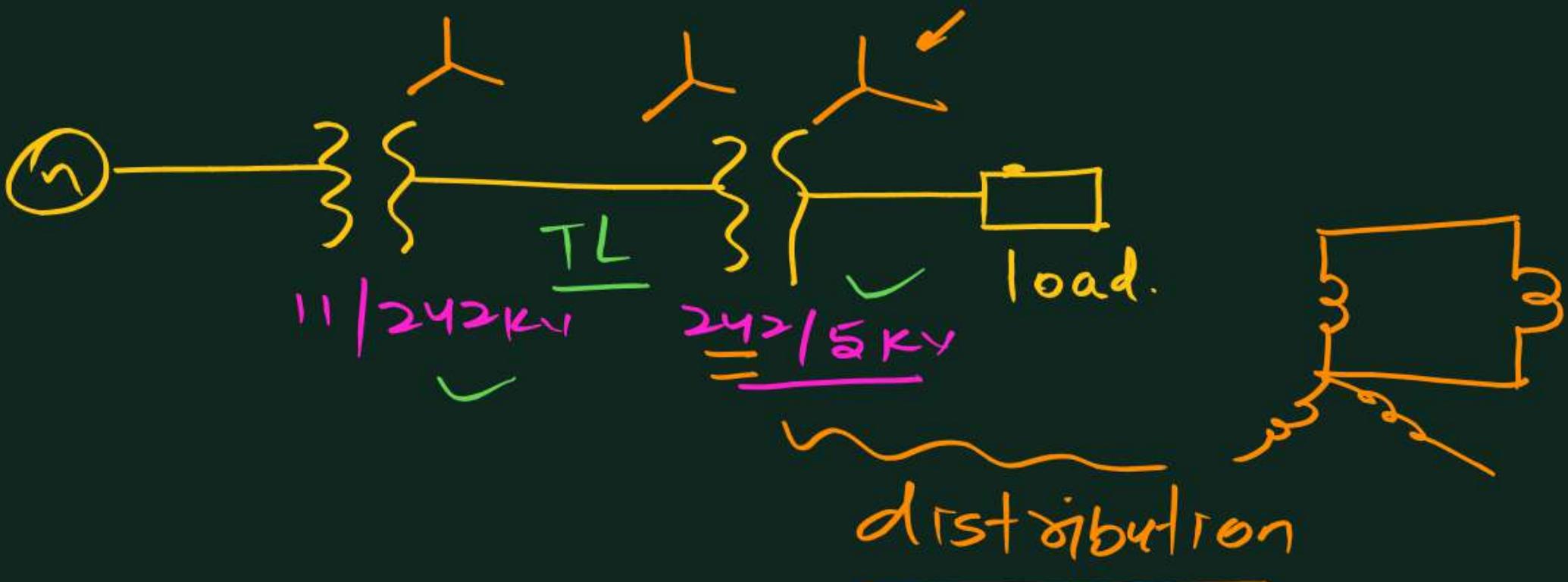

* TLs are supposed to be λ connected.

New Product available on Adda247 App

Adda247

THANKS FOR

Watching
Adda247

