

WELCOME TO GATE Adda 247

PAID COURSES OF GATE 2024/25 ARE
AVAILABLE FOR ALL STREAMS (EE/EC/ME/CE)

USE CODE

(Y503)

FOR BEST MENTORSHIP AND MAXIMUM DISCOUNTS





CONCEPT OF GROUND

70v
Σ

- Carry fault current, in case of insulation breakdown.
 - Some current always flows through ground path due to capacitive and inductive coupling etc.
 - For safety concerns against leakage on residual currents via low impedance path.
 - While phase/ neutral connected to main power wiring, earth may be connected to body of the equipment.
 - Though both neutral and ground are made grounded, they should no be mixed.
- ref Vol., will never affect Potential difference,
but node Vol. definitely changed.

Ex-

Find the current in each element?

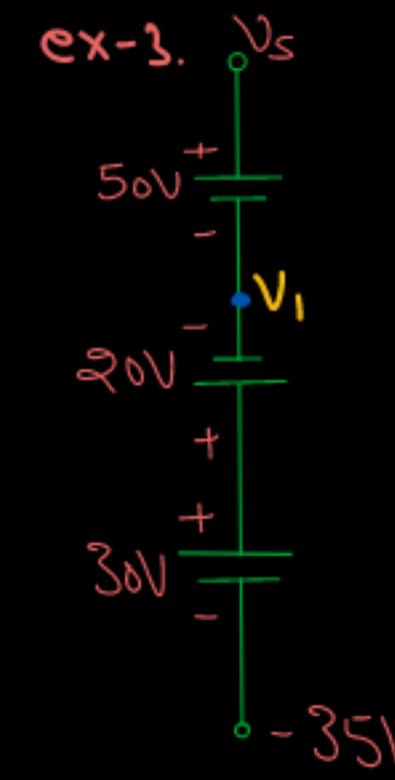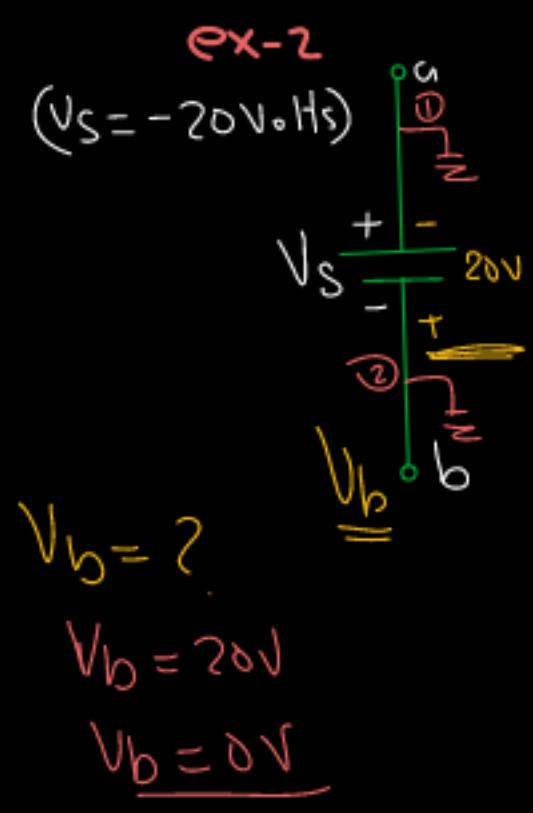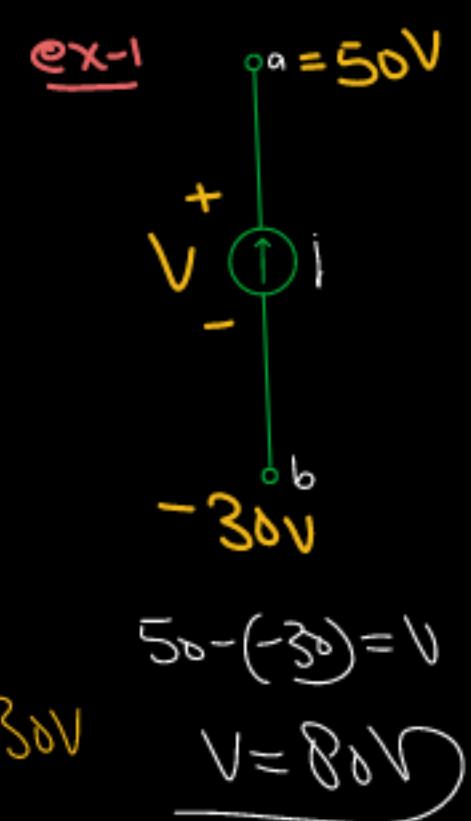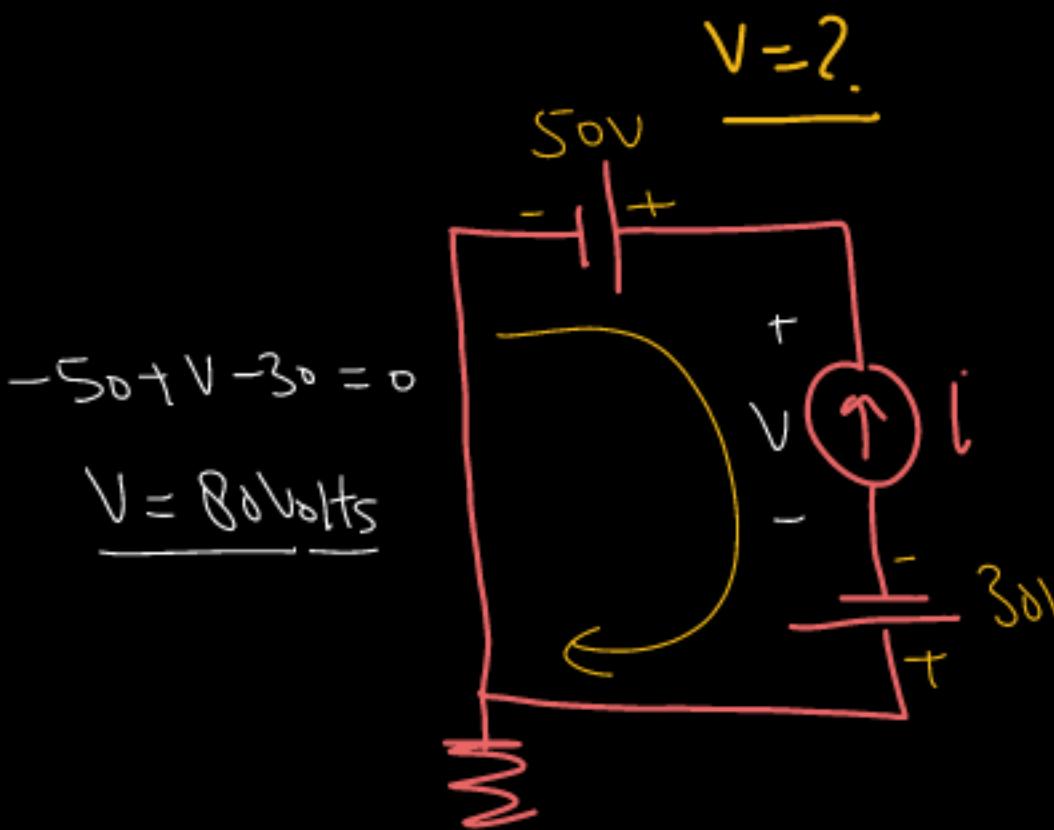

Soluⁿ -
 Potential diff. \Rightarrow
 $V_1 - (-35) = -20 + 30$
 $V_1 + 35 = 10$
 $(V_1 = -25 \text{ Volts})$
 $\Rightarrow V_S - V_1 = +50$
 $V_S - (-25) = 50$
 $\therefore V_S = 25 \text{ Volts}$

The value of


V_S

is $= \underline{\underline{V_S}}$

Soluⁿ \Rightarrow node vol.
 $V_S = 50V$
 $V_S = 0V$
 $V_S = 30V$
 $V_S = 60 \text{ Volts}$

⇒ Ex- Find me Vol. at node 'a'


- a) 0V ✓ b) -50V
- c) 30V ✓ d) 60V

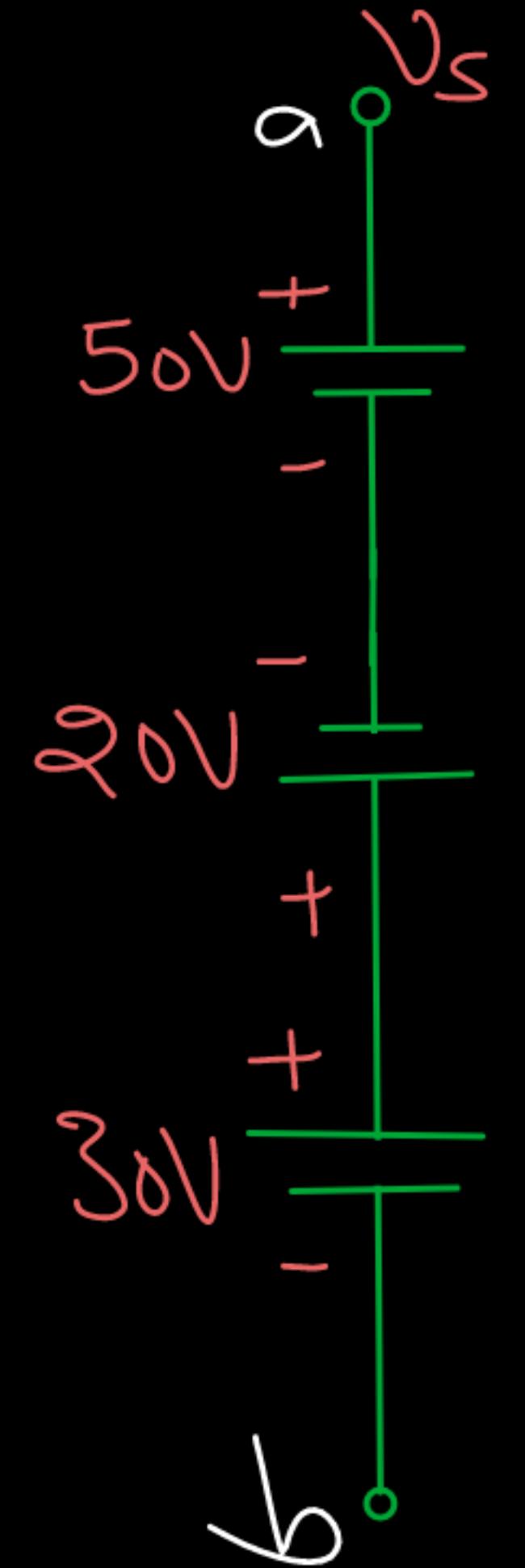


Node voltage

⇒ The Vol. at a particular junction, is called node Vol.

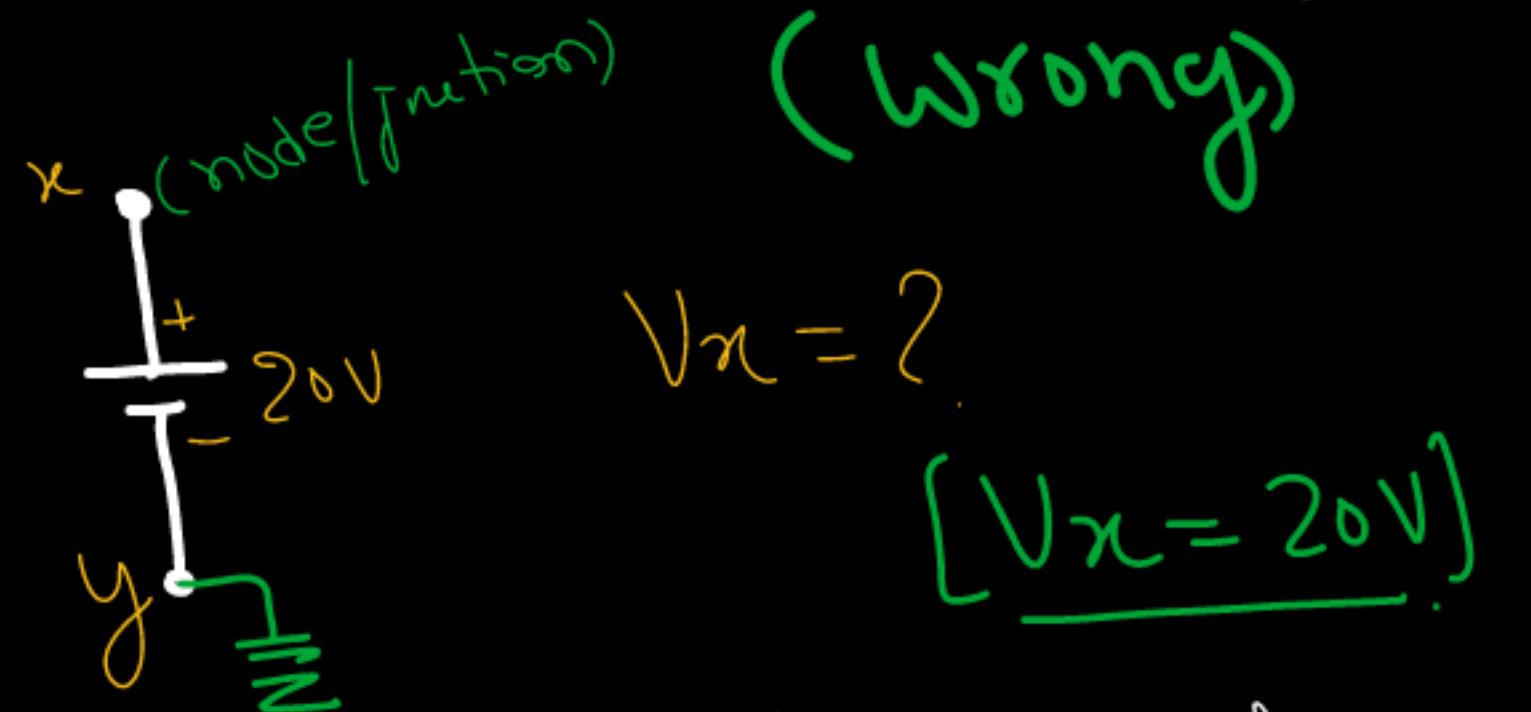⇒ "node Vol. is also called potential difference"



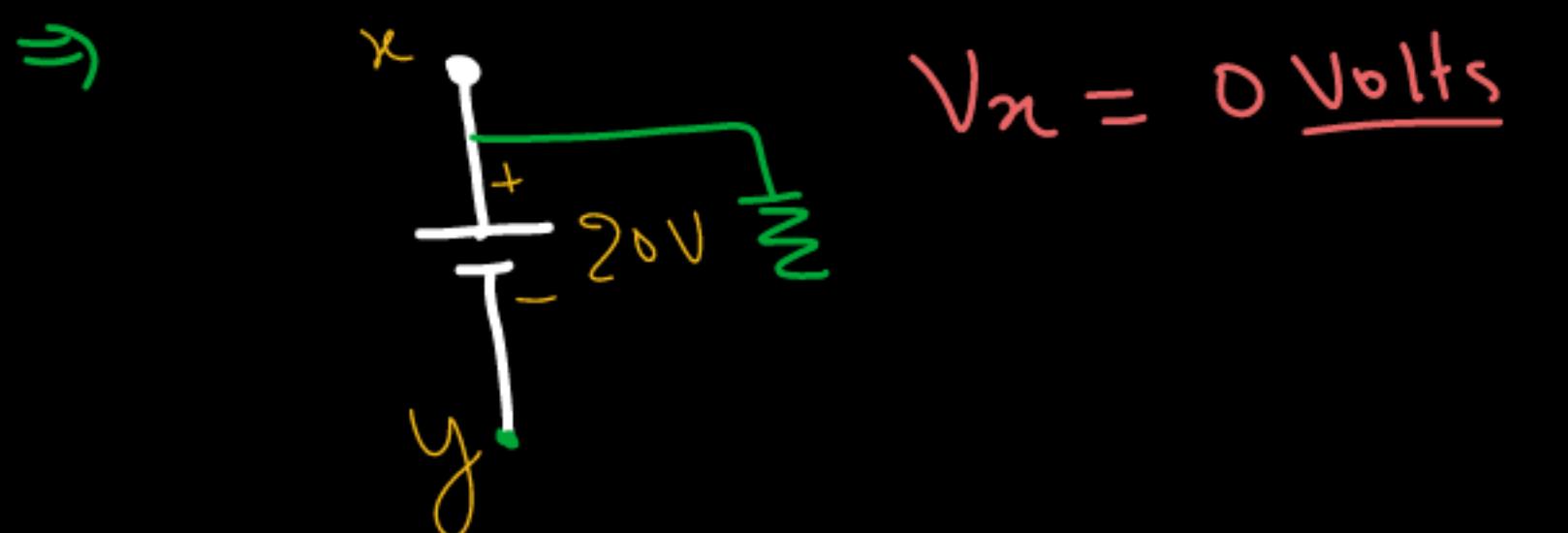* to calculate node Vol, one reference point is mandatory in the circuit.




⇒ Therefore, we can say, node Vol. will affect w.r.t. ref. Vol. location.

Ex-1. $V_a = ?$


- a) 40V b) 20V c) 0V
d) -20V.

(c) 0V

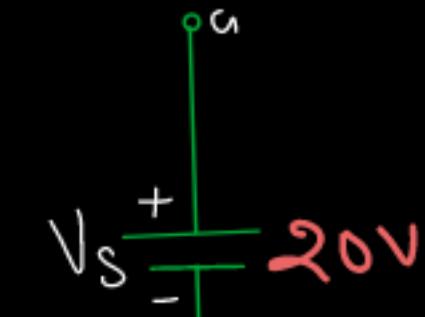

Soluⁿ \Rightarrow in the given question, ref. Point is not given. So - - -

Cyc ① $V_a = 0 \text{ Volts}$

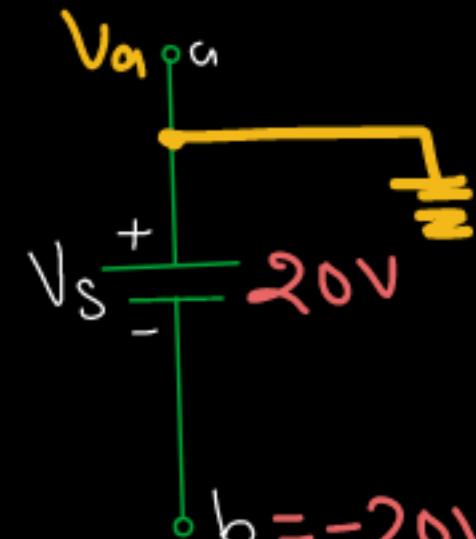


Cyc ②

$V_a = 20V$. $V_s = 20V$



Cyc ③ $V_a - (-20) = 20$

$V_a = 0V$

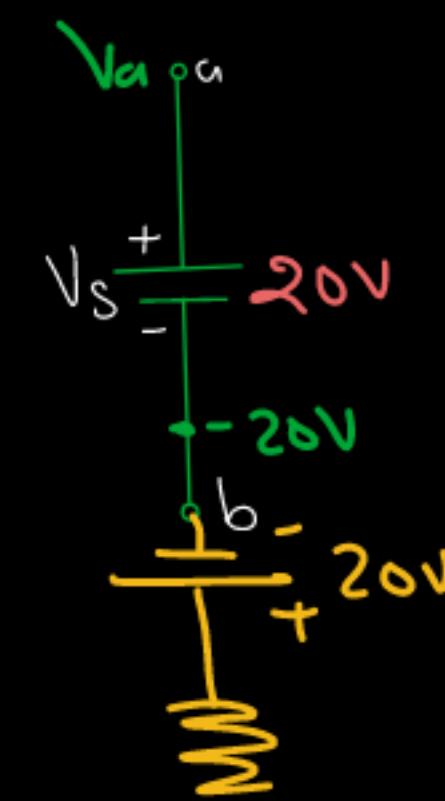

Potential difference

Ex- calculate V_{ab} in each case.



Soln - let $V_x > V_y$

$$V_x - V_y = +20 - 30 + V_{ab}$$

$$10 - (-10) = -10 + V_{ab}$$

$$(V_{ab} = 30 \text{ Volts})$$


2nd way let $V_y > V_x$.

$$V_y - V_x = -V_{ab} + 30 - 20$$

$$-10 - 10 = -V_{ab} + 10$$

$$+30 = +V_{ab}$$

$$\therefore V_{ab} = 30V$$

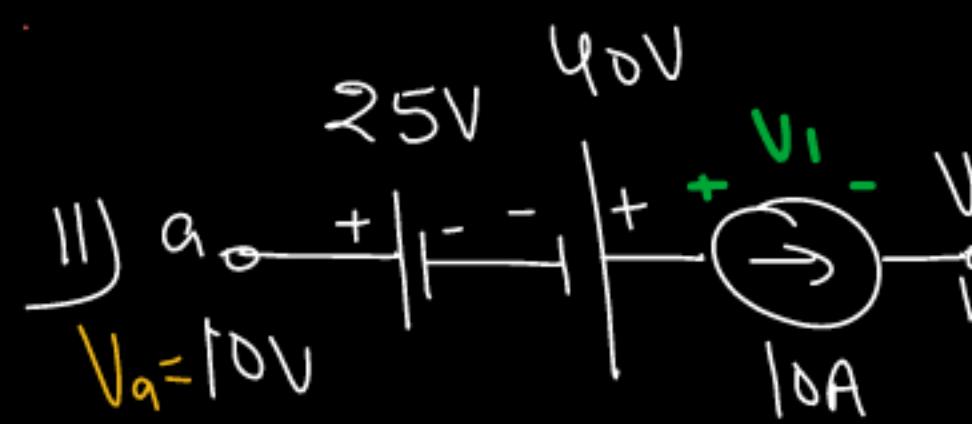

$$V_{ab} = ?$$

\Rightarrow let V_0 across current source = V_1

let $V_a > V_b$.

$$V_a - V_b = 25 - 40 + V_1$$

$$V_{ab} = (-15 + V_1)$$

$$\text{OR } 10 - V_b = V_1 - 15$$

$$(25 - V_1) = V_b$$



Current calculation in Circuit

* to calculate current, we require potential diff.

* Potential difference meas. Vol. diff. in b/w two

* Through (R, L, C), we can determine current by
Ohms law or other method.

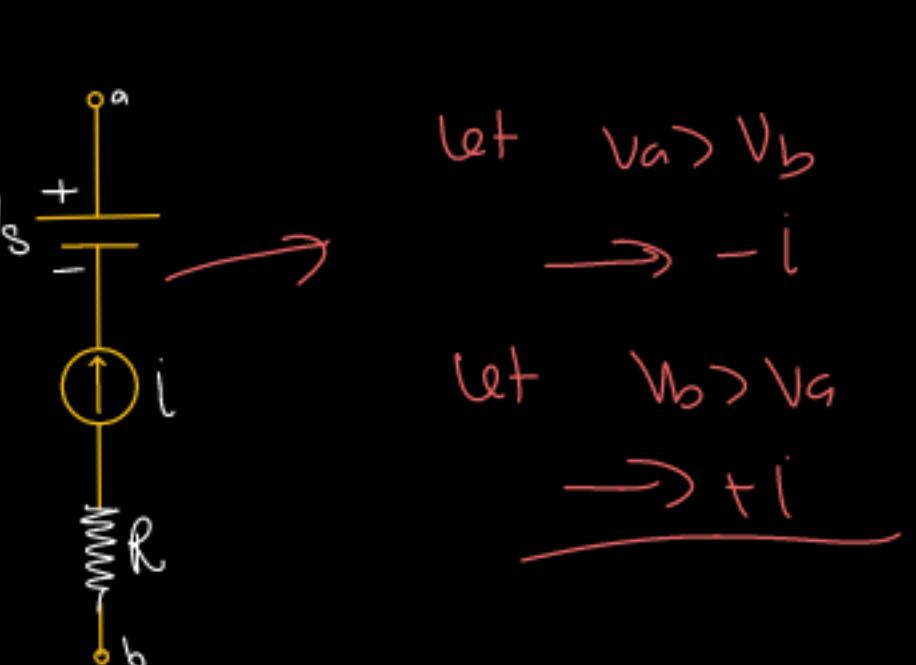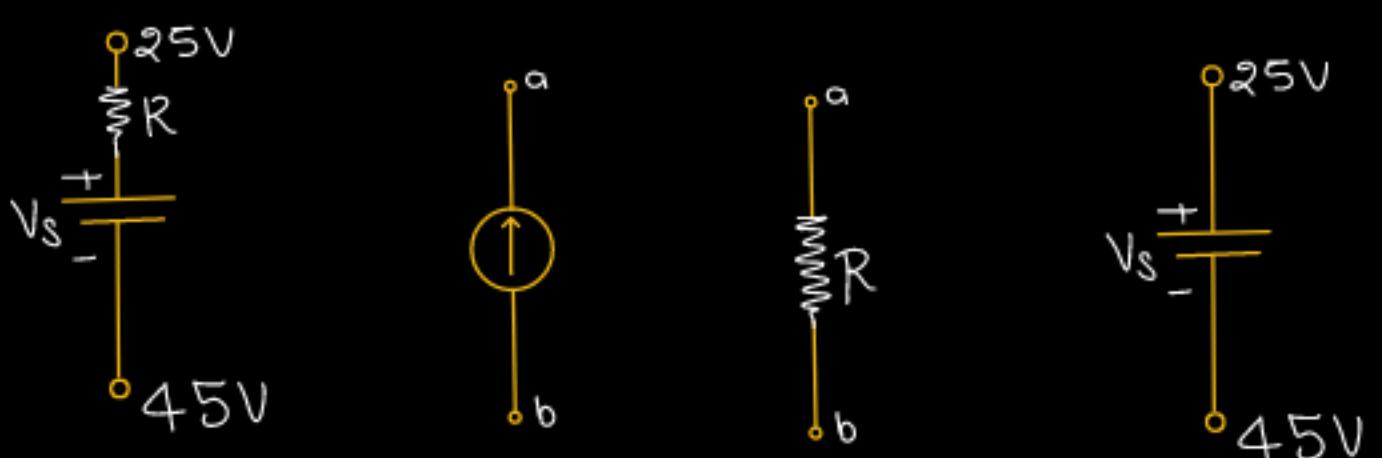but current through Vol. source, can't determine
by Ohms law.



Ex -
Already current
given.
① let $V_a > V_b$ $\rightarrow -I$.
② let $V_b > V_a$ $\rightarrow +I$

Ex - Assume current
Through V. source.



① $V_a > V_b$ $\rightarrow -I$

② $V_b > V_a$

$\rightarrow +I$

let $V_a > V_b$ $\rightarrow -I$
let $V_b > V_a$ $\underline{\underline{\rightarrow +I}}$

Ex-1. Current through "R" will be .

Soluⁿ- Let $V_a > V_b$.



We know that, in resistor current always flows from high potential to low potential.

$$\Rightarrow V_a - V_b = V_R$$

$$\therefore i = \left(\frac{V_a - V_b}{R} \right) \text{Amp.}$$

2nd way:- let $V_b > V_a$.
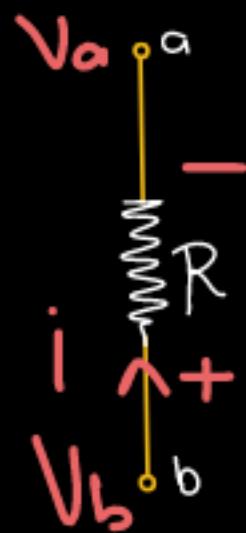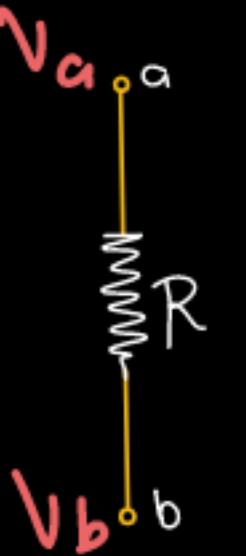
$$i = \left(\frac{V_b - V_a}{R} \right) \text{Amp.}$$




\Rightarrow Ex-2, current through resistors = -?

Soln: To calculate current, we req. Potential diff. across resistors.

$$\Rightarrow \text{let } (25 > V_a)$$

$$\therefore i = \frac{(25 - V_a)}{R}$$
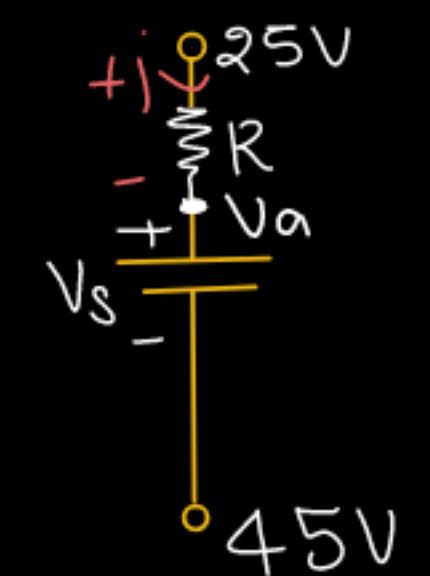
$$\therefore i = \left(\frac{25 - V_s - 45}{R} \right) \text{ Amp.}$$



By P.D.



$$V_a - V_s = V_s$$

$$V_a = (V_s + 45)$$


2nd way - $V_a > 25$.

$$\therefore i = \frac{V_a - 25}{R}$$

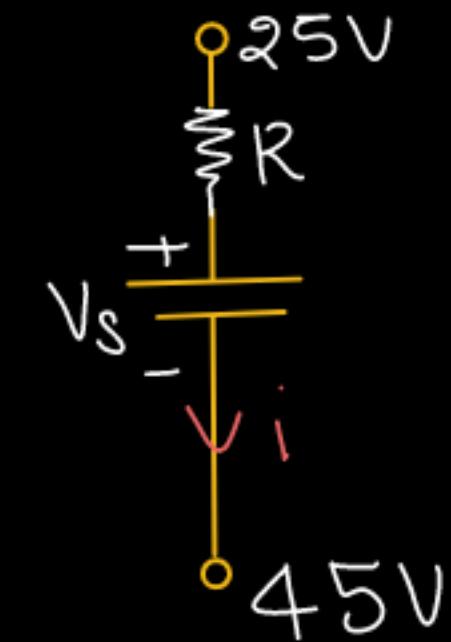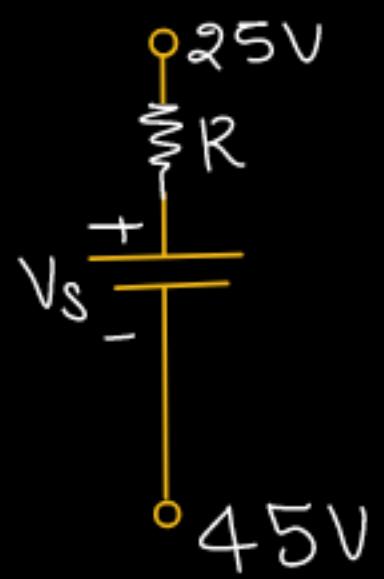
$$i = \left(\frac{V_s + 45 - 25}{R} \right) \text{ Amp.}$$



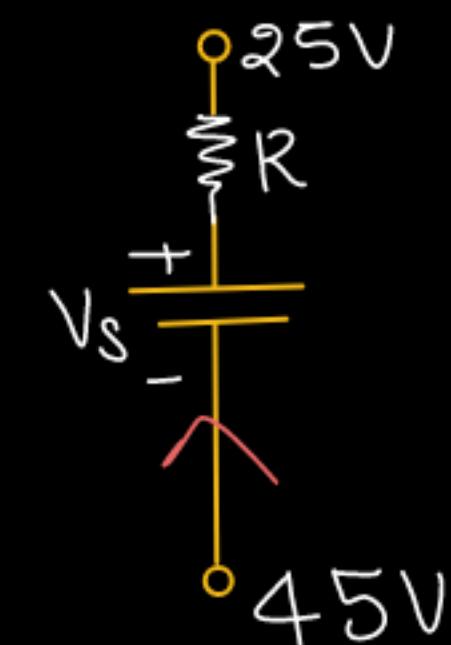
$$i = \left(\frac{25 - 45 - V_s}{R} \right)$$



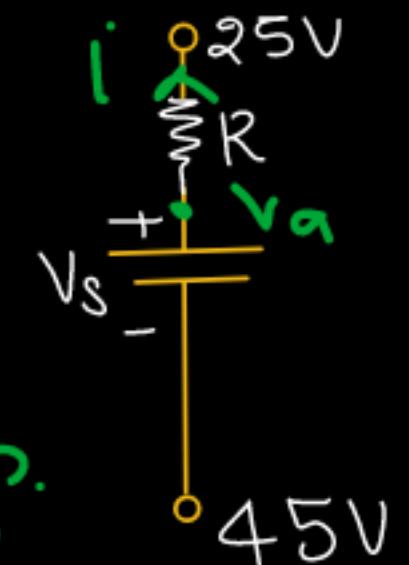
$$i = \left(\frac{V_s - 25 + V_s}{R} \right) \text{ Amp.}$$



Ex- Find the current in each case ?

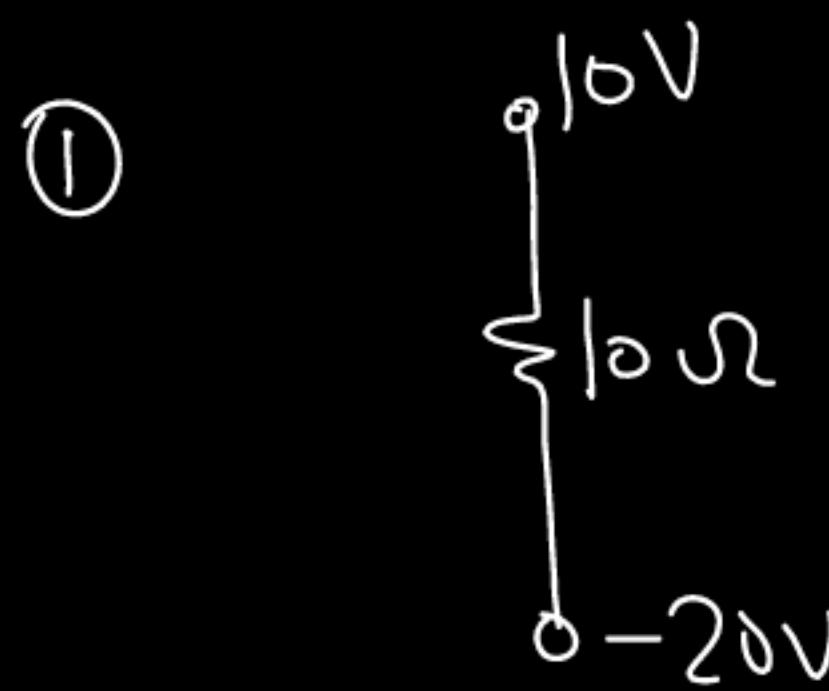

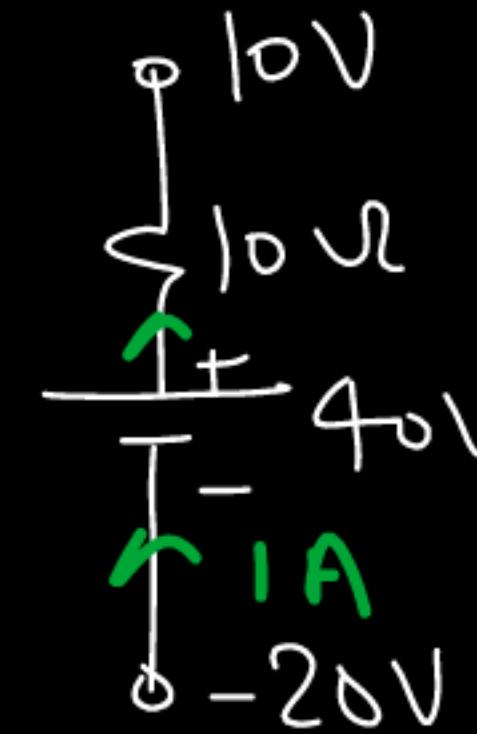
$$i = \frac{10 - (-20)}{10} = \underline{\underline{3A}}$$




$$\frac{10 - (-20) - 40}{10} = i$$

i = -1A

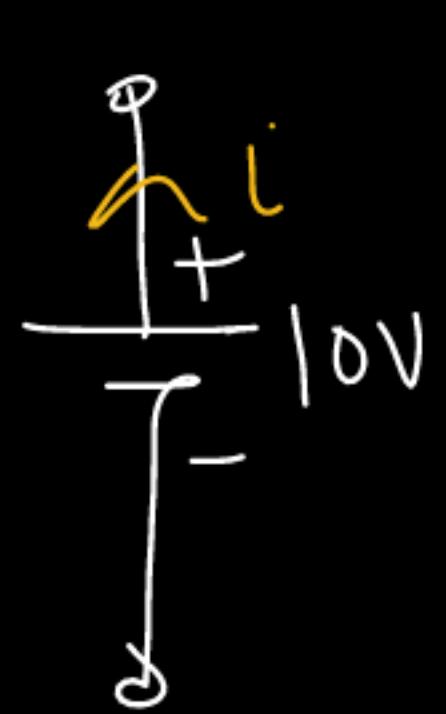

$$i = ?$$

we can't
calculate

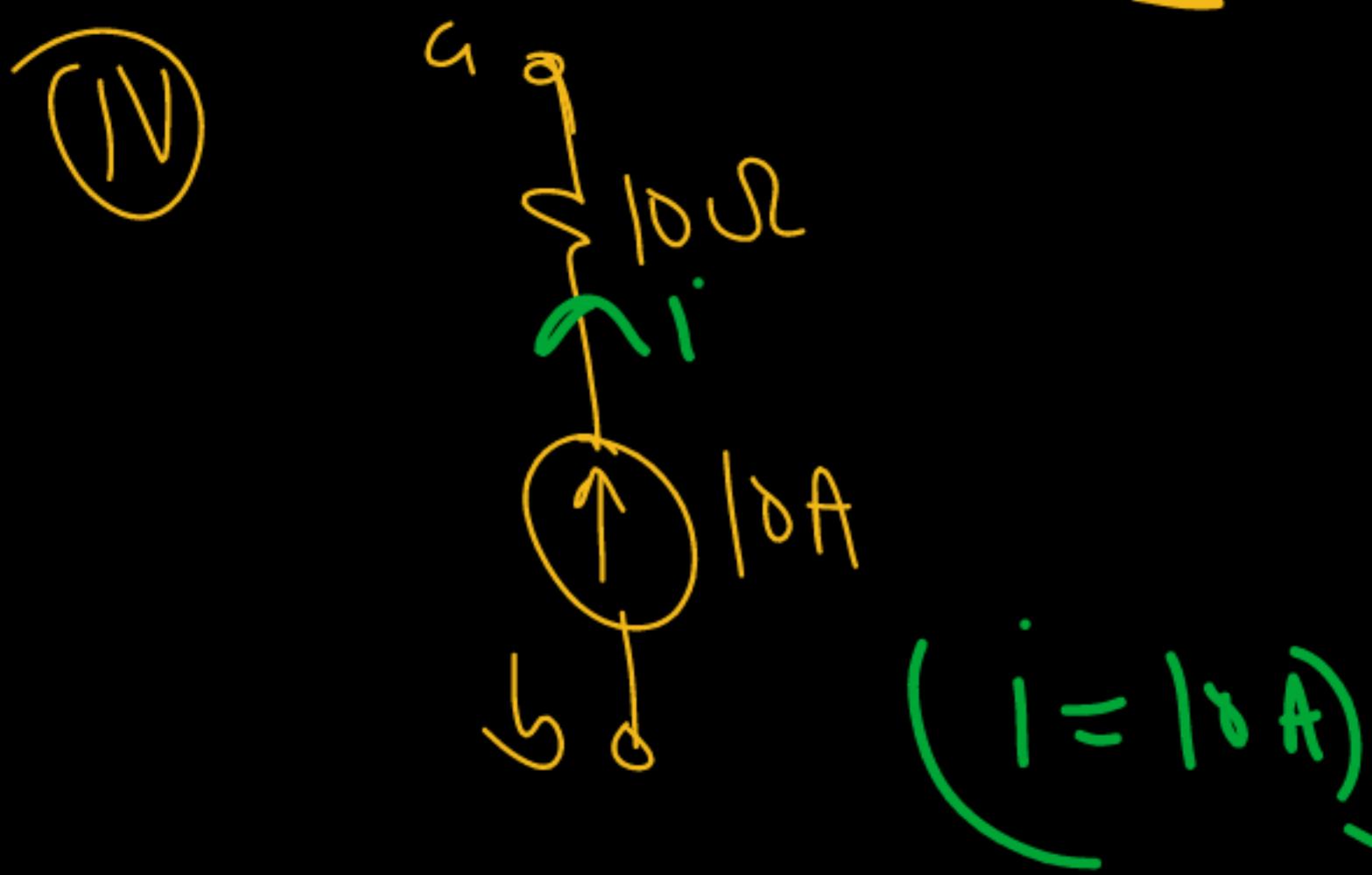


KIRCHHOFF'S CURRENT LAW (KCL)

KEYPOINTS :

- "works on the principle of charge conservation"
- $(\sum \Delta i = 0)$ based on conservation of charge.
- $i = \frac{dq}{dt}$
- Valid for linear-time invariant system.
- To calculate node voltage, it is mandatory to take reference point.
- Always assume an unknown voltage across the dependent/independent current source, before solving the circuit either by KCL or KVL or any other method.
- Nodal analysis = KCL + ohm's law.

$$\left[\sum \Delta i = 0 \right], \quad (i_1 + i_2 + i_3 + i_5 + i_6 = i_4)$$

n

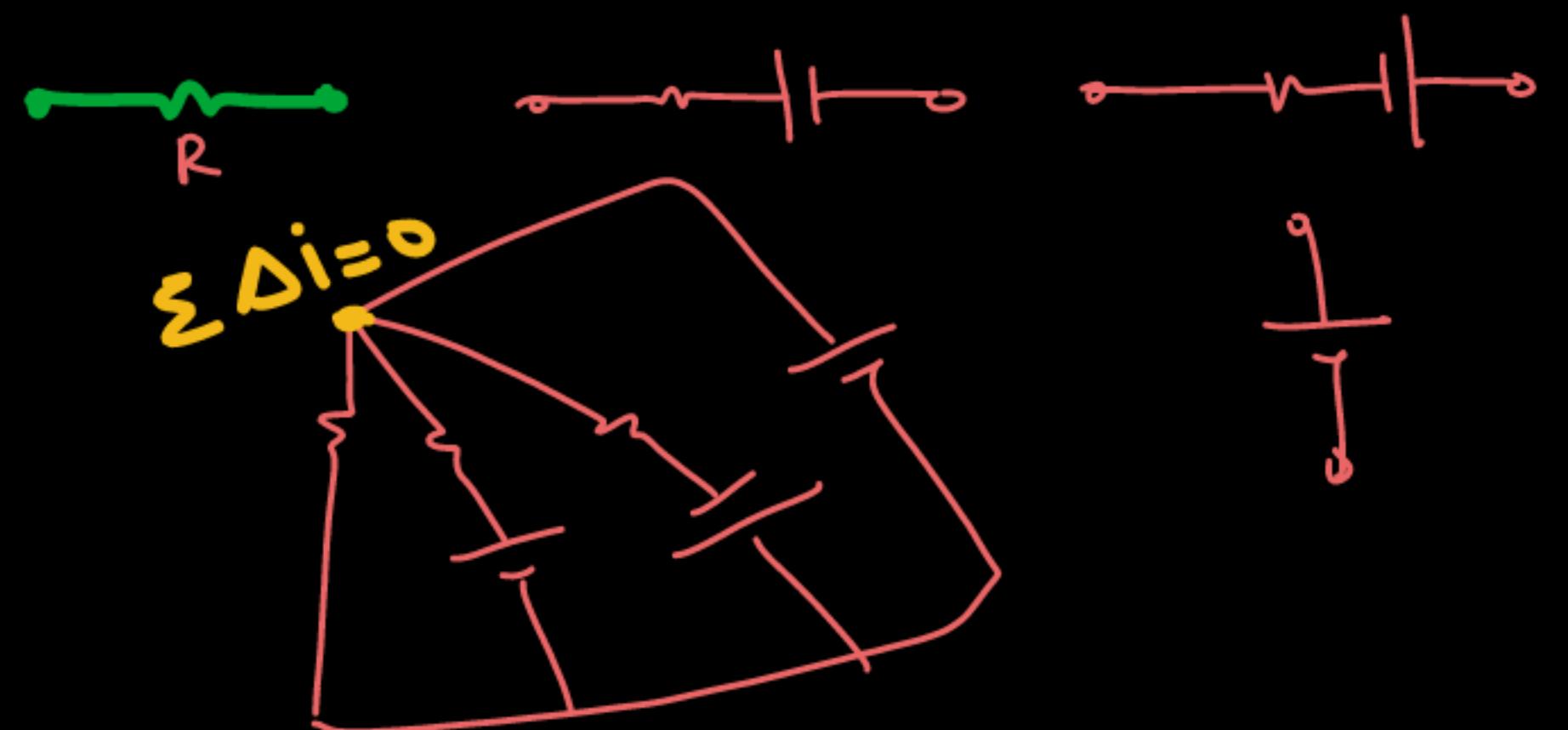


$$\frac{q}{I}$$

STEPS FOR NODAL ANALYSIS

- Identify all the essential nodes, *and define vol. for each node.*
- Select one of the node as a reference node. i.e. ground.
- Apply KCL to each labelled node.
- Assume the voltage to be higher/lower at the node, we are applying KCL at.
- If a current source is given anywhere in the circuit, assume a voltage across that current source.
- If an ideal independent or dependent voltage source is present, without any series resistance in between two nodes, always assume a current through these sources.
- Once all the node voltages are known, we can calculate anything like current, power, energy etc.

Ex-1

Write down KCL equations for each Node

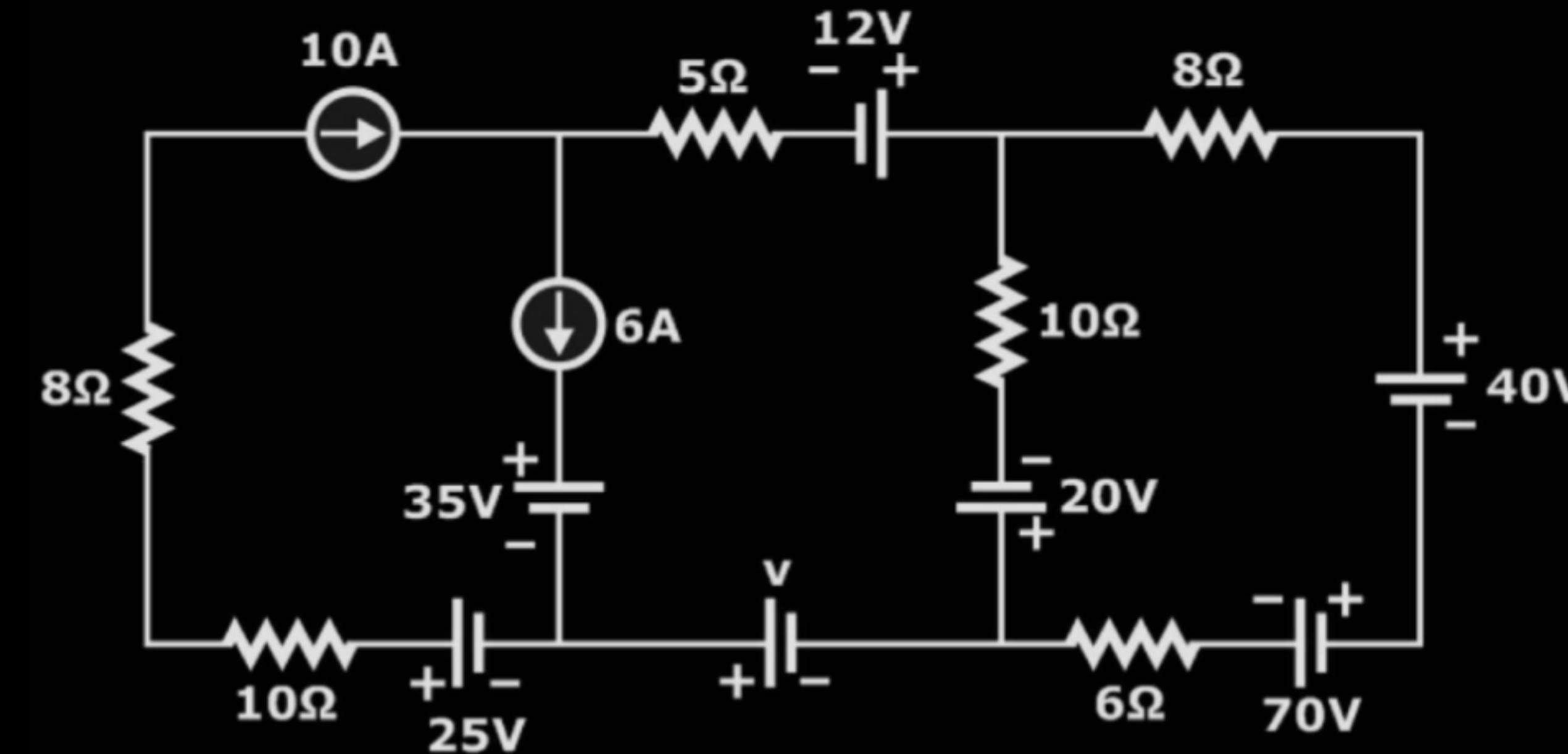

Ex-2


Write down KCL equations for each Node

\Rightarrow KCL at node ①

Let -V_{o1} at node ①

is the highest vol.
of ckt.

* node ①, is connected
with 5 amper.

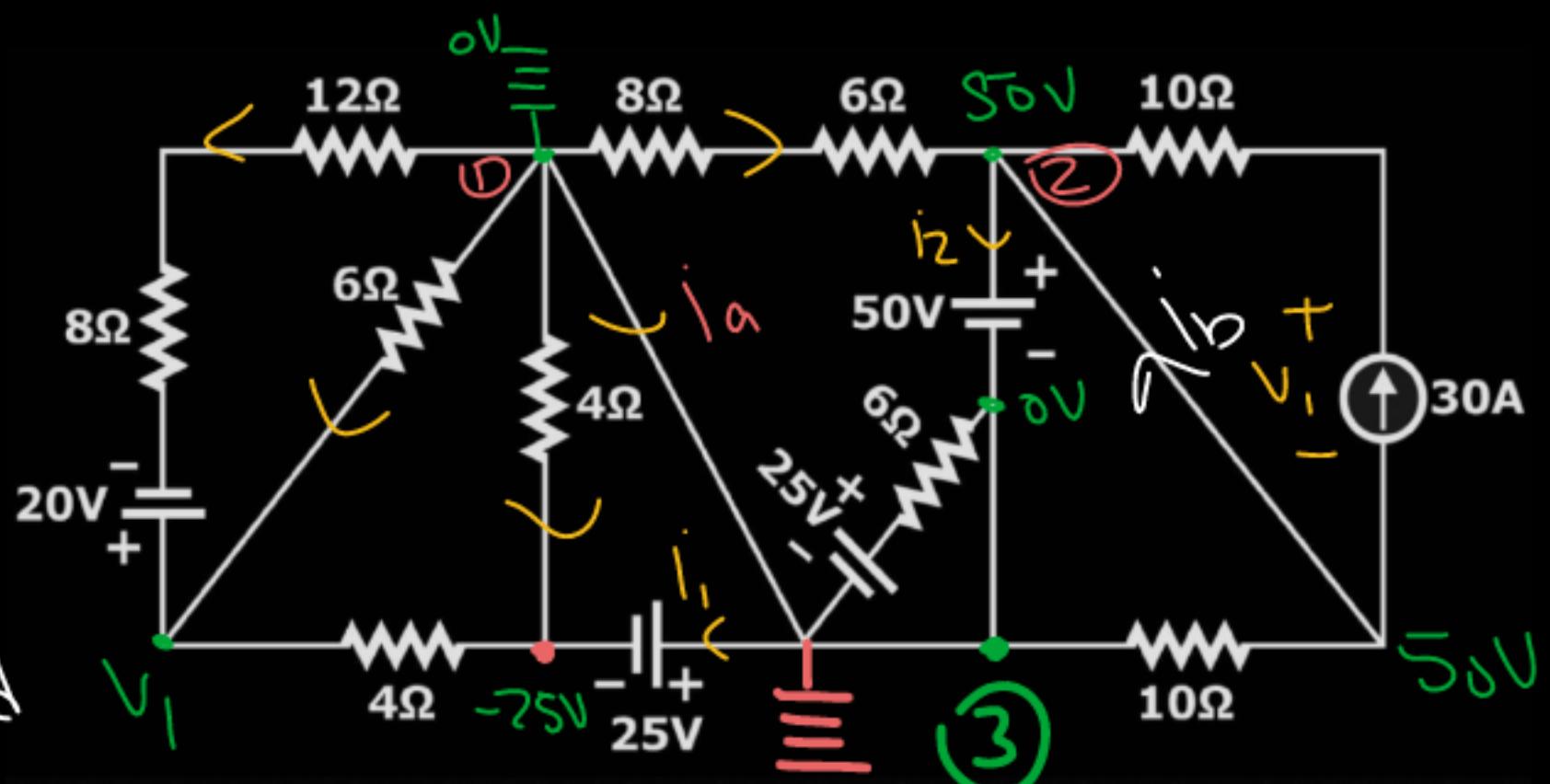

KCL at node (2).

let nod 2, vol. is highest
vol. of ckt.

$$\frac{50-0}{14} + i_2 - 30 - i_b = 0$$

$$\frac{0-V_1}{6} + \frac{0-V_1+20}{20} + \frac{0-(-25)}{4} + \frac{0-50}{14} + i_a = 0$$

Ex-3

Write down KCL equations for each Node

