



**USE CODE (Y503)**

**FOR PAID COURSES OF  
GATE 2024**


**EE/EC/ME/CE**

# Ex. Write down all necessary kcl Equations for given Circuit

Sol<sup>n</sup> →

I) take a ref. point, in the ckt "anywhere"

II) identify the no. of necessary nodes.

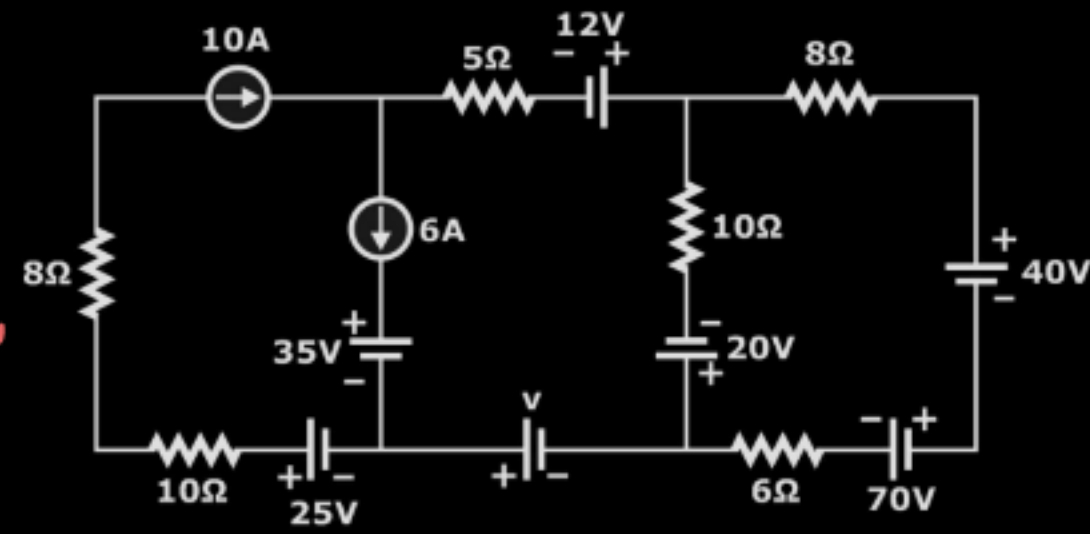


① Node Analysis, at node 1

KCL at node 1

⇒ let  $V_1$  is the highest Vol. of ckt.

$$-10 + 6 + \frac{V_1 - V_2 + 12}{5}$$

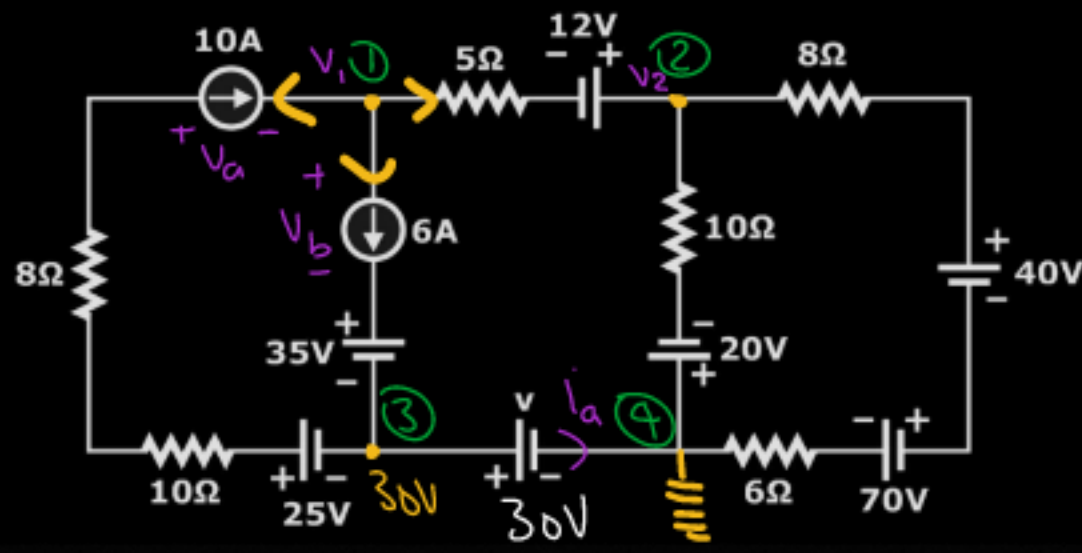


$$\left( \frac{V_1 - V_2 + 12}{5} \right) = 4$$

$$V_1 - V_2 + 12 = 20 \quad \text{OR} \quad V_1 - V_2 = 8 \quad \text{①}$$

⇒ KCL at node (2):-

let  $-V_2$  is highest vol. of ckt.
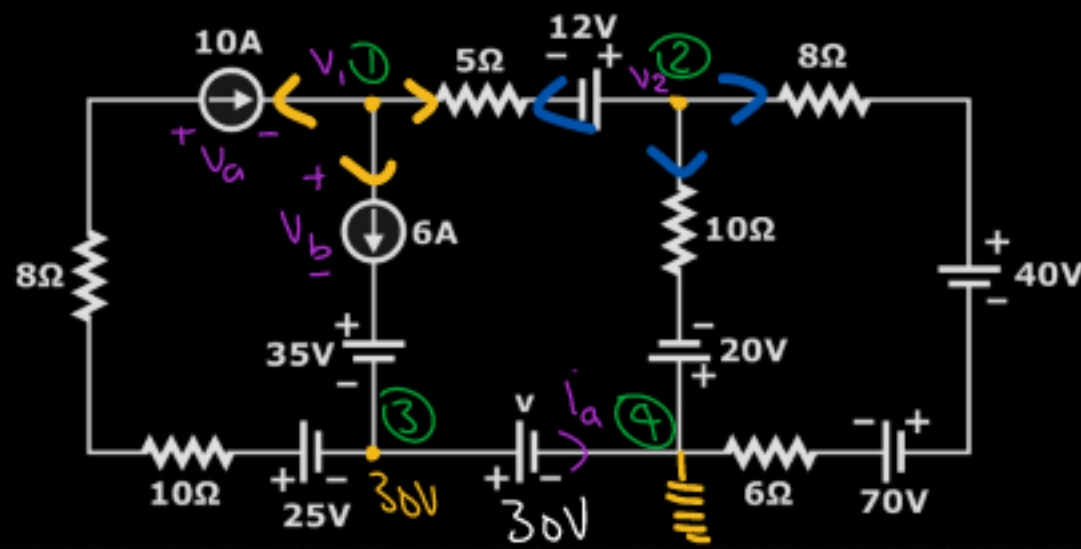
$$\frac{V_2 - V_1 - 12}{5} + \frac{V_2 + 20}{10} +$$



$$\frac{V_2 - 40 - 70}{14} = 0 \quad \text{②}$$




⇒ KCL at node ③

let, Vol. at node ③ is

The highest vol. of ckt.

$$+10 - 6 + i_a = 0$$

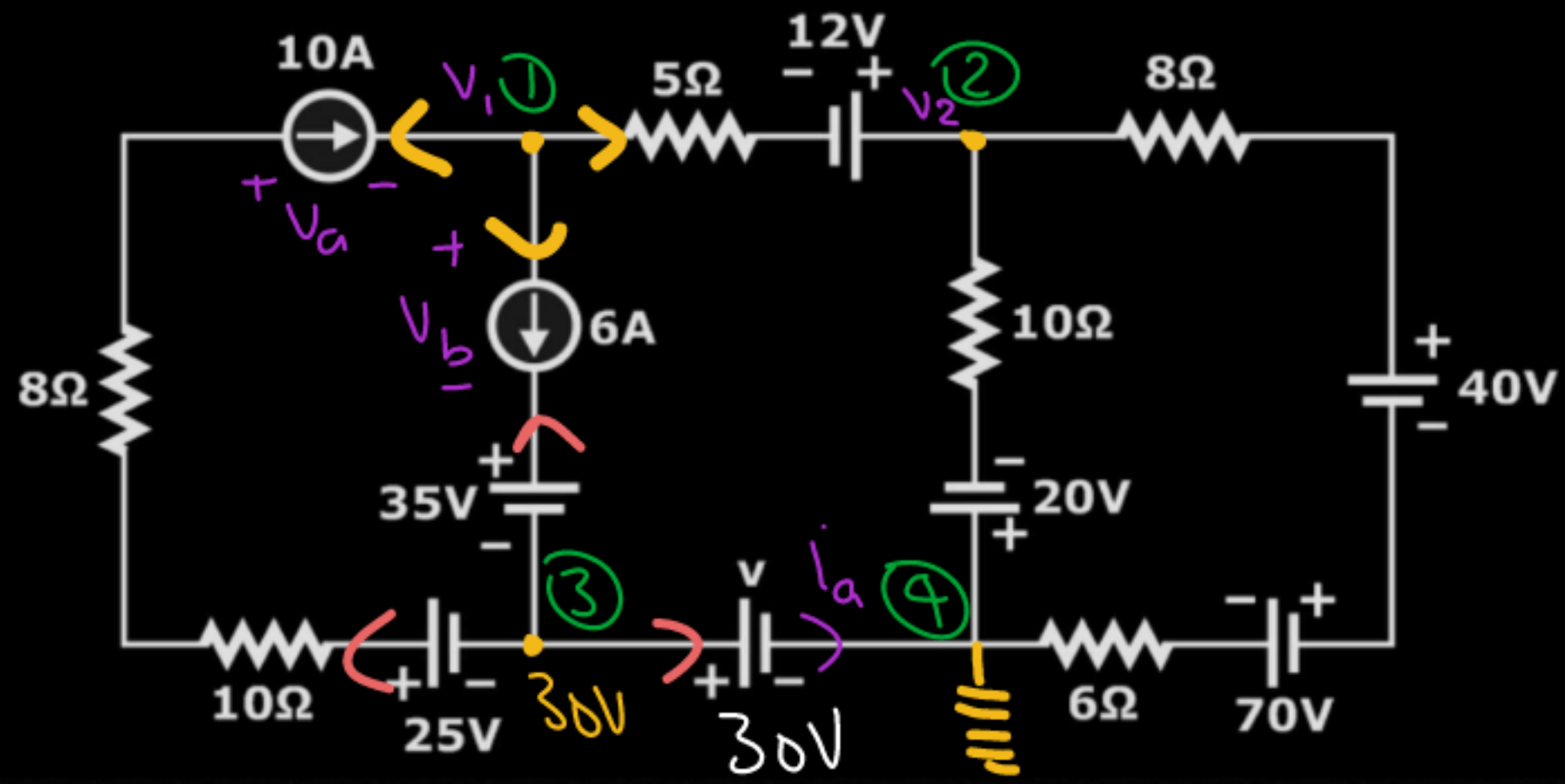

⇒ KCL at node ④


let, Vol. at node ④

is the highest

Vol. of ckt.


$$-i_a + \left( \frac{0 - V_2 - 20}{10} \right) +$$
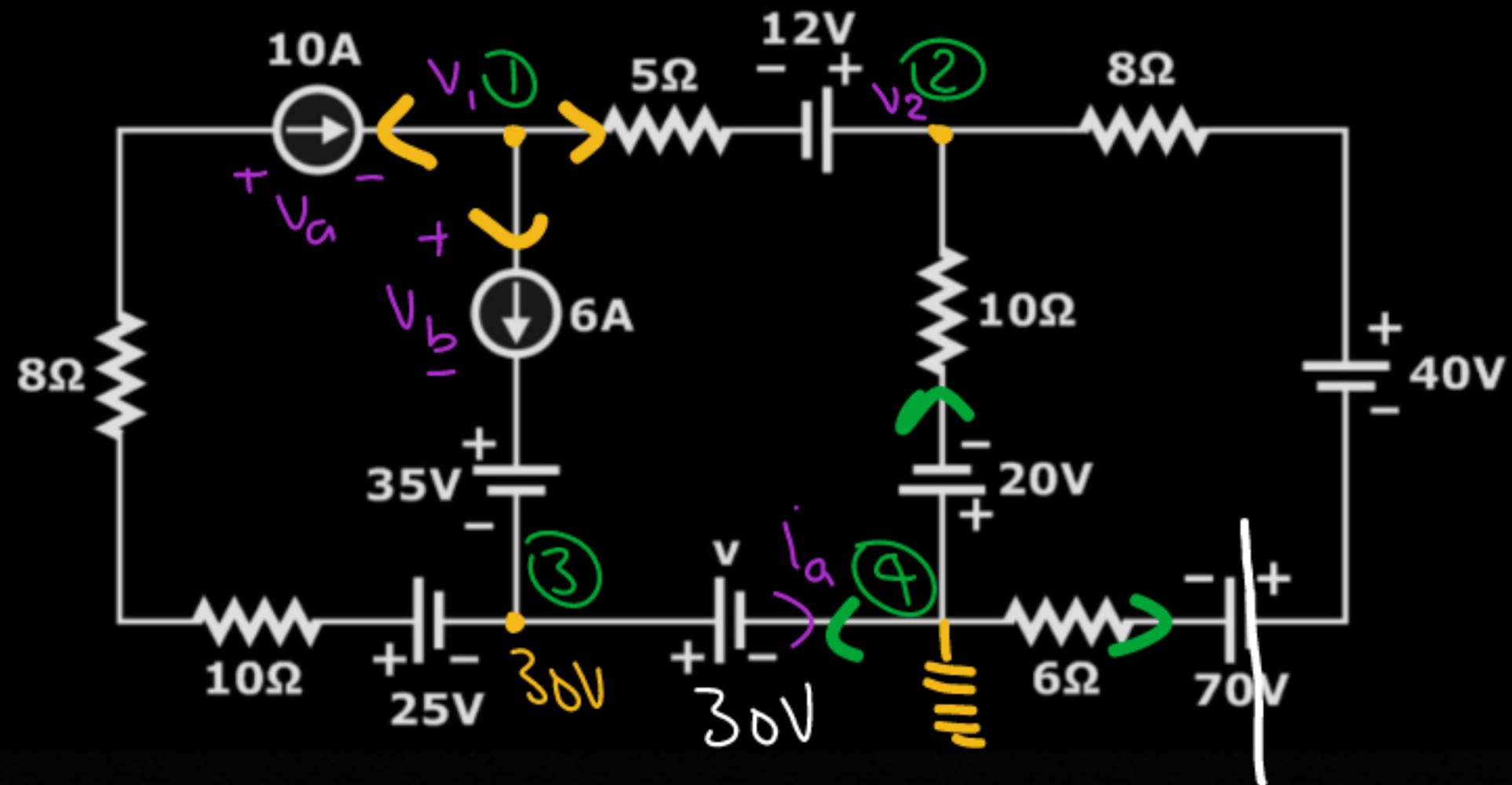
$$\left( \frac{0 - V_2 + 70 + 40}{14} \right) = 0 \quad (1V)$$



Ex. calculate power delivered by both current sources in given Circuit

By use of (KCL + ohm's)

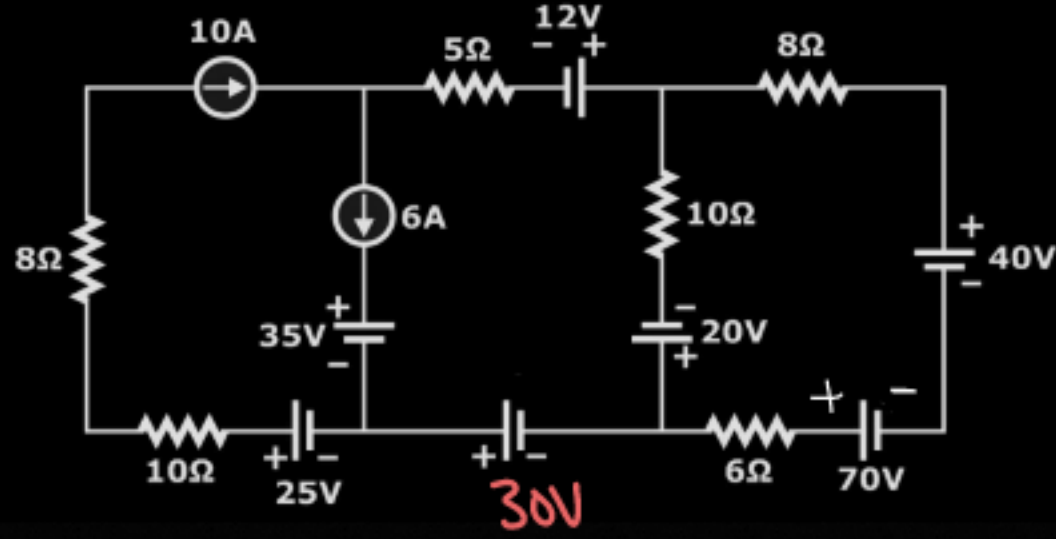

P.D. for  $V_a$

$$V_2 - 30 = -V_a - 80 + 25 - 80$$

$$7.92 - 30 + 160 - 25 = -V_a$$

$$\therefore V_a = -112.92V$$

$$P_{6A} = 6 \times 57.08$$

$$\text{del.} = 342.48W$$

Soln:  $\Rightarrow P_{10A} = (10 \times V_a)W$

$$P_{6A} = (V_b \times 6)W$$

By P.D

$$\Rightarrow V_2 + 0.08 = 20 - 12$$


$$V_2 = 8 - 0.08 = 7.92V$$

By P.D  $\Rightarrow$

$$V_2 - 30 = V_b + 35$$

$$7.92 - 30 - 35 = V_b$$

$$[V_b = -57.08 \text{ Volts}]$$

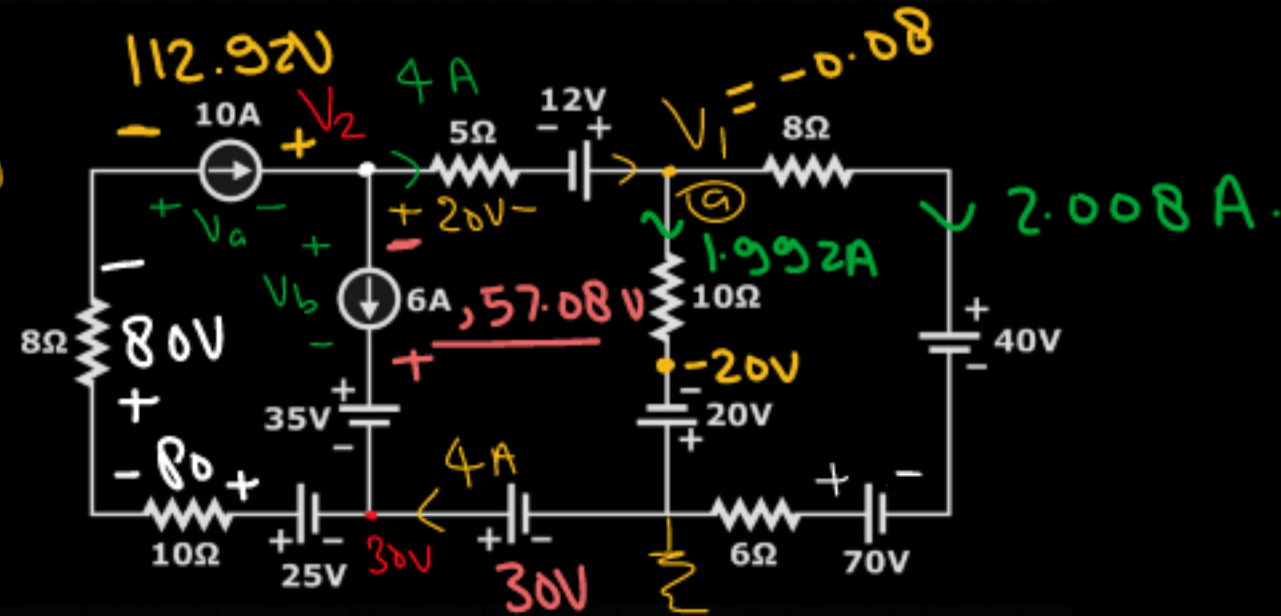

KCL at node 1.

Let - Vol. at node 1, is highest Vol. ofckt.

$$-4 + \frac{V_1 + 20}{10} + \frac{V_1 - 40 + 70}{14} = 0$$

$$V_1 \left( \frac{1}{10} + \frac{1}{14} \right) - 4 + 2 + \frac{30}{14} = 0$$

$$V_1 (0.171428) = -0.14285$$

$$V_1 = -0.083329 \text{ Volts}$$


$$[V_1 = -0.08 \text{ Volts}]$$

$$P_{10A} \text{ del.} = 112.92 \times 10 = 1129.2W$$

# Ex. Write down all necessary kcl Equations for given Circuit

Solu<sup>n</sup> :- KCL at node ① →

let,  $V_1$  is the highest Vol. of ckt.

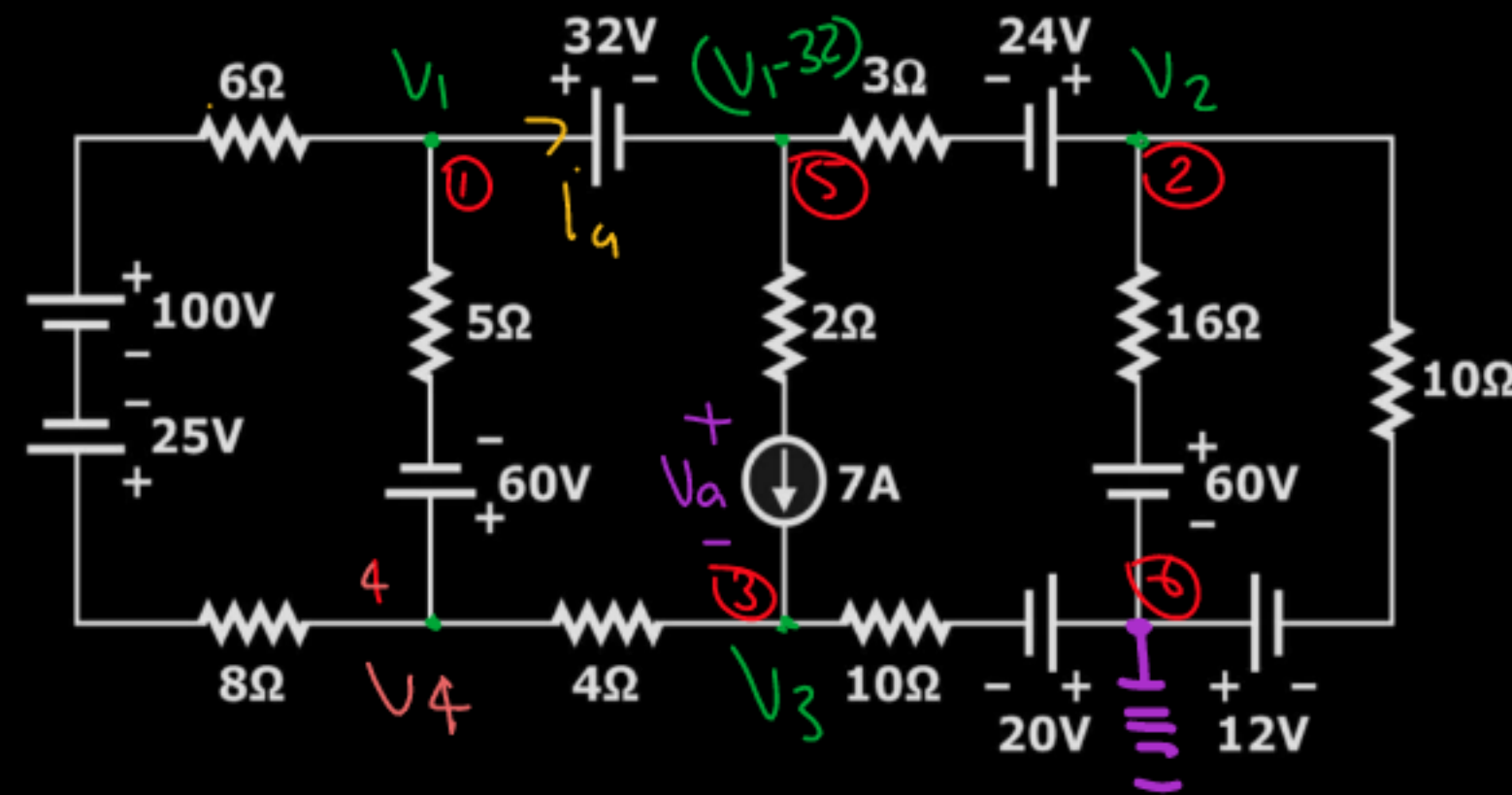

$$\left[ \frac{V_1 - V_4 - 100 + 25}{14} + \right.$$

$$\left. \frac{V_1 - V_4 + 60}{5} + i_a = 0 \right] \text{①}$$


, KCL eq<sup>n</sup> for node ⑥

$$\frac{0 - V_3 - 20}{10} + \left( \frac{0 - V_2 + 60}{16} \right) + \left( \frac{0 - V_2 - 12}{10} \right) = 0.$$


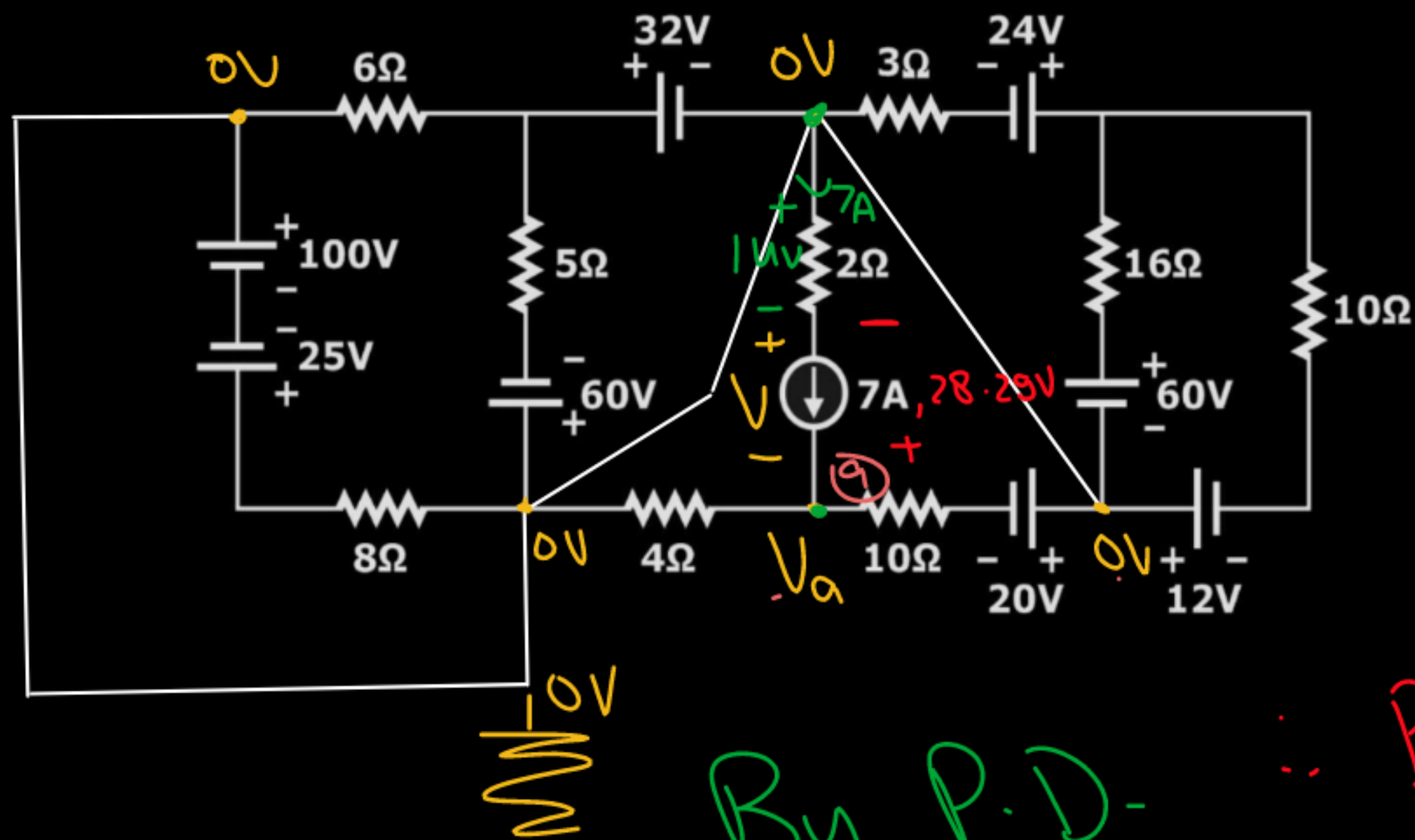
# Ex. calculate power delivered by current sources in given Circuit

Solu<sup>n</sup>: ref. vol. will affect node vol, not potential diff.  
KCL at node (a)



$$\frac{V_a}{4} + \frac{V_a + 20}{10} - 7 = 0$$

$$V_a \left( \frac{1}{4} + \frac{1}{10} \right) = 5$$

$$V_a = \underline{14.29 \text{ Volts}}$$

By P.D.


$$\therefore P_{c.s.} = 7 \times 28.29 = \underline{198 \text{ W}}$$

$$V_a - 0 = -V - 14$$

$$14.29 + 14 = -V$$

$$\therefore V = \underline{-28.29 \text{ Volts}}$$

ex-  $V_a = ?$   
(2 mints)

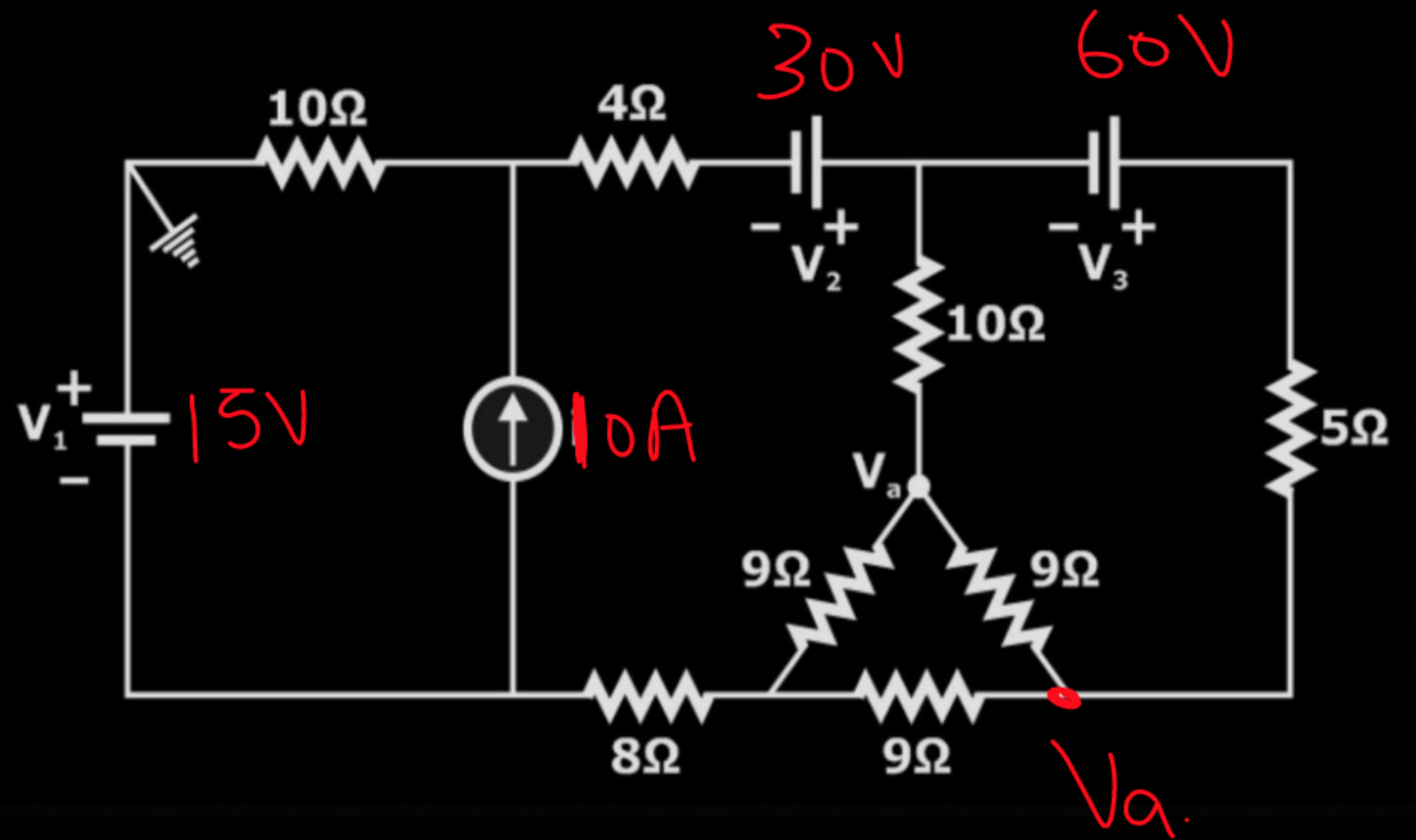

# KIRCHOFF'S VOLTAGE LAW

## KEYPOINTS :

$$\sum \Delta i = 0 \quad \sum \Delta v = 0$$


node/junct'n
mesh/loop

- $\sum \Delta v = 0$ , based on conservation of energy.
- $v = dw/dq \Rightarrow V = dw/dq_v$ .
- Valid for linear – time invariant system.
- Taking ground is not a mandatory condition.
- Always assume an unknown current through the dependent/independent voltage source, before solving the circuit either by KCL or KVL or any other method.
- Mesh analysis = KVL + ohm's law.
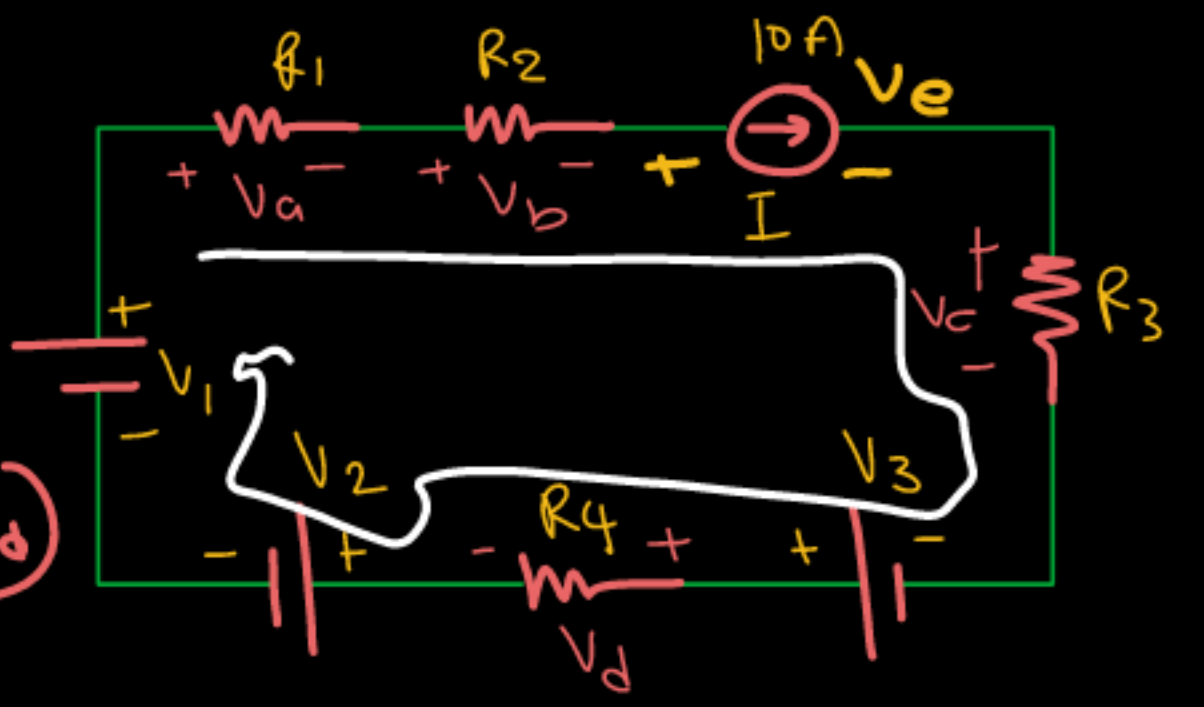
### ⇒ KVL :-

$$-V_1 + V_a + V_b + V_c - V_3 + V_d + V_2 + V_c = 0$$

$$(V_a + V_b + V_c + V_e + V_2 + V_d) = (V_1 + V_3)$$



$$\left[ \sum \Delta v \Big|_{\text{mesh/loop}} = 0 \right]$$




## Steps to apply KVL

1. Find out necessary mesh or loop in the Circuit
2. Assume Current for every ( mesh or loop ) in the (clockwise/anticlockwise) direction.
3. Assume unknown Voltage across every Current source.
4. The (mesh/loop) in which KVL is applying , consider that mesh/loop current is the highest Current of Circuit

## TYPES OF MESH ANALYSIS

1. (Mesh/loop) Current method.
2. Branch Current method

Mesh/Loop

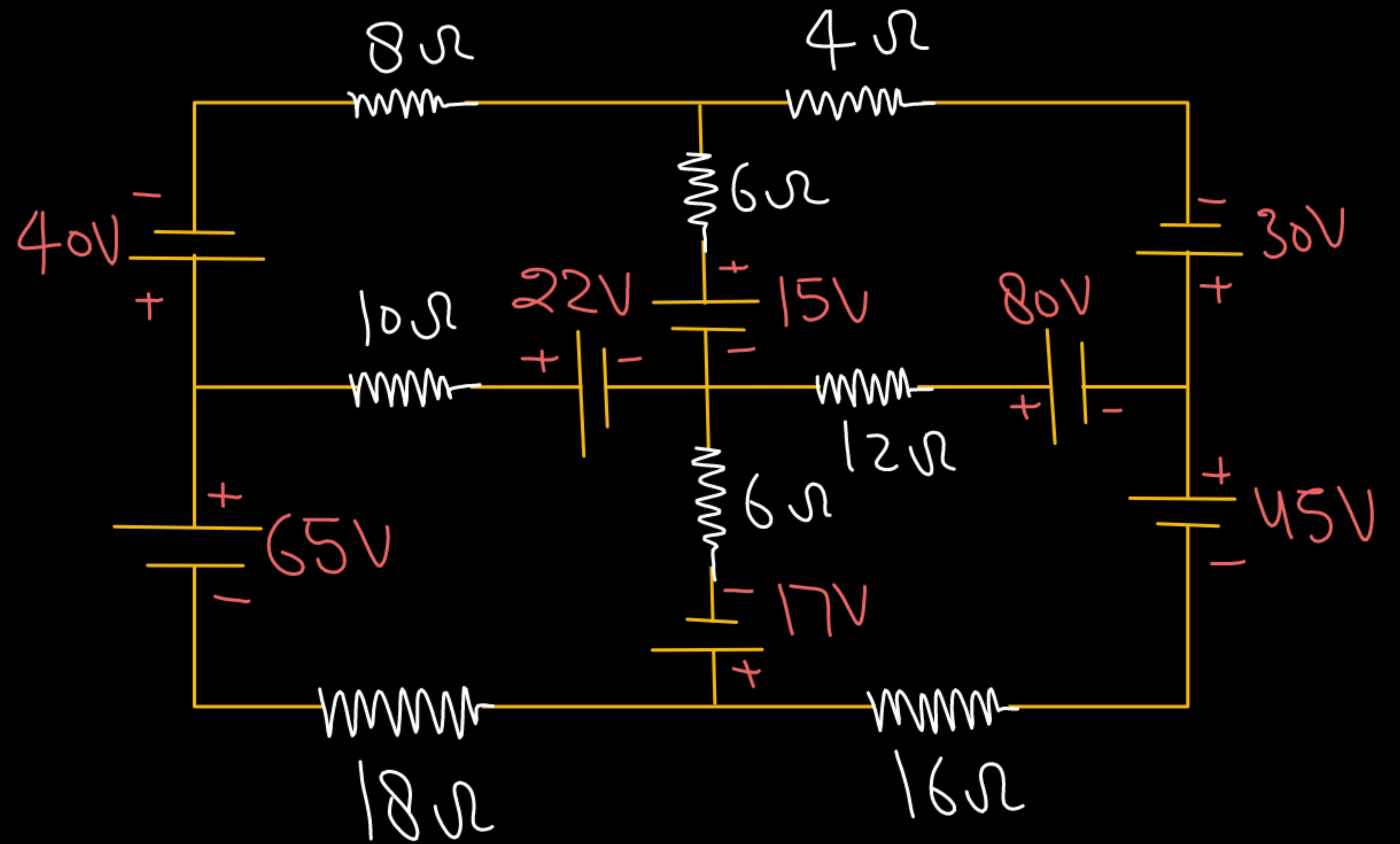



Ex. Write down all possible necessary KVL Equations .

