

WELCOME
TO Adda247

**“STEADY STATE
IS JUST AN
ILLUSION.”**

APP FEATURES



Premium Study Material



Current Affairs



Job Alerts



Daily Quizzes



Subject-wise Quizzes



Magazines



Power Capsule



Notes & Articles



Videos



Download Now

Adda247 APP



SUBSCRIBE NOW

Gate Adda247
YouTube Channel

GATE 2023 RESULT

A
AIR
GATE

Congratulations,
FROM ADDA 247 FAMILY



Inductor's Voltage



From Faraday's law of induction:-

$$\mathcal{E} = N \frac{d\phi}{dt} \cdot \textcircled{I} \quad [L i = N \phi] \textcircled{II}$$

partial diff'n. of eqn:-

$$L \frac{di_L}{dt} + i_L \cancel{\frac{dL}{dt}}^0 = N \frac{d\phi}{dt} + \phi \cancel{\frac{dN}{dt}}^0$$

We know that, L and N both are constant.

$$N \frac{d\phi}{dt} = L \frac{di_L}{dt}$$

$$\left[\mathcal{E} = L \frac{di_L}{dt} \right] = N \frac{d\phi}{dt}$$


V.V. imp

$$V_L(t) = L \frac{di_L}{dt}$$

Inductor's Current

We know that -

Inductor's Vol. is.

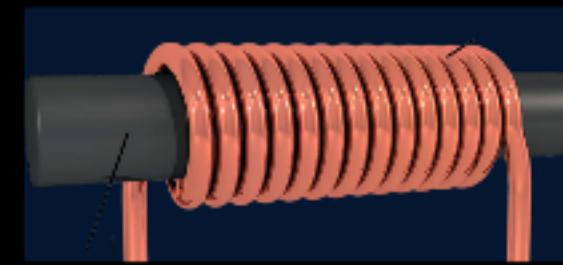

$$V_L(t) = L \frac{di_L}{dt} \quad \textcircled{1}$$

Integ' both side-

$$\int_{-\infty}^t V_L(t) dt = \int_0^{i_L} di_L$$

$$\therefore i_L(t) = \frac{1}{L} \int_{-\infty}^t V_L(t) dt$$

ex. $i_L |_{t=0} = ?$

a) 0A b) -10A

c) 10A d) 25A

ex - At, what time instant,
guaranteed inductor will
be fully charged
i.e. ($i_L = 0 \text{ Amp}$).

a) $t = 0 \text{ sec}$ b) $t = 0^+ \text{ sec}$

c) $t = 5 \text{ sec}$ d) $t = -\infty$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(t) dt$$

$$i_L(t) = \underbrace{\frac{1}{L} \int_{-\infty}^0 v_L(t) dt}_{\text{Initial Value}} + \frac{1}{L} \int_0^t v_L(t) dt$$

$$i_L(t) = (\text{Initial Value}) + \frac{1}{L} \int_0^t v_L(t) dt$$

Inductor equivalent circuit in freq. domain :-


Inductor's Vol. eqn \Rightarrow

$$V_L = L \frac{di_L(t)}{dt} \quad \textcircled{1}$$

Take Lap. transm of eqn \textcircled{1}


$$V_L(s) = L \{ s i_s - i_L^0 \}$$

$$\left\{ V_L(s) = s L i_L(s) - L i_L^0 \right\} \Rightarrow |C| V_L \underline{\text{eqn}}$$

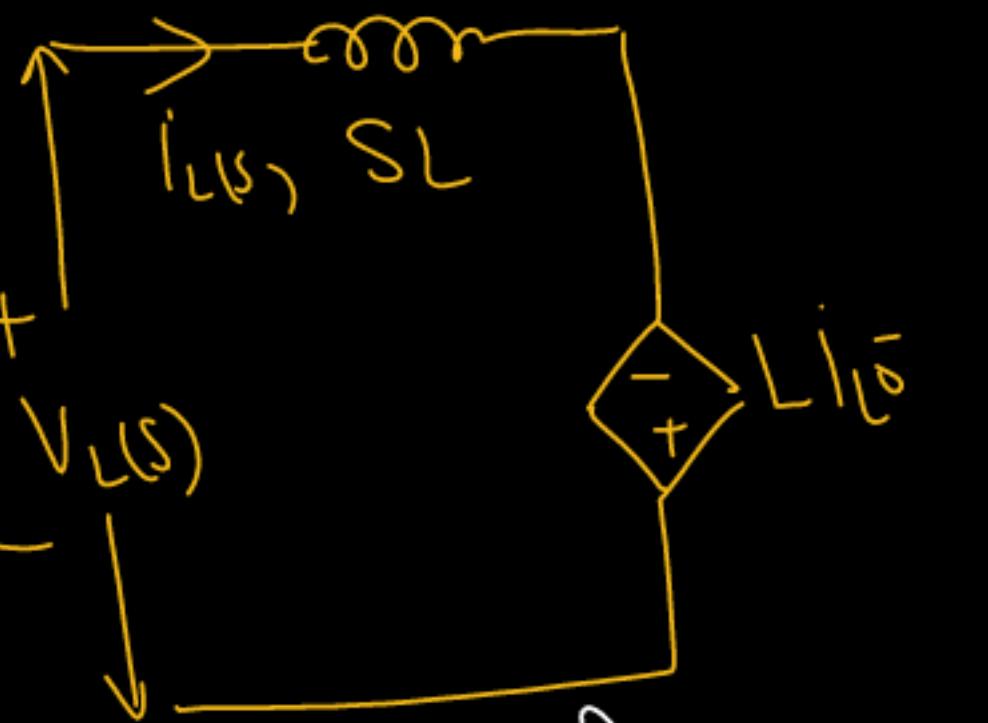

Inductor ckt in freq. domain.

→ From Inducto v Vol.

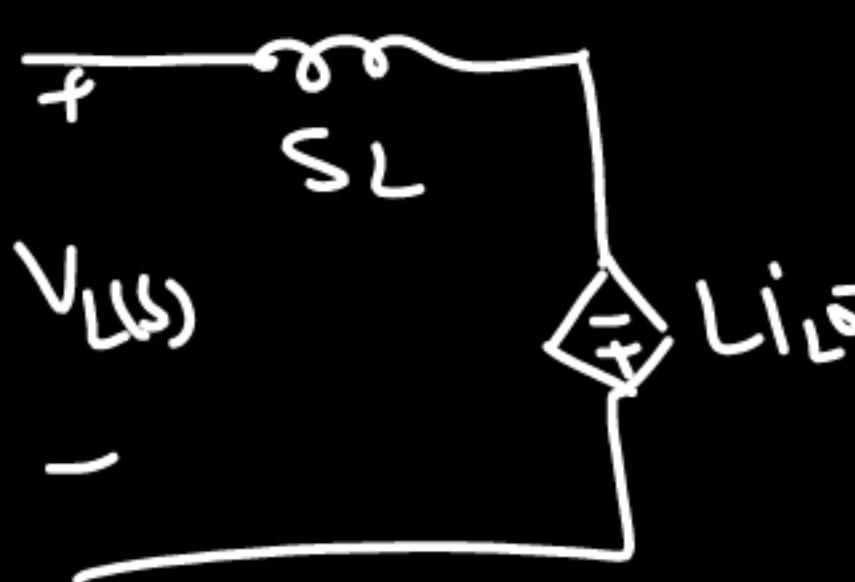

$$\rightarrow V_L(s) = L(i_L(s) - i_L^0).$$

$$V_L(s) = SLi_L(s) - Li_L^0$$

$$SLi_L(s) = V_L(s) + Li_L^0$$

$$\therefore i_L(s) = \frac{V_L(s)}{SL} + \frac{i_L^0}{S}. \quad \underline{\text{K (L eqn)}}$$



Inductor's ckt in freq. domain.

Time constant



* At low freq., Inductor
will not introduce
any cap. effect.



Inductive coil

⇒ we know that, standard transfer function is -

$$T.F = \frac{K(s+z_1)(s+z_2)\dots}{s^n(s+p_1)(s+p_2)\dots}$$

⇒ T.F., in time constant form.

$$T.F = \frac{K \left(\frac{s}{z_1} + 1 \right) \left(\frac{s}{z_2} + 1 \right) \dots}{s^n \left(\frac{s}{p_1} + 1 \right) \left(\frac{s}{p_2} + 1 \right) \dots}$$

$$T.F = \frac{K (s z_1 + 1) (s z_2 + 1) \dots}{s^n (s p_1 + 1) (s p_2 + 1) \dots}$$


Standard T.F. or Natural time constant
form of T.F.

⇒ Natural time constant (N.T.C.) is always a
(+) and non zero value.

⇒ N.T.C. will decide transient response of sys.

time constant :-

$$\tau = L/R.$$

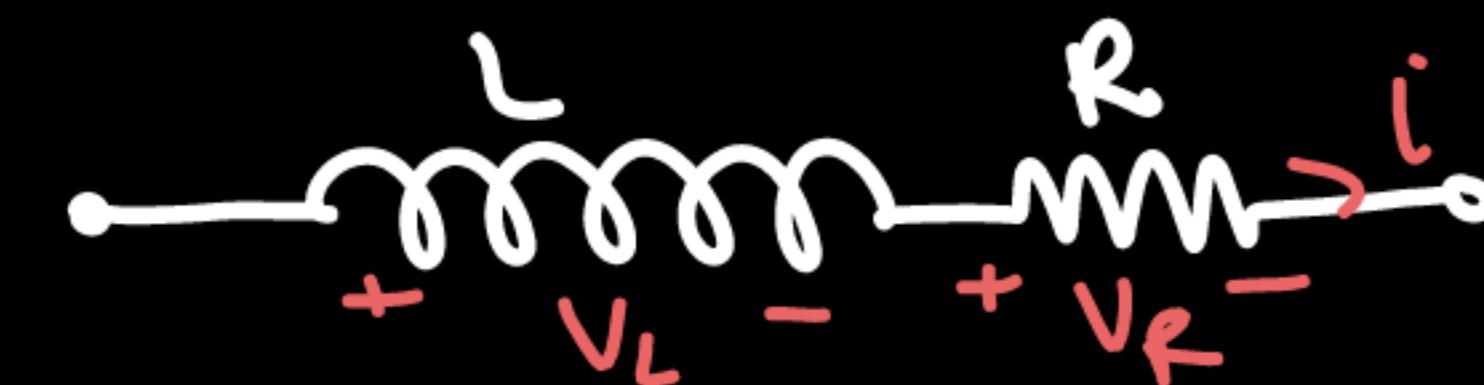

Inductive coil

$$\tau = \frac{L}{R} \left(\frac{V}{A} \right) \text{ sec}$$

$$V_R = iR \quad V_L = L \frac{di_L}{dt}$$

$$R = \left(\frac{V}{A} \right) \quad \left(\frac{V}{A} \right) \text{ sec} = L.$$

$$\boxed{\tau = \frac{L}{R} \text{ sec}}$$

H.T.C.



Ex- Draw the complete resp. of current, for the given circuit.

also determine M.T.C. of the circuit.

$\tau \Rightarrow$ it is mainly defined for first order system.

$$\Rightarrow \tau = \frac{L_{\text{ext}}}{R_{\text{ext}}} \quad ; \quad \text{Reft Always measured across the load.}$$
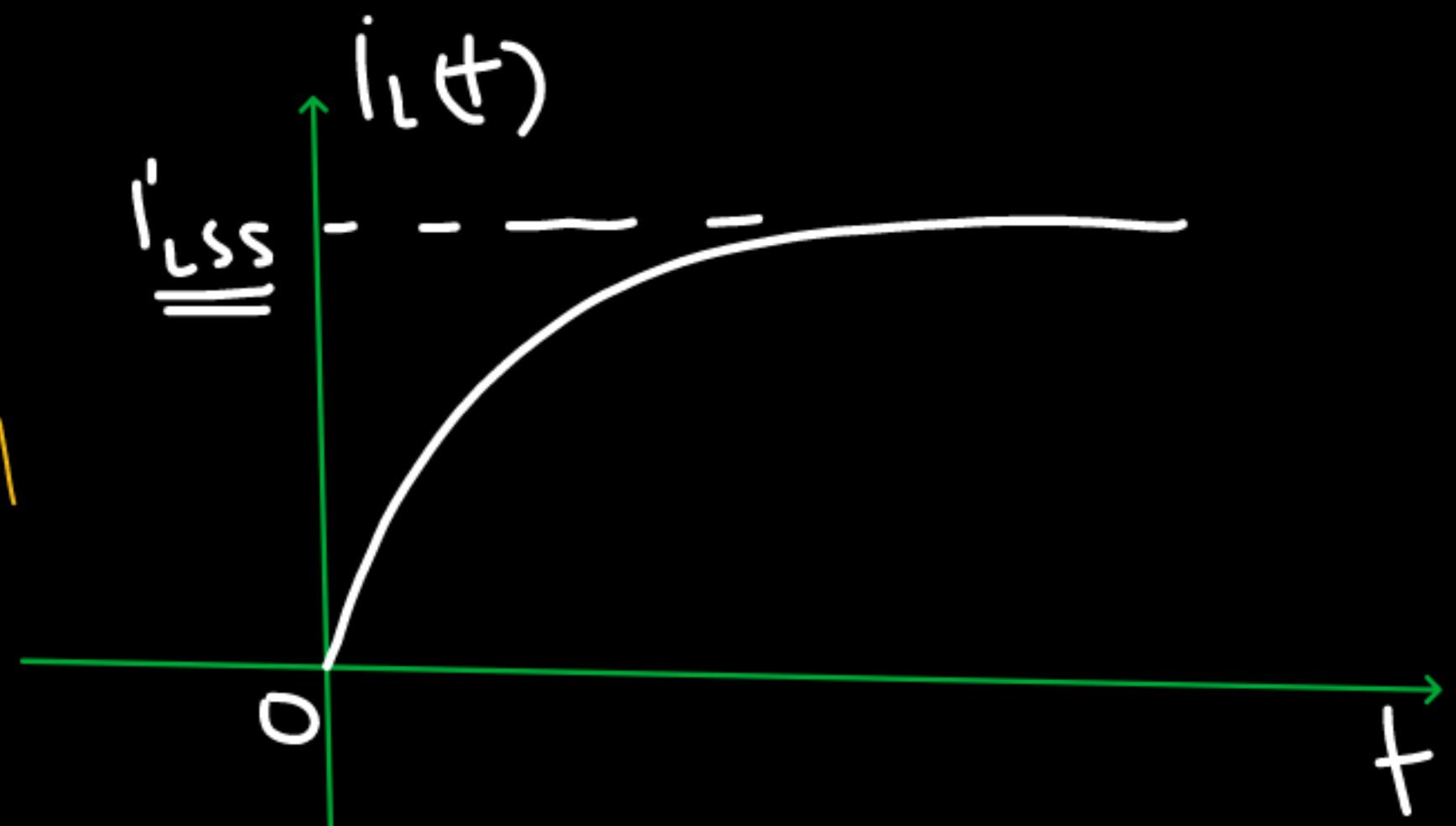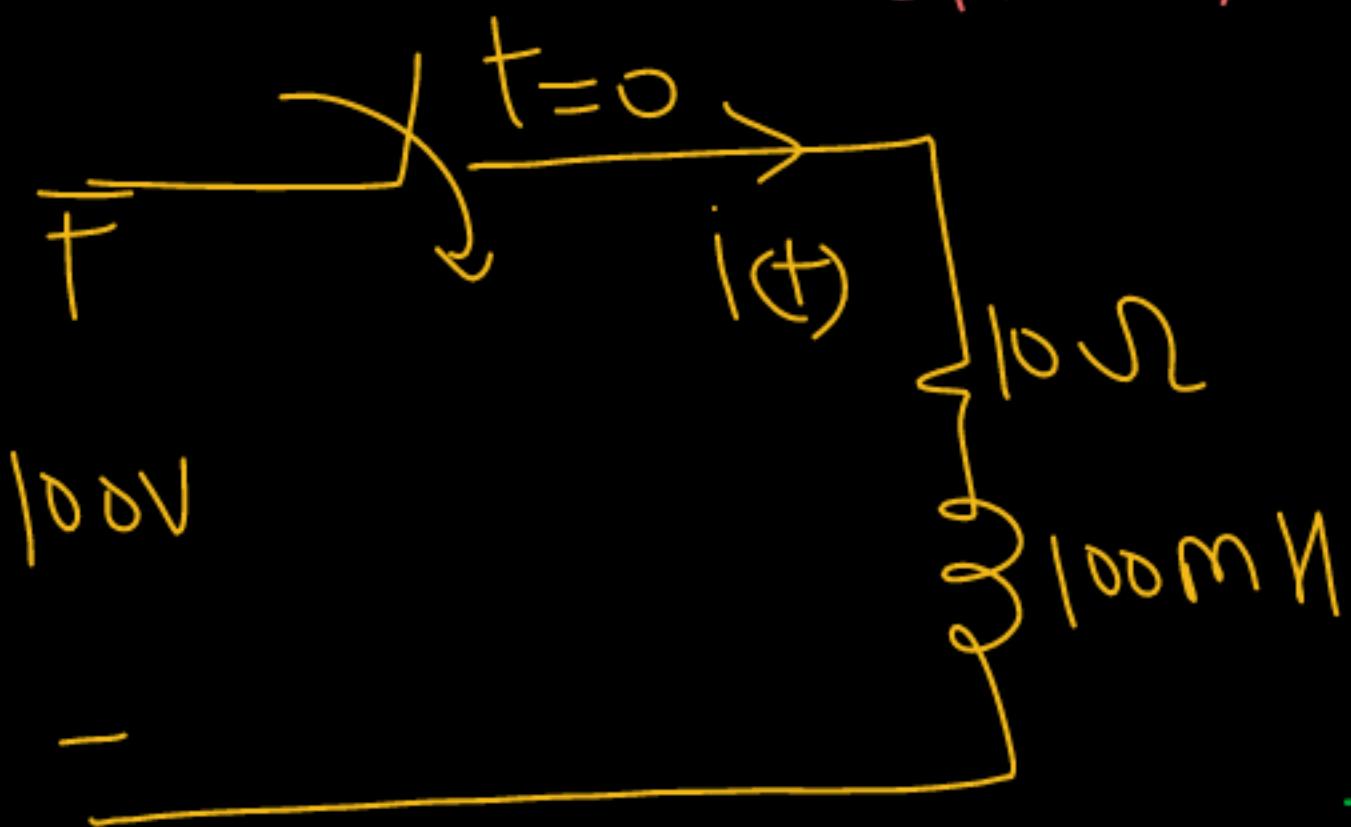
$$\tau = \frac{L}{R} = \frac{100m}{10} = \underline{10 \text{ msec}}$$




First order System with pure Inductive load DC excitation

Let, $R=0$ of ckt. (min)
and inductor is ideal.
and -

- ① $V_s(t) = 10\delta(t)$
- ② $V_s(t) = 10u(t)$
- ③ $V_s = 10\sin t$
- ④ $V_s(t) = 0V$. Draw $i_L(t)$ resp. for all cases.

case ① $V_s(t) = \delta(t)$

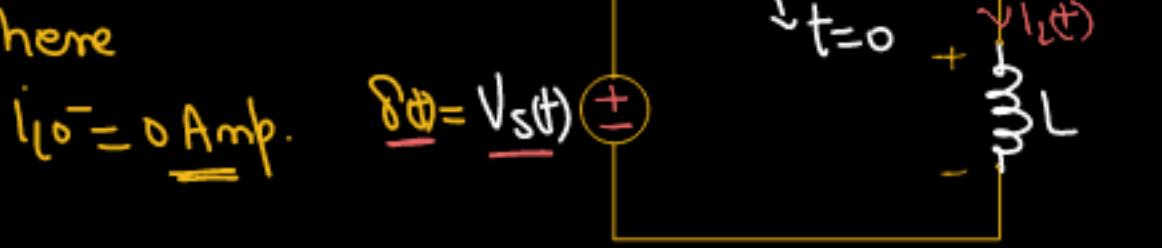


By KVL - ckt in freq. domain.

$$I = SL \cdot I_s. \quad i_L(s) = \frac{1}{L} \cdot \frac{1}{s}$$

Take inv. lap. transf.
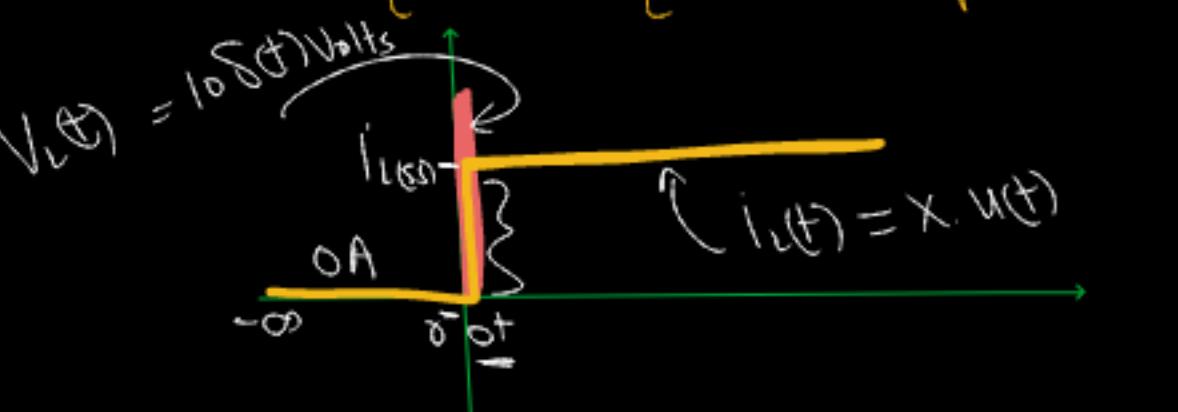
$$i_L(t) = \frac{1}{L} u(t) = \frac{1}{L} ; + > 0 \text{ Amp.}$$




\Rightarrow inductor current comes in to S.S. at $\geq t=0$
if we applied an impulsive vol across inductor

$i_{L0} \neq i_{L0^+}$

$$\textcircled{1} \quad V_S(t) = \underline{\underline{10 u(t)}}$$


circuit in freq. domain: $V_S(t)$
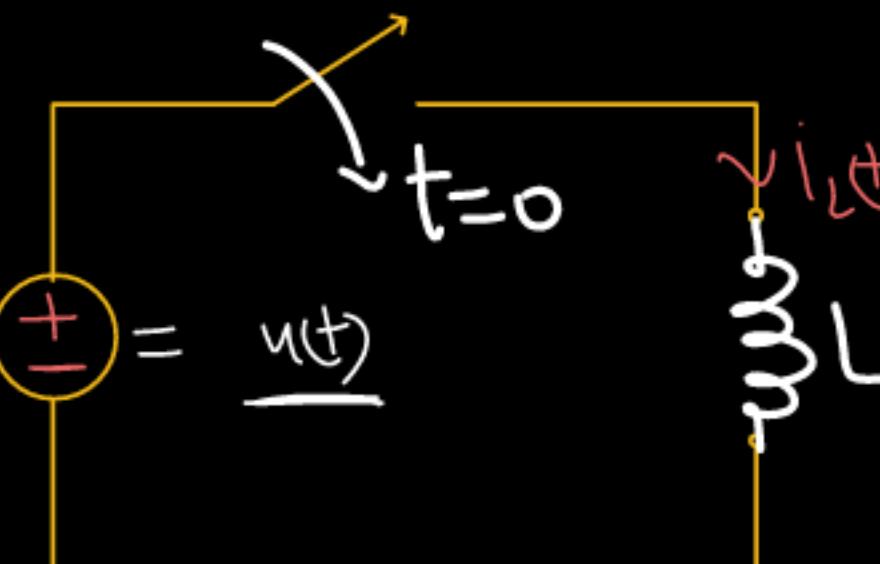
$$\underline{i_L} = \underline{0 \text{ Amp}}$$




$$\frac{1}{s} = sL \cdot i_L(s)$$
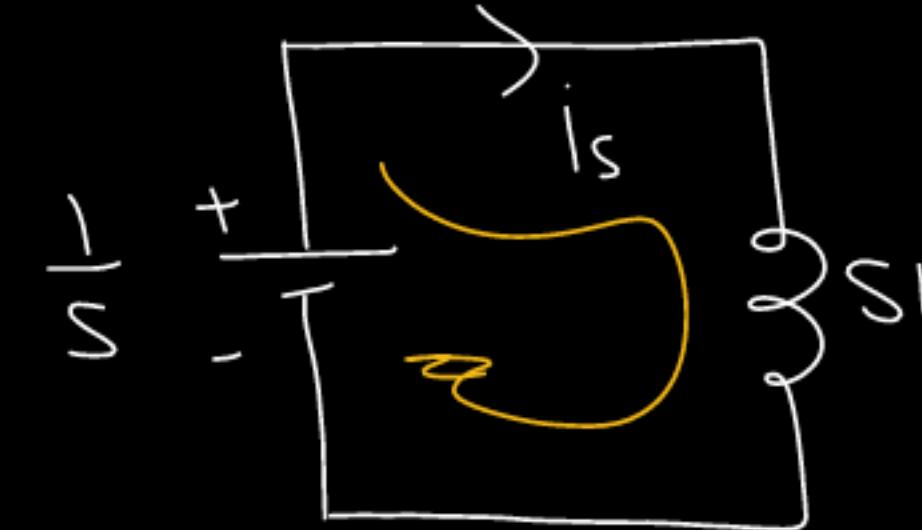
$$\therefore i_L(s) = \frac{1}{L} \cdot \frac{1}{s^2}$$




Take inv. Lap. transf.
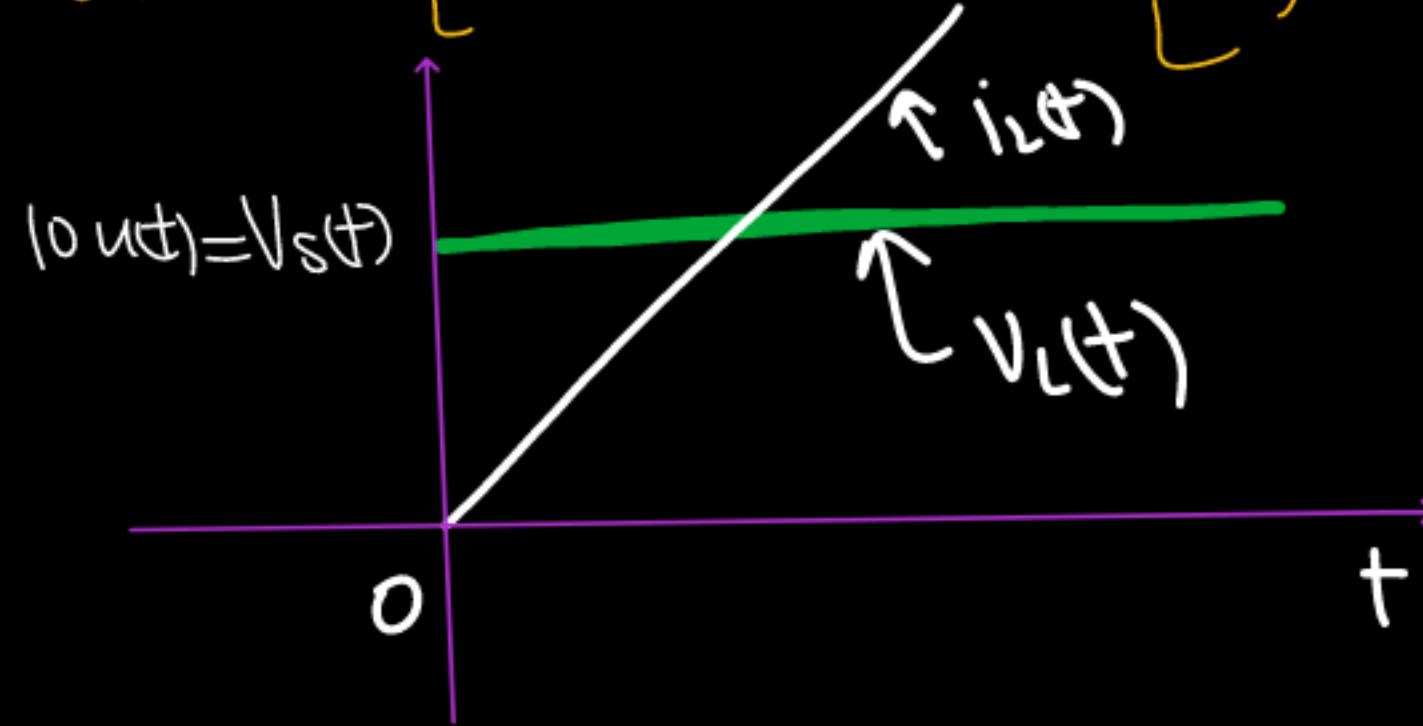
$$i_L(t) = \frac{1}{L} \cdot t + u(t) = \frac{t}{L}; t \geq 0.$$




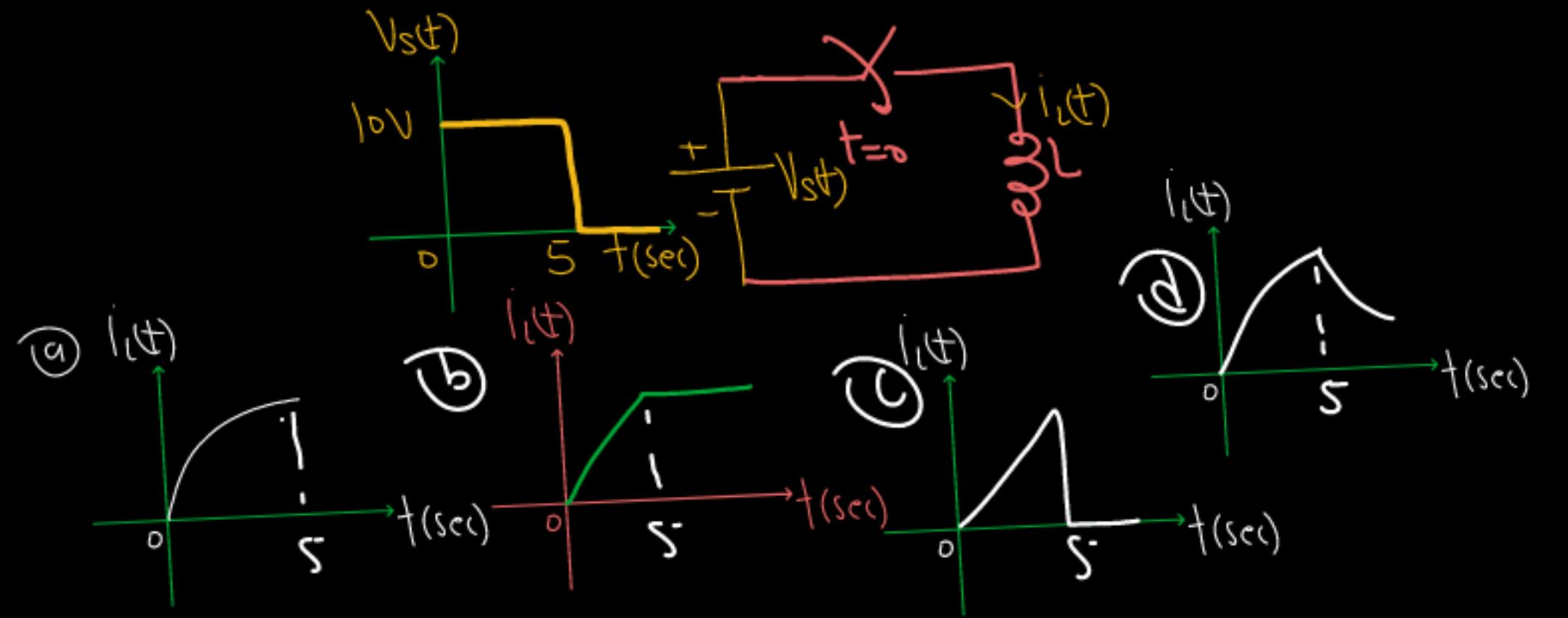Ex:- The response of inductor's current will be, for given ckt.




Soln :-

case ①
0 - 5 sec

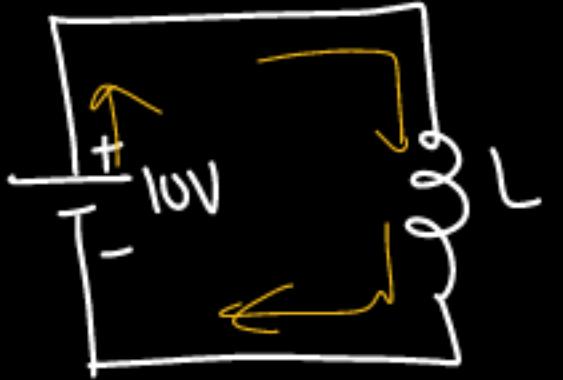


case ② $t \geq 5 \text{ sec}$

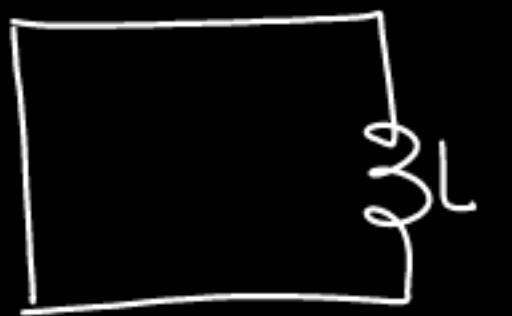


$$I_{L0} = 0 \text{ A}$$

$$V_L = L \frac{di_L}{dt}$$

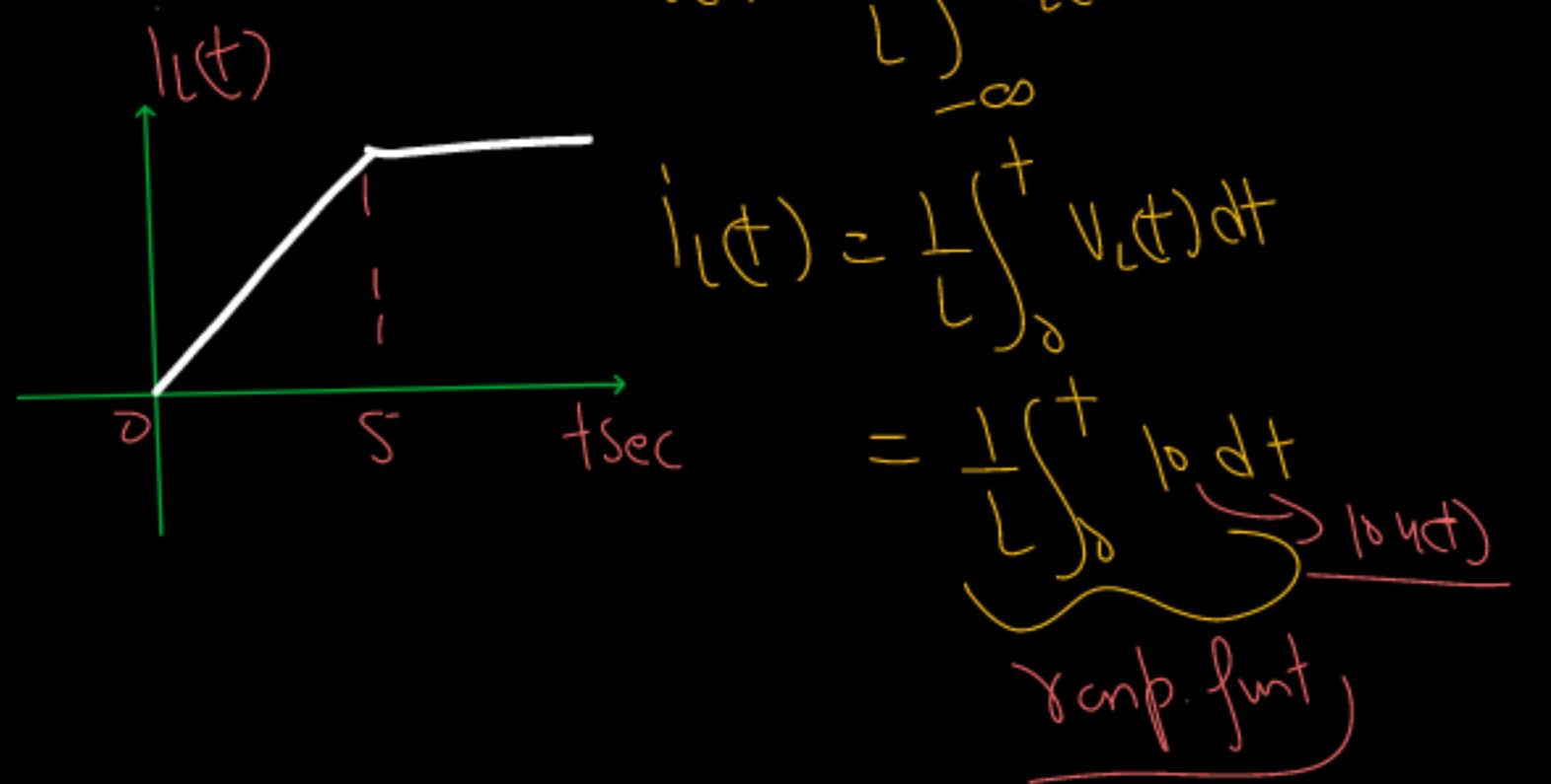

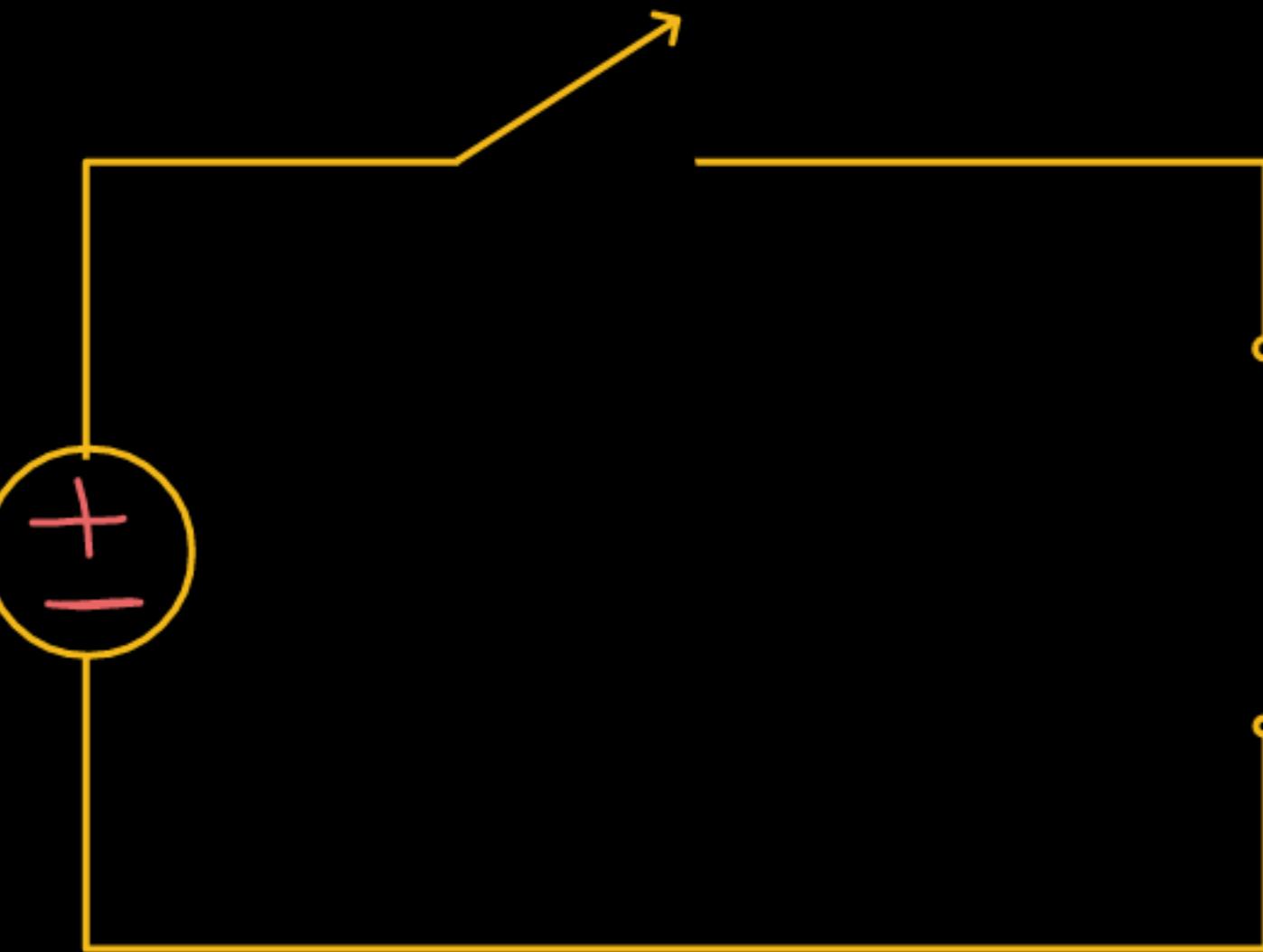First order System with RL load and DC excitation



First order Source free System with RL load and DC excitation

