

WELCOME  
TO **Adda247**



**Download Now**  
**Adda247 APP**

## APP FEATURES



Premium Study Material



Current Affairs



Job Alerts



Daily Quizzes



Subject-wise Quizzes



Magazines



Power Capsule



Notes & Articles




Videos



# First order RL System with DC excitation

Inductor is initially uncharged.

$$i_{L0} = 0 \text{ Amp}$$

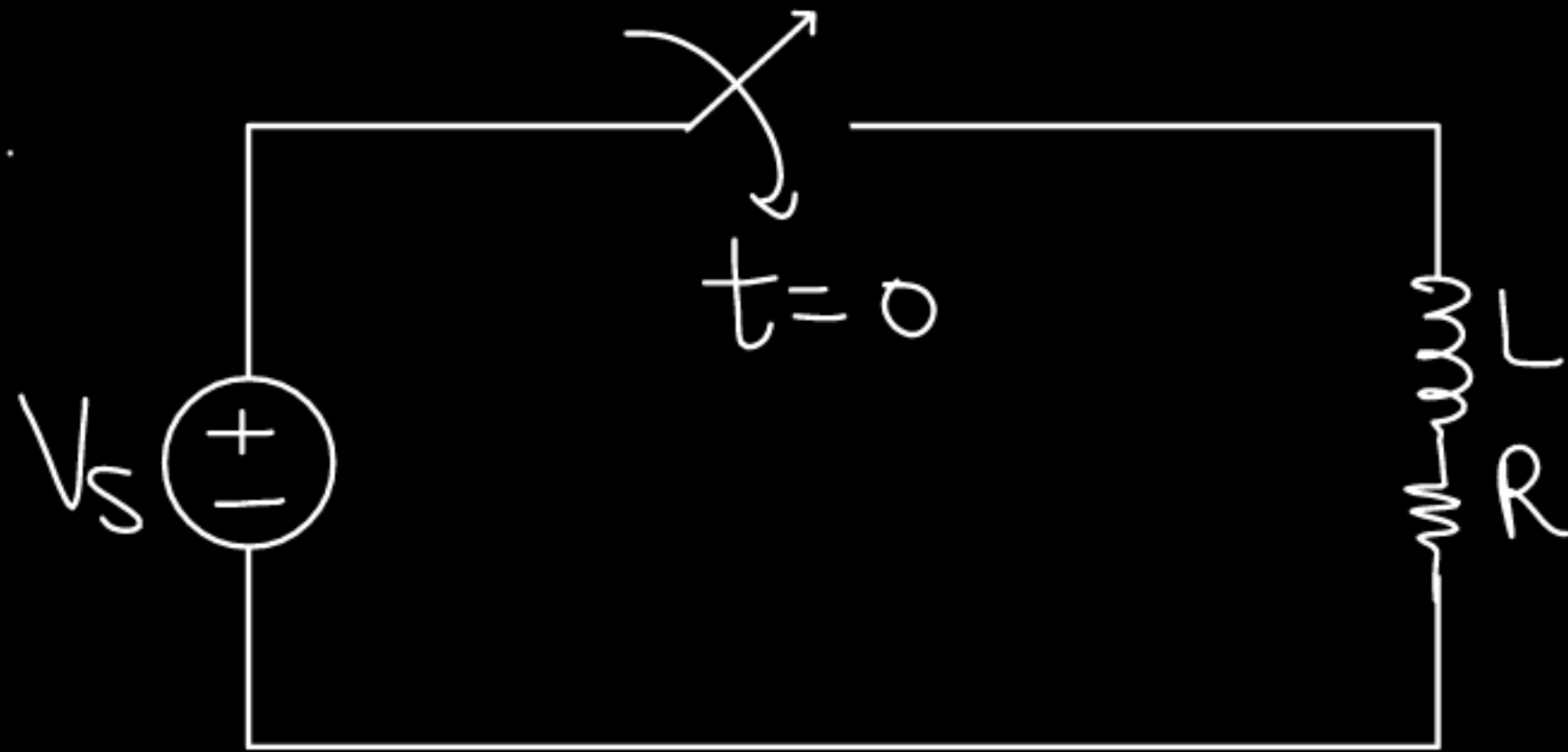


Task - to Draw inductor current, inductor Vol and resist. Vol.

Supply Vol  $\Rightarrow V_s \Rightarrow$  Pure D.C. Vol.;  $t \geq 0$

$$\text{Supply Vol.} = V_s u(t)$$

$$\text{lap. transf}^m = \frac{V_s}{s}$$

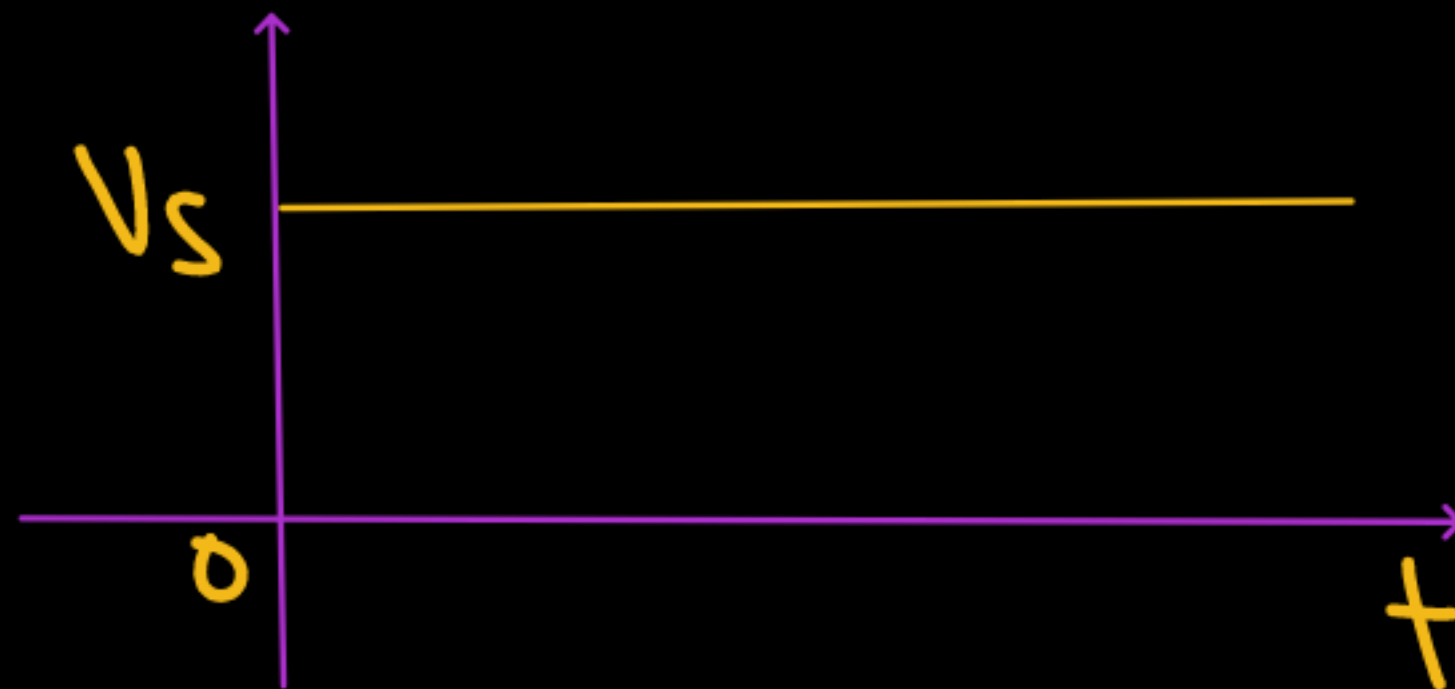

Analysis of circuit in time domain:-


$t \geq 0$  ; SW  $\rightarrow$  closed.

By KVL  $\Rightarrow$

$$V_s = V_L(t) + V_R(t) \text{ (I)}$$

from eq<sup>ns</sup> (I), (II) and (III)

$$V_s = R i(t) + L \frac{di(t)}{dt}$$

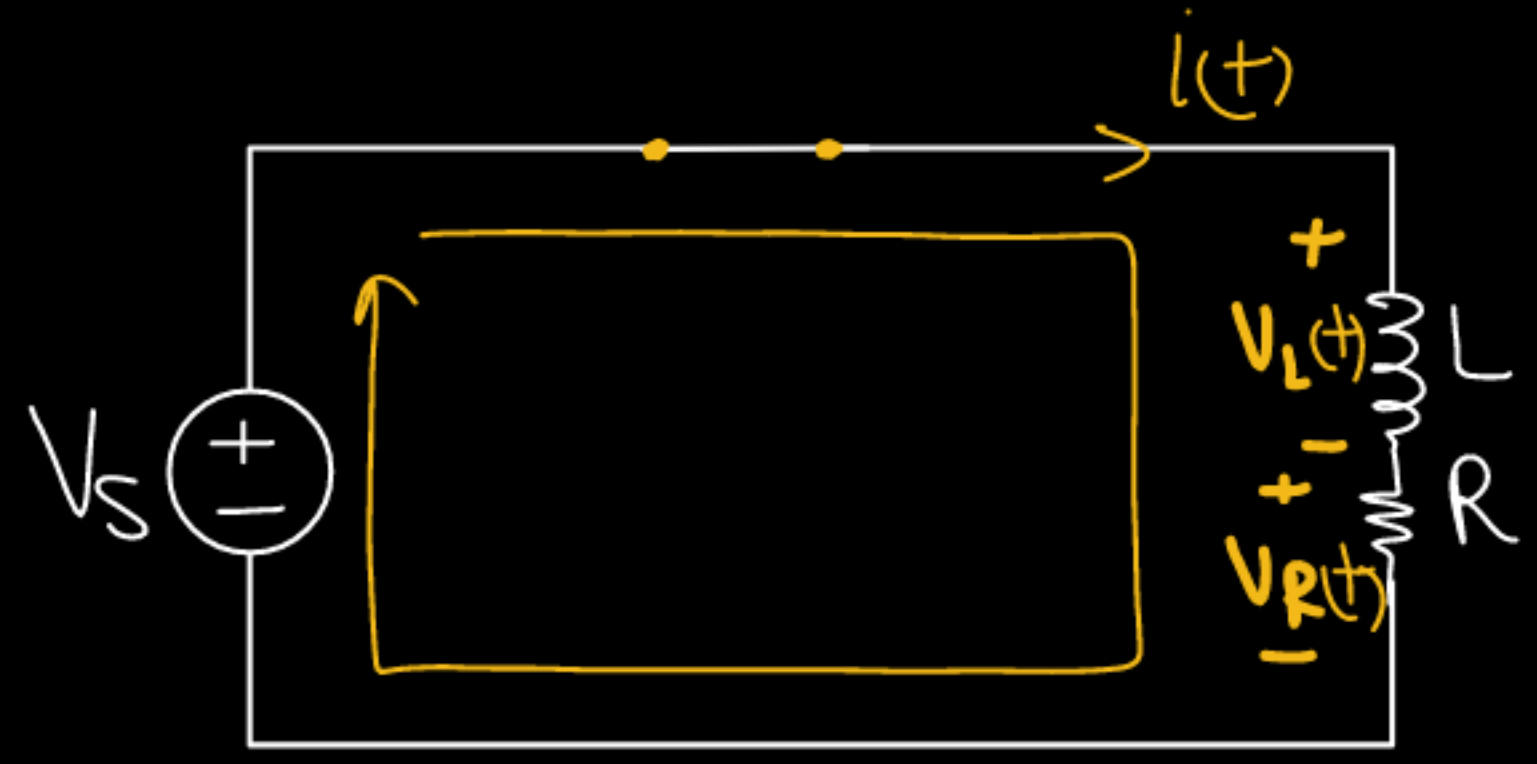

By ohm's law.


$$V_R(t) = R i(t) \text{ (II)}$$

and  $V_L(t) = L \frac{di(t)}{dt}$  by F.L.O.I. (III)

Analysis of circuit:-

$t \geq 0$

By KVL:-

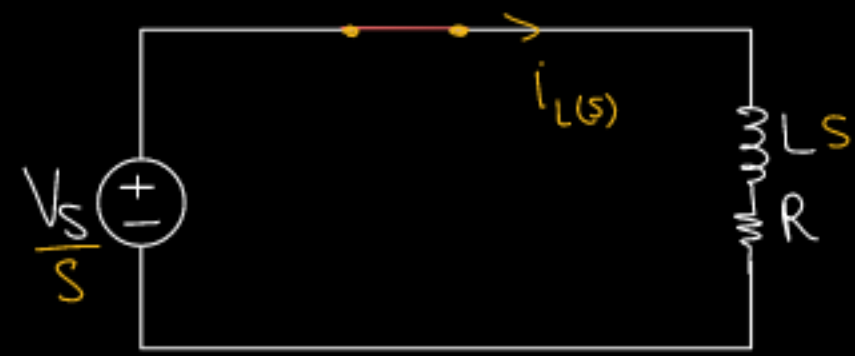

$$\frac{V_s}{s} = i_L(s)(R + sL)$$

$$\frac{V_s}{s} = i_L(s) \left[ s + \frac{R}{L} \right] L$$

$$i_L(s) = \frac{V_s}{L} \left[ \frac{1}{s(s + R/L)} \right] \quad \text{Break by partial fraction.}$$


$$i_L(s) = \frac{V_s}{R} \left[ \frac{1}{s} - \frac{1}{(s + R/L)} \right] \quad \text{; take inverse Lap. transf.}$$

$$i_L(t) = \frac{V_s}{R} (1 - e^{-R/L t})$$

$$i_L(t) = \frac{V_s}{R} (1 - e^{-t/\tau}) \quad \text{; where } \tau = \frac{L}{R} \text{ Secs.}$$

$$V_L(t) = L \frac{di_L(t)}{dt}$$


$$V_L(t) = V_s \cdot e^{-t/\tau}$$

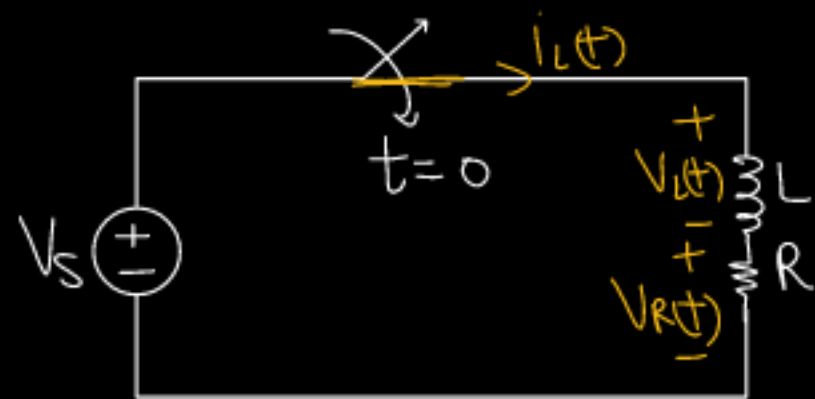

$$\Rightarrow V_R(t) = R i_L(t) = R \left[ \frac{V_s}{R} (1 - e^{-t/\tau}) \right]$$

$$V_R(t) = V_s (1 - e^{-t/\tau})$$



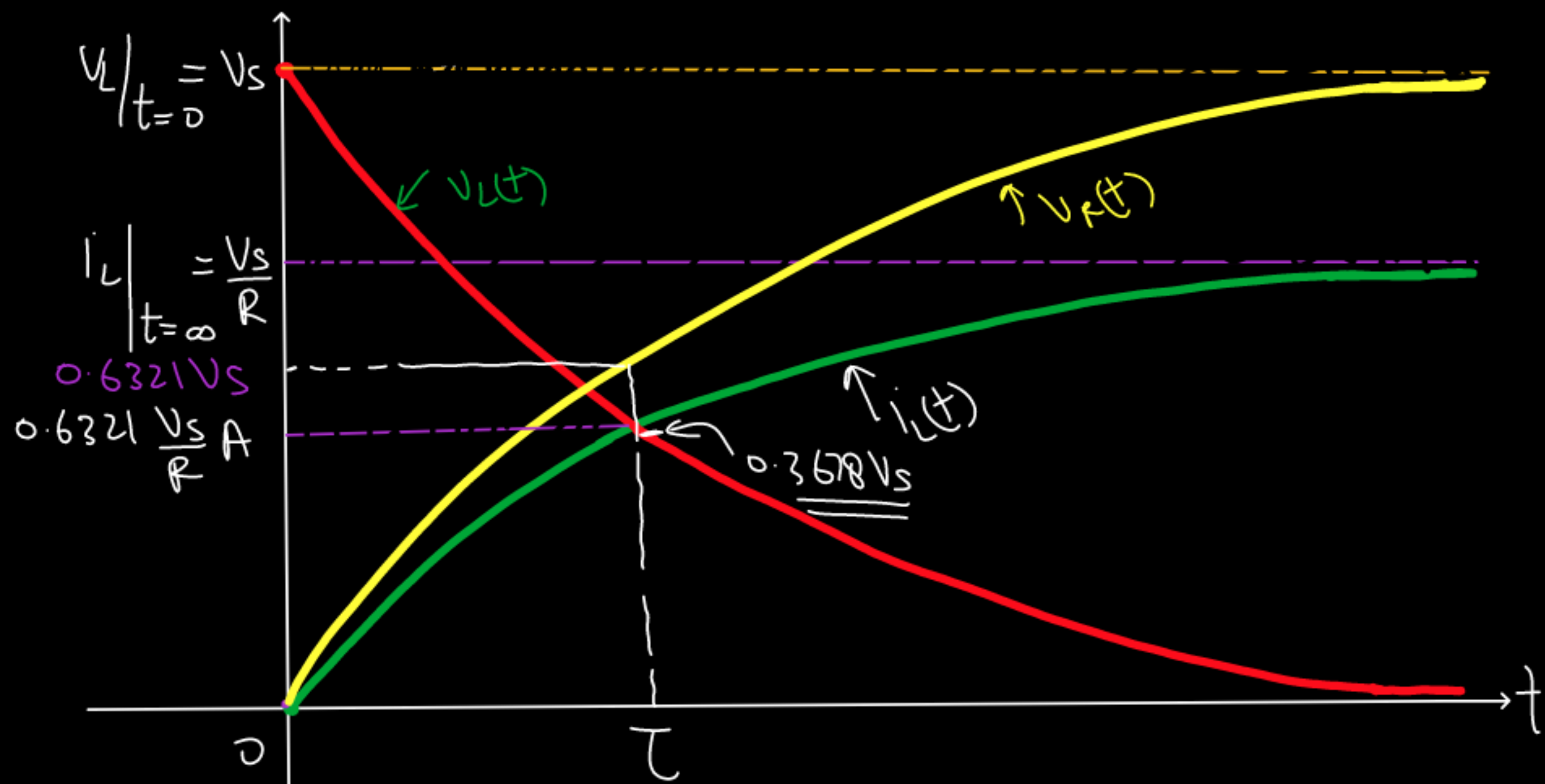


At  $t = \tau$ ,  $i_L = (63.1\% i_{L(ss)})$

$t = \tau$ ,  $V_R = (63.1\%) V_s$

$$i_L(t) = \frac{V_s}{R} (1 - e^{-t/\tau})$$

$$V_s = V_R(t) + V_L(t)$$

$$i_L|_{t=\tau} = \frac{V_s}{R} (1 - e^{-1}) = 0.6321 \frac{V_s}{R}$$

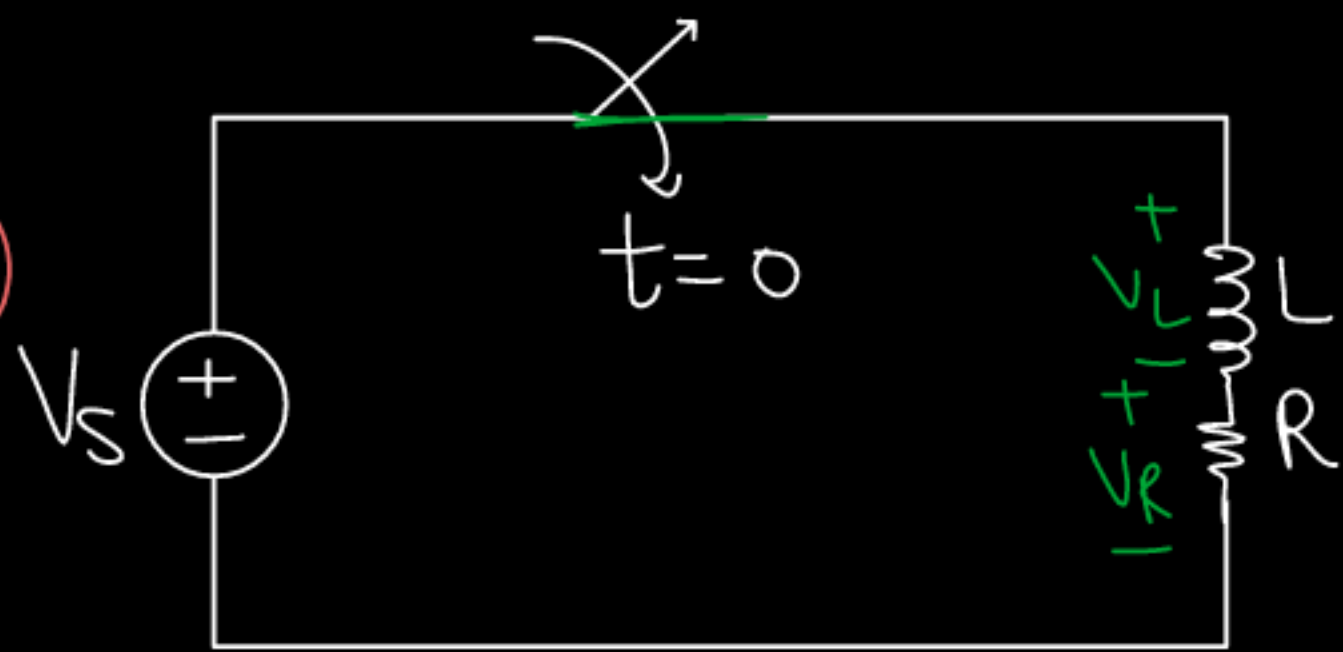

Transfer function :-

$$\frac{V_L(s)}{V_S(s)} = \frac{SL}{(R+SL)}$$


$$= \frac{SL}{[(S+R/L)L]}$$

$$= \frac{S}{\left[\left(\frac{S}{R/L} + 1\right)R/L\right]}$$

$$= \frac{s(L/R)}{\left[\frac{L}{R}s + 1\right]} = \frac{SK}{[s\tau + 1]} ; \text{N.T.C.T.F.}$$

$$\frac{V_R(s)}{V_S(s)} = \frac{R}{(SL+R)} = \frac{(R/L)}{(S+R/L)} = \frac{(R/L)}{\left[\frac{S}{(R/L)} + 1\right]R/L} = \frac{1}{(s\tau + 1)}$$
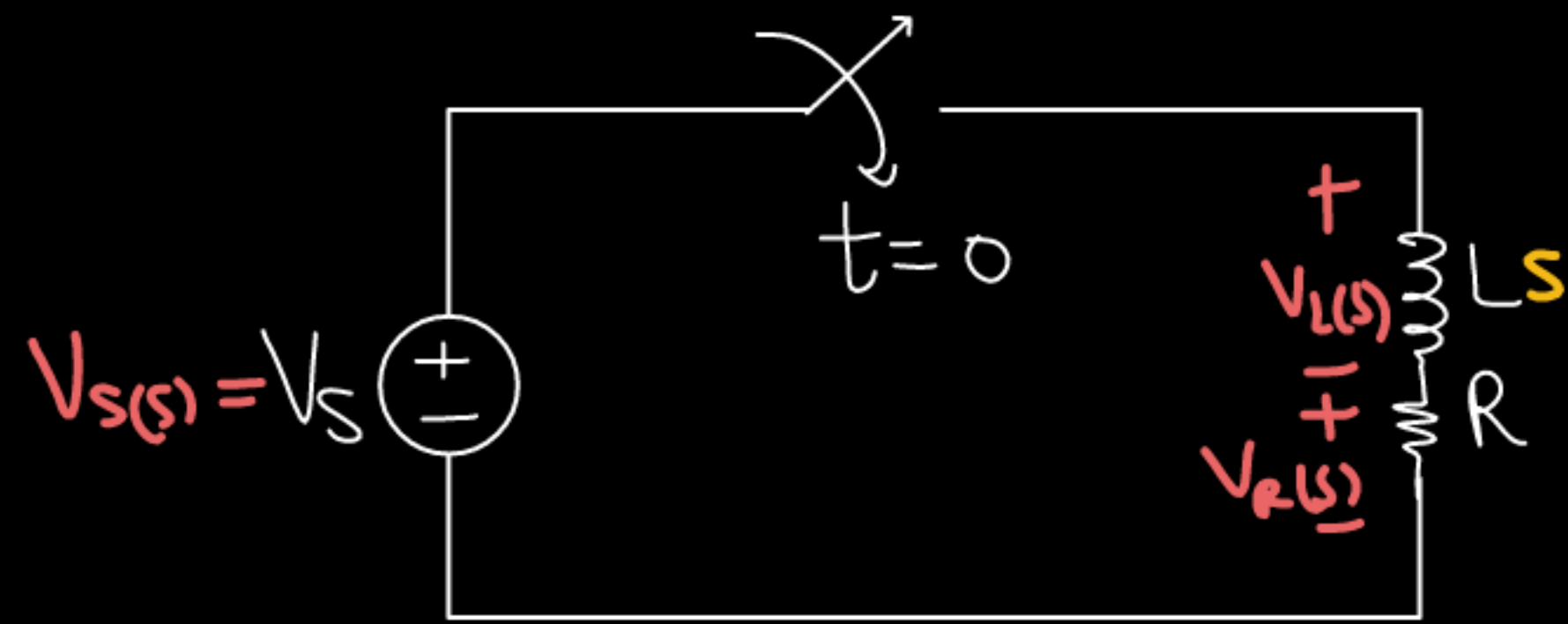
$$\frac{V_S(s)}{I_S(s)} = (R+SL) = (S+R/L)L$$



\* \$V\_S \to\$ unknown D.C. Vol.

inductor current  $\Rightarrow$

$$i_L(t) = \frac{V_s}{R} (1 - e^{-R/Lt})$$

$$i_L(t) = i_L(\infty) (1 - e^{-t/\tau})$$

$$i_L(t) = i_{L(ss)} (1 - e^{-t/\tau})$$

inductor's Vol:  $\Rightarrow$

$$V_L(t) = V_s \cdot e^{-t/\tau}$$

$$V_L(t) = V_{L0} e^{-t/\tau}$$

$$V_L(t) = V_L|_{\text{initial}} \cdot e^{-t/\tau}$$