

Today Topic

Questions session

WELCOME  
TO **Adda247**



**SUBSCRIBE NOW**

**Gate Adda247**  
YouTube Channel

# GATE 2023 RESULT



**Congratulations**  
**FROM ADDA 247 FAMILY**

<b>AIR</b> <b>03</b> <b>ME</b> KUSHAGRA KUMAR	<b>AIR</b> <b>05</b> <b>PI</b> HARSHIT KUMAR	<b>AIR</b> <b>07</b> <b>ME</b> RUSHI PRADIPKUMAR KARTI	<b>AIR</b> <b>11</b> <b>CE</b> VINEET JAIN	<b>AIR</b> <b>30</b> <b>CE</b> RITIK BANSAL	<b>AIR</b> <b>36</b> <b>ECE</b> SUMIT KUMAR
<b>AIR</b> <b>64</b> <b>CE</b> UTKARSH MISHRA	<b>AIR</b> <b>71</b> <b>EE</b> SOMESH SANTAY PANNAR	<b>AIR</b> <b>76</b> <b>CE</b> DIPANKAR DAS	<b>AIR</b> <b>87</b> <b>EC</b> SURAJIT RABI DAS	<b>AIR</b> <b>91</b> <b>EE</b> RESHADEH GOPTA	<b>AIR</b> <b>111</b> <b>ES</b> ANIL GUPTA
<b>AIR</b> <b>130</b> <b>EE</b> SAURAV PATEL	<b>AIR</b> <b>136</b> <b>CE</b> HUPESH SACHIDEVA	<b>AIR</b> <b>200</b> <b>ECE</b> WASIUZZAMA	<b>AIR</b> <b>212</b> <b>IN</b> WASIUZZAMA	<b>AIR</b> <b>217</b> <b>ME</b> VISHAL KUMAR	<b>AIR</b> <b>219</b> <b>ME</b> NITISH KUMAR
<b>AIR</b> <b>258</b>	<b>AIR</b> <b>348</b>	<b>AIR</b> <b>392</b>	<b>AIR</b> <b>403</b>	<b>AIR</b> <b>567</b>	<b>AIR</b> <b>571</b>





**Download Now**  
**Adda247 APP**

# APP FEATURES



**Premium Study Material**



**Current Affairs**



**Job Alerts**



**Daily Quizzes**



**Subject-wise Quizzes**



**Magazines**



**Power Capsule**




**Notes & Articles**



**Videos**
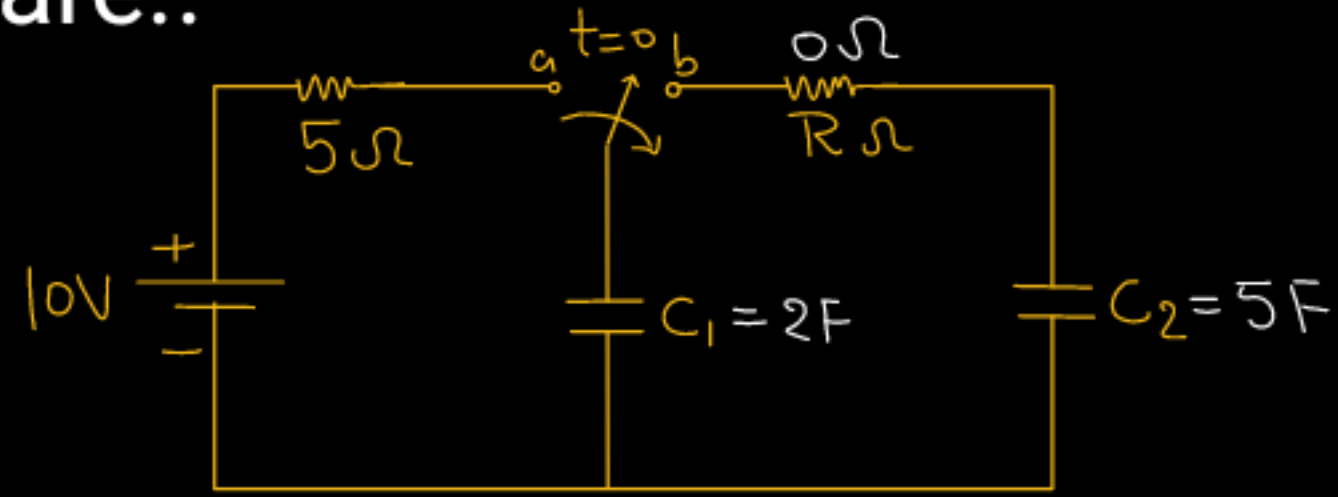
# Ex-1 The Steady State voltage across both Capacitor are..




Solu<sup>n</sup>: Determin initial vol. of both cap.

or ①  $t \leq 0^-$  ;  $-\infty \leq t \leq 0^-$

Switch is connected at point "a".

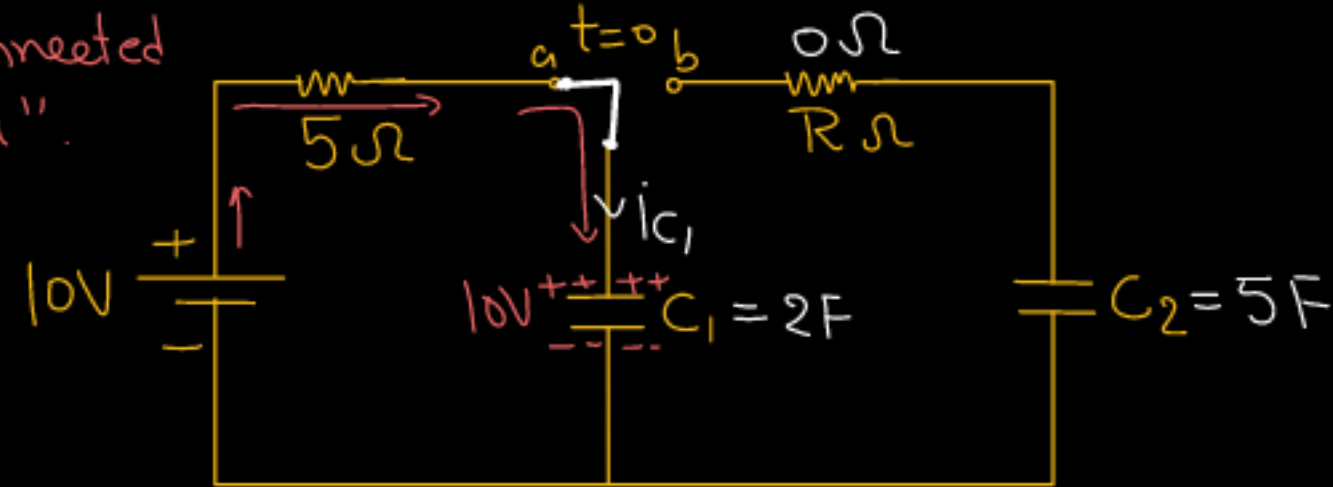\* here, cap-  
C<sub>2</sub> will not charge.




$$V_{C2} = 0V, \quad -\infty \leq t \leq 0^-$$

⇒ cap. C<sub>1</sub> will charge, due to excitation of 10V D.C. Vol. supply.

So, at  $t = 0$ , cap. will reach into S.S. and will maintain 10V.

$$\therefore V_{C1 0} = 10V$$
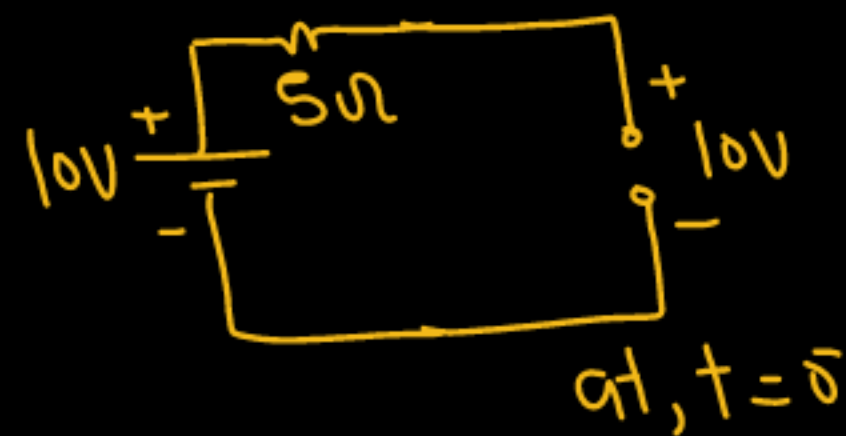
$$\underline{\underline{V_{C2 0} = 0V}}$$



Q2 11  $t \geq 0$

We know that -


$$V_C(t^-) = V_C(t^+);$$

but when cap. current is not impulsive

$\Rightarrow$  Now, switch is connected with point "b"

$$V_{C1}^- = 10V, V_{C2}^- = 0V.$$

ckt in freq. domain.

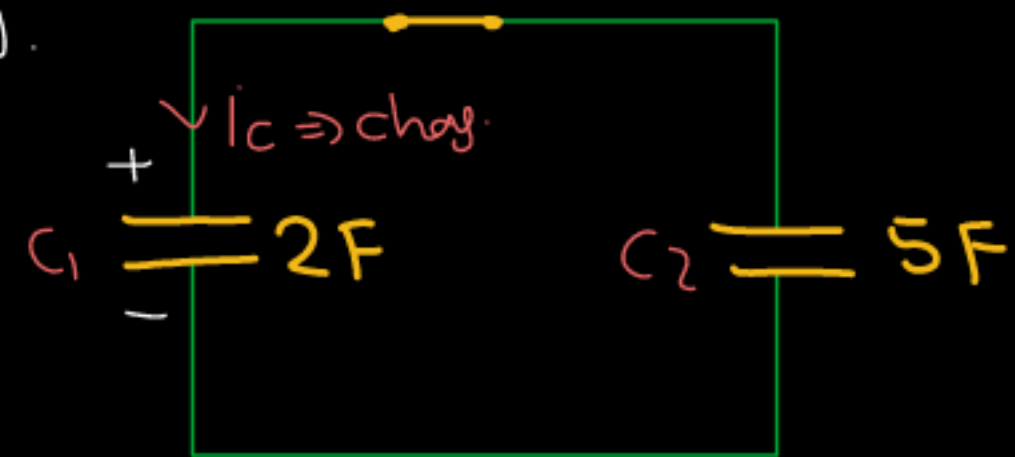


By KVL:-

$$\frac{10}{s} = i_C(s) \left( \frac{1}{2s} + \frac{1}{5s} \right)$$

$$\frac{10}{s} = i_C(s) \left[ \frac{5+2}{10s} \right]$$
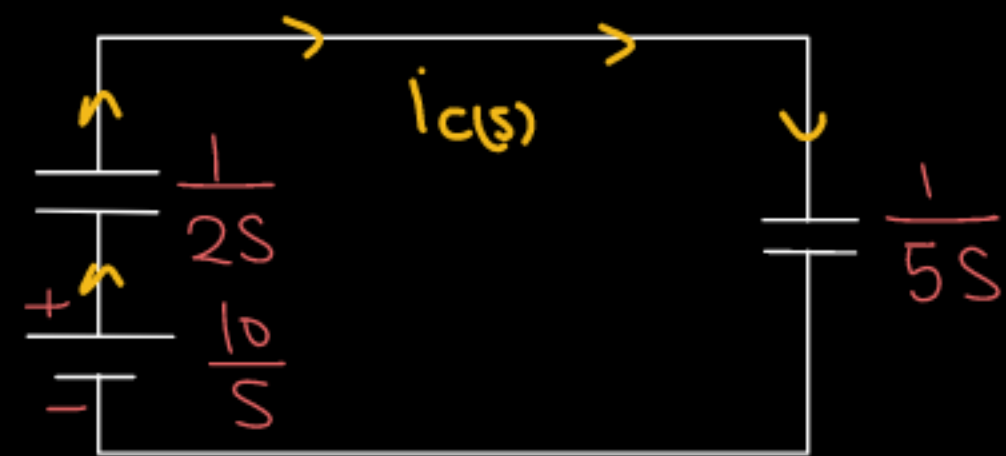
$$\frac{10}{s} = i_C(s) \left[ \frac{0.7}{s} \right]$$



$$i_C(s) = \frac{10}{0.7} = \frac{100}{7} = 14.2857$$

take inv. lap. transfm.

$$i_C(t) = 14.2857 \delta(t)$$

$$i_c(t) = 14.2857 \delta(t) \text{ Amp.}$$

$$V_{C_2} = \frac{1}{C} \int_{-\infty}^t i_c(t) dt$$

$$V_{C_2} = \frac{1}{C_2} \int_0^t i_c(t) dt$$

$$V_{C_2} = \frac{1}{5} \int_0^{t=0^+} 14.2857 \delta(t) dt$$

$$= \left( \frac{14.2857}{5} \right) \left[ \int_0^{0^+} \delta(t) dt = 1 \right]$$

$$= \underline{2.857 \text{ Volts}}$$


$$V_{C_2}^- = 0V \text{ but } V_{C_2}^{0^+} = \underline{2.857 \text{ Volts}} ; t \geq 0$$

$$\left[ V_{C_2}(t) = \underline{2.857 u(t)} \text{ Volts} \right]$$



①  $V_{C_1}(t); t \geq 0$

$i_C(t) = 14.2857 \delta(t) \text{ A}$

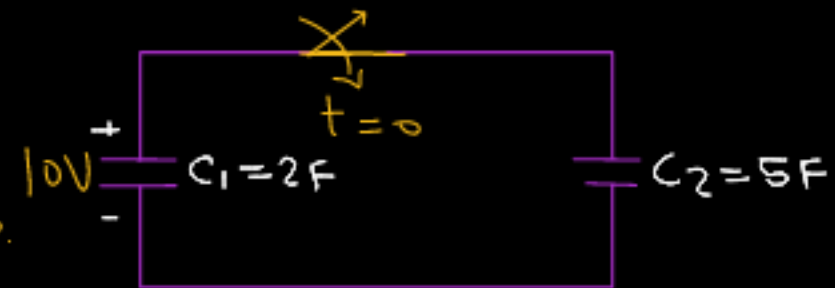

$\Rightarrow$  By KVL  $\Rightarrow V_{C_1}(t) = V_{C_2}(t) = 2.857 u(t)$

$V_{C_1 0^-} = 10V, V_{C_1 0^+} = 2.857V$

method  $\Rightarrow$

$V_{C_1}(t) = \frac{1}{C_1} \int_{-\infty}^t i_C(t) dt \Rightarrow$

$V_{C_1}(t) = \frac{1}{C_1} \int_{-\infty}^{t \leq 0} i_C(t) dt + \frac{1}{C_1} \int_0^{t \geq 0} i_C(t) dt$

$= \frac{V_{C_1}^-}{C_1} + \frac{1}{C_1} \int_0^t -14.2857 \delta(t) dt$



$= 10 + \frac{1}{2} (-14.2857) \left[ \int_0^{0^+} \delta(t) dt = 1 \right]$

$V_{C_1}(t) = 2.857 u(t)$

$\Rightarrow V_{C_1 0^-} = 10V, V_{C_1 0^+} = 2.857V.$   
 $V_{C_2 0^-} = 0V, V_{C_2 0^+} = 2.857V$


$\left. \begin{array}{l} \text{b/c} \\ \text{cap. is} \\ \text{passive} \\ \text{impulsive} \\ \text{current.} \end{array} \right\}$

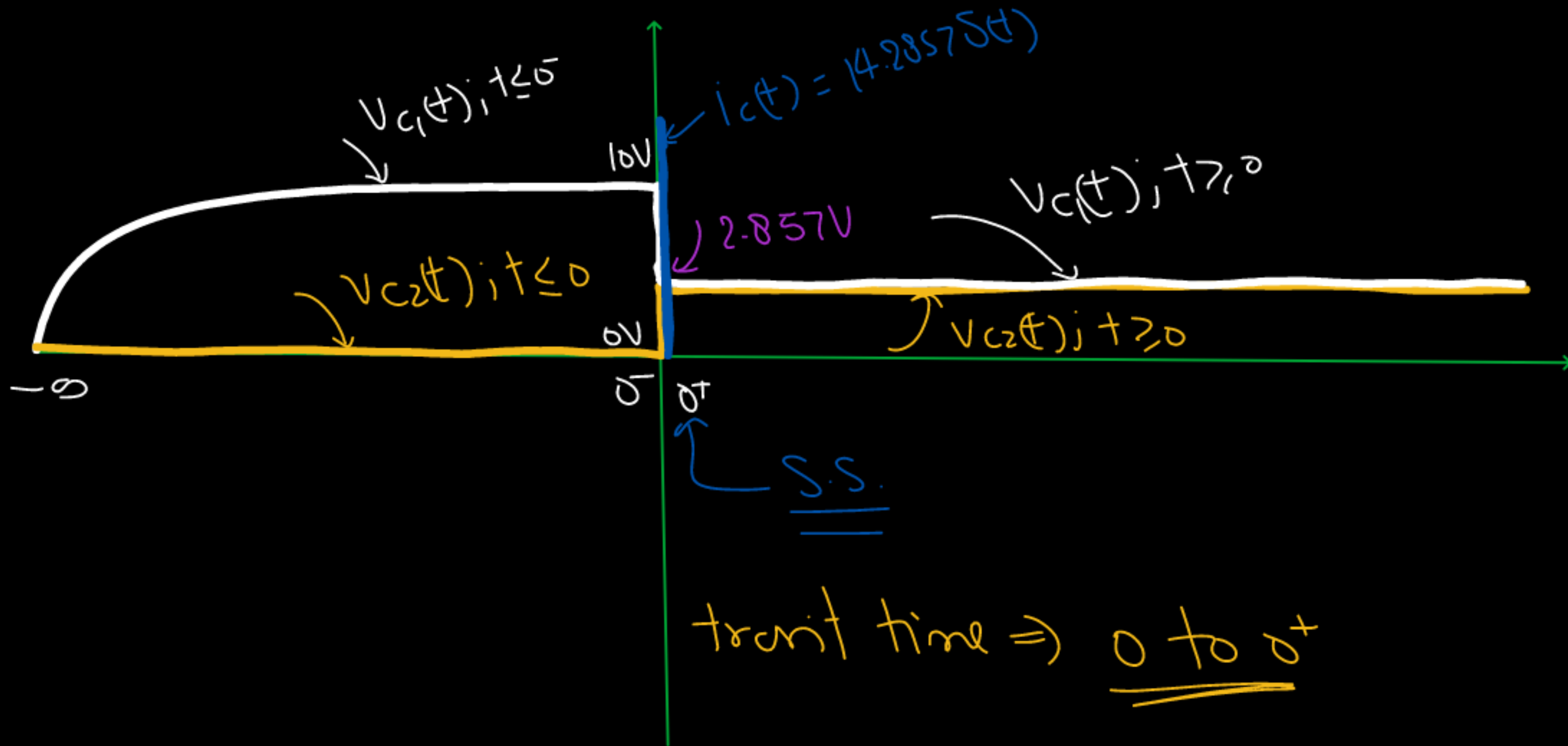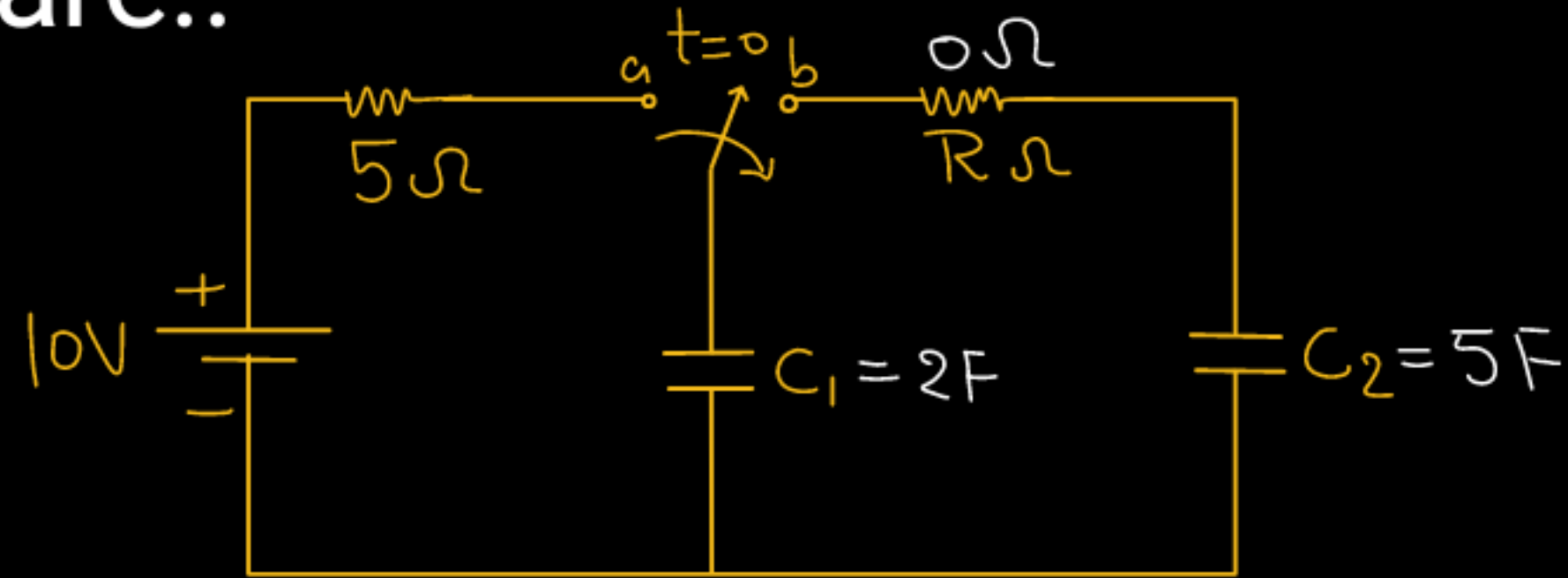**Ex-1** The Steady State voltage across both Capacitor are..





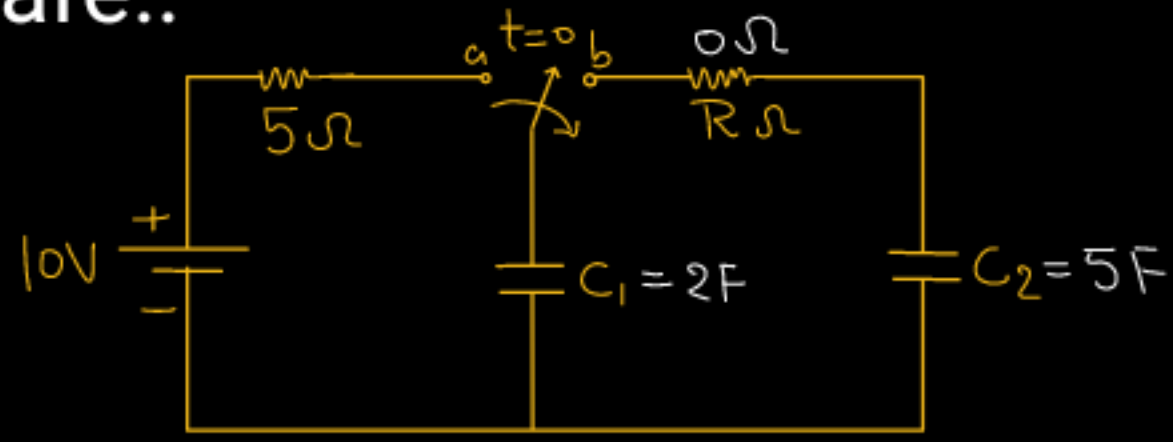Ex-1 The Steady State voltage across both Capacitor are..



$$\Rightarrow V_{C1}^- = 10V \quad ) \quad W_{C1}^- = \frac{1}{2} C_1 V_{C1}^{-2}$$

$$= \frac{1}{2} \times 2 \times 10^2 = 100J$$

$$\Rightarrow W_{C1}^+ = \frac{1}{2} C_1 V_{C1}^{+2} = \frac{1}{2} \times 2 \times 2.857^2$$

$$= 8.16J$$

$$\Rightarrow W_{C2}^+ = \frac{1}{2} \times 5 \times 2.857^2 = 20.41J$$

$$\Rightarrow W_{C1}^+ + W_{C2}^+ = 28.57J$$

$$\Rightarrow \text{energy loss in SW} \rightarrow 100 - 28.57$$

$$= 71.43J$$




## Ex-2

The Steady State voltage across both Capacitor and energy dissipated by resistance in Steady State will be


$$R = 10\Omega$$

$$C_1 = 2F$$



$$C_2 = 5F$$

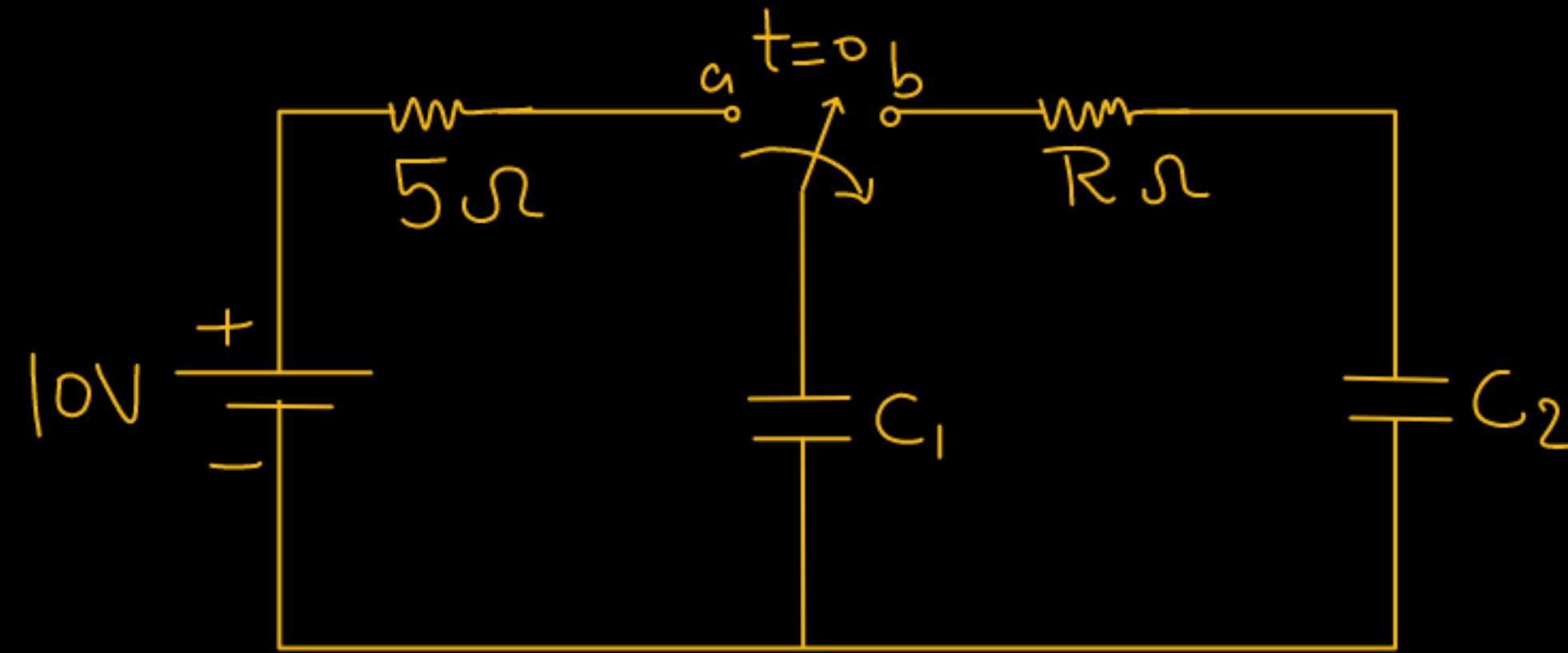

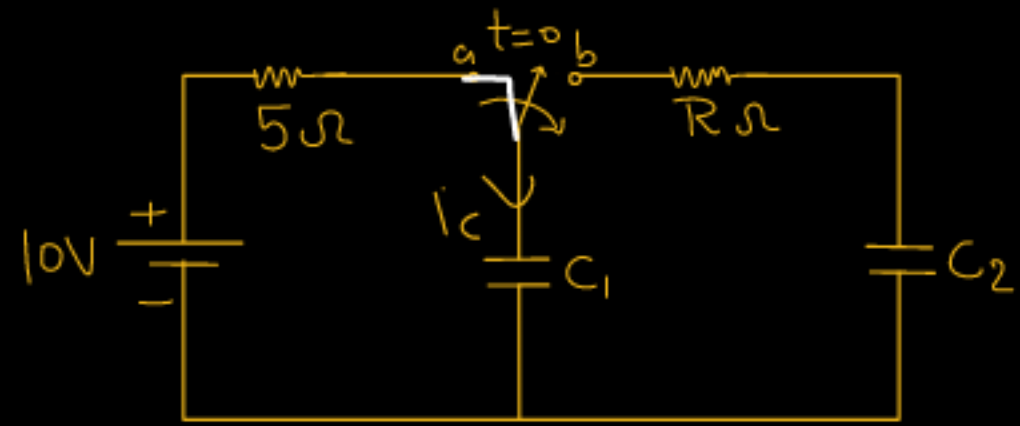$t \leq 0^-$   
 $V_{C1} = 10V$   
 $V_{C2} = 0V$



$t \geq 0$

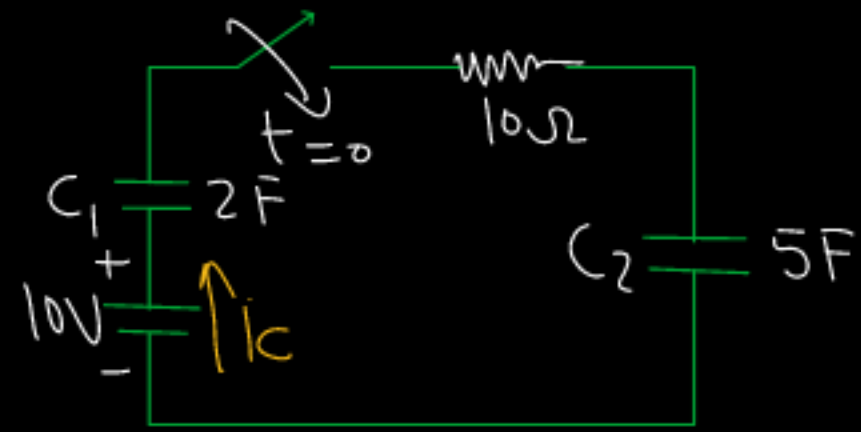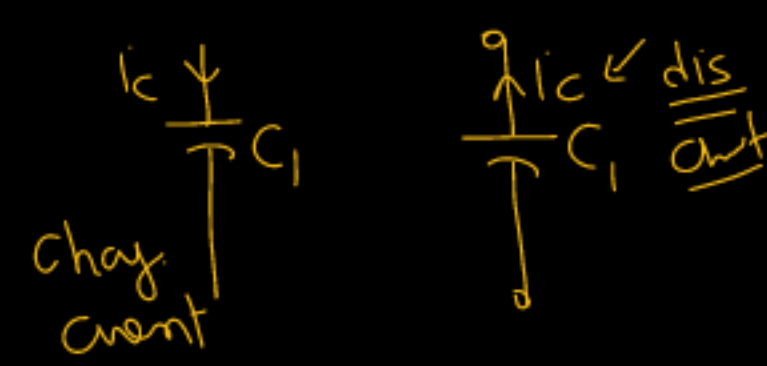

ckt in freq domain-

$$i_c(s) \left[ 10 + \frac{1}{2s} + \frac{1}{5s} \right] = \frac{10}{s}$$


$$i_c(s) \left[ 10 + \frac{0.5}{s} + \frac{0.2}{s} \right] = \frac{10}{s}$$

$$i_c(s) \left[ \frac{10s + 0.7}{s} \right] = \frac{10}{s}$$

$$i_c(s) [s + 0.07] = \frac{10}{s}$$

$$i_c(s) = \frac{1}{(s + 0.07)} \text{ take inv. lap. transf.}$$

$$i_c(t) = (e^{-0.07t}) \text{ Amp.}$$

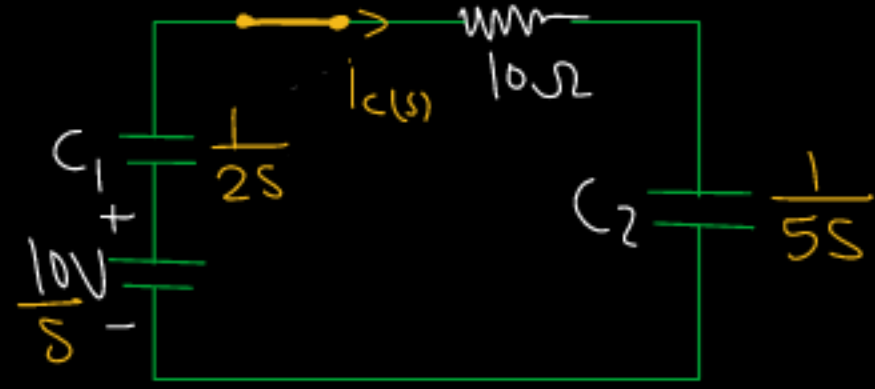

$$V_{C_2}(t) = \frac{1}{C_2} \int_0^t i_C(t) dt = \frac{1}{5} \int_0^t 1 \cdot e^{-0.07t} dt.$$

$$V_{C_1}(t) = 10 - \frac{1}{2} \int_0^t e^{-0.07t} dt$$


energy  $w = \int_t p dt$

$$W_R = \int_0^t i^2 R dt$$


$$= \int_0^t (e^{-0.07t})^2 \times 10 dt \quad \text{J}$$
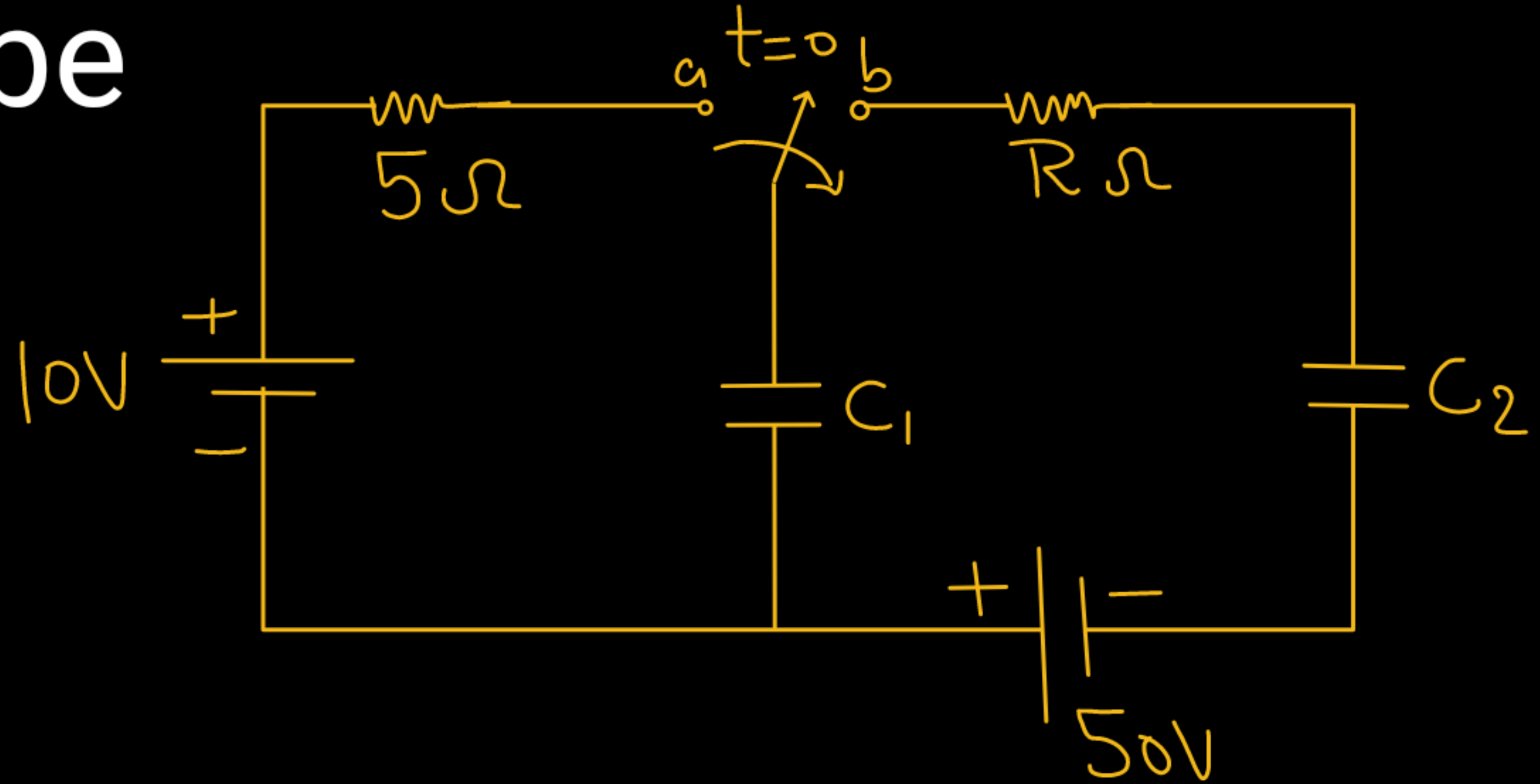
## Ex-1

The Steady State voltage across both Capacitor will be



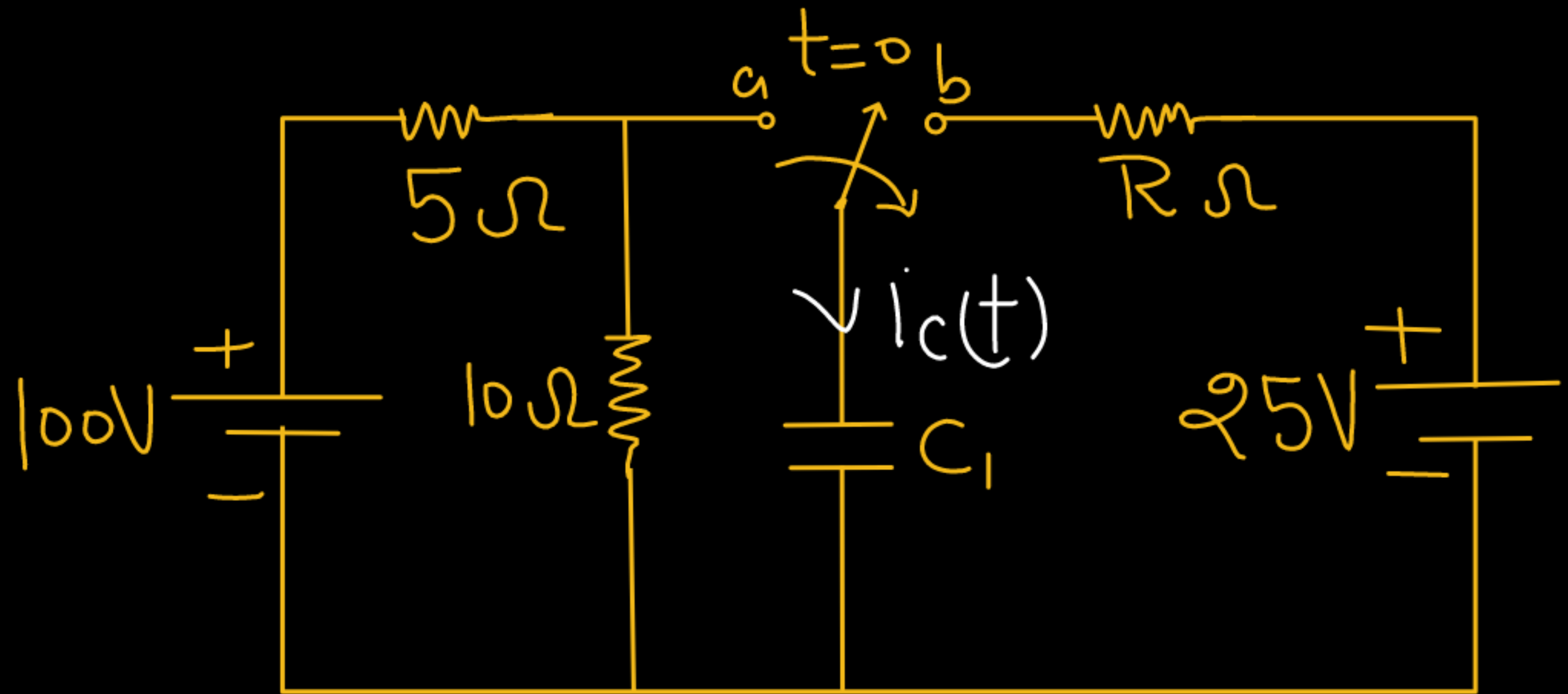The Capacitor's current Response  
for ,  $t > 0$  is..



The Capacitor's voltage Response  
for ,  $t \geq 0$  is..

